



# Electrical Science: 2021-22



## Lecture 19

### Three Phase AC Circuits - Part 3

By **Dr. Sanjay Vidhyadharan**

# Power in Three Phase Circuits

## Star Connection

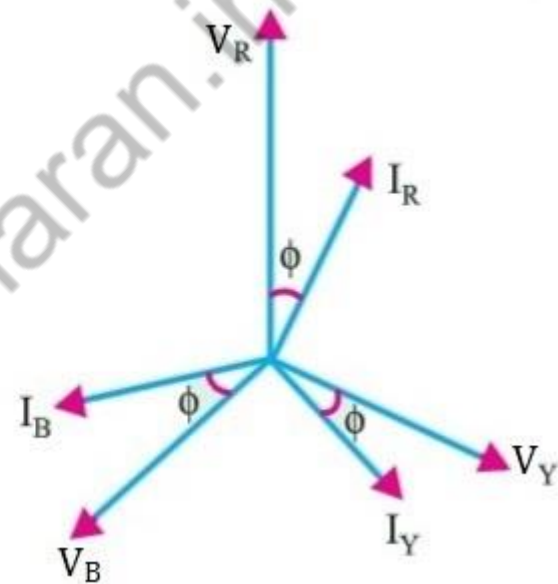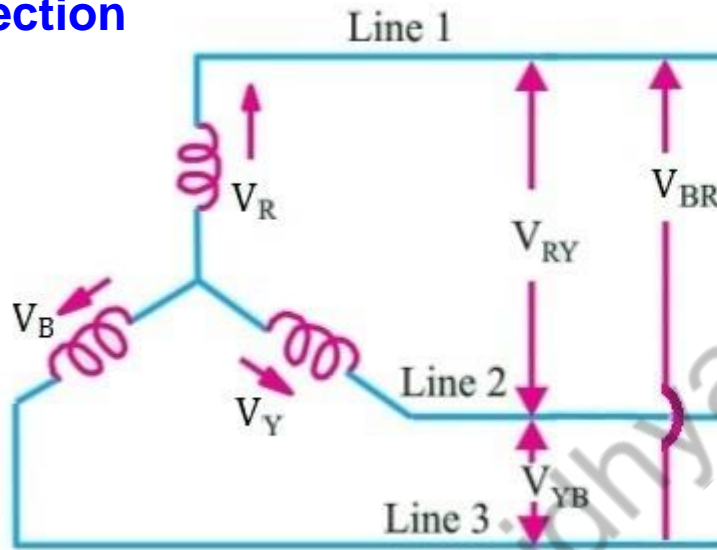

$$P = 3 \times V_{PH} \times I_{PH} \times \cos\phi$$


$$I_L = I_{PH}$$

$$V_{PH} = V_L / \sqrt{3} \quad \dots \text{(From } V_L = \sqrt{3} V_{PH} \text{)}$$

$$P = \sqrt{3} \times V_L \times I_L \times \cos\phi$$

# Power in Three Phase Circuits

## Delta Connection

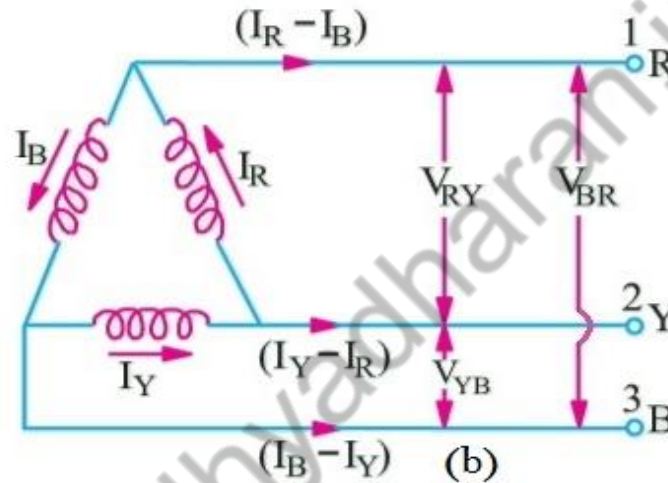

**Power / Phase =  $V_{PH} \times I_{PH} \times \cos\Phi$**

And the total power of three phases;

**Total Power =  $P = 3 \times V_{PH} \times I_{PH} \times \cos\Phi$**

$I_{PH} = I_L / \sqrt{3}$  ..... (From  $I_L = \sqrt{3} I_{PH}$ )

$V_{PH} = V_L$

**$P = 3 \times V_{PH} \times I_{PH} \times \cos\Phi$  .... or**

**$P = \sqrt{3} \times V_L \times I_L \times \cos\Phi$**

# Power in Three Phase Circuits

A three phase 400V, 50 Hz, balanced supply feeds a balanced load consisting of (a) three equal single phase loads of  $(40 + j 30) \Omega$  connected in star, and (b) a three phase heating load (purely resistive) of 1.8 kW.

Determine the supply current, supply power factor, active and reactive power supplied.

*Solution*

(i) Using one-phase diagram (figure 8)

$$Z_{L1} = 40 + j 30 \Omega$$

$$E_p = 400/\sqrt{3} = 230.9\angle 0$$

$$P_p = 1.8/3 = 0.6 \text{ kW} = 600 \text{ W}$$

$$\therefore I_{p1} = \frac{230.9\angle 0}{40 + j30} = \frac{230.9\angle 0}{50\angle 36.87^\circ} = 4.619\angle -36.87^\circ$$

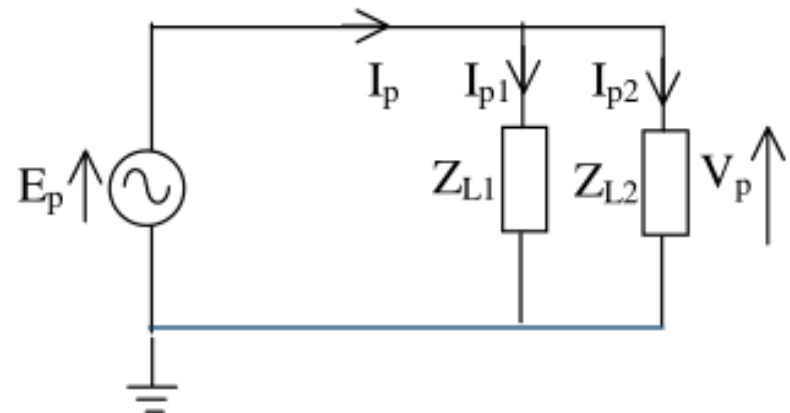


Figure 8 – Single phase diagram

# Power in Three Phase Circuits

A three phase 400V, 50 Hz, balanced supply feeds a balanced load consisting of (a) three equal single phase loads of  $(40 + j 30) \Omega$  connected in star, and (b) a three phase heating load (purely resistive) of 1.8 kW.

Determine the supply current, supply power factor, active and reactive power supplied.

In order to calculate  $I_{p2}$ , we need not calculate  $Z_{L2}$ , but can use  $P = V I \cos \phi$ .

$$\therefore I_{p2} = \frac{600}{230.9 \times 1} = 2.598 \angle 0 \quad [\text{Note: angle is zero because it is purely resistive}]$$

$$\text{Thus } I_p = I_{p1} + I_{p2} = 4.619 \angle -36.87^\circ + 2.598 = 6.293 - j 2.771 = 6.876 \angle -23.77^\circ \text{ A}$$

$$\therefore \text{ supply current} = 6.876 \angle -23.77^\circ \text{ A}$$

$$\text{supply power factor} = \cos (0 - (-23.77)) = 0.915 \text{ lag}$$

$$\text{active power supplied} = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 400 \times 6.876 \times 0.915 = 4360 \text{ W}$$

$$\text{reactive power supplied} = \sqrt{3} V_L I_L \sin \phi = \sqrt{3} \times 400 \times 6.876 \times \sin (-23.77) = 1920 \text{ var}$$

# Unbalanced Loads

The unbalanced Y-load of Figure below has balanced phase voltage of 100 V and the acb sequence. Calculate the line currents and the neutral current.

$Z_A = 15 \Omega$ ,  $Z_B = 10 + j5 \Omega$ ,  $Z_C = 6 - j8 \Omega$ .

The line currents are,


$$I_a = \frac{100 \angle 0^\circ}{15} = 6.67 \angle 0^\circ \text{ A}$$

$$I_b = \frac{100 \angle 120^\circ}{10 + j5} = 8.94 \angle 93.44^\circ \text{ A};$$

$$I_c = \frac{100 \angle -120^\circ}{6 - j8} = 10 \angle -66.87^\circ \text{ A}$$

The current in the neutral line is:

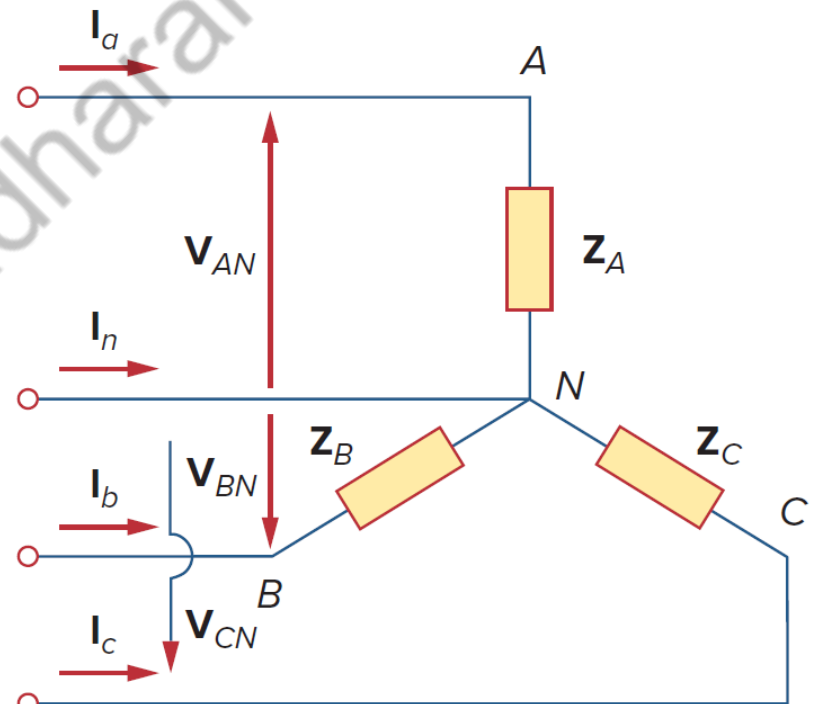
$$\begin{aligned} I_n &= -(I_a + I_b + I_c) = -(6.67 - 0.54 + j8.92 + 3.93 - j9.2) \\ &= -10.06 + j0.28 = 10.06 \angle 178.4^\circ \text{ A} \end{aligned}$$



# Measurement of Power

- (i) Three-Wattmeter Method :** This is simplest and straight forward method.
- (ii) Two-Wattmeter Method :** This can be used for any balanced or unbalanced load, star- or delta-connected.
- (iii) One-Wattmeter Method :** This can be used only for a star-connected **balanced** load.


# Measurement of Power

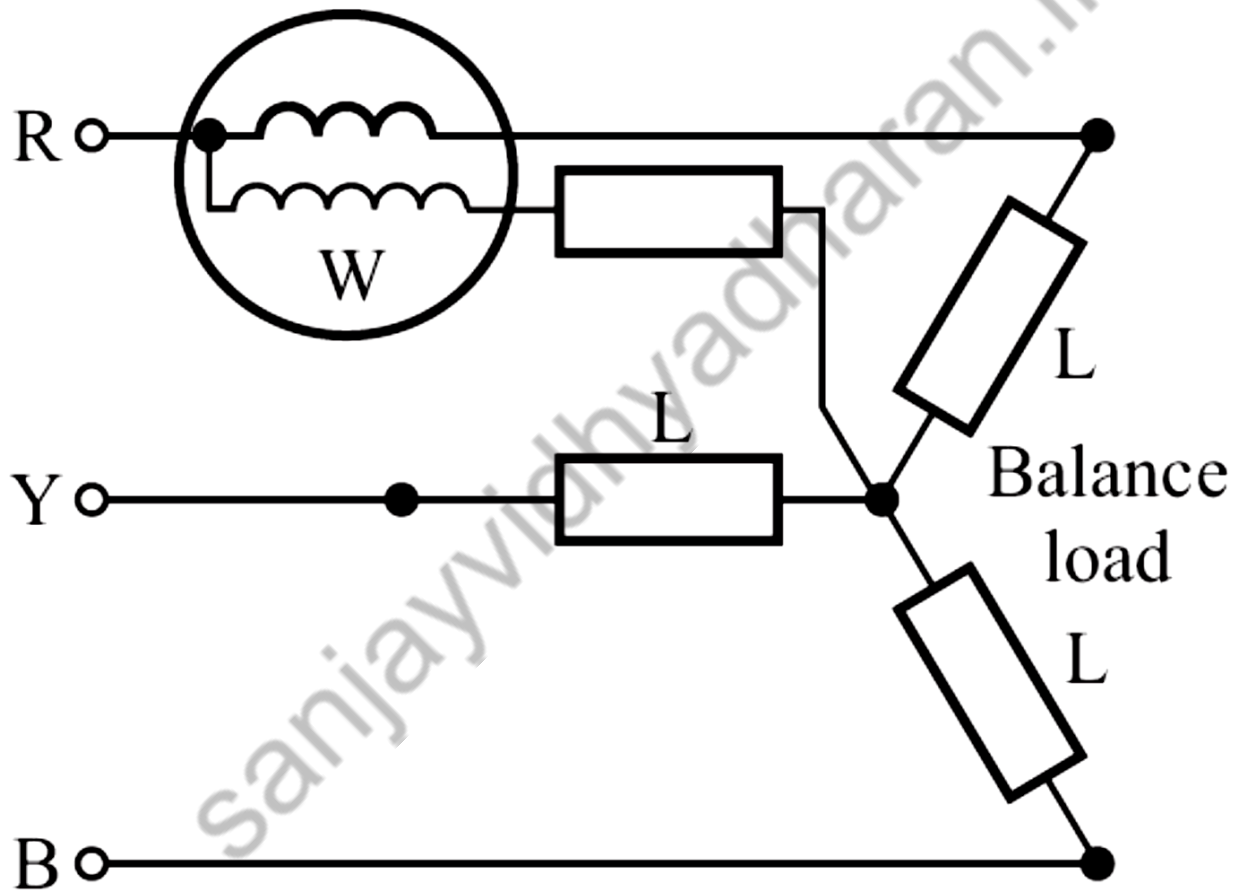



# Measurement of Power

## Two-Wattmeter Method

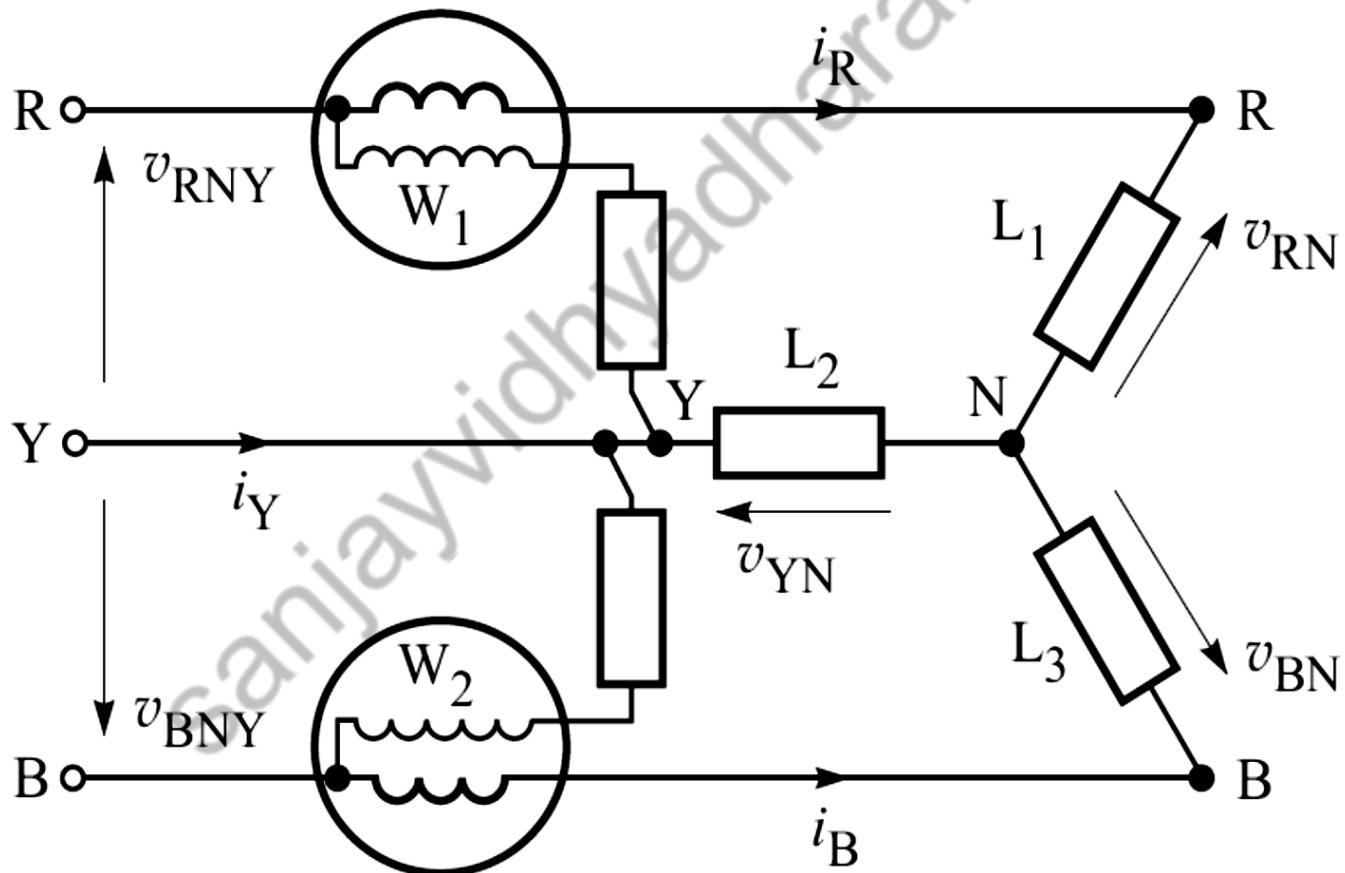

# Measurement of Power

## Two-Wattmeter Method

The sum of the wattmeter readings gives the average value of the total power absorbed by the three phases

Total instantaneous power

$$= i_R v_{RN} + i_Y v_{YN} + i_B v_{BN}$$

The instantaneous power measured by  $W_1$ ,

$$p_1 = i_R (v_{RN} - v_{YN})$$


The instantaneous power measured by  $W_2$ ,

$$p_2 = i_B (v_{BN} - v_{YN})$$

$$\begin{aligned} \therefore p_1 + p_2 &= i_R (v_{RN} - v_{YN}) + i_B (v_{BN} - v_{YN}) \\ &= i_R v_{RN} + i_B v_{BN} - (i_R + i_B) v_{YN} \end{aligned}$$

$$\text{By KCL, } i_R + i_Y + i_B = 0 \Rightarrow (i_R + i_B) = -i_Y$$
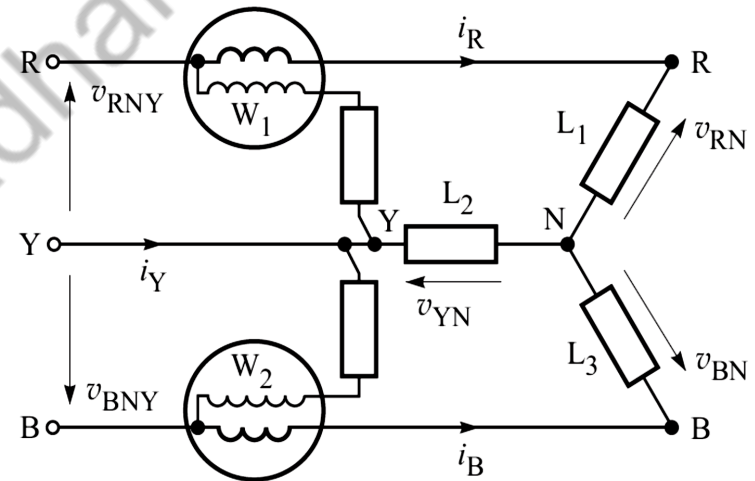
$$\begin{aligned} \therefore p_1 + p_2 &= i_R v_{RN} + i_B v_{BN} + i_Y v_{YN} \\ &= \text{total instantaneous power} \end{aligned}$$




Since we did **not** assume a **balanced load** or a **sinusoidal waveform**, it follows that the sum of the two wattmeter readings gives the total power under all conditions.

# Measurement of Power
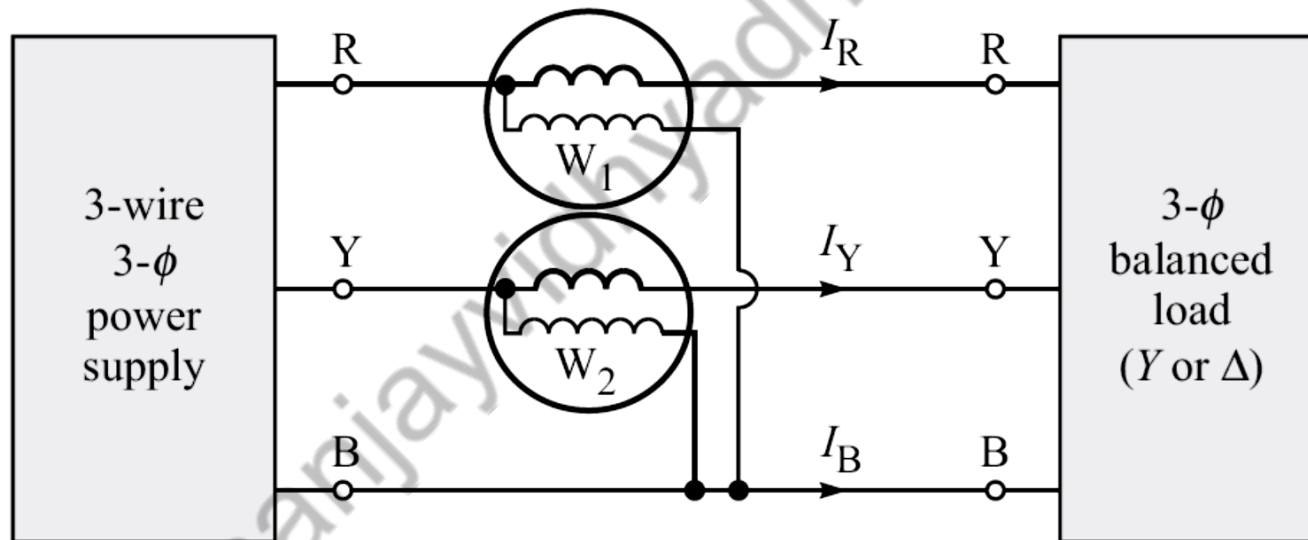
## Power Factor Measurement by Two-Wattmeter Method

Concept of 'power factor' is meaningful only if the load is balanced.





# Measurement of Power
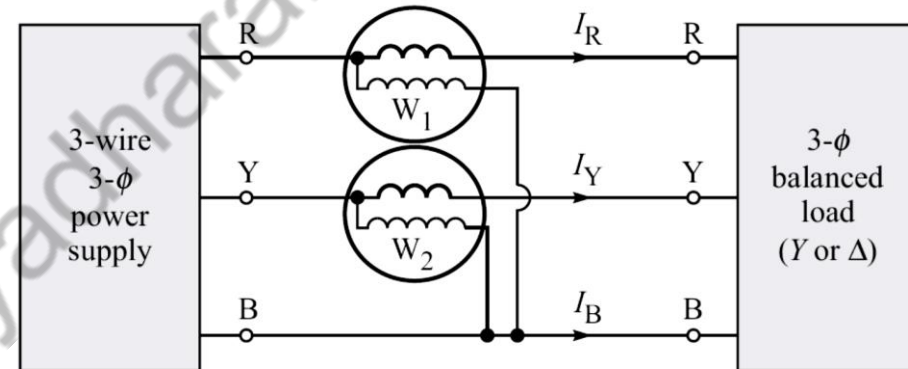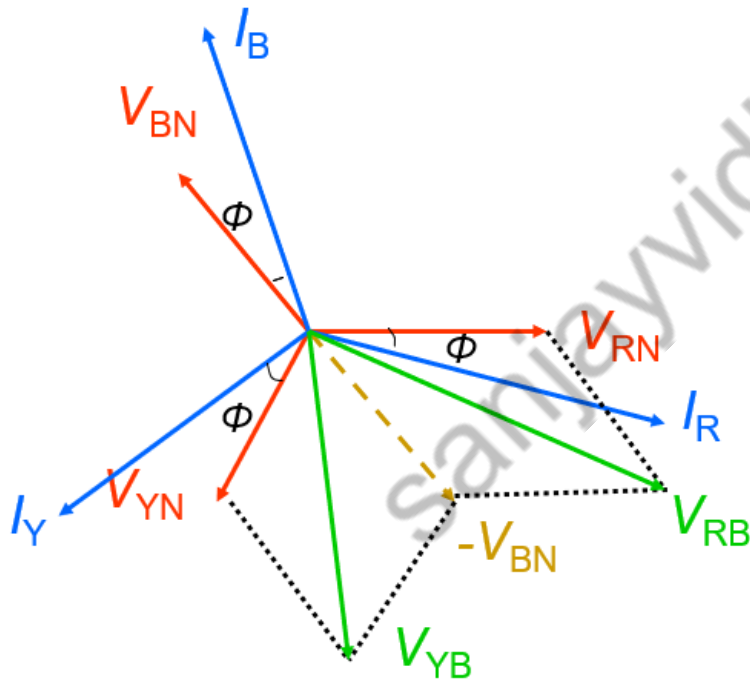
## Power Factor Measurement by Two-Wattmeter Method

$$I_R = I_Y = I_B = I_L \text{ (say)}$$

and  $V_{RN} = V_{YN} = V_{BN} = V_{ph} \text{ (say)}$



12

$$P_1 = V_{RB} I_R \cos(\varphi) = \sqrt{3} V_{RN} I_R \cos(-30^\circ - \varphi)$$

$$= \sqrt{3} V_{RN} I_R \cos(30^\circ + \varphi)$$

$$P_2 = V_{YB} I_Y \cos(\varphi) = \sqrt{3} V_{YN} I_Y \cos(30^\circ - \varphi)$$

# Measurement of Power

## Power Factor Measurement by Two-Wattmeter Method

$$P_1 = \sqrt{3} V_{RN} I_R \cos(30^\circ + \phi)$$


$$P_2 = \sqrt{3} V_{YN} I_Y \cos(30^\circ - \phi)$$

$$\therefore \frac{P_1}{P_2} = \frac{\cos(30^\circ - \phi)}{\cos(30^\circ + \phi)}$$

By applying componendo and dividendo

$$\begin{aligned} \frac{P_1 - P_2}{P_1 + P_2} &= \frac{\cos(30^\circ - \phi) - \cos(30^\circ + \phi)}{\cos(30^\circ - \phi) + \cos(30^\circ + \phi)} \\ &= \frac{2 \sin 30^\circ \sin \phi}{2 \cos 30^\circ \cos \phi} = \tan 30^\circ \tan \phi \end{aligned}$$
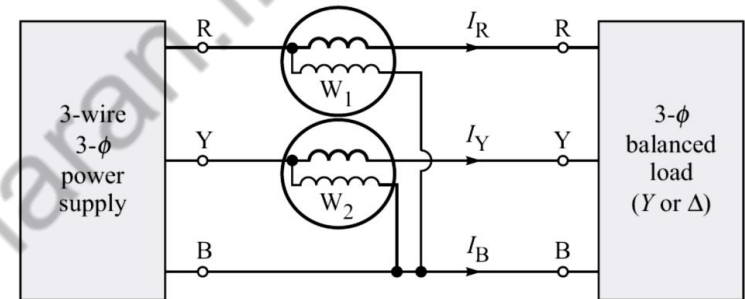
$$\therefore \tan \phi = \sqrt{3} \left[ \frac{P_1 - P_2}{P_1 + P_2} \right]$$



# Measurement of Power

## Important Points :

- If  $\Phi = 0^\circ$ ,  $P_1 = P_2$ .
- If  $\Phi < 60^\circ$ , both  $P_1$  and  $P_2$  are positive; and
$$P = P_1 + P_2$$
- If  $\Phi = 60^\circ$ ,  $P_2$  is zero.
- If  $\Phi > 60^\circ$ , (i.e., if  $pf < 0.5$ ),  $P_2$  is negative.

In such case, the connection of either the current coil or the potential coil has to be reversed to make positive deflection.

The value  $P_2$  should then be taken as negative while calculating the power factor or the total power.

# Measurement of Power

## Example:

- Two-wattmeter method was used to determine the input power to a three-phase motor. The readings were 5.2 kW and -1.7 kW, and the line voltage was 415 V. Calculate
  - (a) the total power,
  - (b) the power factor, and
  - (c) the line current.

# Measurement of Power

## Solution :

(a) The total power,

$$P = P_1 + P_2 = 5.2 \text{ kW} - 1.7 \text{ kW} = \mathbf{3.5 \text{ kW}}$$

$$(b) \tan \phi = \sqrt{3} \left[ \frac{P_1 - P_2}{P_1 + P_2} \right] = \sqrt{3} \left[ \frac{5.2 - (-1.7)}{5.2 + (-1.7)} \right] = 3.41$$

$$\therefore \phi = \tan^{-1} 3.41 = 73^\circ 39'$$

$$\therefore pf = \cos \phi = \cos 73^\circ 39' = \mathbf{0.281}$$


$$(c) \quad 3500 = \sqrt{3} \times 415 \times I_L \times 0.281$$

$$\Rightarrow \quad I_L = \mathbf{17.3 \text{ A}}$$



# Measurement of Power

## Three-Wattmeter Method

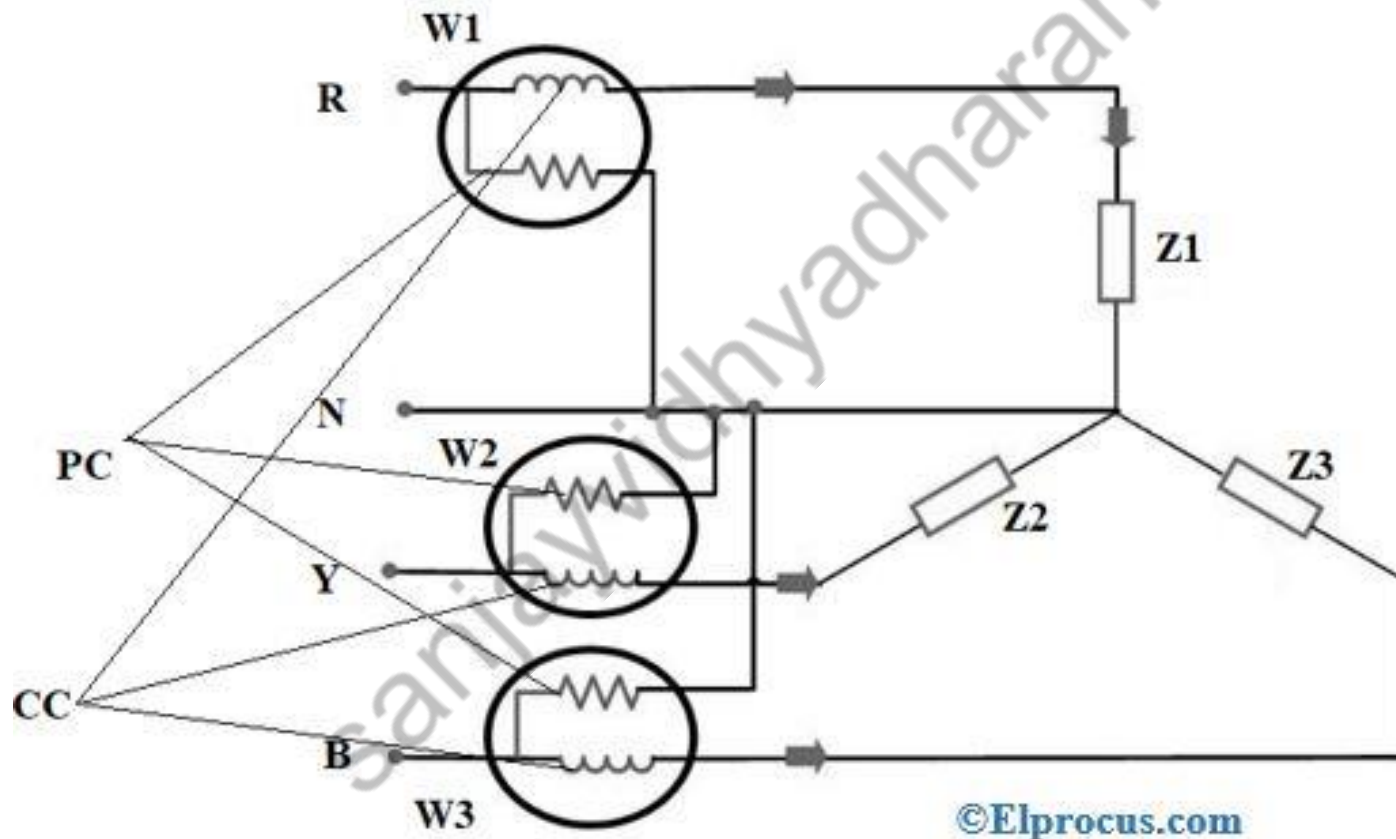


# Measurement of Power

## Three-Wattmeter Method

Three wattmeters  $W_1$ ,  $W_2$ , and  $W_3$  are connected, respectively, to phases A, B, and C of an unbalanced Y-connected load as in figure. The balanced source is Y-connected with phase voltage 100 V in negative (acb) sequence.

Find

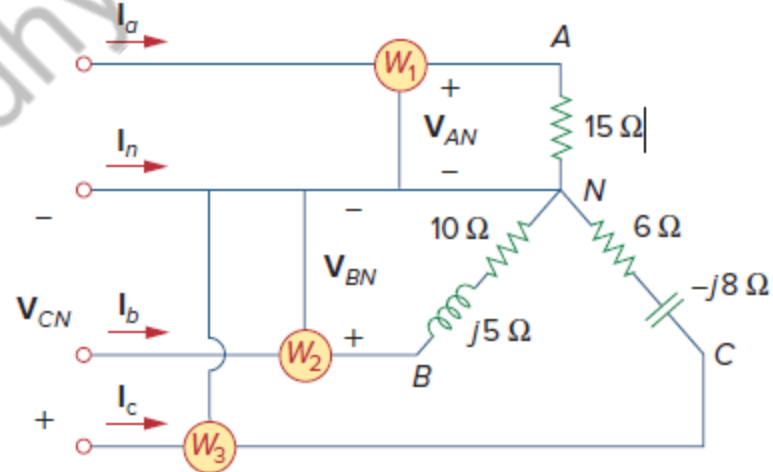- (a) the wattmeter readings
- (b) the total power absorbed by the load.



# Measurement of Power


## Three-Wattmeter Method

**Solution:** The line currents are,

$$I_a = \frac{100 \angle 0^\circ}{15} = 6.67 \angle 0^\circ A$$

$$I_b = \frac{100 \angle 120^\circ}{10 + j5} = 8.94 \angle 93.44^\circ A$$
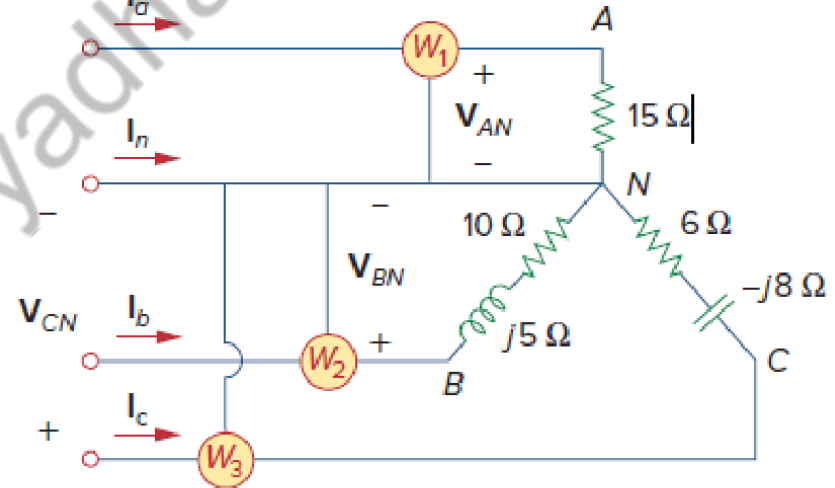
$$I_c = \frac{100 \angle -120^\circ}{6 - j8} = 10 \angle -66.87^\circ A$$



# Measurement of Power

## Three-Wattmeter Method

(a) The wattmeter readings are,

$$P_1 = \text{Re}(V_{AN} I_a^*) = V_{AN} I_a \cos(\theta_{V_{AN}} - \theta_{I_a}) = 100 * 6.67 * \cos(0^\circ - 0^\circ) = 667W$$

$$P_2 = \text{Re}(V_{BN} I_b^*) = V_{BN} I_b \cos(\theta_{V_{BN}} - \theta_{I_b}) = 100 * 8.94 * \cos(120^\circ - 93.44^\circ) = 800W$$

$$P_3 = \text{Re}(V_{CN} I_c^*) = V_{CN} I_c \cos(\theta_{V_{CN}} - \theta_{I_c}) = 100 * 10 * \cos(-120^\circ + 66.87^\circ) = 600W$$

(b) The total power absorbed is  $P_T = P_1 + P_2 + P_3 = 667 + 800 + 600 = 2067W$

The power absorbed can also be calculated as the power dissipated across the resistors,

$$P_T = |I_a|^2 (15) + |I_b|^2 (10) + |I_c|^2 (6) = 6.67^2 (15) + 8.94^2 (10) + 10^2 (6) = 667 + 800 + 600 = 2067W$$

**Thank you**

sanjayvidhyadharan.in