




Electrical Science: 2021-22

Lecture 25

BJT Amplifiers-Part1

By Dr. Sanjay Vidhyadharan

BJT Currents in Forward-Active Mode

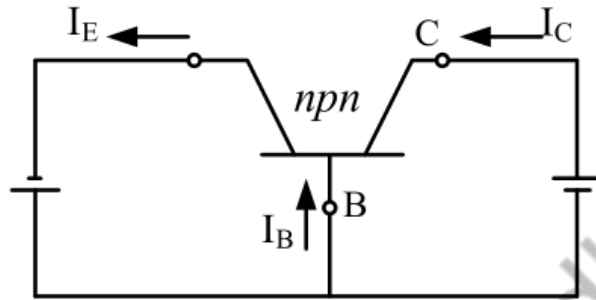

1. $I_E = I_B + I_C$

2. $I_C = \beta I_B$

3. $\beta = \frac{\alpha}{1-\alpha}$ (20 – 200)

4. $\alpha = \frac{\beta}{1+\beta}$ (0.95 – 0.995)

BJT DC and Small Signal Equivalent



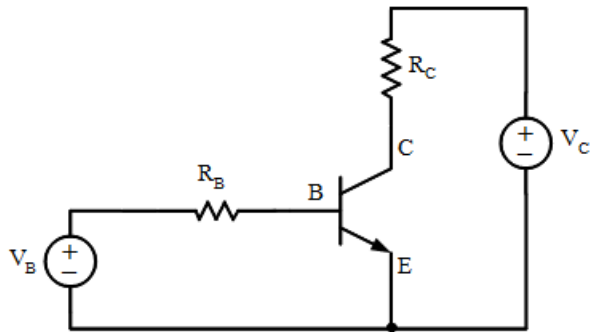
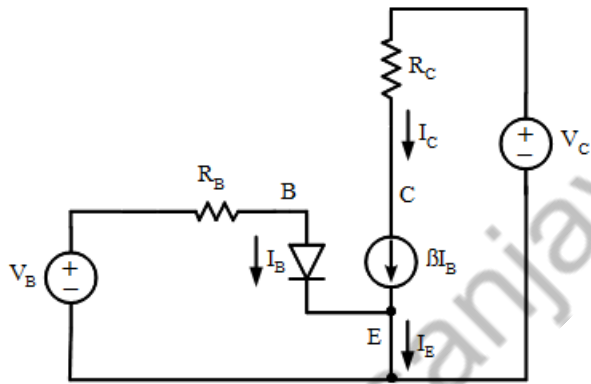


Fig 1: BJT Switch

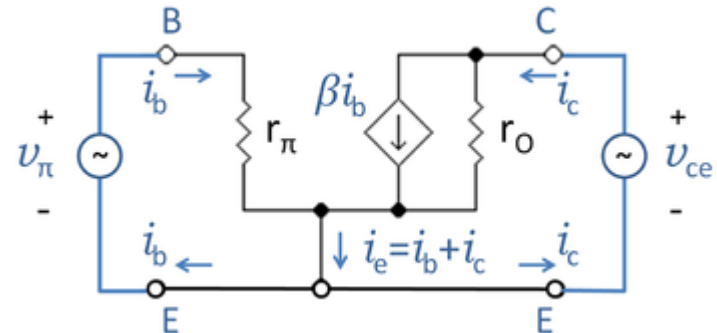

DC Equivalent Circuit

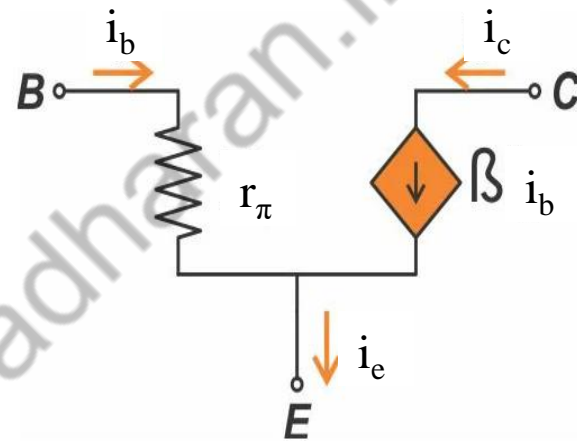


AC Equivalent Circuit

BJT Amplifier/Circuit Configurations



- Common-Emitter Configuration
- Common-Collector Configuration
- Common-Base Configuration

sanjayvichayacharan.in



Common-Emitter Configuration

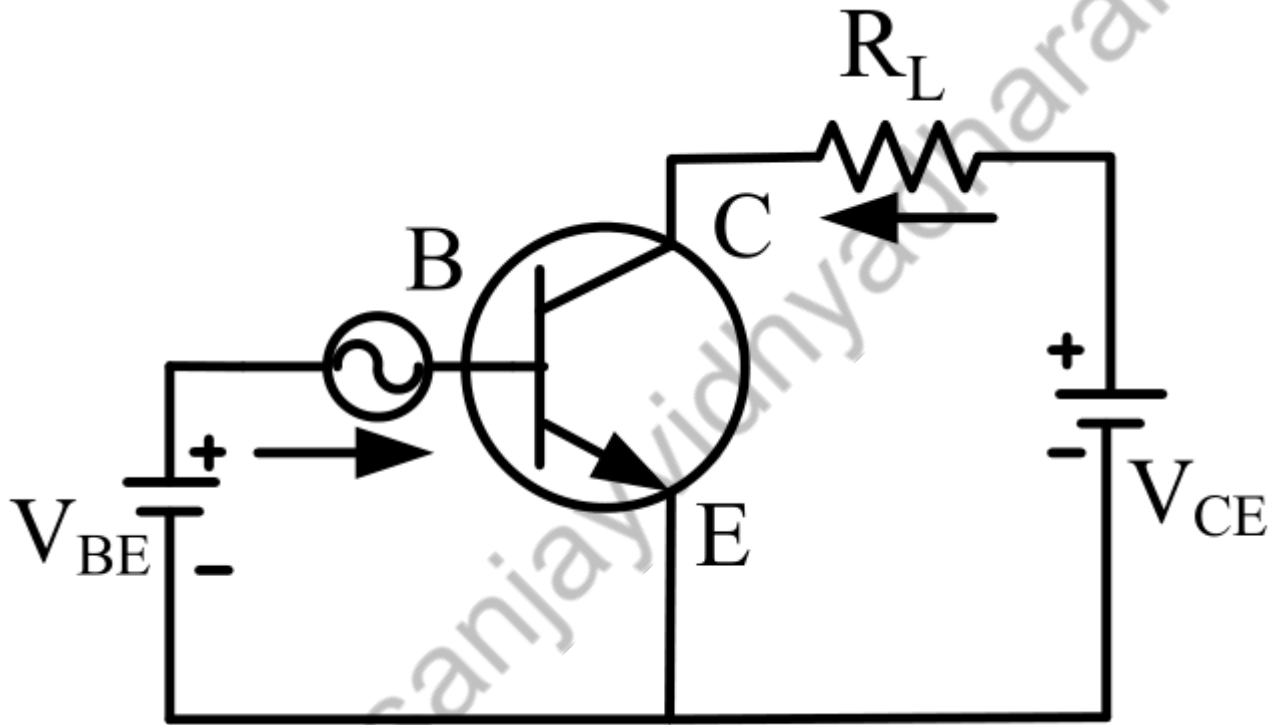

Common-Emitter Configuration

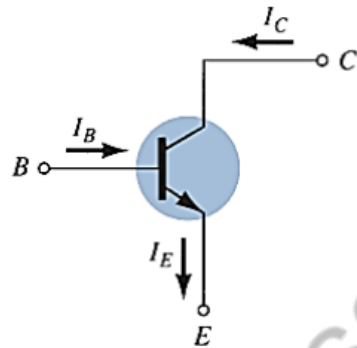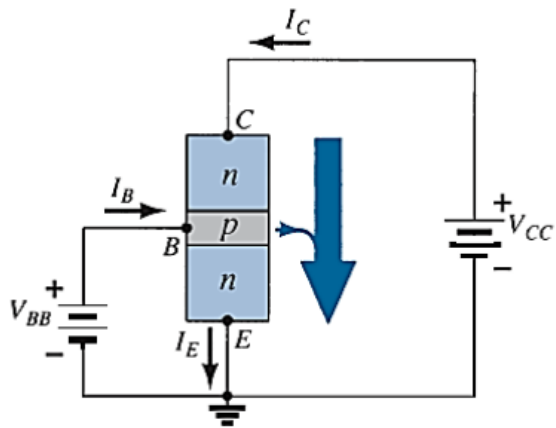

(a) *n*pn transistor

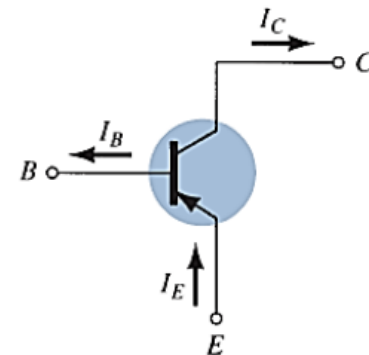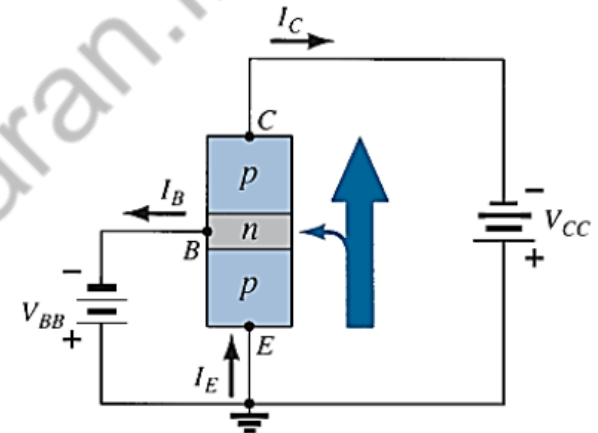


(b) *p*np transistor

The arrows in the graphics define the direction of current through the device.

Common-Emitter Configuration

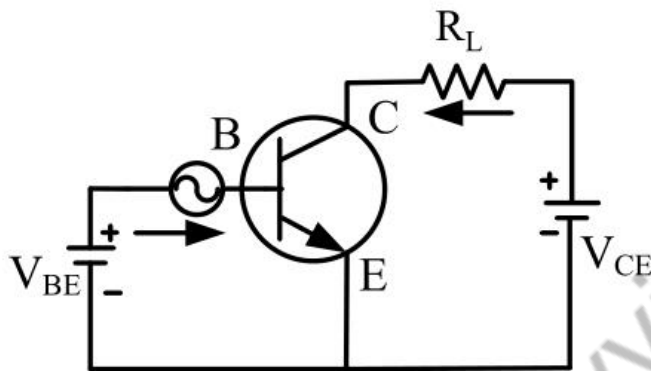Input dc characteristics in Common-Emitter configuration




Notation:

Input current (I_B)



Input voltage (V_{BE})

Output voltage (V_{CE})

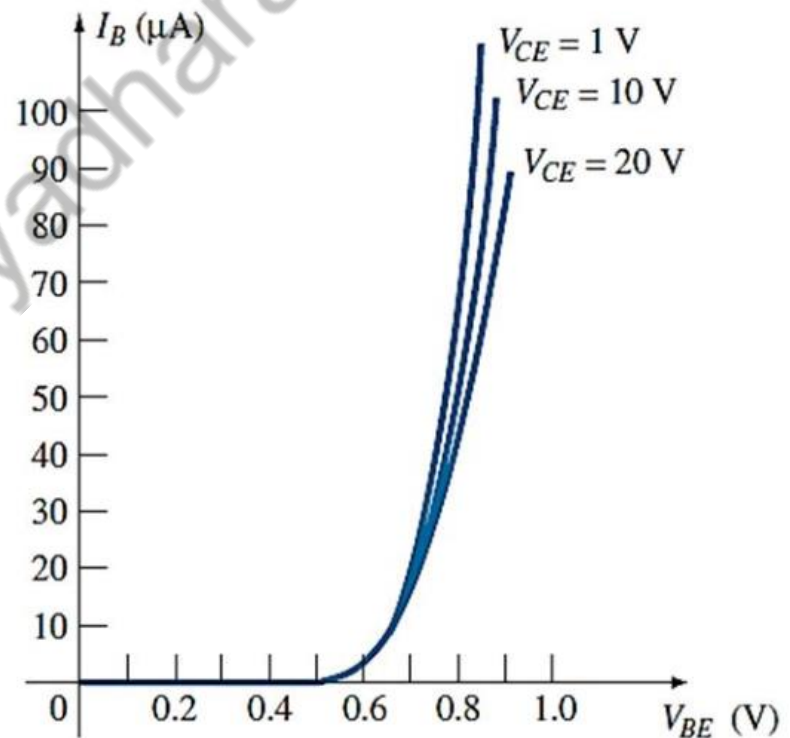

Common-Emitter Configuration

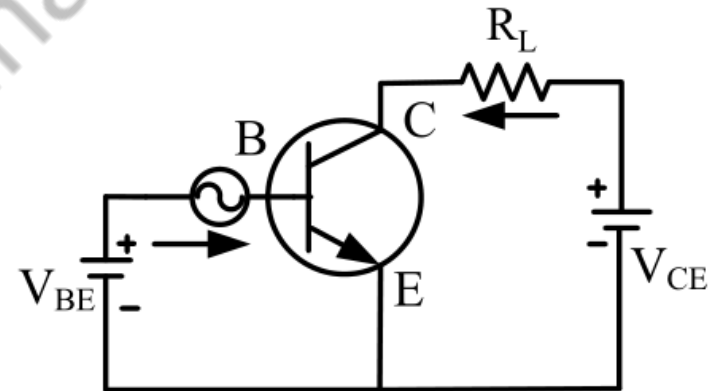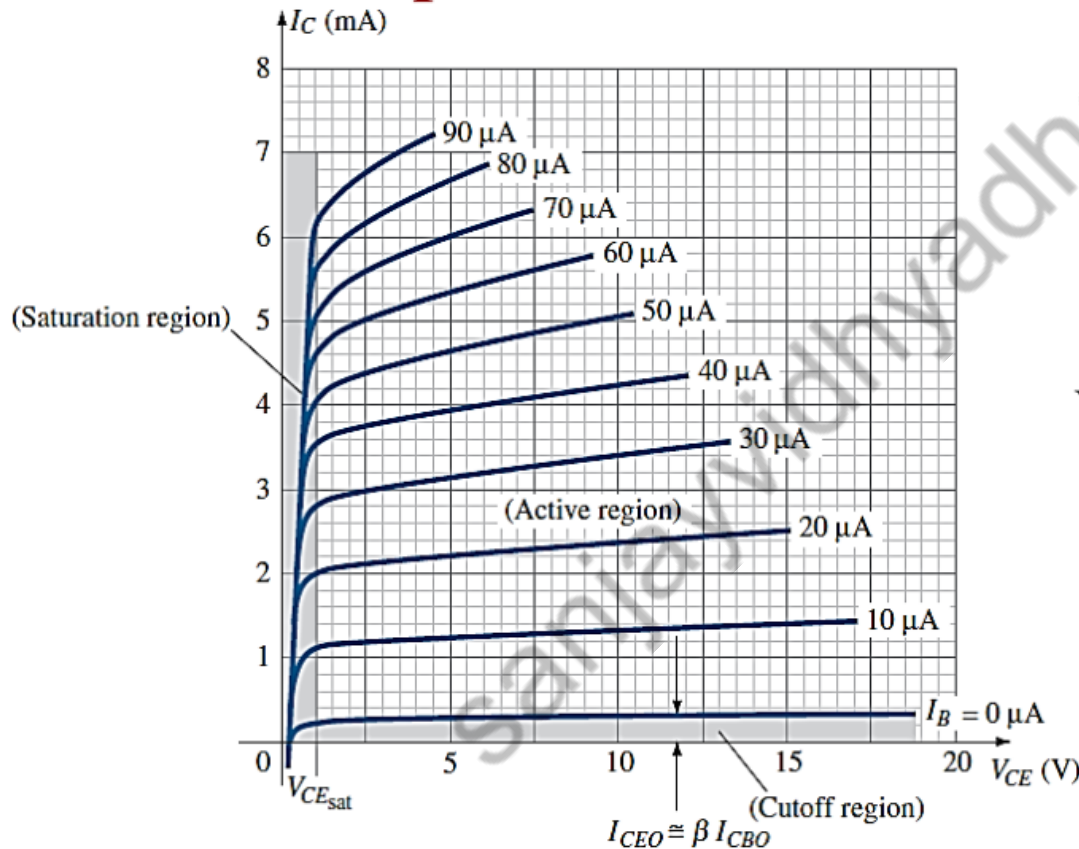
Output dc characteristics in Common-Emitter configuration





Notation:

- Output current (I_C)
- Output voltage (V_{CE})
- Input current (I_B)

Common-Emitter Configuration

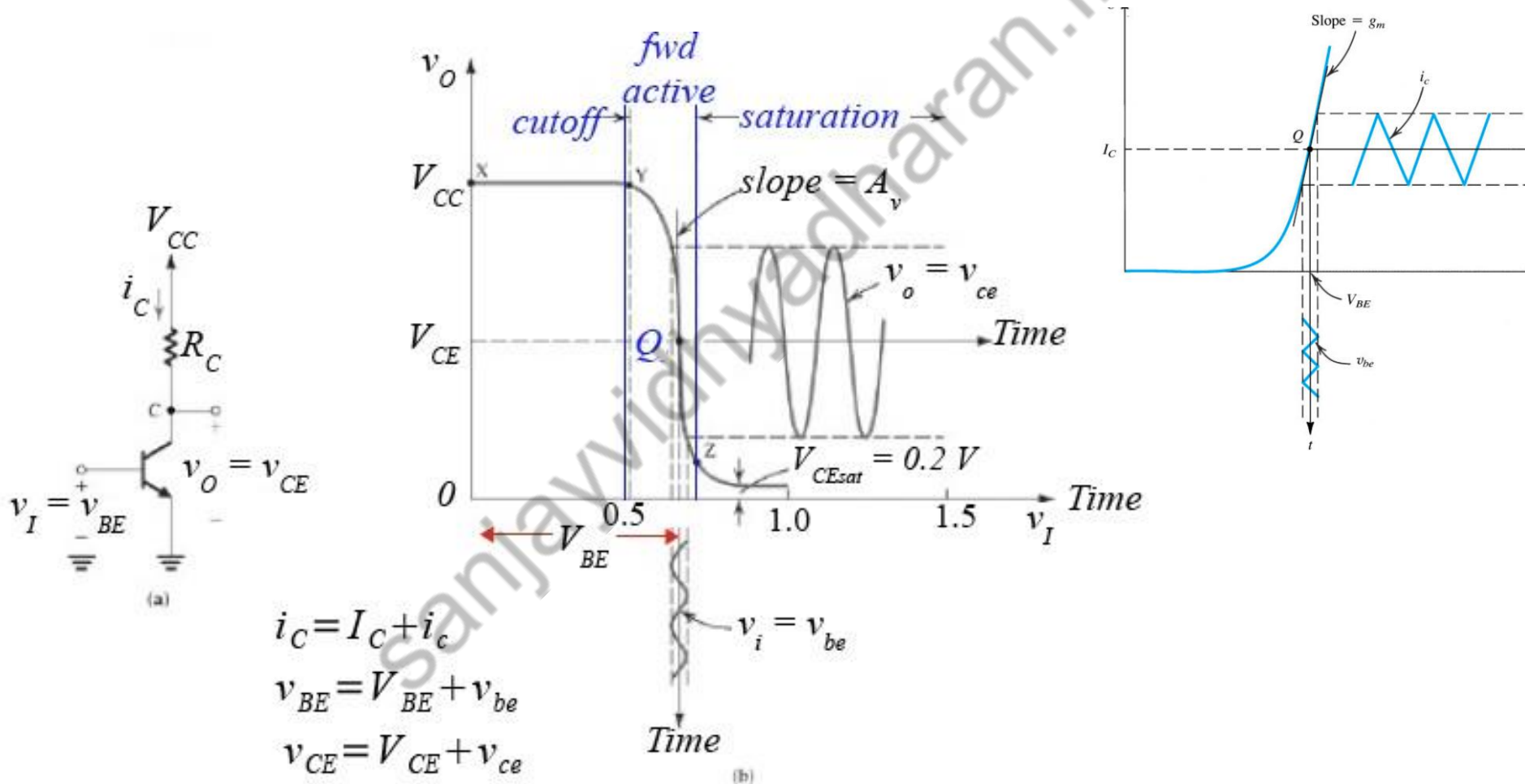

Common-Emitter Configuration

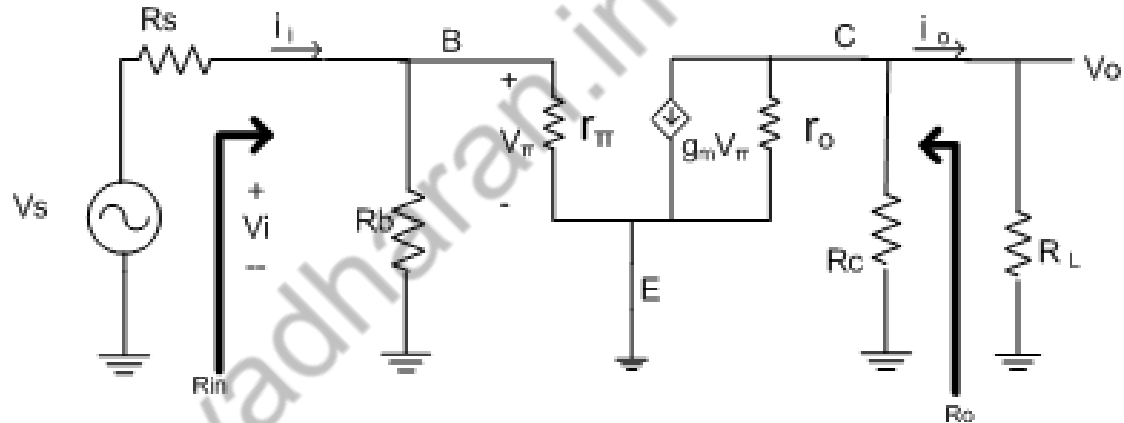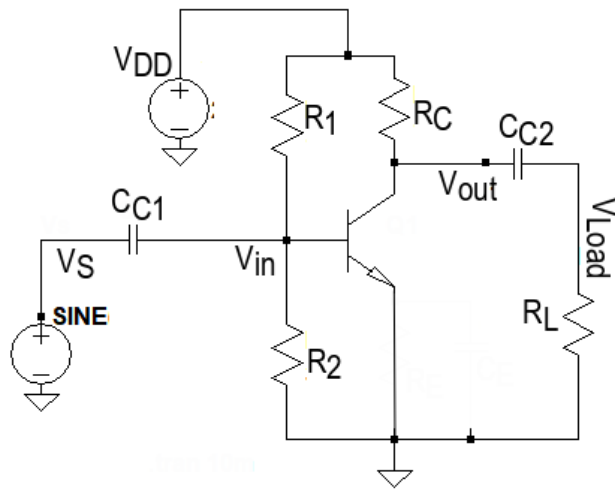

$$g_m V_\pi = \beta i_b$$


$$g_m = \frac{\beta i_b}{V_\pi} = \frac{\beta}{r_\pi}$$

$$V_{in} = i_b r_\pi \quad (R_s \ll r_\pi, \ll R_b)$$



$$i_c = \beta i_b$$

$$V_{out} = -i_c R_C \quad (r_o \gg R_C, R_L \gg R_C)$$
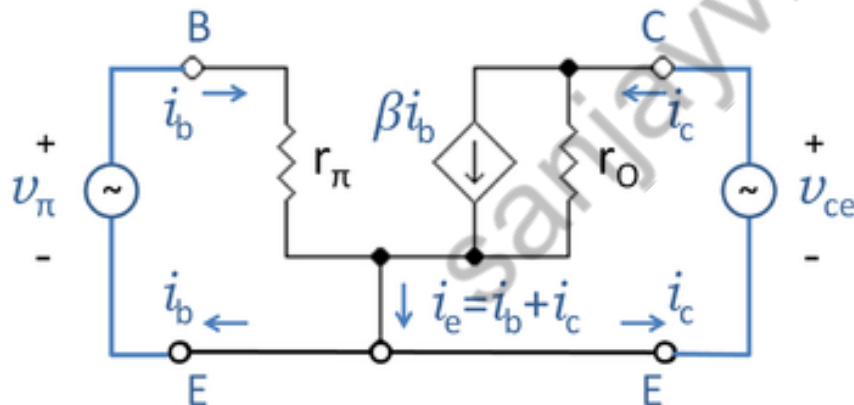
$$\text{Gain} = -\frac{\beta R_C}{r_\pi}$$



Common-Emitter Configuration

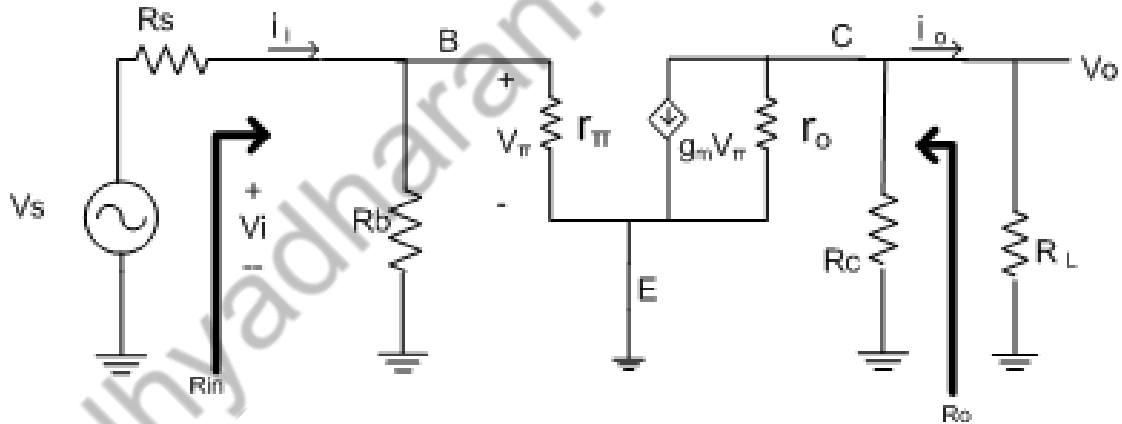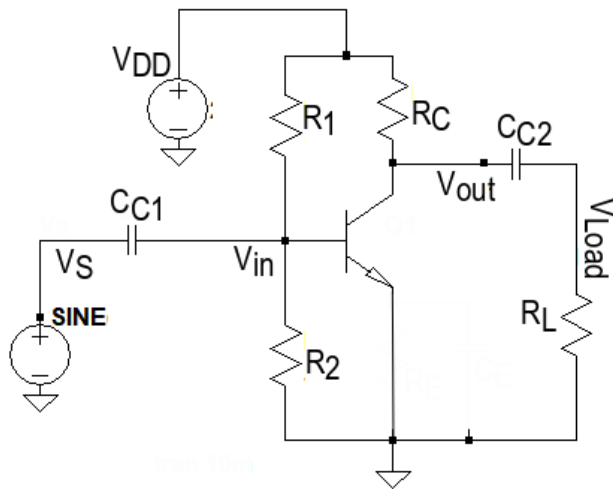

Input Resistance $h_{ie} = R_b || r_{\pi}$

Output Resistance $h_{oe} = R_C || r_o$

Input Resistance $h_{ie} = r_{\pi} (R_b \gg r_{\pi})$


Voltage Gain $= - \frac{\beta(R_C || r_o || R_L)}{r_{\pi}} \frac{(R_b || r_{\pi})}{(R_b || r_{\pi} + R_S)}$

Current Gain

Power Gain

Common-Emitter Configuration

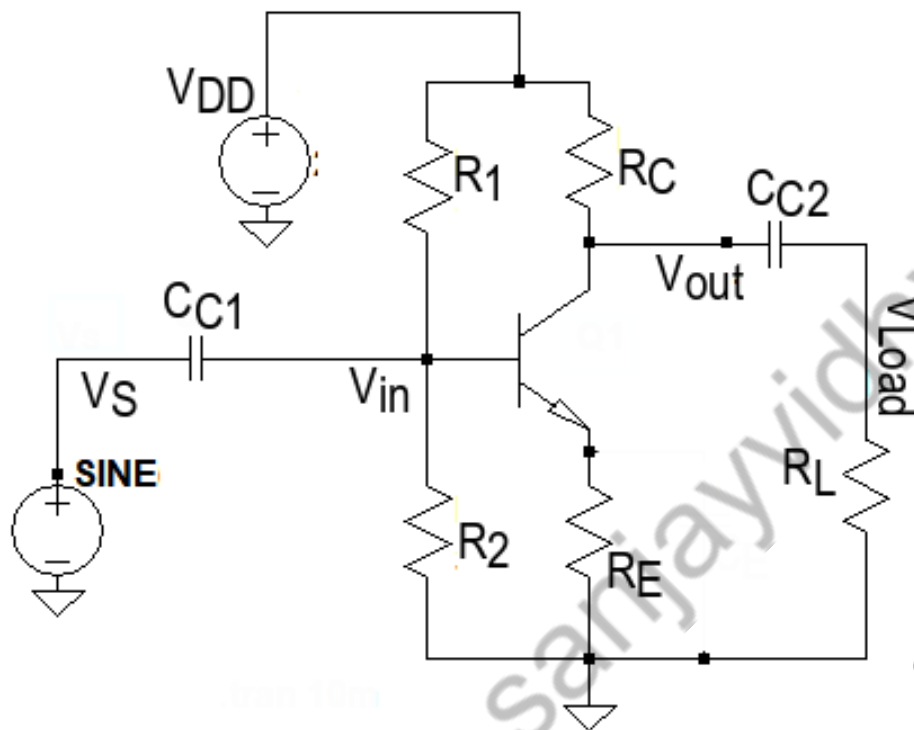Common-Emitter Configuration with Un-Bypassed Emitter Resistance



$$V_{in} = (r_{\pi} * i_b) + (i_e * R_E)$$

$$V_{in} = i_b * (r_{\pi} + (1 + \beta)R_E)$$

$$i_b = V_{in} / (r_{\pi} + (1 + \beta)R_E)$$


$$\text{Voltage Gain} = -R_C / R_E$$

$$\text{Input Resistance} = h_{ie} = r_{\pi} + (1 + \beta)R_E$$

$$\text{Output Resistance } h_{oe} = R_C || (r_o + R_E)$$

Common-Emitter Configuration

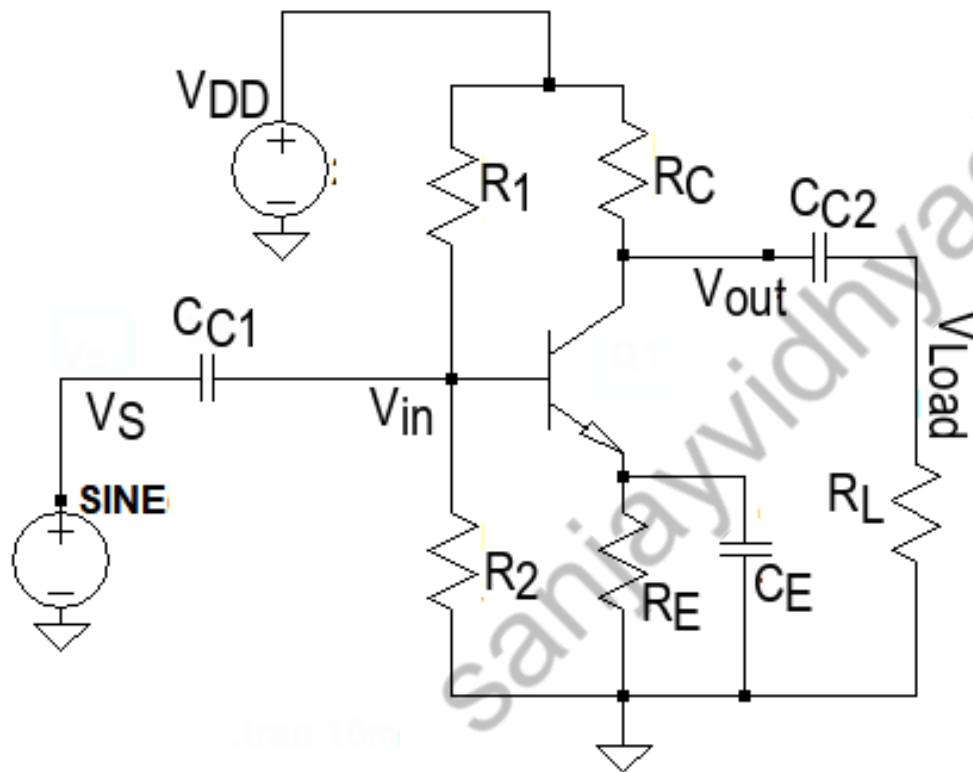Common-Emitter Configuration with Bypassed Emitter Resistance



$$V_{in} = r_{\pi} * i_b$$

$$i_c = \beta * i_b$$

$$V_{out} = -i_c R_C$$

$$\text{Gain} = -\beta R_C / r_{\pi}$$

$$\text{Input Resistance } h_{ie} = R_b || r_{\pi}$$

$$\text{Input Resistance } h_{ie} = r_{\pi} (R_b \gg r_{\pi})$$

$$\text{Voltage Gain} = -\frac{\beta(R_C || r_o || R_L)}{r_{\pi}} \frac{(R_b || r_{\pi})}{(R_b || r_{\pi} + R_S)}$$

$$\text{Output Resistance } h_{oe} = R_C || r_o$$

Current Gain

Power Gain

Common-Emitter Configuration

Design of Amplifier



24 V, 35 AH Battery



Microphone (10 mV)




Speakers (8 Ohms) 1 V p-p
Gain 100



Audio Amplifier

Common-Emitter Configuration

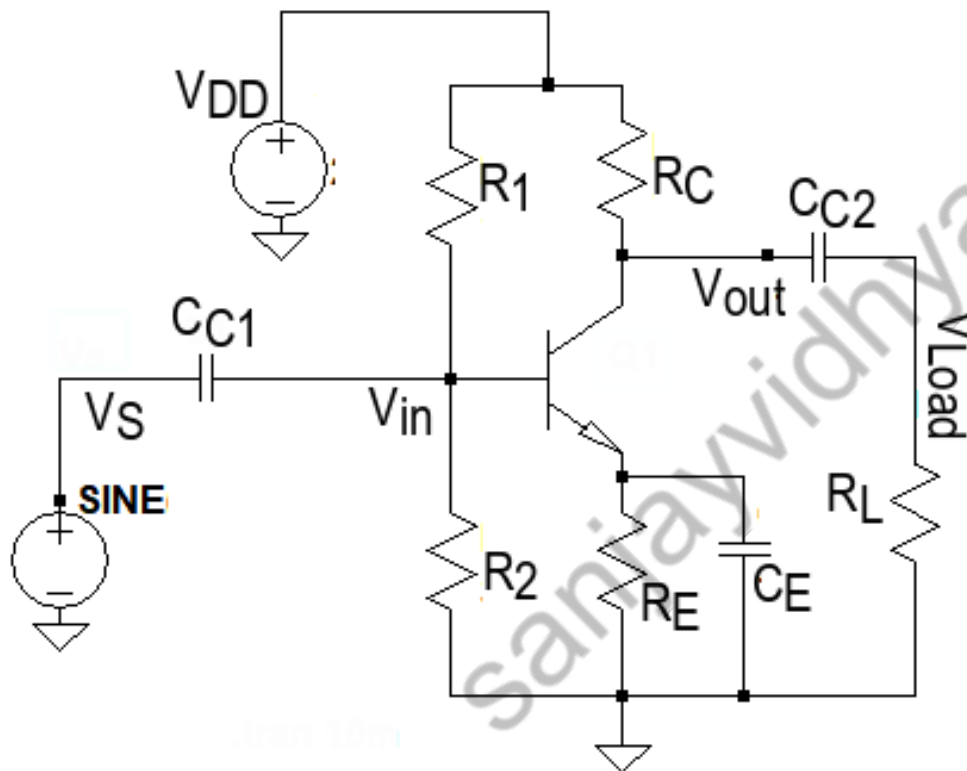

$$R_C = \frac{24 - (2.4 + 0.2)}{2 \times 1 \text{mA}} \approx 10 \text{ K}$$


$$R_E = \frac{2.4}{2 \times 1 \text{mA}} \approx 2.2 \text{ K}$$

$$V_{BB} \approx 3.1 \text{ V}$$

$$R_2 = \frac{3.1 \times 50}{10 \times 1 \text{mA}} \approx 15 \text{ K}$$

$$R_1 = \frac{21 \times 50}{10 \times 1 \text{mA}} \approx 220 \text{ K}$$

Common-Emitter Configuration

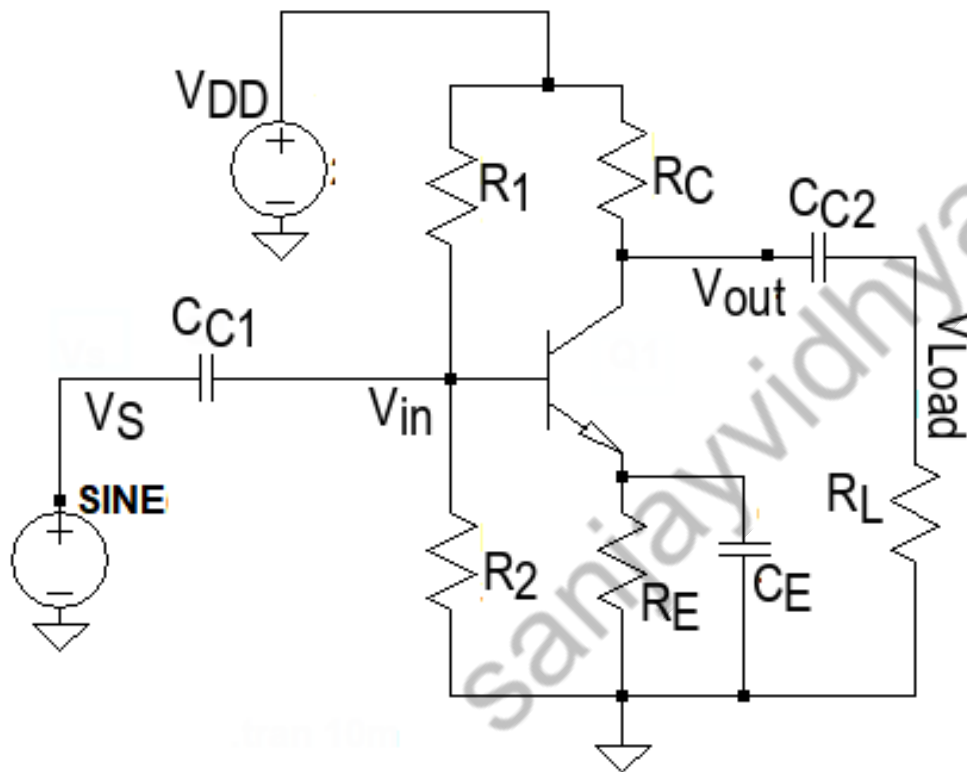

$$R_C = \frac{24 - (2.4 + 0.2)}{2 \times 1 \text{mA}} \approx 10 \text{ K}$$

$$R_E = \frac{2.4}{1 \text{mA}} \approx 2.2 \text{ K}$$



$$V_{BB} \approx 3.1 \text{ V}$$

$$R_2 = \frac{3.1 \times 50}{10 \times 1 \text{mA}} \approx 15 \text{ K}$$

$$R_1 = \frac{21 \times 50}{10 \times 1 \text{mA}} \approx 120 \text{ K}$$

Common-Emitter Configuration

Design of Amplifier

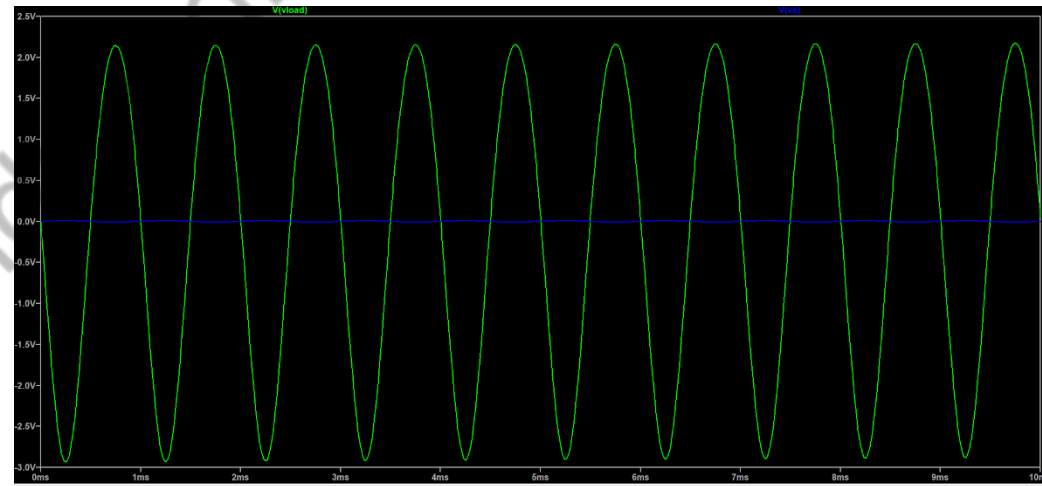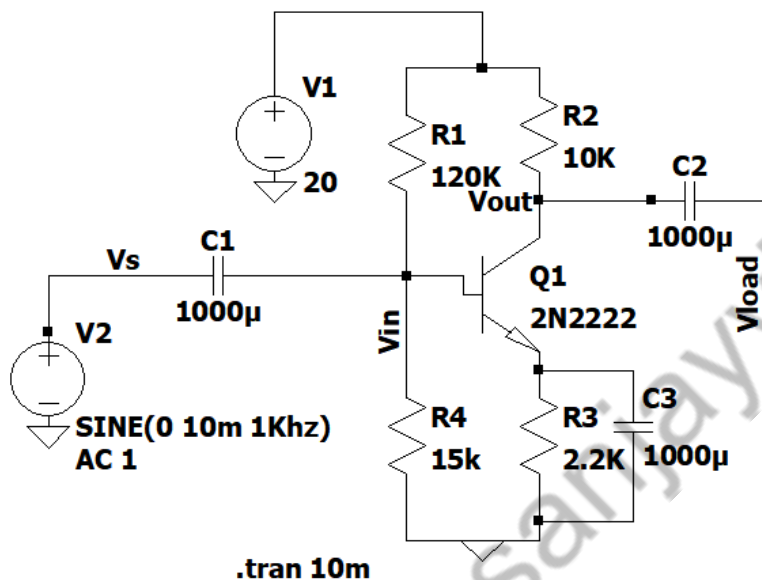

$$Gain = -\beta R_C / r_{\pi}$$

Thank you

sanjayvidhyadharan.in