



# **Electrical Science: 2021-22**

## **Lecture 2**

# **Basic Electrical Quantities and Resistance**

**By Dr. Sanjay Vidhyadharan**

sanjayvidhyadharan.in

# Basic Electrical Quantities

- **Four quantities?**

- Charge (C)
- Current (Amps)
- Voltage (Volts)
- Power (Watt)

- **Charge**

- Unit?
  - Coulomb (C)
  - SI unit
  - $q = -1.6 \times 10^{-19} \text{ C}$
  - How many electrons with 1C charge?
  - $1 \text{ C} = 1/1.6 \times 10^{-19}$  electrons
  - $6.25 \times 10^{18}$  electrons
- Charge of an electron?C

# Basic Electrical Quantities

- Current

- Time rate of change of electric charge
- $I = dq/dt$
- Unit ?
  - Ampere (SI)
- 1 Amp = 1 Coulomb/sec
- Types of current?
  - DC current
    - batteries
  - AC current
    - household current which varies with time

# Basic Electrical Quantities

- **Voltage**



- Energy required to move a unit charge through an element
- Electromotive force or potential
- Unit ?
  - Volt

- **Power**


- $P = I \times V$
- Unit?
  - Watt
- 1 Watt = 1 Volt·Amp = 1 Joule/sec
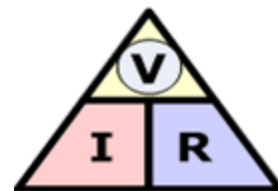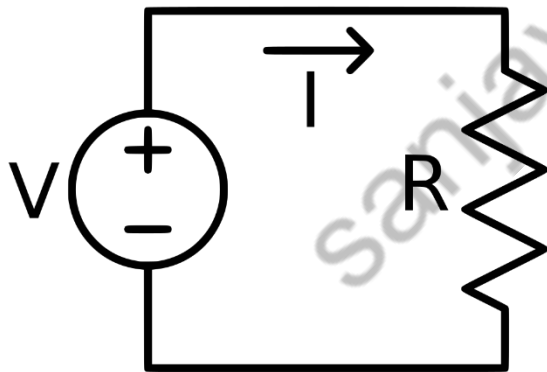
# Resistors


- *Resistance* - The capacity of a material to impede flow of electric charge.
- The circuit element used to model this behavior is *resistor*.
- Resistance is measured in Ohms ( $\Omega$ )



$$\textcircled{V} = I \times R$$

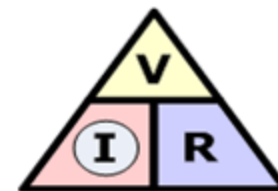

$$\textcircled{I} = \frac{V}{R}$$


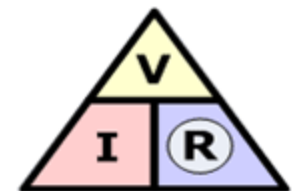


$$\textcircled{R} = \frac{V}{I}$$


Ohms Law
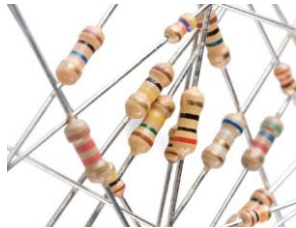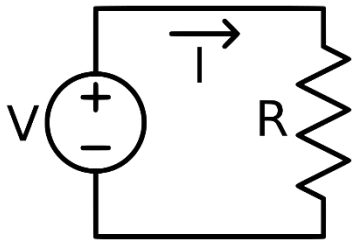
# Resistors


- Power Dissipated as heat  $P = VI = V^2/R = I^2R$



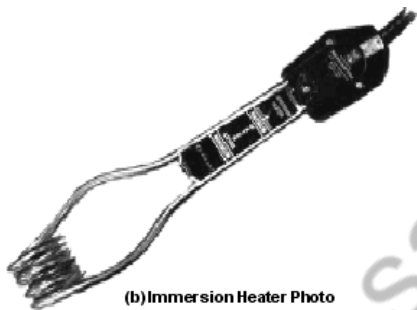
- Real-world devices that are modeled by resistors:
  - heating elements (stoves, heaters, etc.)
  - long wires
- Conductance  $G = 1/R$  mho



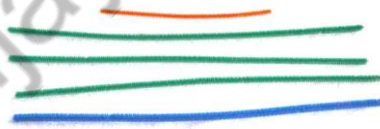(b) Immersion Heater Photo  
Fig. 3.4: Immersion Heater



# Resistors

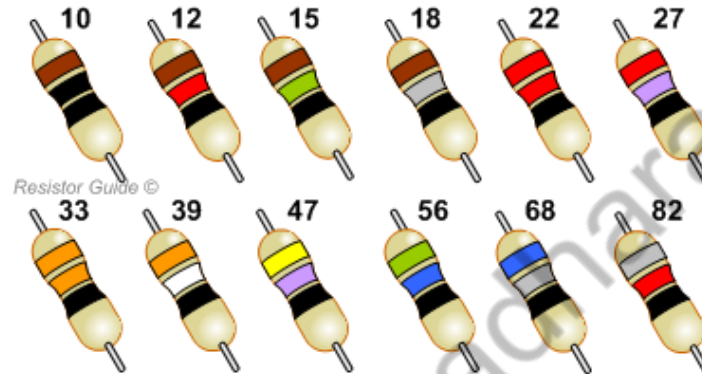

In 1952, the IEC (International Electrotechnical Commission) decided to define the resistance and tolerance values into a norm, to ease the mass manufacturing of resistors. These are referred to as "preferred values" or "E-series", and they are published in standard IEC 60063:1963.

very decade (0.1-1.0, 1-10, 10-100, etc.) is divided in 12 steps on a logarithmic scale.

The size of every step is equal to:  $10^{(1/12)} = 1.21$

# Resistors

Color	Value	Multiplier	Tolerance
Black	0	$\times 10^0$	$\pm 20\%$
Brown	1	$\times 10^1$	$\pm 1\%$
Red	2	$\times 10^2$	$\pm 2\%$
Orange	3	$\times 10^3$	$\pm 3\%$
Yellow	4	$\times 10^4$	- 0, + 100%
Green	5	$\times 10^5$	$\pm 0.5\%$
Blue	6	$\times 10^6$	$\pm 0.25\%$
Violet	7	$\times 10^7$	$\pm 0.10\%$
Gray	8	$\times 10^8$	$\pm 0.05\%$
White	9	$\times 10^9$	$\pm 10\%$
Gold	-	$\times 10^{-1}$	$\pm 5\%$
Silver	-	$\times 10^{-2}$	$\pm 10\%$

**4-band resistor**



**270 ohms  $\pm 5\%$**



**5-band resistor**



**100k ohms  $\pm 1\%$**



# Resistors

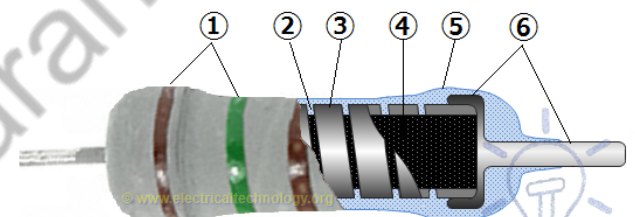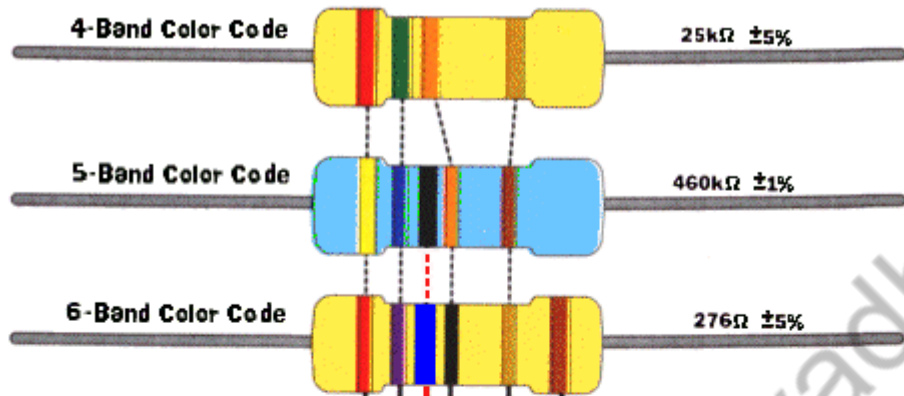


- ① Color Codes / Bands
- ② Helixing
- ③ Film
- ④ Substrates
- ⑤ Insulation
- ⑥ Terminations / Leads

## Carbon Film Resistors

1st Digit	2nd Digit	3rd Digit	Multiplier	Tolerance	Temperature Coefficient
0	0	0	0.01 Silver	±10% Silver	100ppm
1	1	1	0.1 Gold	±5% Gold	50ppm
2	2	2	1	±1%	15ppm
3	3	3	10	±2%	25ppm
4	4	4	100		
5	5	5	1k		
6	6	6	10k	±0.5%	
7	7	7	100k	±0.25%	
8	8	8	1M	±0.1%	
9	9	9	10M		

The temperature coefficient (ppm/K)

# Resistors

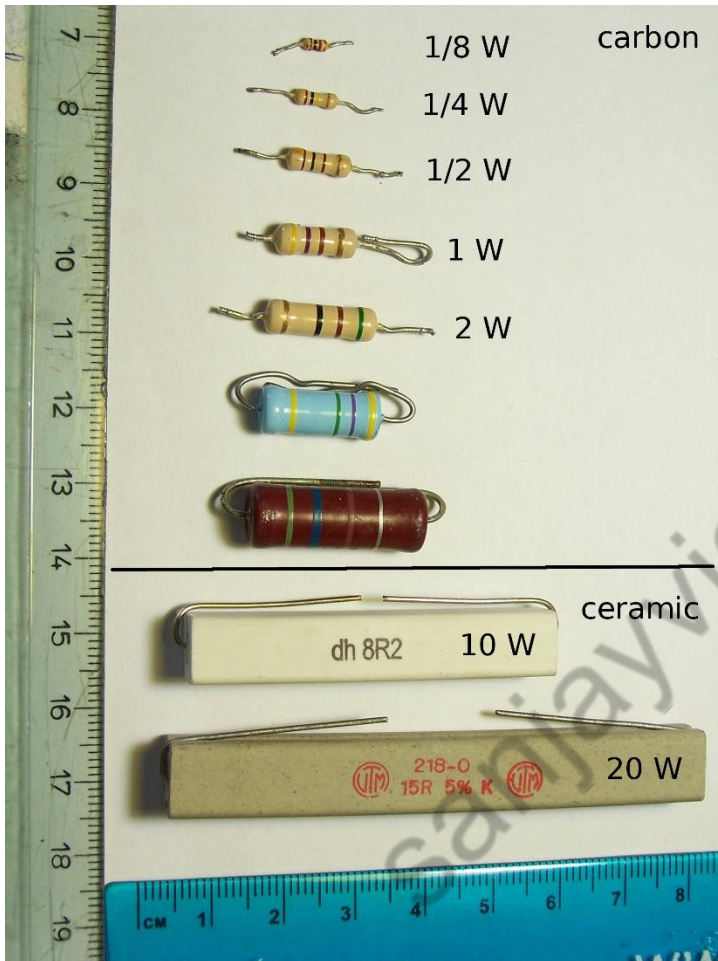


# Resistors

- Potentiometers



# Resistors

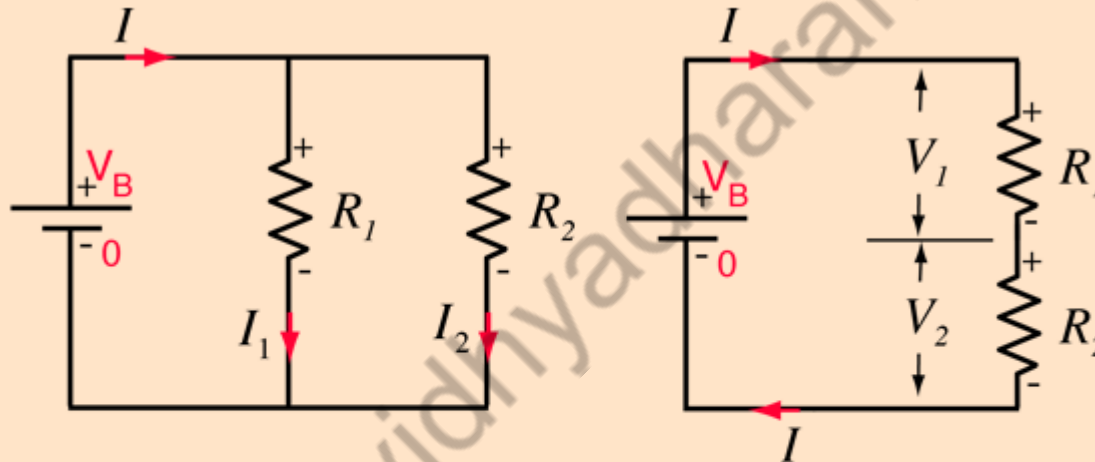

Parallel resistors


$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Series resistors

$$R_{equivalent} = R_1 + R_2$$


# Star and Delta Connections

## Star Connection (Y Or WYE)

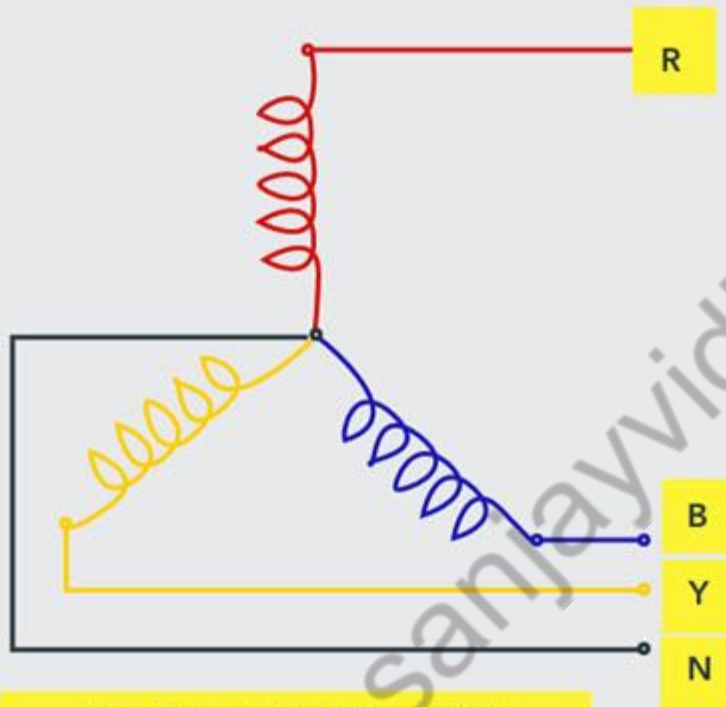


Star Connection (Y or WYE)

## Delta Connection ( $\Delta$ )

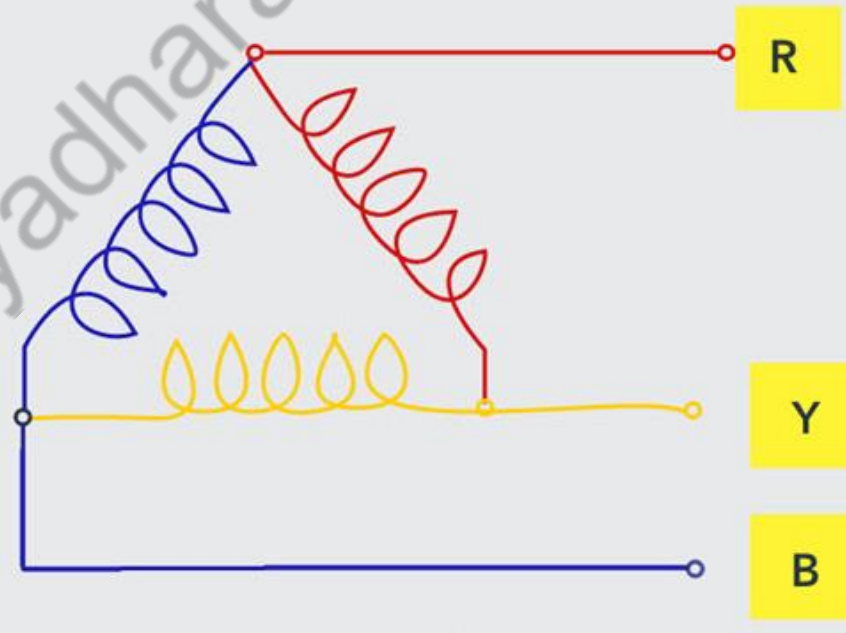

# Star and Delta Connections

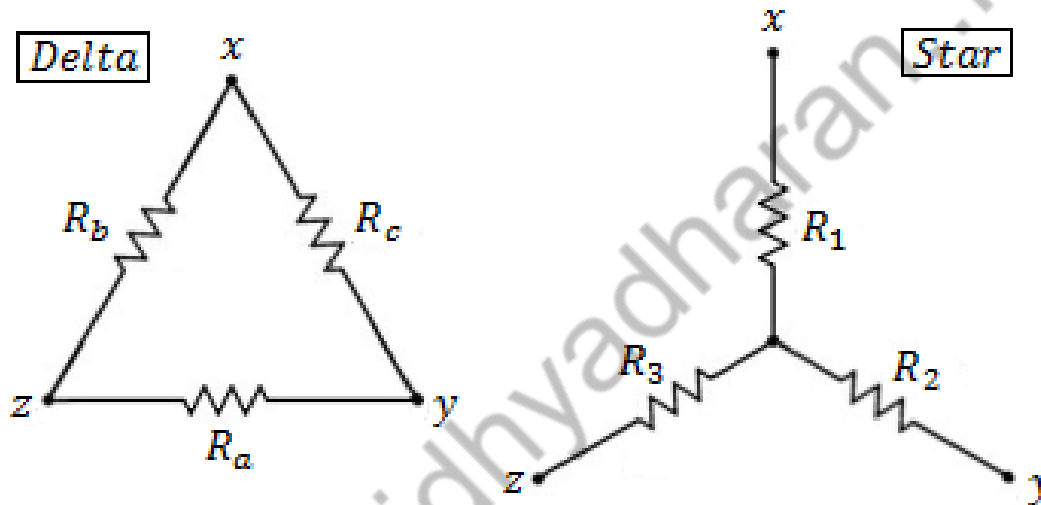

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

# Resistors

- Applications


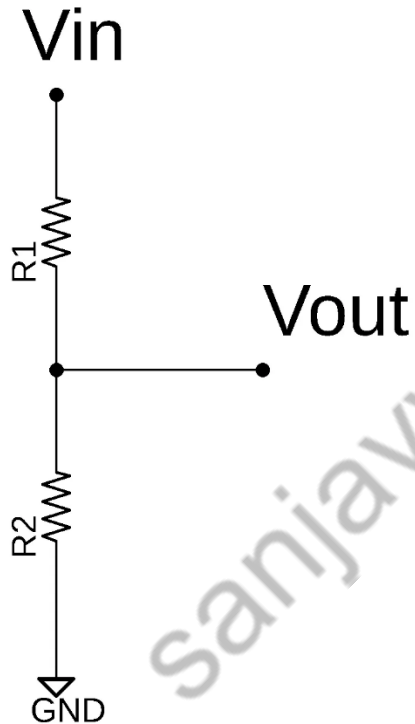


Voltage/Potential Divider

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

# Resistors

- Applications

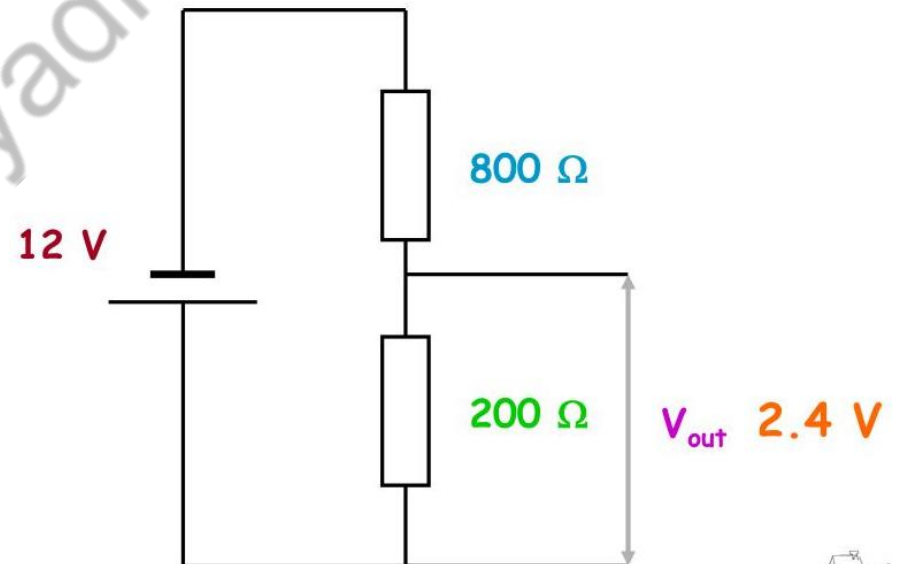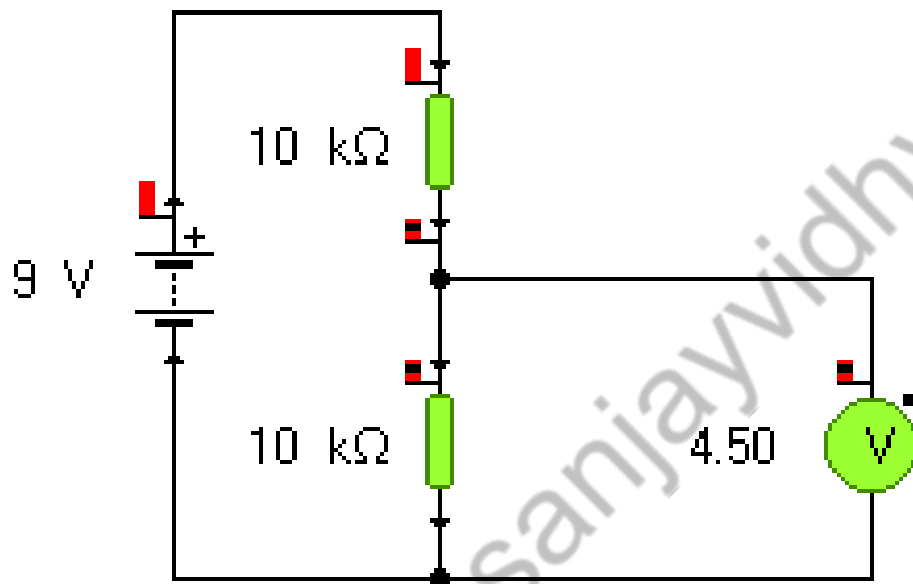





# Resistors

- Applications

**OPEN CIRCUIT BEHAVIOR**

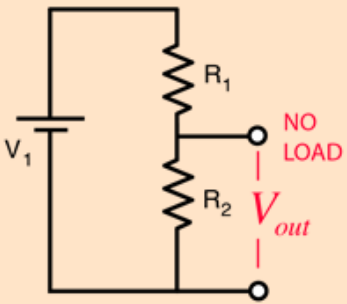

**BEHAVIOR UNDER LOAD**

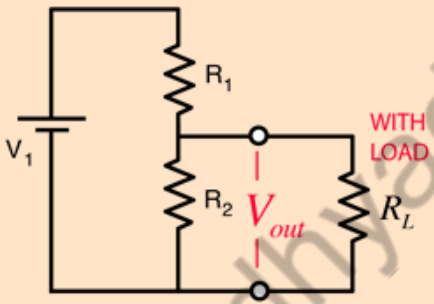

$$V_{out} = V_1 \frac{IR_2}{I(R_1 + R_2)} = \frac{V_1 R_2}{(R_1 + R_2)}$$

OUTPUT VOLTAGE UNDER "NO LOAD" CONDITION (open circuit)

**OUTPUT VOLTAGE UNDER LOAD**


$$V_{out} = V_1 \frac{IR_2}{I(R_1 + R_2)} = \frac{V_1 (R_2 \parallel R_L)}{(R_1 + R_2 \parallel R_L)}$$

Voltage division concept is used in making radios, amplifiers and electronic devices for adjusting signal levels.




# Resistors

- Applications

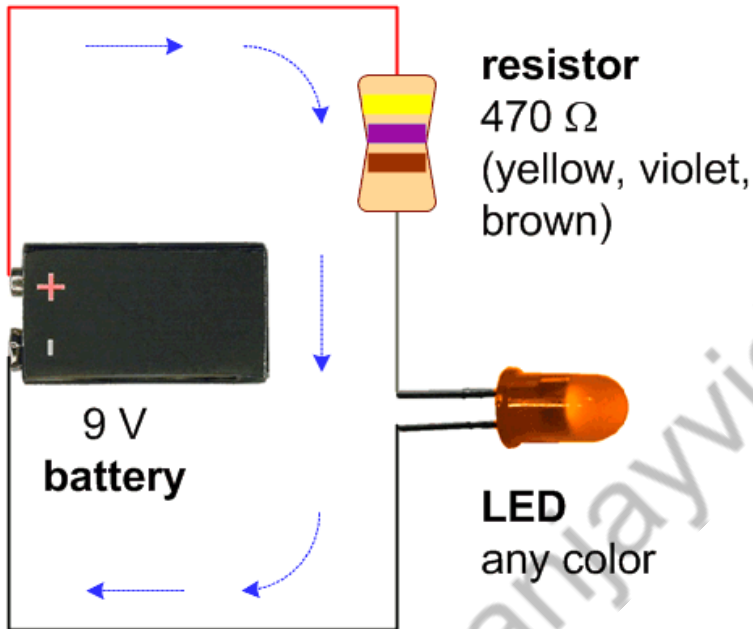



3mm Round LEDs (Water Clear)		Forward voltage		Dominant wavelength		Luminous Intensity		Viewing angle
Part number	Emitting Color	(V) IF=20mA		IF=20mA		(mcd) IF=20mA		
		TYP	MAX	MIN	MAX	TYP	MAX	(degree)
LED-WR3MMR	Red	1.8	2.3	620	640	2000	3000	20-30
LED-WR3MMY	Yellow	1.8	2.3	585	595	2000	3000	20-30
LED-WR3MMB	Blue	3.2	3.4	465	475	3000	5000	20-30
LED-WR3MMG	Green	3.2	3.4	520	530	8000	9000	20-30
LED-WR3MMW	White	3.2	3.4	/	/	8000	9000	20-30

$$R = \frac{9 - 1.8}{.02} = 360$$

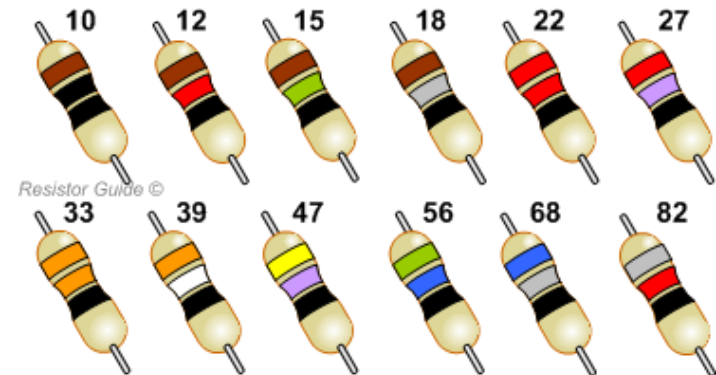


# Resistors

- Applications

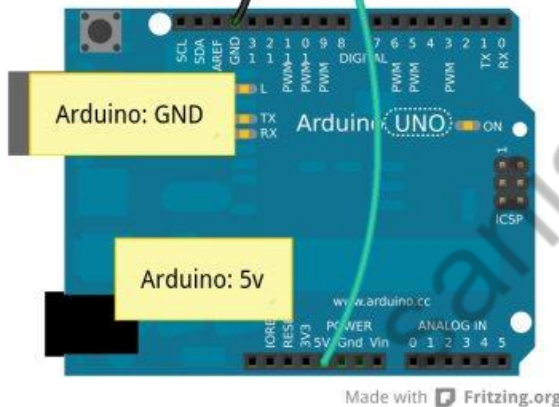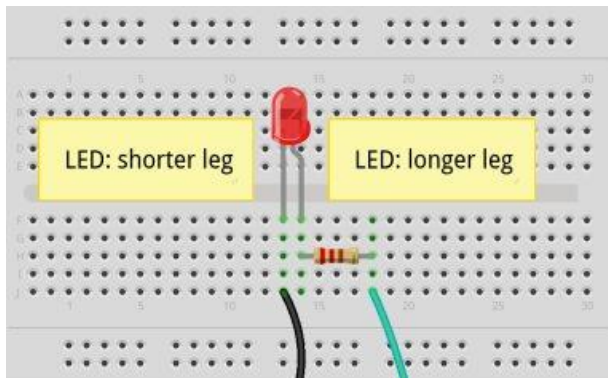

3mm Round LEDs (Water Clear)		Forward voltage		Dominant wavelength		Luminous Intensity		Viewing angle
Part number	Emitting Color	(V) IF=20mA		IF=20mA		(mcd) IF=20mA		
		TYP	MAX	MIN	MAX	TYP	MAX	(degree)
LED-WR3MMR	Red	1.8	2.3	620	640	2000	3000	20-30
LED-WR3MMY	Yellow	1.8	2.3	585	595	2000	3000	20-30
LED-WR3MMB	Blue	3.2	3.4	465	475	3000	5000	20-30
LED-WR3MMG	Green	3.2	3.4	520	530	8000	9000	20-30
LED-WR3MMW	White	3.2	3.4	/	/	8000	9000	20-30

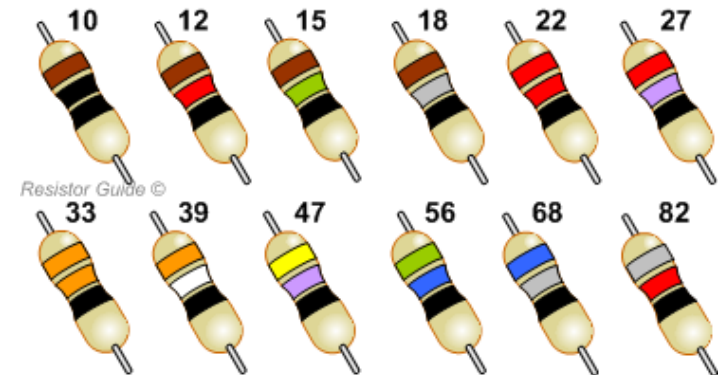

$$R = \frac{5-1.8}{.02} = 160$$

**Thank you**

sanjayvidhyadharam.in