



# **Electrical Science: 2021-22**

## **Lecture 7**

### **Superposition Theorem**

**By Dr. Sanjay Vidhyadharan**

sanjayvidhyadharan.in


# Superposition Theorem

## Applications of Superposition Theorem

- Helps in analyzing a linear circuit with more than one independent source.
- It is used to find the value of voltage/current through a particular element of circuit
- Contribution by each independent source is computed separately.
- The output of a circuit is determined by summing the individual responses of each independent source.
- The idea of superposition rests on the linearity property (specifically, additivity)

# Superposition Theorem

LINEARITY – ADDITIVE PROPERTY

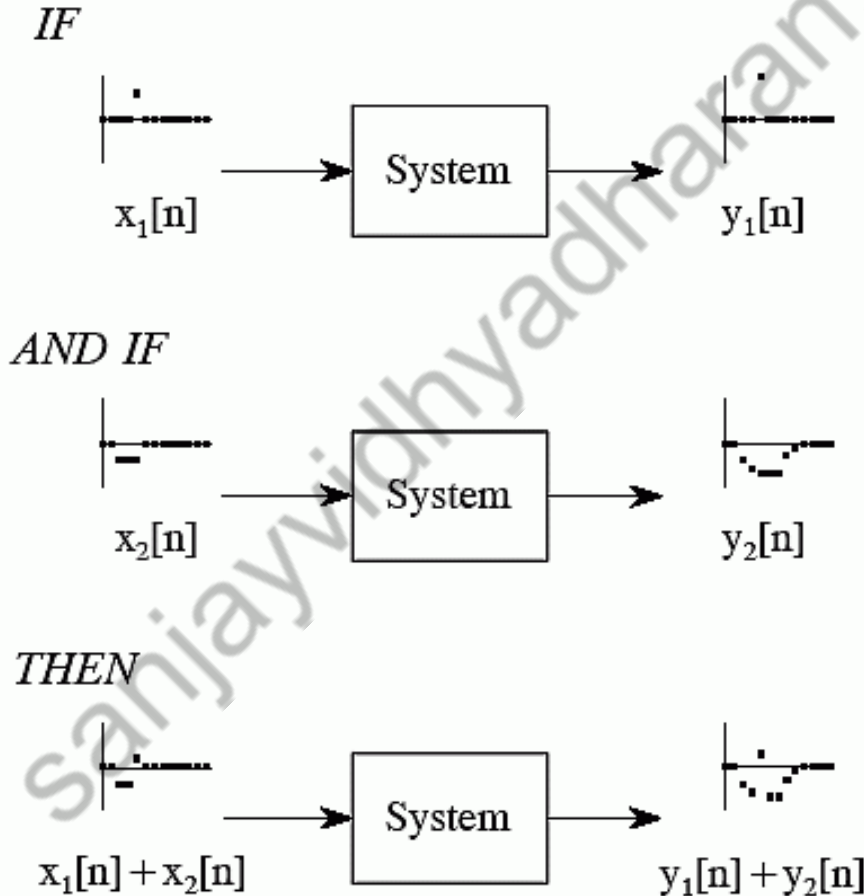

# Superposition Theorem

## LINEARITY – ADDITIVE PROPERTY

Example: Ohm's Law

Voltage (output) developed across a resistor in response to applied current (input)

$$V_1 = i_1 R \text{ (for applied current } i_1 \text{ )}$$

and

$$V_2 = i_2 R \text{ (for applied current } i_2 \text{ )}$$

Then applying current  $(i_1 + i_2)$  gives

$$V = (i_1 + i_2)R = i_1 R + i_2 R = V_1 + V_2$$

# Superposition Theorem


In any **linear bilateral network** containing two or more independent sources (voltage and/or current sources), the resultant current / voltage in any branch is the algebraic sum of currents / voltages caused by each independent source (with all other independent sources turned off).

sanjayvihar@yahoo.com.in

# Superposition Theorem


## Rules for Applying Superposition Theorem

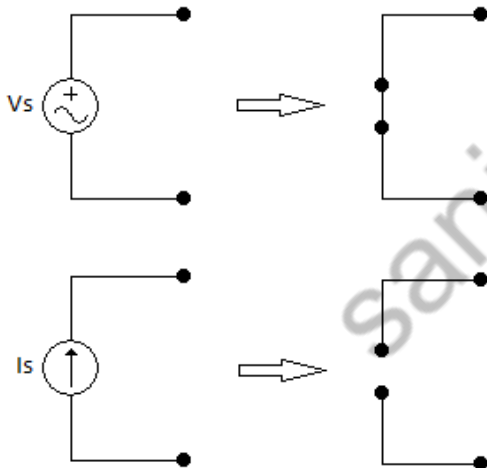1. To turn off a voltage source: Replace by its **internal resistance** (for non-ideal source) or short circuit (for ideal source).
2. To turn off a current source: Replace by its **internal resistance** (for non-ideal source) or open circuit (for ideal source).
3. Dependent sources should be retained as it is.





# Superposition Theorem

Find  $V$  in the circuit given below:

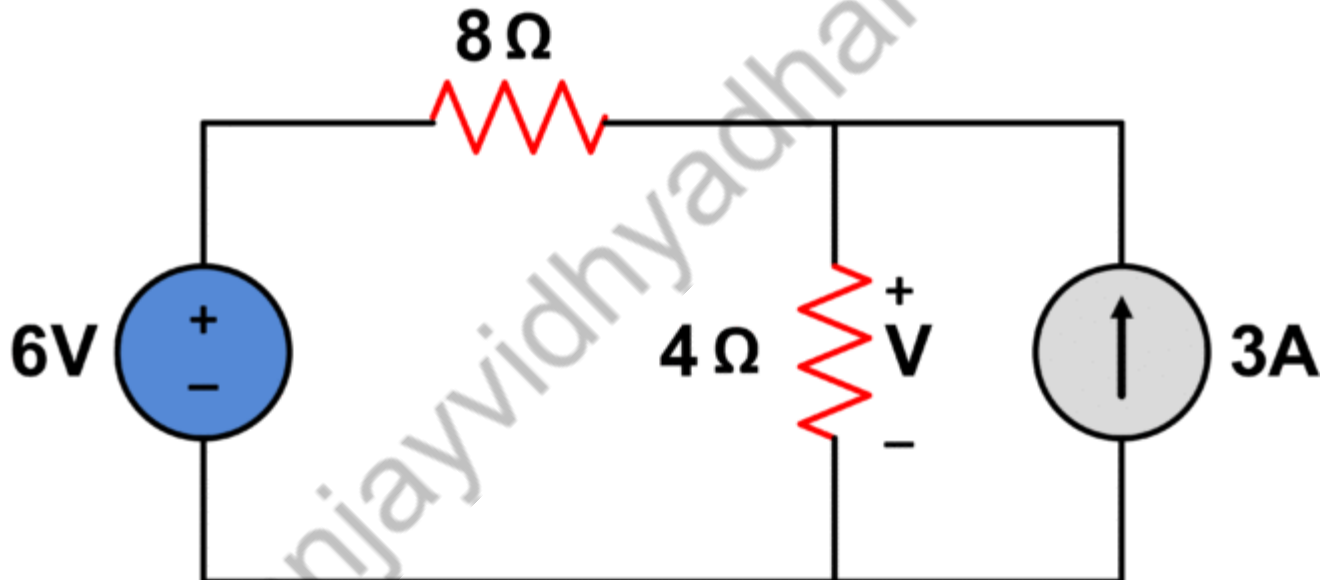


# Superposition Theorem

Find  $V$  in the circuit given below:

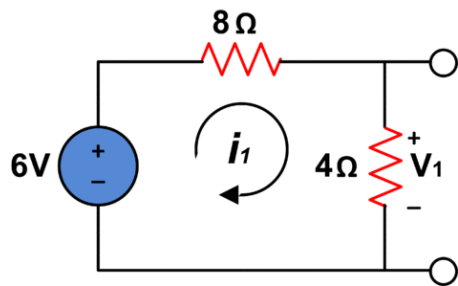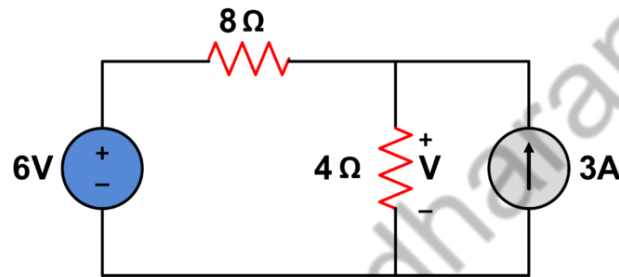

$$V_1 = \left(\frac{4}{8+4}\right) 6 = 2 \text{ V}$$
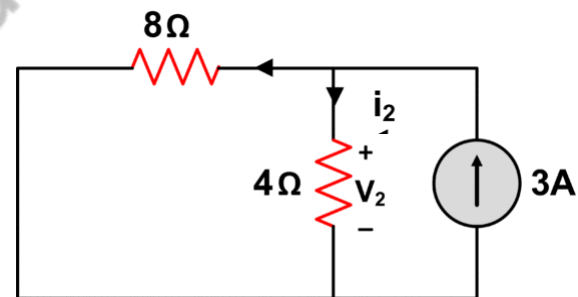
$$i_1 = \left(\frac{6}{12}\right) = 0.5 \text{ A}$$



$$i_2 = \left(\frac{8}{8+4}\right) 3 = 2 \text{ A}$$

$$V_2 = 2 * 4 = 8 \text{ V}$$


$$V = 2 + 8 = 10 \text{ V}$$

$$i = 0.5 + 2 = 2.5 \text{ A}$$



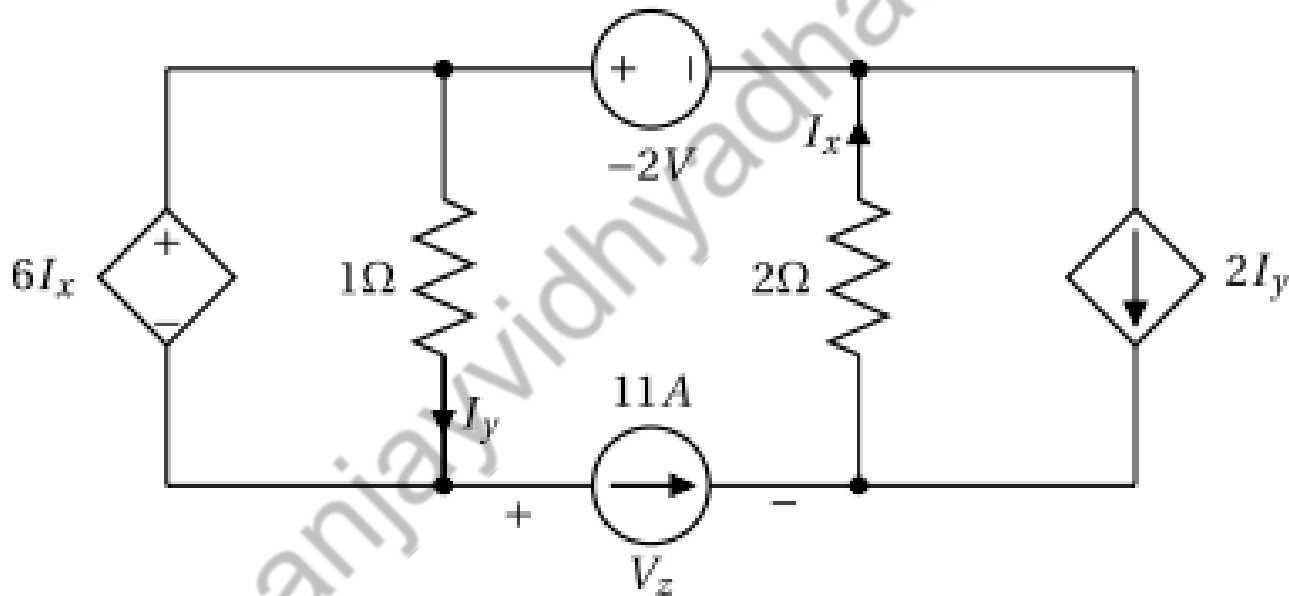
# Superposition Theorem

Find  $I_x$ ,  $I_y$  and  $V_z$  in the circuit given below:


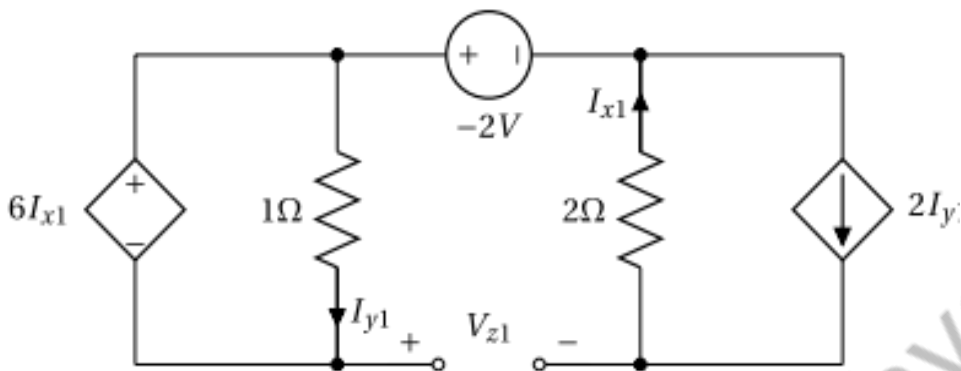
# Superposition Theorem

Find  $I_x$ ,  $I_y$  and  $V_z$  in the circuit given below:




$$6I_{x1} = I_{y1}$$

$$I_{x1} = I_{y1} = 0$$

$$V_{z1} = -2 \text{ V}$$

$$I_{x1} = 2I_{y1}$$

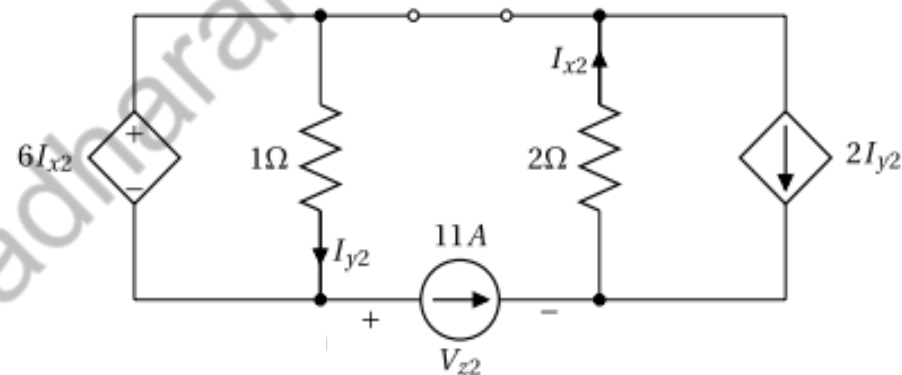

$$\begin{cases} 6I_{x2} = I_{y2} \\ I_{x2} - 2I_{y2} = 11 \end{cases} \rightarrow \begin{cases} I_{x2} = -1 \text{ A} \\ I_{y2} = -6 \text{ A} \end{cases}$$

$$+2\Omega \times I_{x2} + 1\Omega \times I_{y2} + V_{z2} = 0 \rightarrow V_{z2} = 8 \text{ V}$$

$$I_x = I_{x1} + I_{x2} = -1 \text{ A}$$

$$I_y = I_{y1} + I_{y2} = -6 \text{ A}$$

$$V_z = V_{z1} + V_{z2} = 6 \text{ V}$$


# Superposition Theorem

## Limitations of Superposition Theorem


- Applicable only for linear circuits.
- There must be more than one source to apply this theorem

sanjayvidhyadarshan.in

# Superposition Theorem

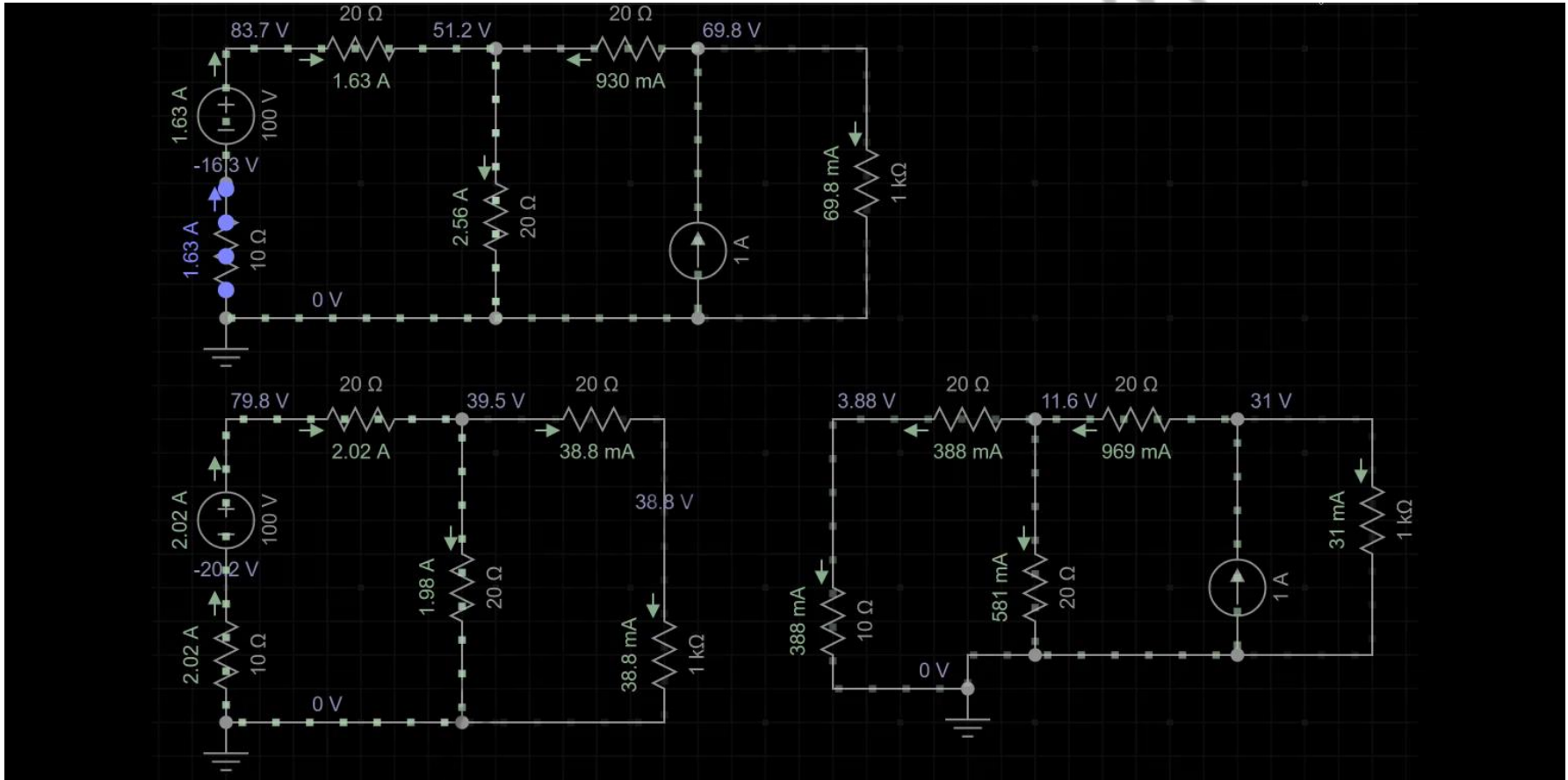

# Superposition Theorem

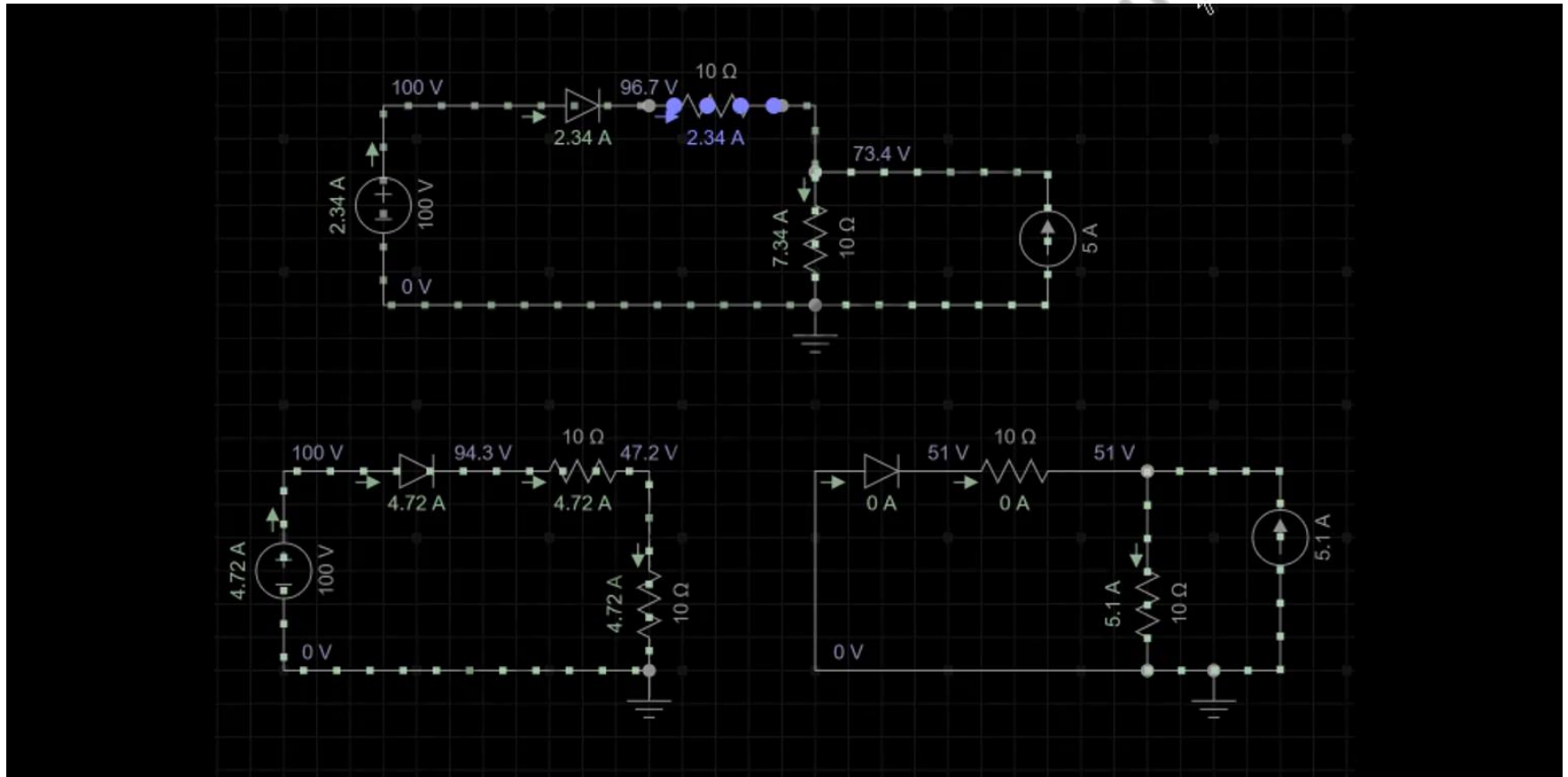

**Thank you**

sanjayvidhyadharan.in