



# **Electrical Science: 2021-22**

## **Tutorial 5**

### **Second Order Circuits**

**By Dr. Sanjay Vidhyadharan**

sanjayvidhyadharan

# Problem 1

1. The Switch is kept at position 1 for a long time and toggled to position 2 at  $t=0$ .  $R=40\ \Omega$ ,  $L=4\ \text{H}$ , and  $C=1/4\ \text{F}$ . Calculate the characteristic roots of the circuit. Is the circuit overdamped, underdamped, or critically damped?

$$R=40\ \Omega, L=4\ \text{H}, C=1/4\ \text{F} \Rightarrow \alpha = \frac{R}{2L} = 5; \omega_0 = \frac{1}{\sqrt{LC}} = 1$$



$$\text{The roots are, } s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -5 + \sqrt{5^2 - 1}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -5 - \sqrt{5^2 - 1}$$

$$y(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


( $A_1$  and  $A_2$  are arbitrary constants and are determined from the initial conditions)

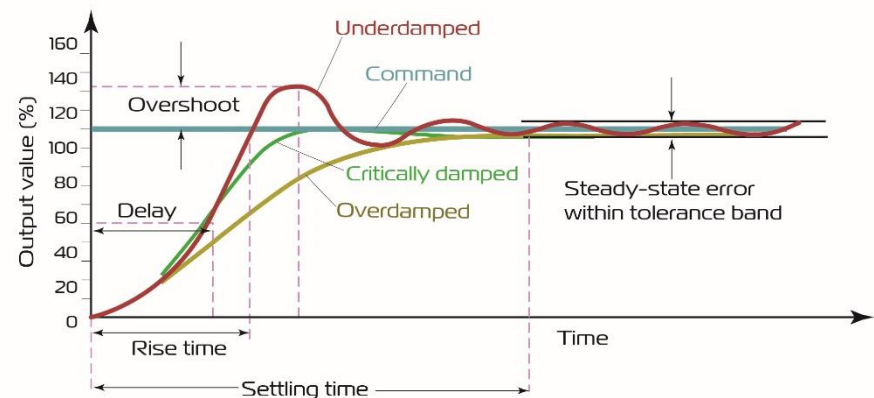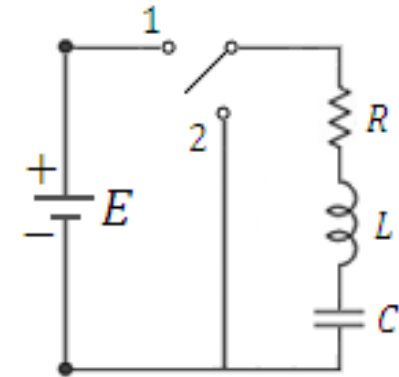Since  $\alpha > \omega_0$ , we conclude that the response is *overdamped*.




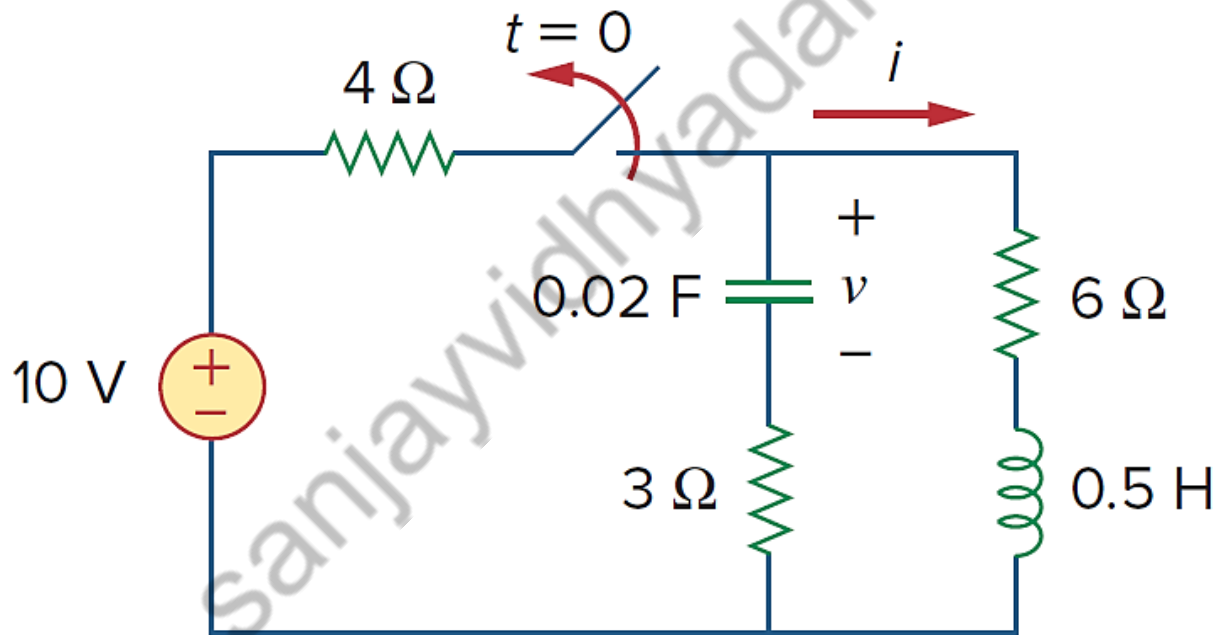
## Problem 2

Find  $i(t)$  for  $t > 0$ . Assume that the circuit has reached steady state before the switch is opened.


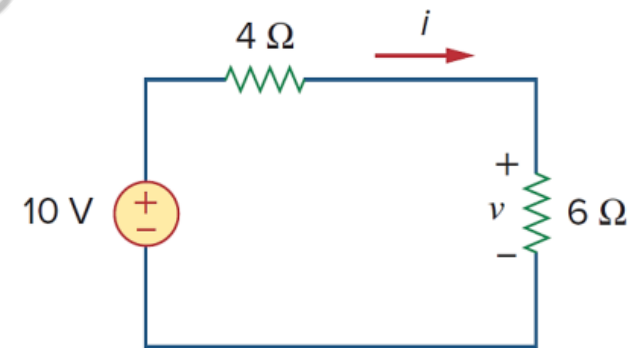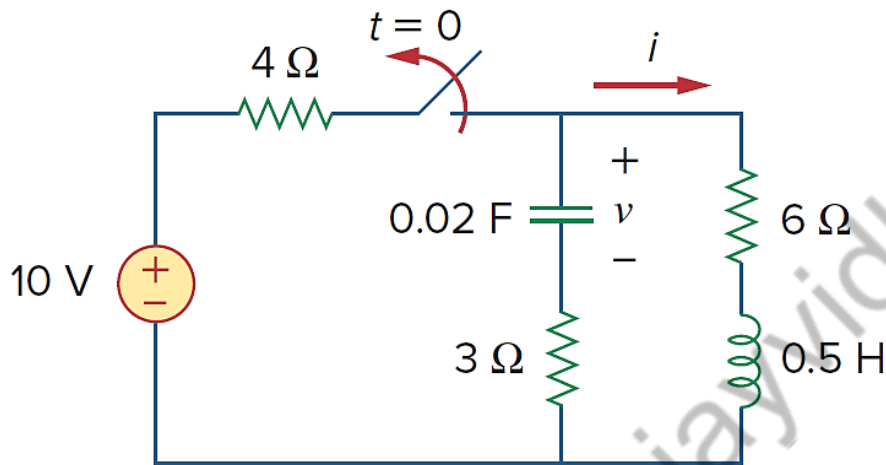
# Problem 2

Find  $i(t)$  for  $t > 0$ . Assume that the circuit has reached steady state before the switch is opened.





(a) for  $t < 0$

$$i(0) = \frac{10}{4+6} = 1\text{A}; \quad v(0) = 6i(0) = 6\text{V}$$
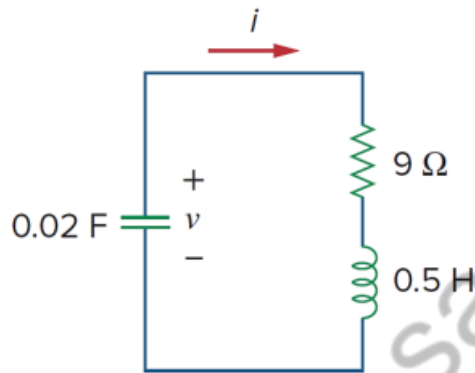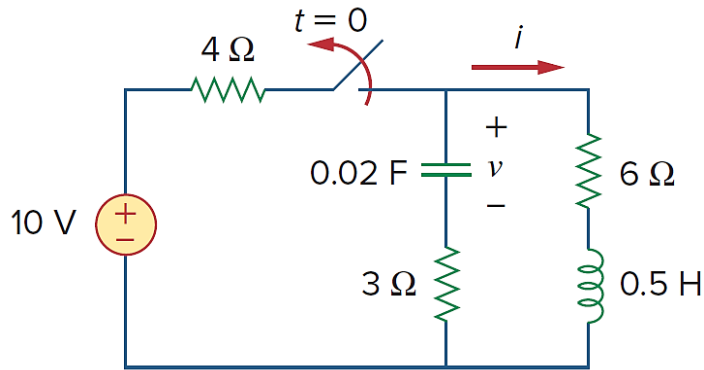
# Problem 2

Find  $i(t)$  for  $t > 0$ . Assume that the circuit has reached steady state before the switch is opened.



(b) for  $t > 0$ .


$$\alpha = \frac{R}{2L} = 9; \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10$$

$$s_1 = -9 + \sqrt{9^2 - 100}$$

$$s_2 = -9 - \sqrt{9^2 - 100}$$

Under-damped response  $s_{1,2} = -9 \pm j4.359$

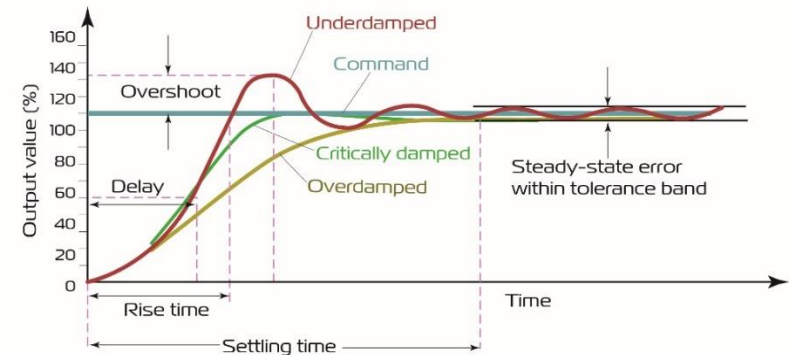Hence,  $i(t) = e^{-9t} [A_1 (\cos 4.359t) + A_2 (\sin 4.359t)]$



# Problem 2

Find  $i(t)$  for  $t > 0$ . Assume that the circuit has reached steady state before the switch is opened.

$$\text{Hence, } i(t) = e^{-9t} [A_1(\cos 4.359t) + A_2(\sin 4.359t)]$$


$A_1$  and  $A_2$  are found using the initial conditions.

$$\text{At } t = 0, i(0) = 1 = A_1$$

$$\left. \frac{di}{dt} \right|_{t=0} = -\frac{1}{L} [Ri(0) - v(0)] = -6 \text{ A/s}$$

Taking the derivative of  $i(t)$
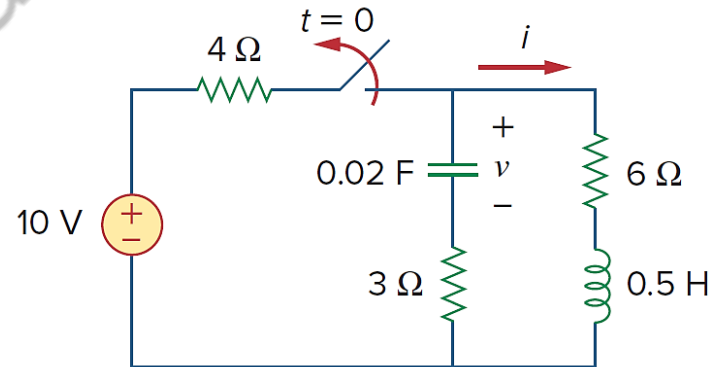
$$\begin{aligned} \frac{di}{dt} &= -9e^{-9t} [A_1(\cos 4.359t) + A_2(\sin 4.359t)] \\ &\quad + e^{-9t} (4.359) [-A_1(\sin 4.359t) + A_2(\cos 4.359t)] \end{aligned}$$



# Problem 2


Find  $i(t)$  for  $t > 0$ . Assume that the circuit has reached steady state before the switch is opened.

$$-6 = -9(A_1 + 0) + 4.359(-0 + A_2)$$

substituting  $A_1 = 1$ ,

$$-6 = -9 + 4.359A_2$$

$$\Rightarrow A_2 = 0.6882$$

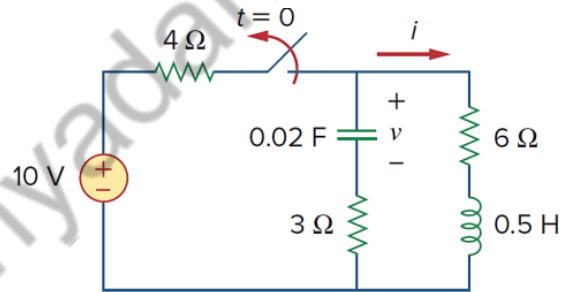

Substituting the values of  $A_1$  and  $A_2$  yields the complete solution as,

$$i(t) = e^{-9t}[(\cos 4.359t) + 0.6882(\sin 4.359t)] \text{ A} \quad \text{for } t > 0$$

# Problem 3

The switch has been closed for a sufficiently long time and then it is opened at (see fig.11.6(a)). Find the expression for (a)  $v(t)$ , (b)  $i_c(t)$ ,  $t > 0$  for  $L = 0.5 \text{ H}$

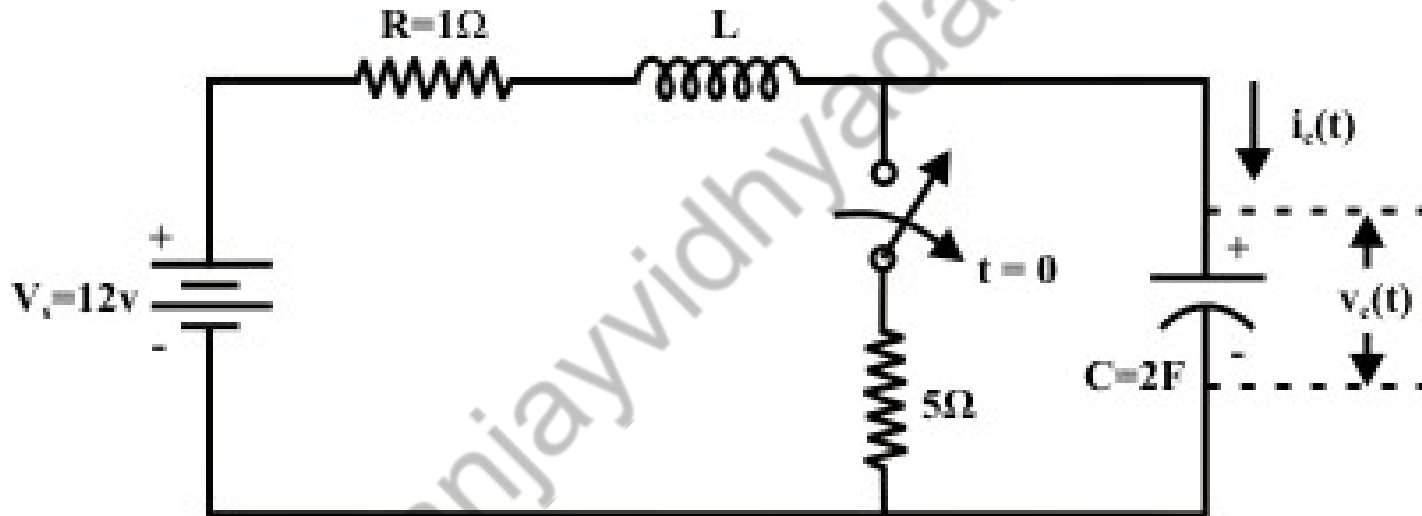


Fig. 11.6(a)



# Problem 3

The switch has been closed for a sufficiently long time and then it is opened at (see fig.11.6(a)). Find the expression for (a)  $v(t)$ , (b)  $i_c(t)$ ,  $t > 0$  for  $L = 0.5 \text{ H}$

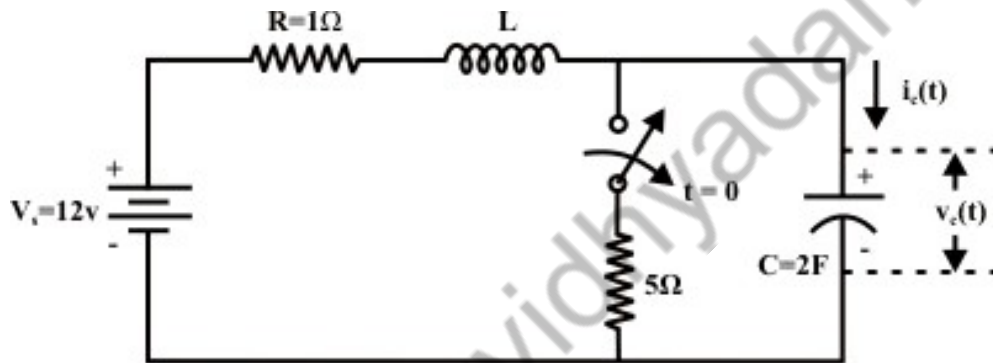


Fig. 11.6(a)

$$i_L(0^+) = i_L(0^-) = \frac{12}{1+5} = 2A$$

$$v_c(0^+) = v_c(0^-) = 10 \text{ volt.}$$

# Problem 3

The switch has been closed for a sufficiently long time and then it is opened at (see fig.11.6(a)). Find the expression for (a)  $v(t)$ , (b)  $i_c(t)$ ,  $t > 0$  for  $L=0.5$  H

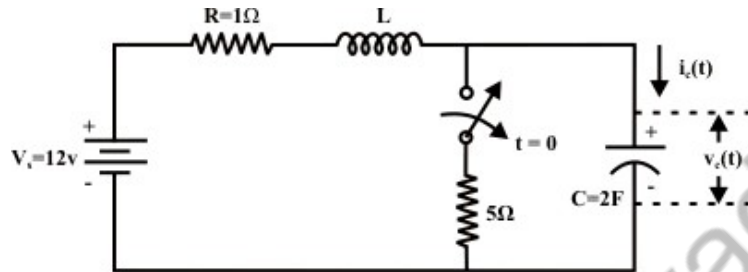


Fig. 11.6(a)

$$i_L(0^+) = i_L(0^-) = \frac{12}{1+5} = 2A$$

$$v_c(0^+) = v_c(0^-) = 10 \text{ volt.}$$

**Case-1:**  $L=0.5H$ ,  $R=1\Omega$  and  $C=2F$

$$V_s = Ri(t) + L \frac{di(t)}{dt} + v_c(t) \Rightarrow V_s = RC \frac{dv_c(t)}{dt} + LC \frac{d^2v_c(t)}{dt^2} + v_c(t)$$

The solution of the above differential equation is given by

$$v_c(t) = v_{cn}(t) + v_{cf}(t)$$

# Problem 3

The switch has been closed for a sufficiently long time and then it is opened at (see fig.11.6(a)). Find the expression for (a)  $v(t)$ , (b)  $i_c(t)$ ,  $t > 0$  for  $L=0.5$  H

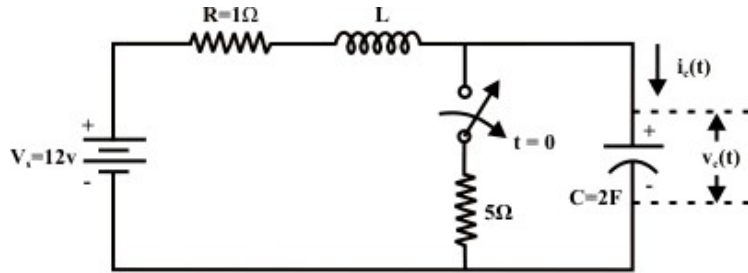


Fig. 11.6(a)

**Case-1:**  $L=0.5H$ ,  $R=1\Omega$  and  $C=2F$

$$\frac{d^2 v_c(t)}{dt^2} + \frac{R}{L} \frac{dv_c(t)}{dt} + \frac{1}{LC} v_c(t) = 0$$

$$\alpha = \frac{R}{2L}; \quad \omega_n = \frac{1}{\sqrt{LC}}$$

$$v_{cn}(t) = (A_1 t + A_2) e^{\alpha t} \quad (\text{where } \alpha = \alpha_1 = \alpha_2 = -1)$$

$$v_c(t) = (A_1 t + A_2) e^{\alpha t} + A$$

$$i_L(0^+) = i_L(0^-) = \frac{12}{1+5} = 2A$$

$$v_c(0^+) = v_c(0^-) = 10 \text{ volt.}$$

At  $t=0^+$ ;

$$v_c(t) \Big|_{t=0^+} = A_2 e^{-1 \times 0} + A = A_2 + A \Rightarrow A_2 + A = 10$$

$$\frac{dv_c(t)}{dt} = \alpha (A_1 t + A_2) e^{\alpha t} + A_1 e^{\alpha t} = -(A_1 t + A_2) e^{-t} + A_1 e^{-t}$$

$$\frac{dv_c(t)}{dt} \Big|_{t=0^+} = A_1 - A_2 \Rightarrow A_1 - A_2 = 1$$

$$(\text{note, } C \frac{dv_c(0^+)}{dt} = i_c(0^+) = i_L(0^+) = 2 \Rightarrow \frac{dv_c(0^+)}{dt} = 1 \text{ volt / sec.})$$

$$v_c(\infty) = A \Rightarrow A = 12$$

$$A_1 = -1; \quad A_2 = -2.$$

$$v_c(t) = -(t+2) e^{-t} + 12 = 12 - (t+2) e^{-t};$$

$$i(t) = C \frac{dv_c(t)}{dt} = 2 \times [(t+2) e^{-t} - e^{-t}] = 2 \times (t+1) e^{-t}$$

# Problem 4

The switch 'S1' in the circuit of Fig. 11.7(a) was closed in position '1' sufficiently long time and then kept in position '2'. Find (a)  $v_c(t)$ , (b)  $i_c(t)$ , for  $t \geq 0$  if  $C = 1/9$  F

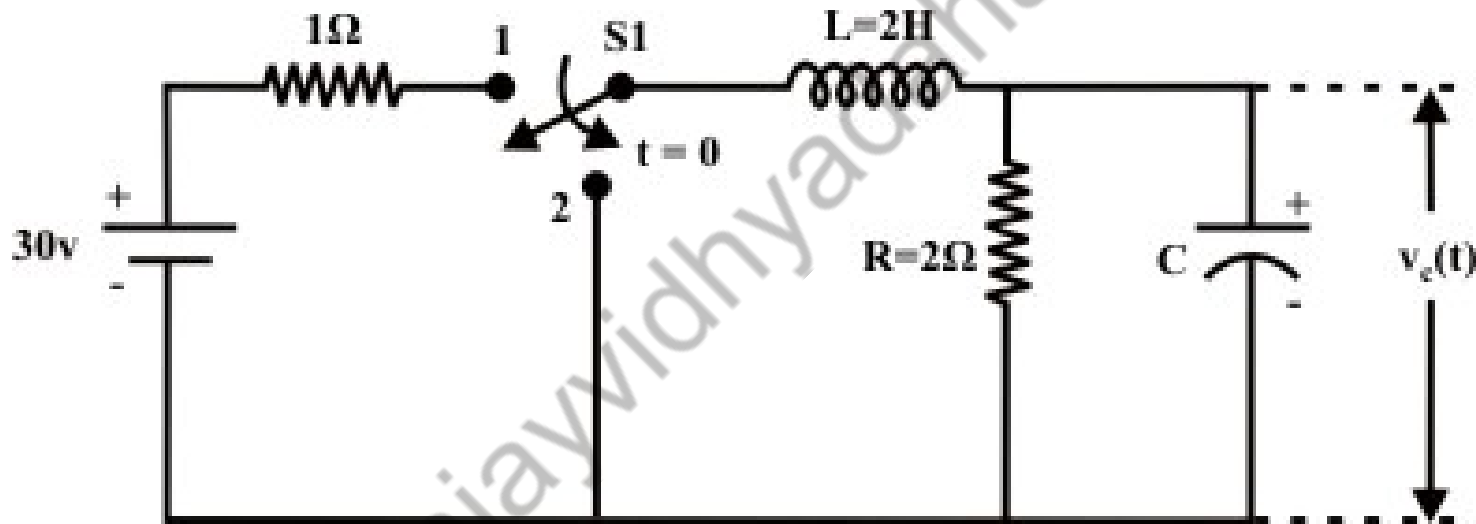


Fig. 11.7(a)

# Problem 4

The switch 'S' in the circuit of Fig. 11.7(a) was closed in position '1' sufficiently long time and then kept in position '2'. Find (a)  $v_c(t)$ , (b)  $i_c(t)$ , for  $t \geq 0$  if  $C = 1/9$  F

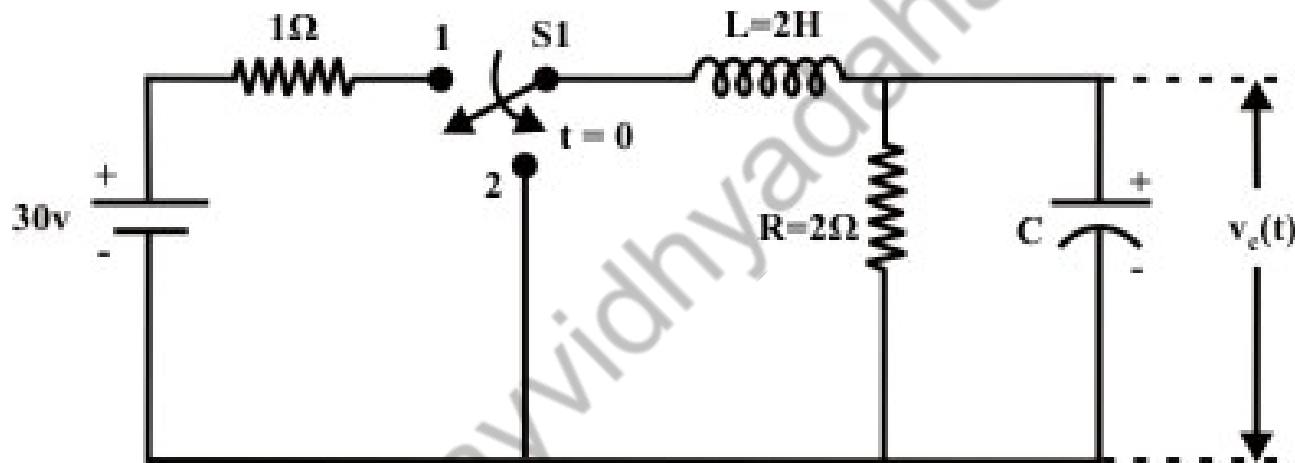




Fig. 11.7(a)

When the switch was in position '1', the steady state current in inductor is given by

$$i_L(0^-) = \frac{30}{1+2} = 10\text{A}, \quad v_c(0^-) = i_L(0^-)R = 10 \times 2 = 20 \text{ volt.}$$
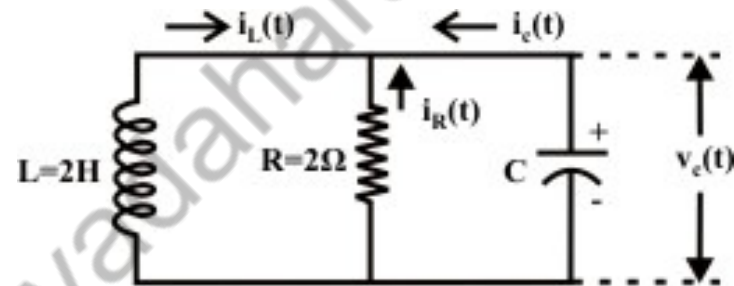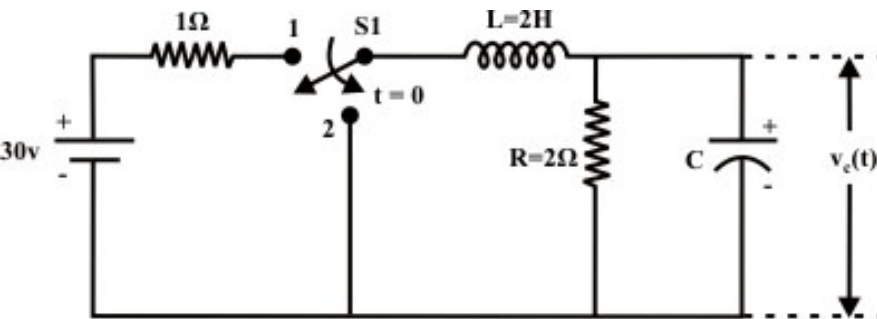
# Problem 4

The switch 'S1' is kept in position '2' and corresponding circuit diagram is shown in Fig.11.7 (b)



$$\frac{v_c(t)}{R} + i_c(t) + i_L(t) = 0$$

$$\frac{v_c(t)}{R} + C \frac{dv_c(t)}{dt} + i_L(t) = 0$$

$$\frac{L}{R} \frac{di_L(t)}{dt} + C.L \frac{d^2 i_L(t)}{dt^2} + i_L(t) = 0 \quad [\text{note: } v_c(t) = L \frac{di_L(t)}{dt}]$$

$$\frac{d^2 i_L(t)}{dt^2} + \frac{1}{RC} \frac{di_L(t)}{dt} + \frac{1}{LC} i_L(t) = 0$$

# Problem 4

The switch ' ' is kept in position '2' and corresponding circuit diagram is shown in Fig.11.7 (b)

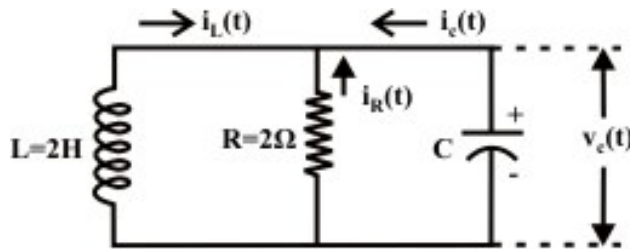


Fig. 11.7(b)

$$\frac{d^2 i_L(t)}{dt^2} + \frac{1}{RC} \frac{di_L(t)}{dt} + \frac{1}{LC} i_L(t) = 0$$

$$\alpha_1 = \frac{-\frac{1}{RC} + \sqrt{\left(\frac{1}{RC}\right)^2 - 4/LC}}{2} = \frac{-\frac{9}{2} + \sqrt{\left(\frac{9}{2}\right)^2 - \frac{4 \times 9}{2}}}{2} = -1.5$$

$$\alpha_2 = \frac{-\frac{1}{RC} - \sqrt{\left(\frac{1}{RC}\right)^2 - 4/LC}}{2} = \frac{-\frac{9}{2} - \sqrt{\left(\frac{9}{2}\right)^2 - \frac{4 \times 9}{2}}}{2} = -3.0$$

$$s_{1,2} = \frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	$\alpha = \frac{1}{2RC}$	$\omega_0 = \frac{1}{\sqrt{LC}}$
--	--------------------------	----------------------------------

The transient or neutral solution of the homogeneous equation is given by

$$i_L(t) = A_1 e^{-1.5t} + A_2 e^{-3.0t}$$

To determine  $A_1$  and  $A_2$ , the following initial conditions are used.

At  $t=0^+$ ;

$$i_L(0^+) = i_L(0^-) = A_1 + A_2$$

$$10 = A_1 + A_2$$

$$v_C(0^+) = v_C(0^-) = v_L(0^+) = L \left. \frac{di_L(t)}{dt} \right|_{t=0^+}$$

$$20 = 2 \times [A_1 \times -1.5 e^{-1.5t} - 3.0 \times A_2 e^{-3.0t}]$$

$$= 2[-1.5A_1 - 3A_2] = -3A_1 - 6A_2$$

Solving equations (11.31) and (11.32) we get,  $A_2 = -16.66$ ,  $A_1 = 26.666$ .

The natural response of the circuit is

$$i_L = \frac{80}{3} e^{-1.5t} - \frac{50}{3} e^{-3.0t} = 26.66 e^{-1.5t} - 16.66 e^{-3.0t}$$


$$L \frac{di_L}{dt} = 2 [26.66 \times -1.5 e^{-1.5t} - 16.66 \times -3.0 e^{-3.0t}]$$

$$v_L(t) = v_C(t) = [100 e^{-3.0t} - 80 e^{-1.5t}]$$

$$i_C(t) = C \frac{dv_C(t)}{dt} = \frac{1}{9} (-300.0 e^{-3.0t} + 120 e^{-1.5t}) = (13.33 e^{-1.5t} - 33.33 e^{-3.0t})$$
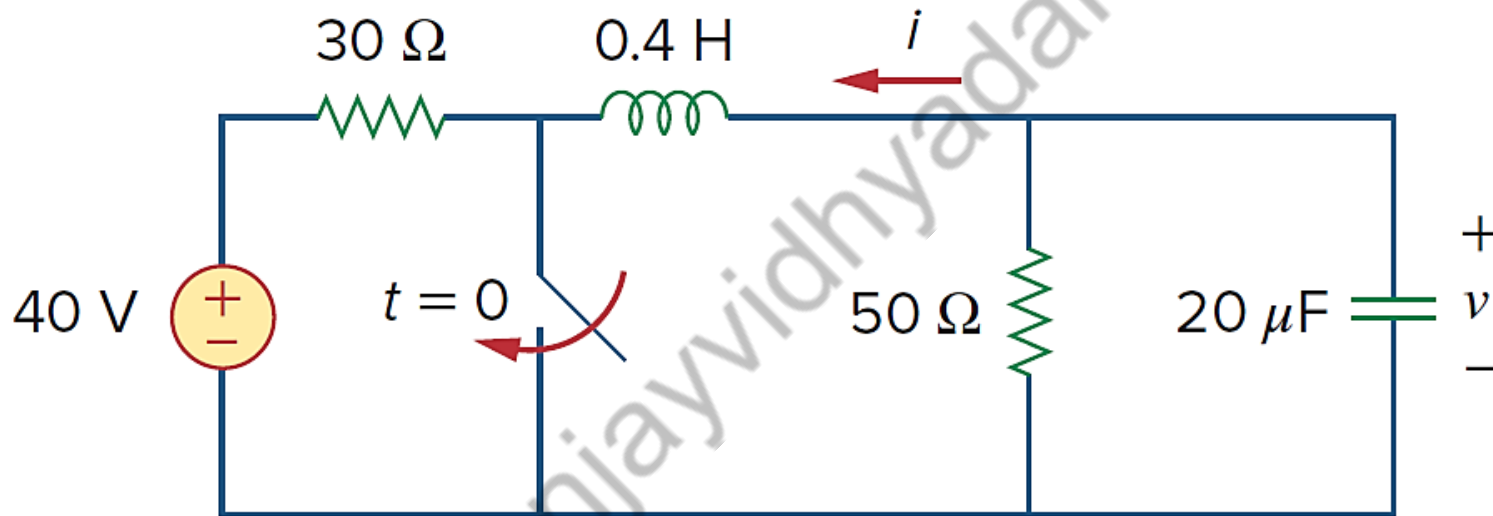
# Problem 5

Find  $v(t)$  for  $t > 0$  in the RLC circuit. Assume that the switch has been open for a long time before closing.






# Problem 5

Find  $v(t)$  for  $t > 0$  in the RLC circuit. Assume that the switch has been open for a long time before closing.
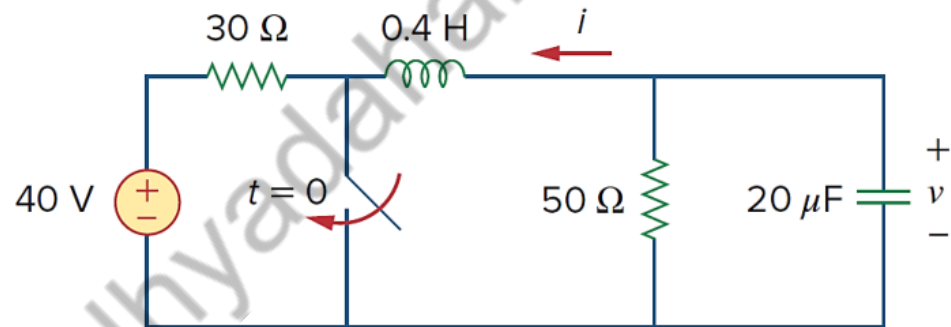
## Solution:

- For  $t < 0$ , the switch is open.
- Inductor acts like a short circuit, capacitor behaves like an open circuit.
- The initial voltage across the capacitor is the same as the voltage across the 50- $\Omega$  resistor.



$$v(0) = \frac{50}{30 + 50} (40) = 25;$$

$$i(0) = \frac{40}{30 + 50} = -0.5 A$$

$$\frac{dv(0)}{dt} = -\frac{v(0) + Ri(0)}{RC} = 0$$


# Problem 5

Find  $v(t)$  for  $t > 0$  in the RLC circuit. Assume that the switch has been open for a long time before closing.

For  $t > 0$ , the switch is closed. The voltage source along with the  $30\text{-}\Omega$  resistor is separated from the rest of the circuit.

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 50 \times 20 \times 10^{-6}} = 500;$$
$$\omega_0 = \frac{1}{\sqrt{LC}} = 354$$

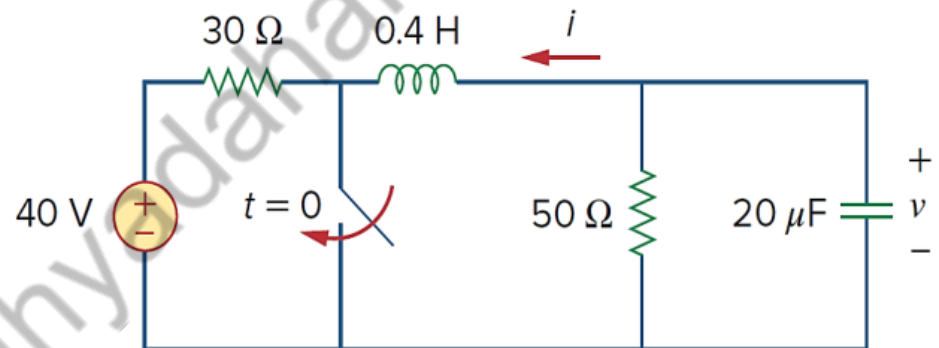Since  $\alpha > \omega_0$ , we have the **overdamped** response.



$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -500 \pm 354$$
$$s_1 = -854; s_2 = -146$$

$$v(t) = A_1 e^{-854t} + A_2 e^{-146t}$$

# Problem 5

Find  $v(t)$  for  $t > 0$  in the RLC circuit. Assume that the switch has been open for a long time before closing.

Applying initial conditions,


$$v(0) = 25 = A_1 + A_2$$

on differentiating,

$$\frac{dv}{dt} = -854A_1e^{-854t} + -146A_2e^{-146t}$$

$$\frac{dv(0)}{dt} = 0 = -854A_1 - 146A_2$$

$$A_1 = -5.156; A_2 = 30.16$$

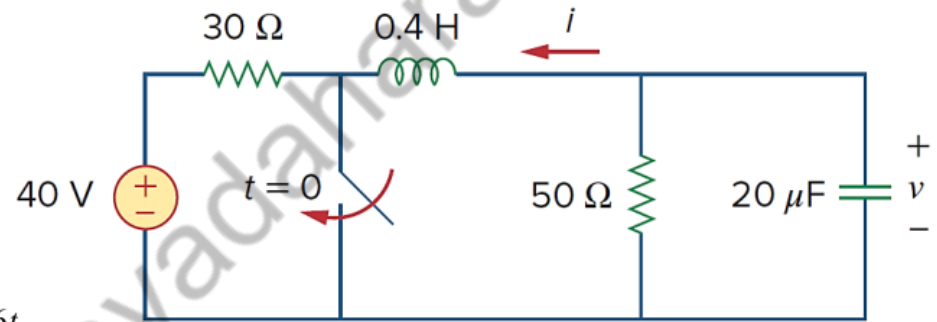

Thus, the complete solution is given as,

$$v(t) = -5.156e^{-854t} + 30.16e^{-146t} \text{ V}$$

**Thank you**

sanjayvidhyadahan