



# **Electrical Science: 2021-22**

## **Tutorial 7**


### **Frequency Domain Analysis of RLC Circuit**

**By Dr. Sanjay Vidhyadharan**


# Example 1

For the series  $RL$  circuit shown in Figure determine:

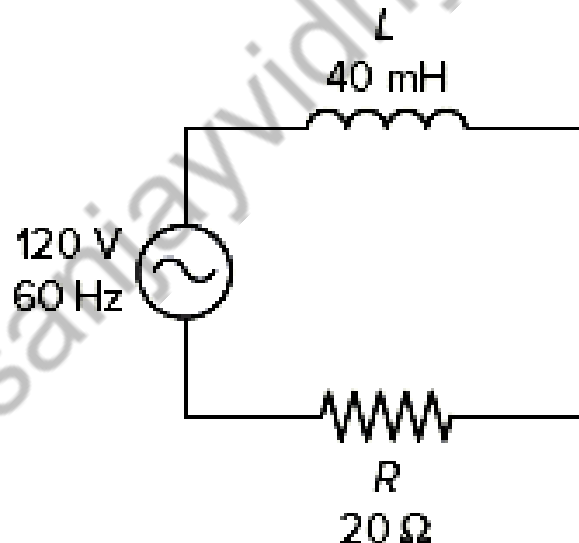1. Inductive reactance ( $X_L$ ).
2. Impedance ( $Z$ ).
3. Current ( $I$ ).
4. Voltage drop across the resistor ( $E_R$ ) and inductor ( $E_L$ ).
5. The angle theta ( $\theta$ ) and power factor (PF) for the circuit.
6. True power (W), reactive power (VARs), apparent power (VA).



# Example 1

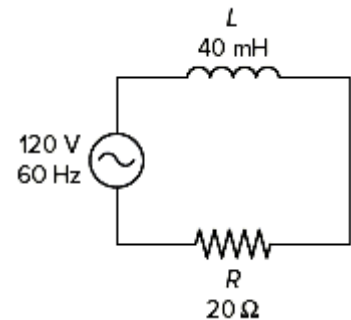

	E	I	L	R/X <sub>L</sub> /Z	W/VA/VARS	∠θ	PF
R			N/A	20 Ω		0°	N/A
L			40 mH			90°	
Total	120 V		N/A				

	E	I	L	R/X <sub>L</sub> /Z	W/VA/VARS	∠θ	PF
R	95.6 V	4.78 A	N/A	20 Ω	457 W	0°	N/A
L	72.2 V	4.78 A	40 mH	15.1 Ω	345 VARs	90°	
Total	120 V	4.78 A	N/A	25.1 Ω	574 VA	37.1°	79.7%

$$X_L = 2\pi fL$$

$$= 2 \times 3.14 \times 60 \times 0.04$$

$$= 15.1 \Omega$$

$$I_T = \frac{E_T}{Z}$$

$$= \frac{120}{25.1}$$

$$= 4.78 \text{ A}$$

$$I_T = I_R = I_L = 4.78 \text{ A}$$

$$\text{Cosine } \theta = \frac{R}{Z}$$

$$= \frac{20}{25.1}$$

$$= 0.797$$

$$\text{Angle } \theta = 37.1^\circ$$

$$\text{Power factor} = \cos \theta$$

$$= 0.797 \text{ or } 79.7\% \text{ lagging}$$

$$E_R = I \times R$$

$$= 4.78 \times 20$$

$$= 95.6 \text{ V}$$

$$E_L = I \times X_L$$

$$= 4.78 \times 15.1$$

$$= 72.2 \text{ V}$$

$$W = E_R \times I_R$$

$$= 95.6 \times 4.78$$

$$= 457 \text{ watts}$$

$$\text{VARs} = E_L \times I_L$$

$$= 72.2 \times 4.78$$

$$= 345 \text{ VARs}$$

$$\text{VA} = E_T \times I_T$$

$$= 120 \times 4.78$$

$$= 574 \text{ VA}$$

# Applying the theorem for AC circuits

- Thevenin's theorem
- Norton's theorem
- Nodal and Mesh analysis
- Superposition theorem
- Source transformation

sanjayvishnyadharan.in

## Example 2

If  $I = 33 \angle -13^\circ \text{ A}$ , find the Thevenin's equivalent circuit to the left of terminals  $x$ - $y$  in the network of figure.

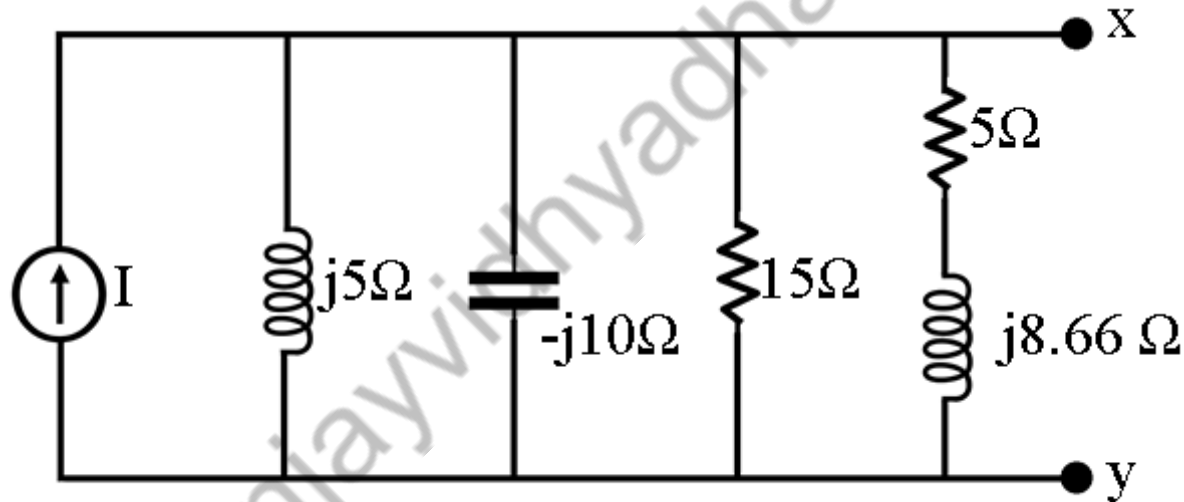


Figure: 1

# Example 2

If  $I = 33 \angle -13^\circ \text{ A}$ , find the Thevenin's equivalent circuit to the left of terminals  $x-y$  in the network of figure.

$$Y_{eq} = Y_1 + Y_2 + Y_3 + Y_4$$

where  $Y_1, Y_2, Y_3$  and  $Y_4$  is the branch admittance

$$Y_1 = \frac{1}{j5} = -j0.2 \text{ mho}$$

$$Y_2 = \frac{1}{-j10} = j0.1 \text{ mho}$$

$$Y_3 = \frac{1}{15} = 0.067 \text{ mho}$$

$$Y_4 = \frac{1}{5 + j8.66} = \frac{1}{10 \angle 60^\circ} = (0.05 - j0.0866) \text{ mho}$$

$$\therefore Y_{eq} = (0.117 - j0.7866) \text{ mho}$$

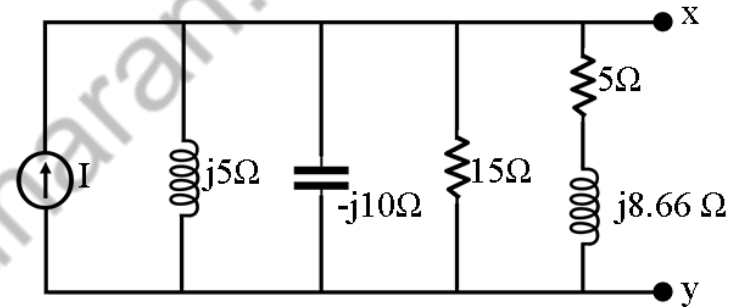


Figure: 1

$$Z_{in} = \frac{1}{Y_{eq}} = \frac{1}{0.117 - j0.1866}$$

$$= \frac{1}{0.22 \angle -58^\circ} = 4.54 \angle 58^\circ \text{ ohm}$$

$$V_{x-y} (= V_{o.c}) = \frac{I}{Y_{eq}}$$

$$= 150 \angle 45^\circ \text{ V}$$

## Example 2

If  $I = 33 \angle -13^\circ \text{ A}$ , find the Thevenin's equivalent circuit to the left of terminals  $x$ - $y$  in the network of figure.



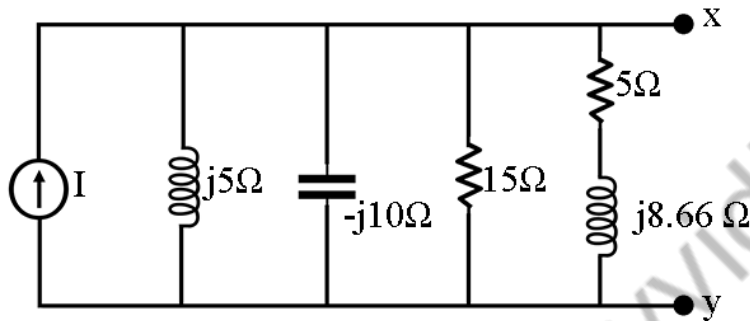


Figure: 1

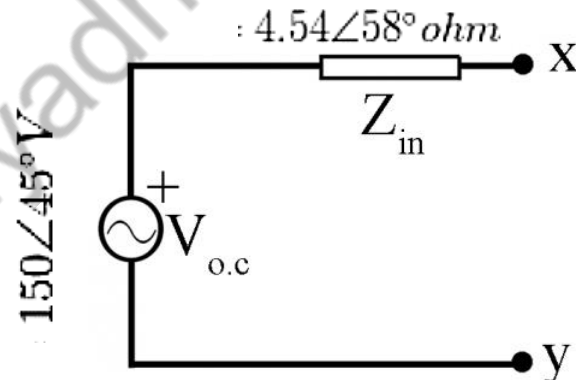
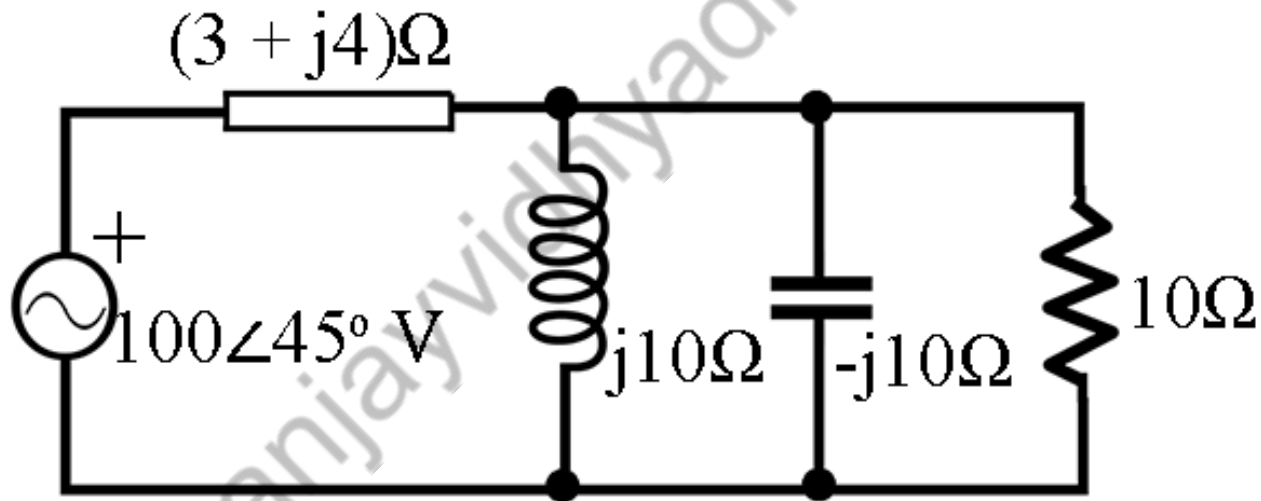
# Example 3



*Find the current through  $10\Omega$  resistor using Thevenin's theorem*




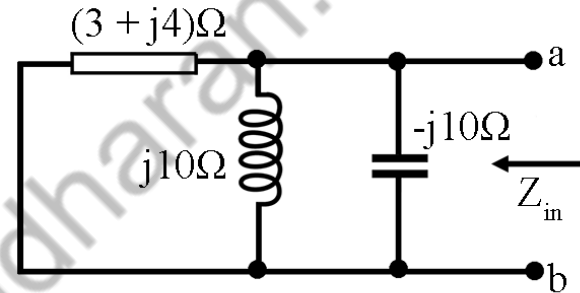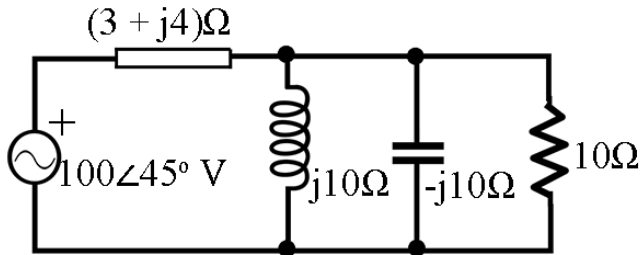
# Example 3

Find the current through  $10\Omega$  resistor using Thevenin's theorem (figure 5).



$$Z_{int} = \frac{1}{Y_{int}}$$
$$= \frac{1}{\frac{1}{-j10} + \frac{1}{j10} + \frac{1}{3 + j4}} = (3 + j4)\text{ohm}$$


$$Z_{in} = (3 + j4)\Omega$$

and  $V_{o.c} = 100\angle 45^\circ V$

$$I_L = \frac{V_{o.c}}{Z_{in} + Z_L} = \frac{100\angle 45^\circ}{(3 + j4) + 10} = 7.35\angle 28.3^\circ A$$

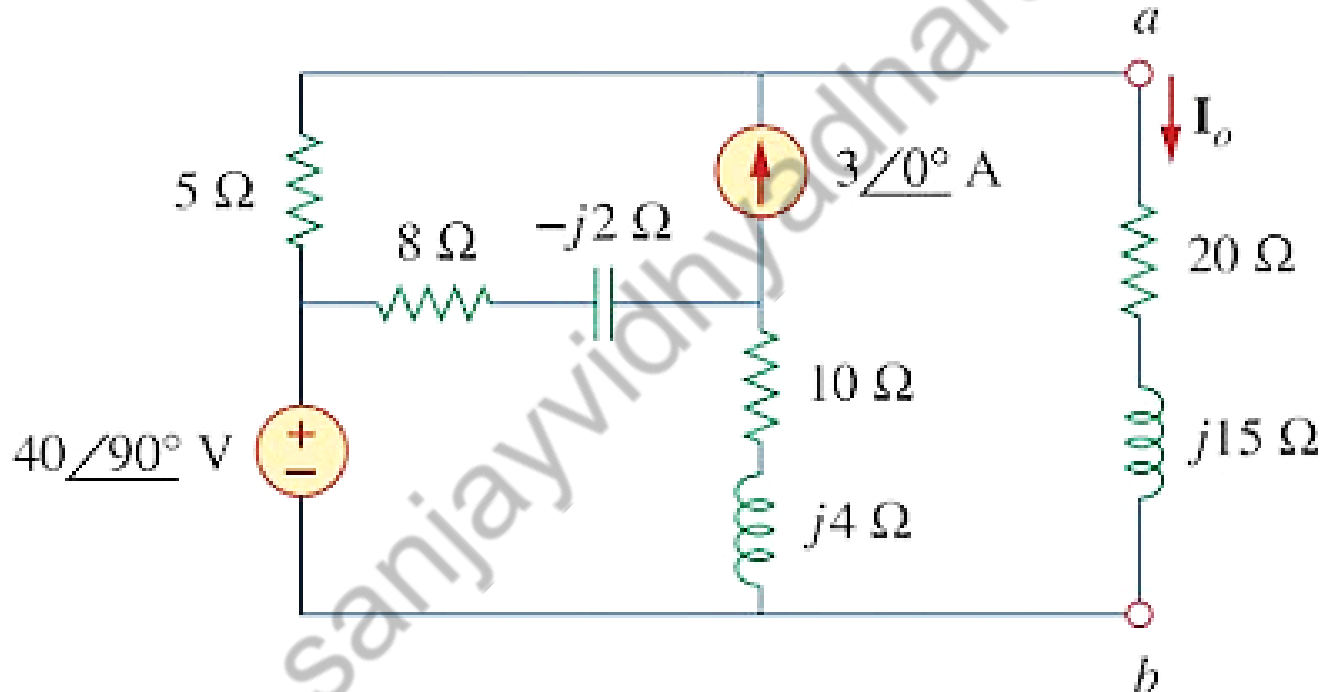
# Example 4

Find the current  $I_o$  using Norton's theorem


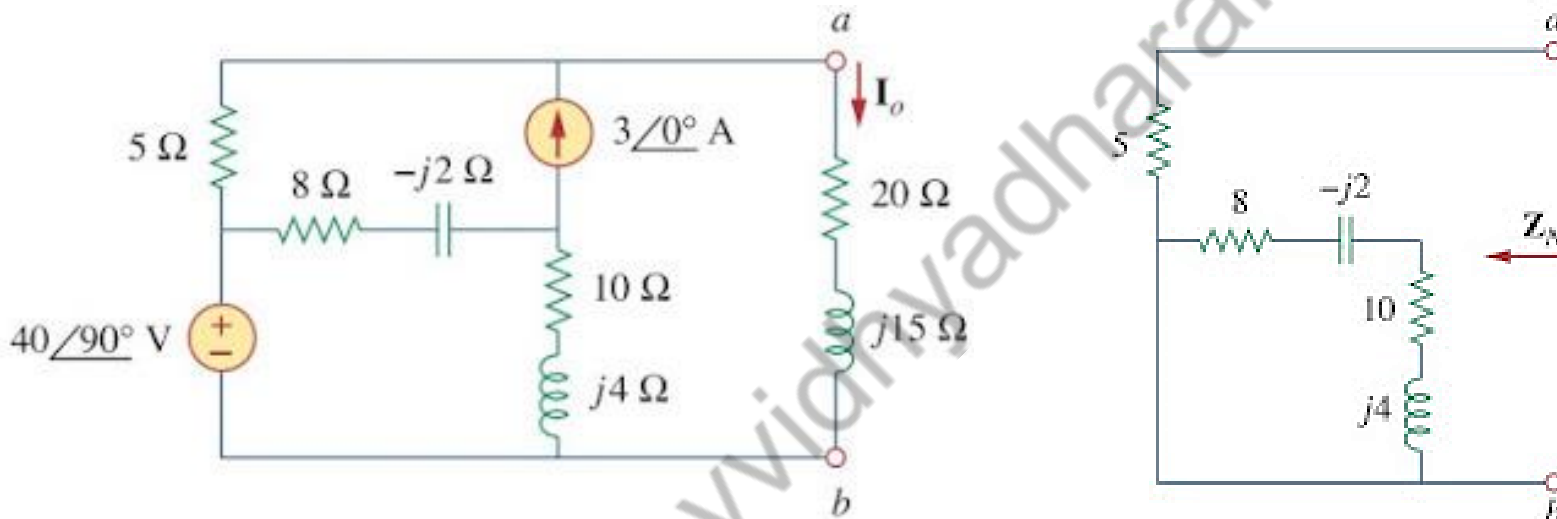
# Example 4

Find the current  $I_o$  using Norton's theorem





$$Z_N = 5 \Omega$$

(a)
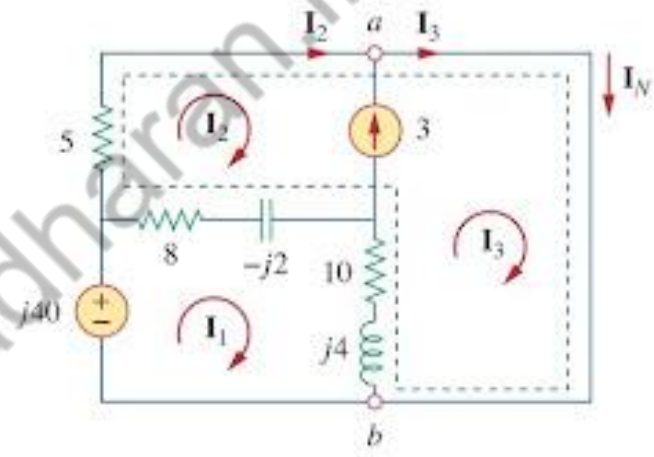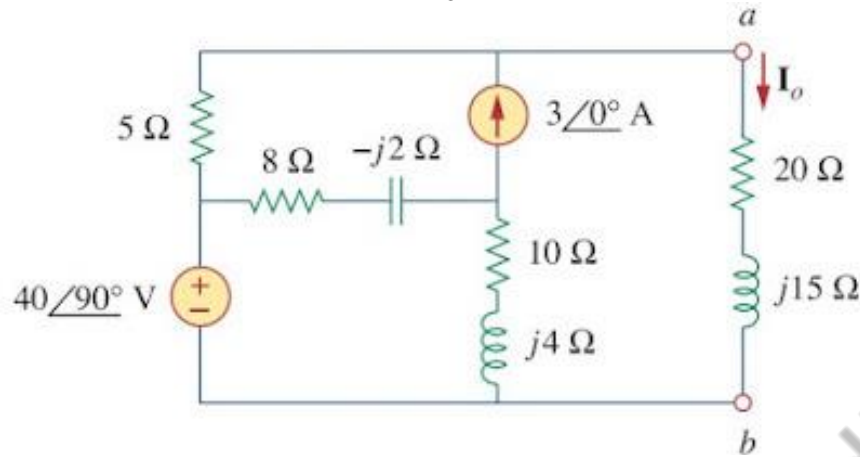
# Example 4

Find the current  $I_o$  using Norton's theorem



For mesh 1,

$$-j40 + (18 + j2)\mathbf{I}_1 - (8 - j2)\mathbf{I}_2 - (10 + j4)\mathbf{I}_3 = 0$$

For the supermesh,

$$(13 - j2)\mathbf{I}_2 + (10 + j4)\mathbf{I}_3 - (18 + j2)\mathbf{I}_1 = 0$$


At node  $a$ , due to the current source between meshes 2 and 3,

$$\mathbf{I}_3 = \mathbf{I}_2 + 3$$

$$\mathbf{I}_N = \mathbf{I}_3 = (3 + j8) \text{ A}$$
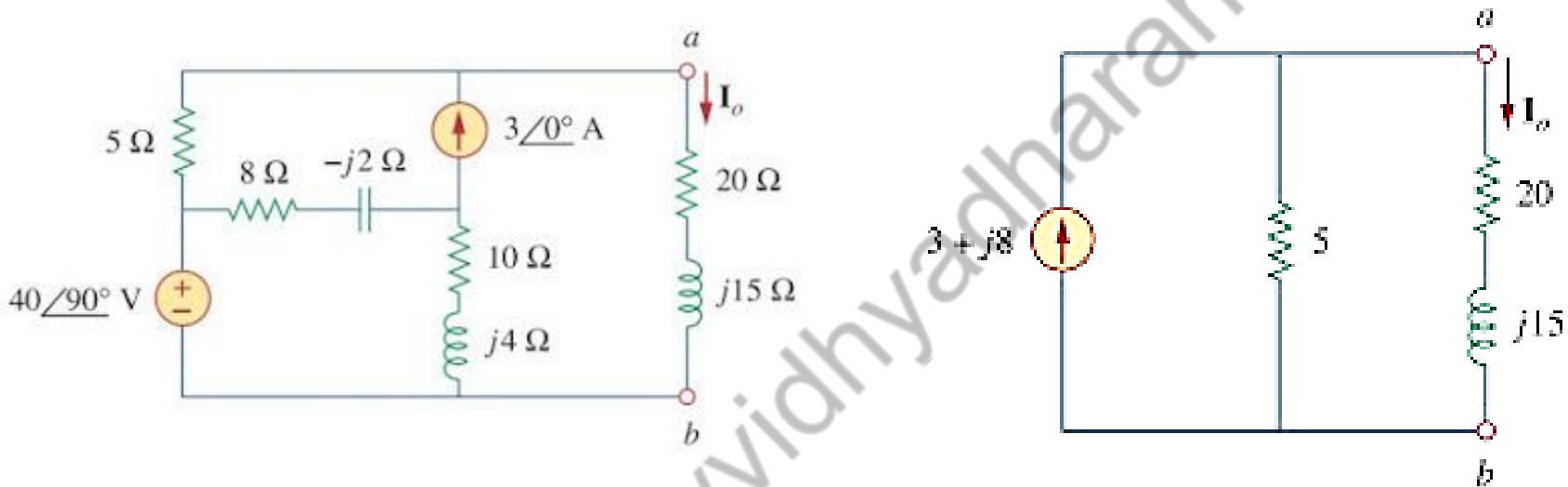
# Example 4

Find the current  $I_o$  using Nortons's theorem




$$\mathbf{I}_N = \mathbf{I}_3 = (3 + j8) \text{ A}$$

$$\mathbf{Z}_N = 5\ \Omega$$

$$\mathbf{I}_o = \frac{5}{5 + 20 + j15} \mathbf{I}_N = \frac{3 + j8}{5 + j3} = 1.465\angle 38.48^\circ \text{ A}$$


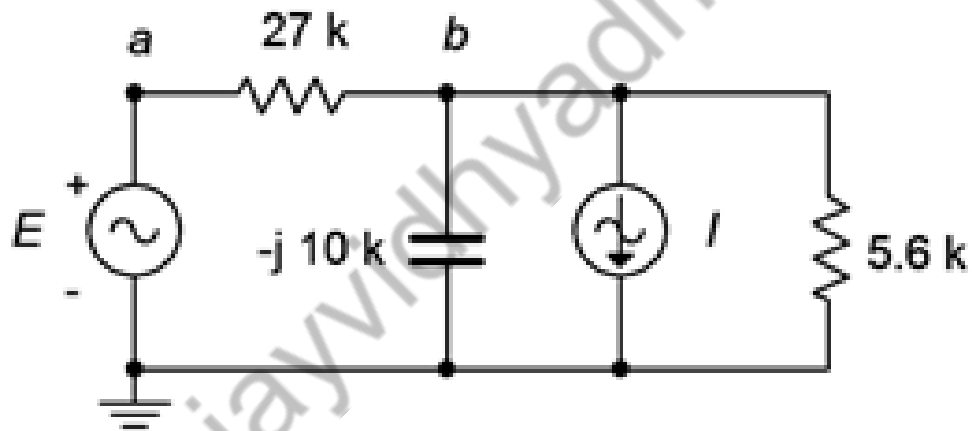
# Example 5

For the circuit of Figure 5.3.2, determine  $V_b$  using superposition.  $I=2E-3\angle 90^\circ$  amps peak and  $E=10\angle 0^\circ$  volts peak.


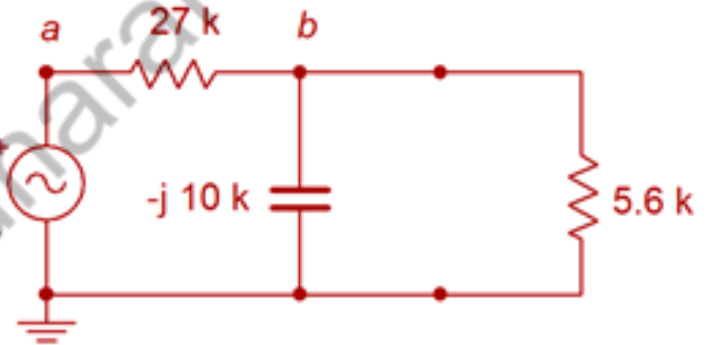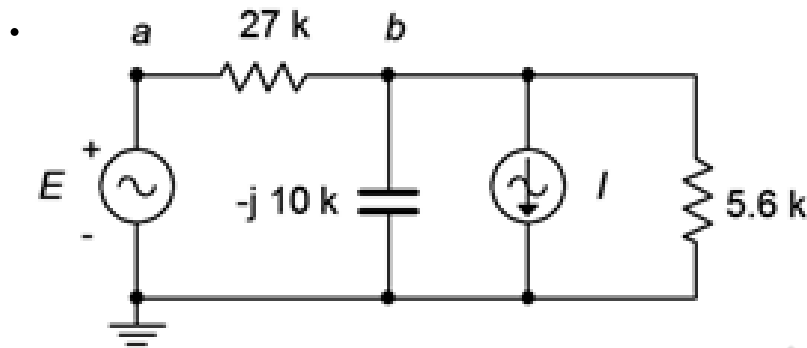
# Example 5

For the circuit of Figure 5.3.2, determine  $V_b$  using superposition.  $I = 2E - 3 \angle 90^\circ$  amps peak and  $E = 10 \angle 0^\circ$  volts peak.



$$Z_{right2} = \frac{R \times jX_C}{R - jX_C}$$

$$Z_{right2} = \frac{5.6k\Omega \times (-j10k\Omega)}{5.6k\Omega - j10K}$$

$$Z_{right2} = 4886 \angle -29.2^\circ \Omega$$



$$v_{b1} = E \frac{Z_{right2}}{Z_{right2} + R_1}$$

$$v_{b1} = 10 \angle 0^\circ V \frac{4886 \angle -29.2^\circ \Omega}{4886 \angle -29.2^\circ \Omega + 27k\Omega}$$

$$v_{b1} = 1.558 \angle -24.88^\circ V$$
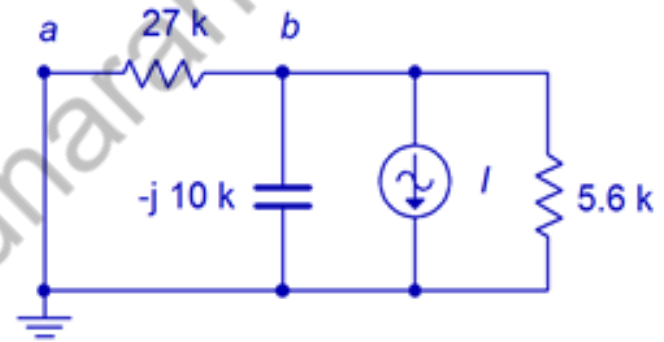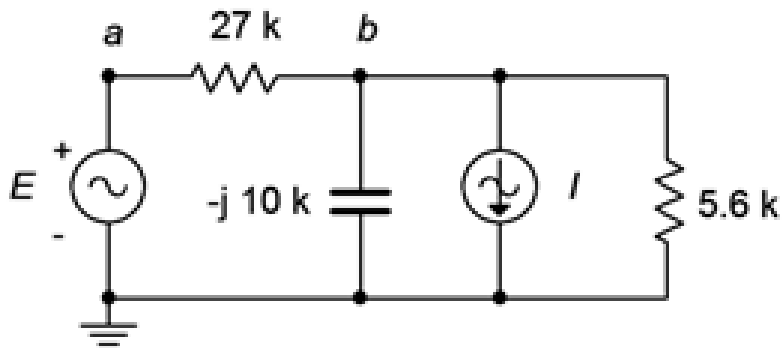
# Example 5

For the circuit of Figure 5.3.2, determine  $v_b$  using superposition.  $I = 2E - 3 \angle 90^\circ$  amps peak and  $E = 10 \angle 0^\circ$  volts peak.



$$Z_{total} = \frac{1}{\frac{1}{X_C} + \frac{1}{R_1} + \frac{1}{R_2}}$$

$$Z_{total} = \frac{1}{\frac{1}{-j10k\Omega} + \frac{1}{27k\Omega} + \frac{1}{5.6k\Omega}}$$

$$Z_{total} = 4208 \angle -24.9^\circ \Omega$$

$$v_{b2} = I \times Z_{total}$$

$$v_{b2} = -2E - 3 \angle 90^\circ A \times 4208 \angle -24.9^\circ \Omega$$

$$v_{b2} = 8.416 \angle -114.9^\circ V$$

$$v_b = 1.558 \angle -24.88^\circ V + 8.416 \angle -114.9^\circ V$$


$$v_b = 8.558 \angle -104.4^\circ V$$


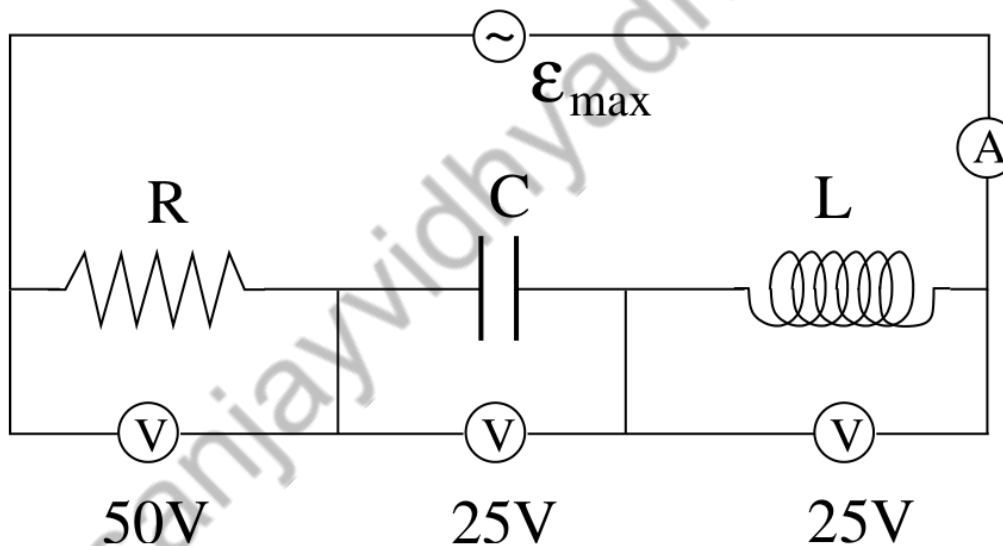
# Example 6

In this RLC circuit, we know the voltage amplitudes  $V_R, V_C, V_L$  across each device, the current amplitude  $I_{\max} = 5\text{A}$ , and the angular frequency  $\omega = 2\text{rad/s}$ .


- Find the device properties  $R, C, L$  and the voltage amplitude  $E_{\max}$  of the ac source.


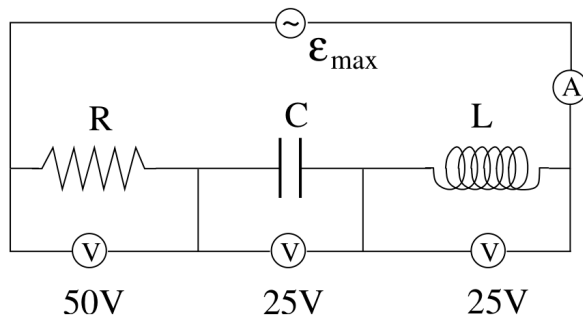
# Example 6

In this RLC circuit, we know the voltage amplitudes  $V_R, V_C, V_L$  across each device, the current amplitude  $I_{\max} = 5\text{A}$ , and the angular frequency  $\omega = 2\text{rad/s}$ .

- Find the device properties  $R, C, L$  and the voltage amplitude  $E_{\max}$  of the ac source.



$$X_R = \frac{50\text{V}}{5\text{A}} = 10\Omega, \quad X_C = \frac{25\text{V}}{5\text{A}} = 5\Omega, \quad X_L = \frac{25\text{V}}{5\text{A}} = 5\Omega.$$

The device properties follow directly:

$$R = 10\Omega, \quad C = 0.1\text{F}, \quad L = 2.5\text{H}.$$

The general expression for the EMF is, we recall from the previous lecture,

$$\mathcal{E}_{\max} = \sqrt{V_R^2 + (V_L - V_C)^2}.$$

$$\mathcal{E}_{\max} = V_R = 50\text{V}.$$

# Example 7

A 50Ω resistor, a 20mH coil and a 5μF capacitor are all connected in parallel across a 50V, 100Hz supply. Calculate the total current drawn from the supply, the current for each branch, the total impedance of the circuit and the phase angle. Also construct the current triangles representing the circuit.

1). Inductive Reactance, ( $X_L$ ):

$$X_L = \omega L = 2\pi fL = 2\pi \cdot 100 \cdot 0.02 = 12.6\Omega$$


2). Capacitive Reactance, ( $X_C$ ):

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot 100 \cdot 5 \times 10^{-6}} = 318.3\Omega$$

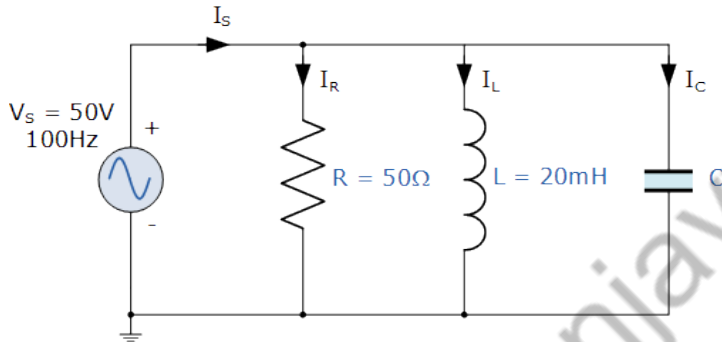3). Impedance, ( $Z$ ):

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_C} - \frac{1}{X_L}\right)^2}} = \frac{1}{\sqrt{\left(\frac{1}{50}\right)^2 + \left(\frac{1}{318.3} - \frac{1}{12.6}\right)^2}}$$

$$Z = \frac{1}{\sqrt{0.0004 + 0.0058}} = \frac{1}{0.0788} = 12.7\Omega$$



# Example 7

A  $50\Omega$  resistor, a  $20\text{mH}$  coil and a  $5\mu\text{F}$  capacitor are all connected in parallel across a  $50\text{V}$ ,  $100\text{Hz}$  supply. Calculate the total current drawn from the supply, the current for each branch, the total impedance of the circuit and the phase angle. Also construct the current triangles representing the circuit.

4). Current through resistance,  $R$  ( $I_R$ ):

$$I_R = \frac{V}{R} = \frac{50}{50} = 1.0(\text{A})$$

5). Current through inductor,  $L$  ( $I_L$ ):


$$I_L = \frac{V}{X_L} = \frac{50}{12.6} = 3.9(\text{A})$$

6). Current through capacitor,  $C$  ( $I_C$ ):

$$I_C = \frac{V}{X_C} = \frac{50}{318.3} = 0.16(\text{A})$$


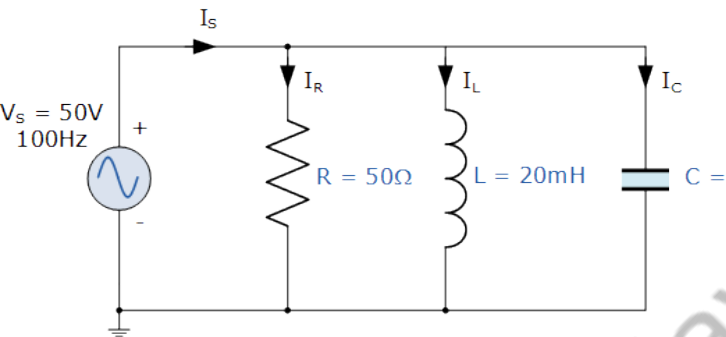
7). Total supply current, ( $I_S$ ):

$$I_S = \sqrt{I_R^2 + (I_L - I_C)^2} = \sqrt{1^2 + (3.9 - 0.16)^2} = 3.87(\text{A})$$


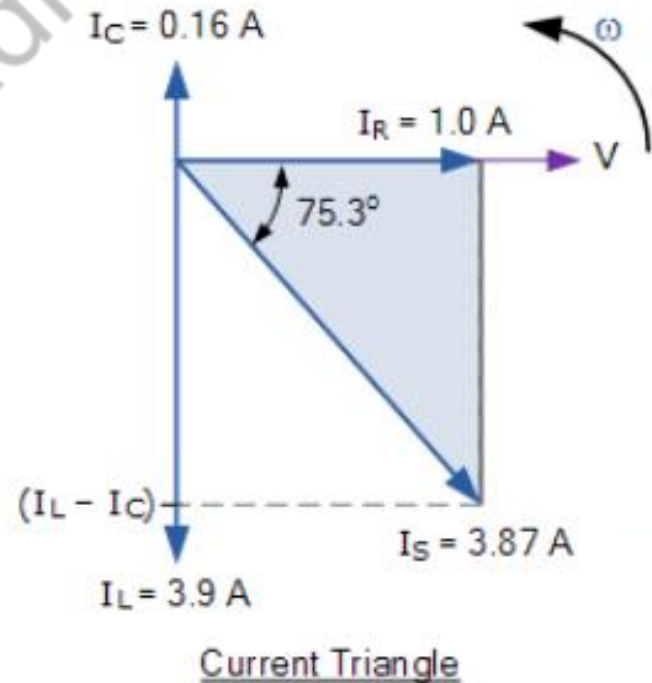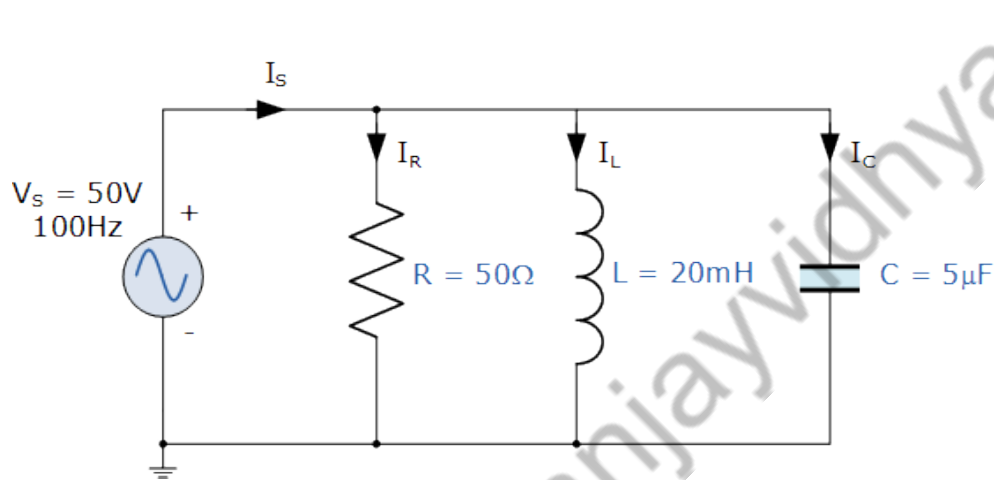
# Example 7

A  $50\Omega$  resistor, a  $20\text{mH}$  coil and a  $5\mu\text{F}$  capacitor are all connected in parallel across a  $50\text{V}$ ,  $100\text{Hz}$  supply. Calculate the total current drawn from the supply, the current for each branch, the total impedance of the circuit and the phase angle. Also construct the current triangles representing the circuit.



# Example 8

A parallel resonance network consisting of a resistor of  $60\Omega$ , a capacitor of  $120\mu\text{F}$  and an inductor of  $200\text{mH}$  is connected across a sinusoidal supply voltage which has a constant output of  $100$  volts at all frequencies. Calculate, the resonant frequency, the quality factor and the bandwidth of the circuit, the circuit current at resonance and current magnification.

1. Resonant Frequency,  $f_r$

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.2 \cdot 120 \cdot 10^{-6}}} = 32.5\text{Hz}$$

2. Inductive Reactance at Resonance,  $X_L$

$$X_L = 2\pi fL = 2\pi \cdot 32.5 \cdot 0.2 = 40.8\Omega$$

3. Quality factor,  $Q$

$$Q = \frac{R}{X_L} = \frac{R}{2\pi fL} = \frac{60}{40.8} = 1.47$$



4. Bandwidth,  $BW$

$$BW = \frac{f_r}{Q} = \frac{32.5}{1.47} = 22\text{Hz}$$

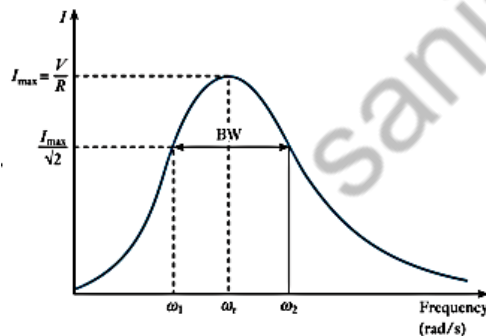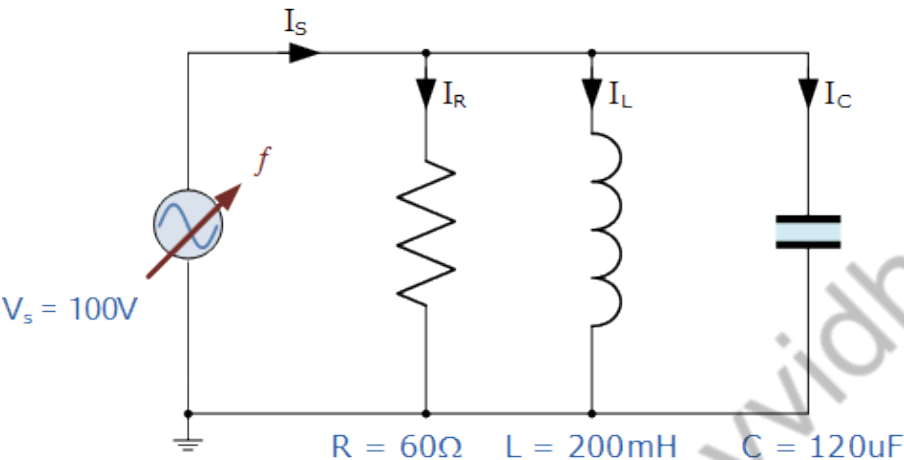5. The upper and lower -3dB frequency points,  $f_H$  and  $f_L$


$$f_L = f_r - \frac{1}{2}BW = 32.5 - \frac{1}{2}(22) = 21.5\text{Hz}$$

$$f_H = f_r + \frac{1}{2}BW = 32.5 + \frac{1}{2}(22) = 43.5\text{Hz}$$


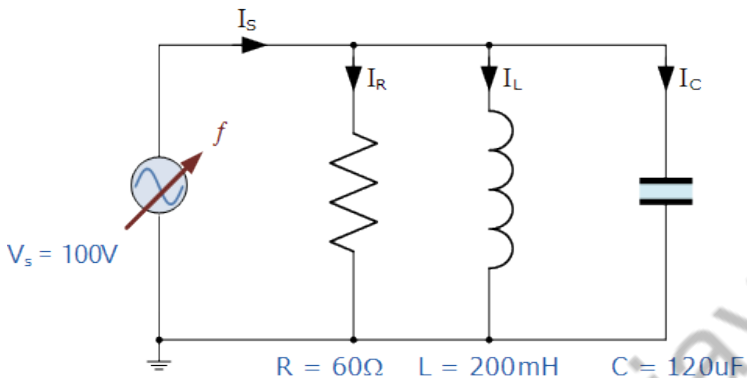
# Example 8

A parallel resonance network consisting of a resistor of  $60\Omega$ , a capacitor of  $120\mu\text{F}$  and an inductor of  $200\text{mH}$  is connected across a sinusoidal supply voltage which has a constant output of 100 volts at all frequencies. Calculate, the resonant frequency, the quality factor and the bandwidth of the circuit, the circuit current at resonance and current magnification.



6. Circuit Current at Resonance,  $I_T$

At resonance the dynamic impedance of the circuit is equal to  $R$

$$I_T = I_R = \frac{V}{R} = \frac{100}{60} = 1.67\text{A}$$

7. Current Magnification,  $I_{\text{mag}}$

$$I_{\text{MAG}} = Q \times I_T = 1.47 \times 1.67 = 2.45\text{A}$$

Note that the current drawn from the supply at resonance (the resistive current) is only 1.67 amps, while the current flowing around the LC tank circuit is larger at 2.45 amps. We can check this value by calculating the current flowing through the inductor (or capacitor) at resonance.

$$I_L = \frac{V}{X_L} = \frac{V}{2\pi fL} = \frac{100}{2\pi \cdot 32.5 \cdot 0.2} = 2.45\text{A}$$

# Example 9


You have a parallel RLC circuit with a  $16 \Omega$  resistor,  $8 \Omega$  inductor,  $20 \Omega$  capacitor, and a 120-V power supply what are the following values?

- a. Current through the resistor ( $I_R$ ).  $I_R = V_s / R = 120 / 16 = 7.5 \text{ A}$
- b. Current through the inductor ( $I_L$ ).  $I_L = V_s / X_L = 120 / 8 = 15 \text{ A}$
- c. Current through the capacitor ( $I_C$ ).  $I_C = V_s / X_C = 120 / 20 = 6 \text{ A}$
- d. Net reactive current ( $I_X$ ).  $I_X = I_L - I_C = 9 \text{ A}$
- e. Total line current ( $I_T$ ).  $I_T = \sqrt{(I_R^2 + (I_L - I_C)^2)} = \sqrt{(7.5^2 + 9^2)} = 11.71 \text{ A}$


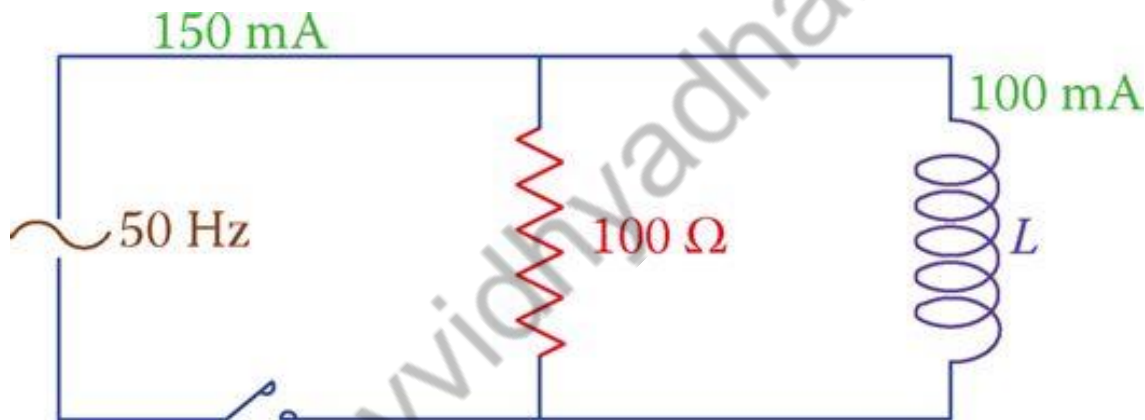
# Example 10

In the circuit shown in Figure, the total current is 150 mA and the current through the inductor is 100 mA. Determine what the applied voltage is. Also, knowing that the frequency is 50 Hz, find the value of  $L$ .



$$I_R = \sqrt{I^2 - I_L^2} = \sqrt{150^2 - 100^2} = 0.1118A$$


$$V = 100 * 11.8 = 11.18V$$

$$X_L = 11.18 \div 0.100 = 111.8\Omega$$

$$L = \frac{X_L}{2\pi f} = \frac{111.8}{2\pi * 50} = 35.6mH$$
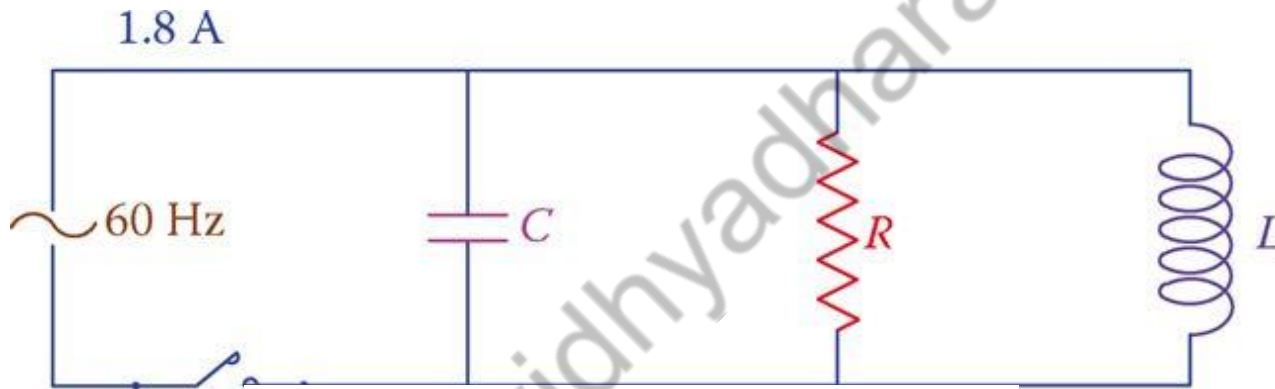
# Example 11

In the circuit shown in Figure,  $R = 55 \Omega$ ,  $L = 0.08 \text{ H}$ , and  $C = 1 \mu\text{F}$ , find the impedance of the circuit and the applied voltage.



$$X_L = 2 * 3.14 * 60 * 0.08 = 30.16 \Omega$$

$$X_C = \frac{1}{2 * 3.14 * 60 * 0.000001} = 26.5 \Omega$$

$$\frac{1}{Z} = \sqrt{\left(\frac{1}{55}\right)^2 + \left(\frac{1}{55} - \frac{1}{26.5}\right)^2} = \frac{1}{53.33}$$

$$Z = 53.33 \Omega$$

$$\text{Applied voltage} = V = ZI = (53.33)(1.8) = \mathbf{96 \text{ V.}}$$

**Thank you**

sanjayvidhyadharan.in