



Electrical Science: 2021-22


Tutorial 9

Passive Filters & Transformers

By Dr. Sanjay Vidhyadharan


Example 1

Calculate the cutoff frequency for the circuit shown in the figure

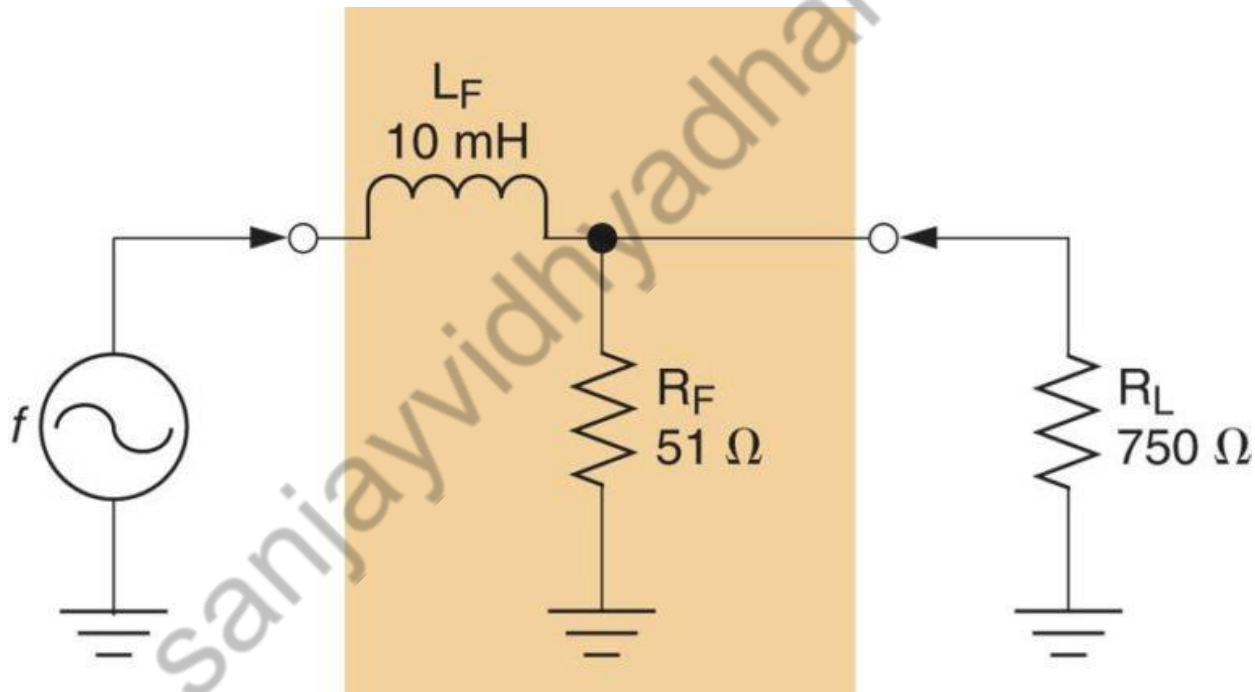

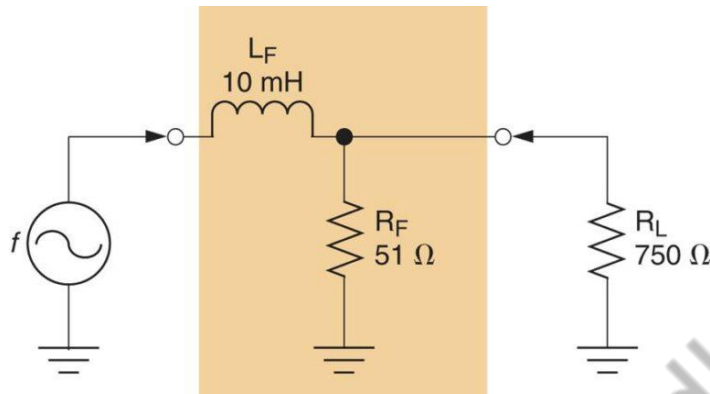Example 1

Calculate the cutoff frequency for the circuit shown in the figure




First, the value of R_{EQ} is found as:

$$R_{EQ} = R_F || R_L = \frac{51 \times 750}{51 + 750} = 47.8 \Omega$$

Now, the cutoff frequency of the circuit can be found as:



$$f_c = \frac{R_{EQ}}{2\pi L} = \frac{47.8 \Omega}{2\pi \times 10 \text{ mH}} = 761 \text{ Hz}$$

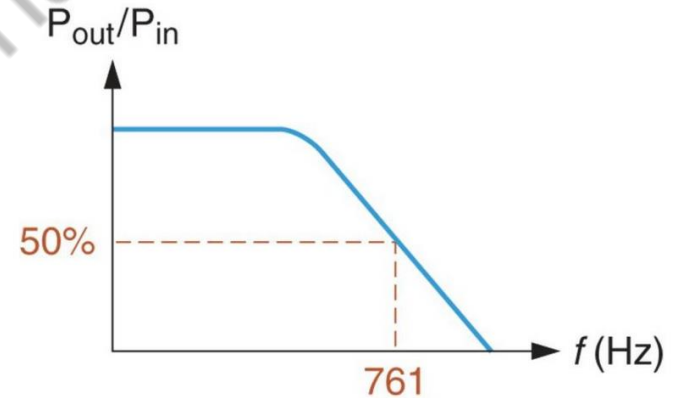


Example 2

The following circuit diagram shows a band-pass filter connected to a signal generator, with V_{IN} set to 10 V. The inductor has a resistance r_L of 3 Ω . V_{IN} is kept at 10 V as the frequency is increased to find the maximum value of V_{OUT} .

- Calculate the frequency at which V_{OUT} is a maximum.
- Calculate the dynamic resistance, R_D , of the filter and hence determine the maximum value of the voltage V_{OUT} when V_{IN} is set to 10 V.
- Determine the bandwidth of this filter.
- Sketch the frequency response of the filter

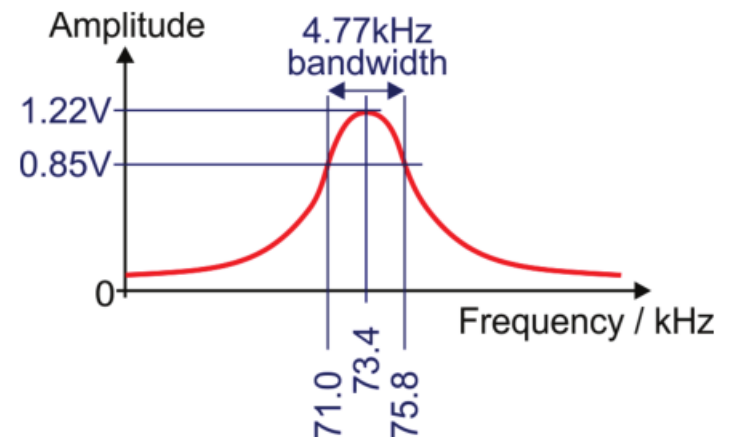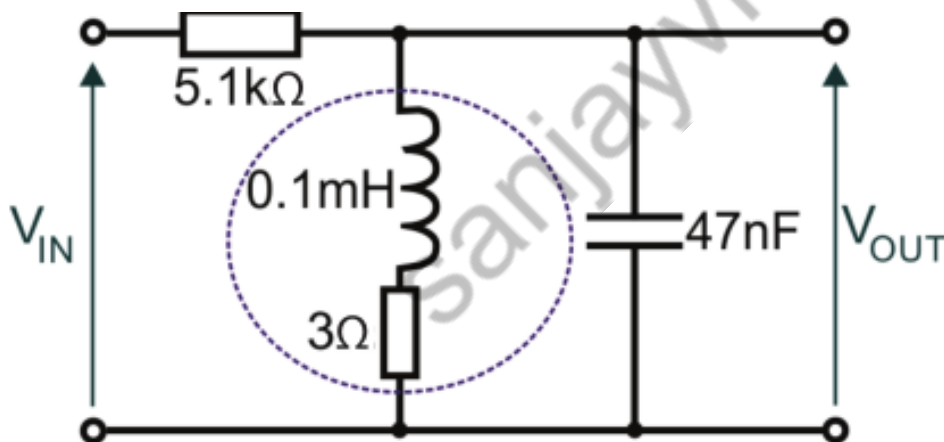

Example 2

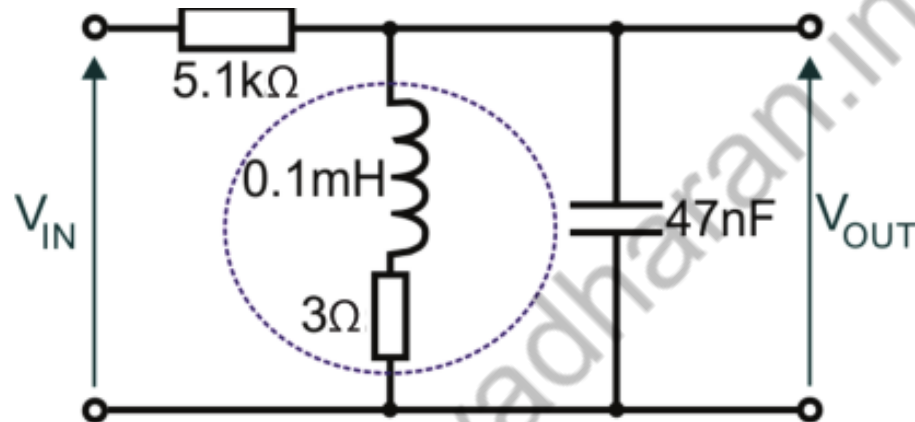

- (a) Calculate the frequency at which V_{OUT} is a maximum.



$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 10^{-3} \times 47 \times 10^{-9}}} = 73413\text{Hz} = 73.4\text{kHz}$$

- (b) Calculate the dynamic resistance, R_D , of the filter and hence determine the maximum value of the voltage V_{OUT} when V_{IN} is set to 10 V.

$$R_D = \frac{L}{r_L C} = \frac{0.1 \times 10^{-3}}{3 \times 47 \times 10^{-9}} = 709.2\Omega$$

$$V_{OUT} = V_{IN} \times \frac{R_D}{R_D + R} = \frac{10 \times 709}{709 + 5100} = 1.22\text{V}$$

Example 2

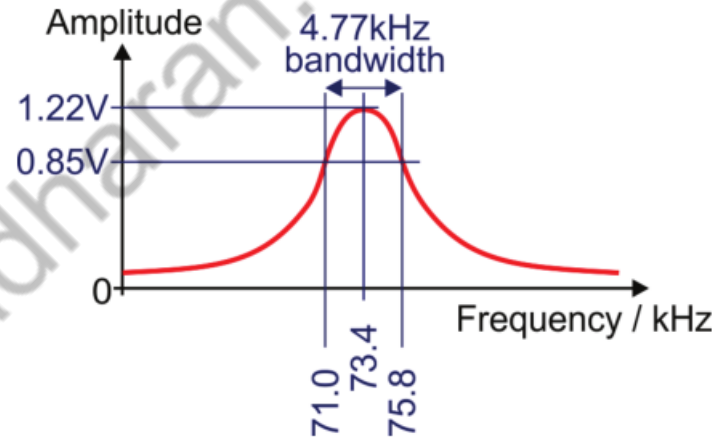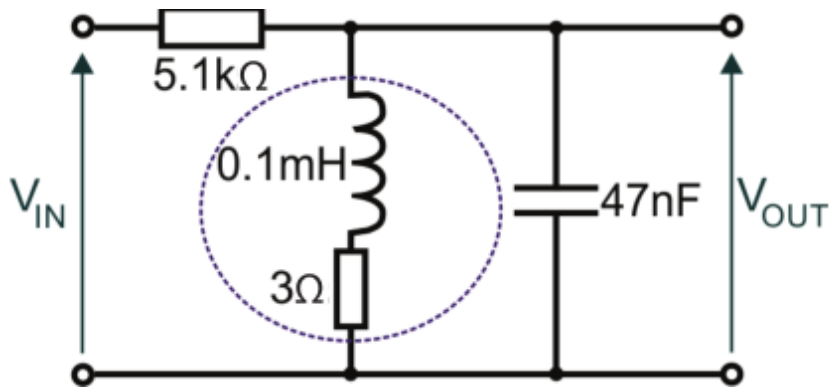

- (c) Determine the bandwidth of this filter.

$$Q = \frac{2\pi f_0 L}{r_L} = \frac{2 \times \pi \times 73413 \times 0.1 \times 10^{-3}}{3} = 15.38$$

$$\text{Bandwidth} = \frac{f_0}{Q} = \frac{73413}{15.38} = 4773\text{ Hz}$$

Example 3

If the bandstop filter in Figure.(8) is to reject a 200-Hz sinusoid while passing other frequencies, calculate the values of L and C . Take $R = 150\Omega$ and the bandwidth as 100 Hz.

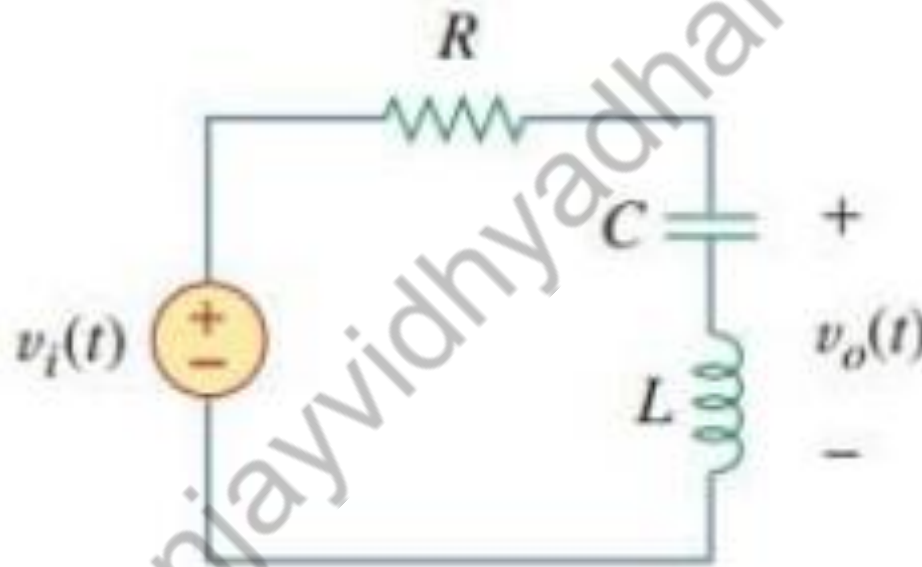


Figure 8. A bandstop filter.

Example 3

If the bandstop filter in Figure.(8) is to reject a 200-Hz sinusoid while passing other frequencies, calculate the values of L and C. Take $R = 150\Omega$ and the bandwidth as 100 Hz.

$$B = 2\pi(100) = 200\pi \text{ rad/s}$$

But

$$B = \frac{R}{L} \Rightarrow L = \frac{R}{B} = \frac{150}{200\pi} = 0.2387 \text{ H}$$

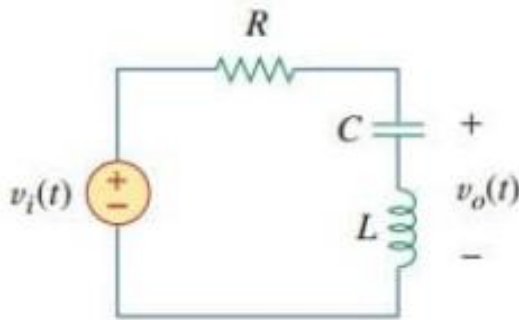


Figure 8. A bandstop filter.

Rejection of the 200-Hz sinusoid means that f_0 is 200 Hz, so that ω_0 in Figure.(9)


$$\omega_0 = 2\pi f_0 = 2\pi(200) = 400\pi$$

Since $\omega_0 = 1/\sqrt{LC}$,

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(400\pi)^2(0.2387)} = 2.653 \mu\text{F}$$

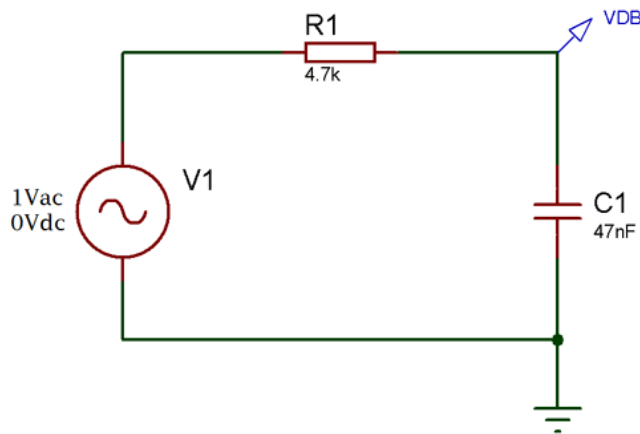Example 4

Find the cut-off frequency and Output voltage at 500Hz.



$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 4700 \times 47 \times 10^{-9}}$$

720 Hz


$$X_c = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 500 \times 47 \times 10^{-9}} = 6773 \text{ Ohms}$$

Then the Vout is when applied 5V Vin at 500Hz:-


$$V_{out} = V_{in} \times \frac{X_c}{\sqrt{R^2 + X_c^2}} = 5 \times \frac{6773}{\sqrt{4700^2 + 6773^2}} = 4.11V \text{ (Approx)}$$

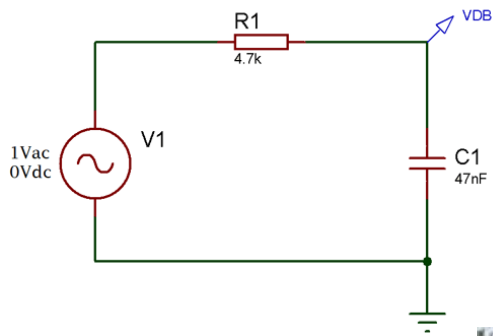Example 4

Find the cut-off frequency and Output voltage at 500Hz.




Demonstration in LT SPICE

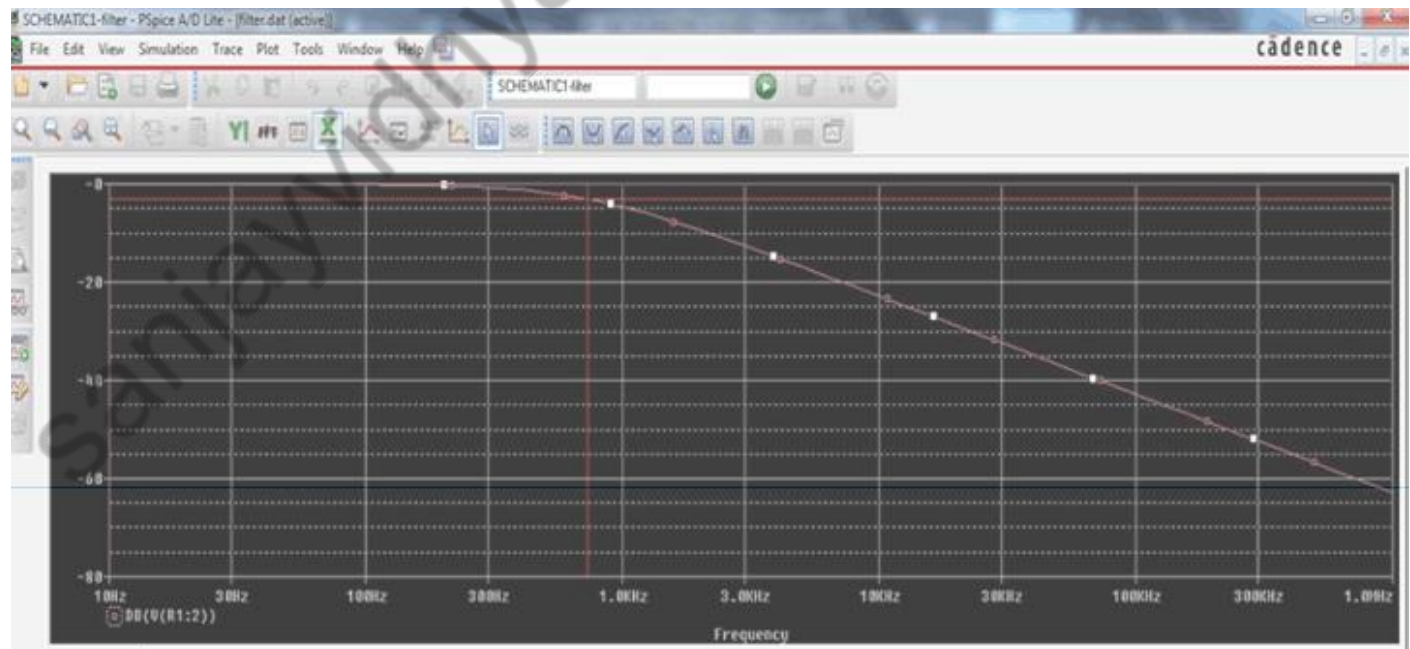


Example 5

Second Order Low Pass Filter:


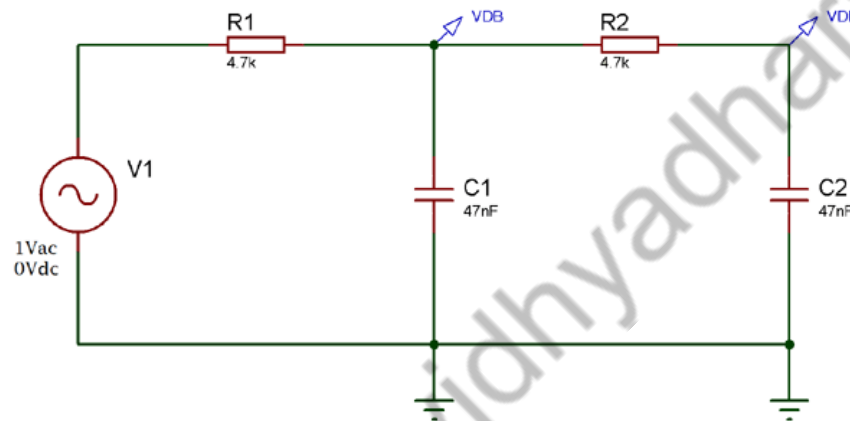


Demonstration in LT SPICE

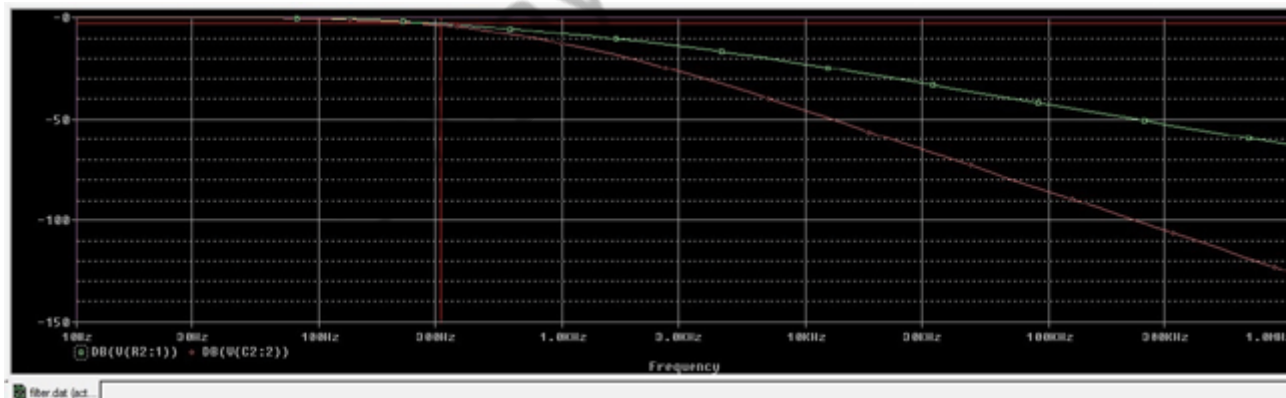


Example 6

Find equivalent RL Filter at

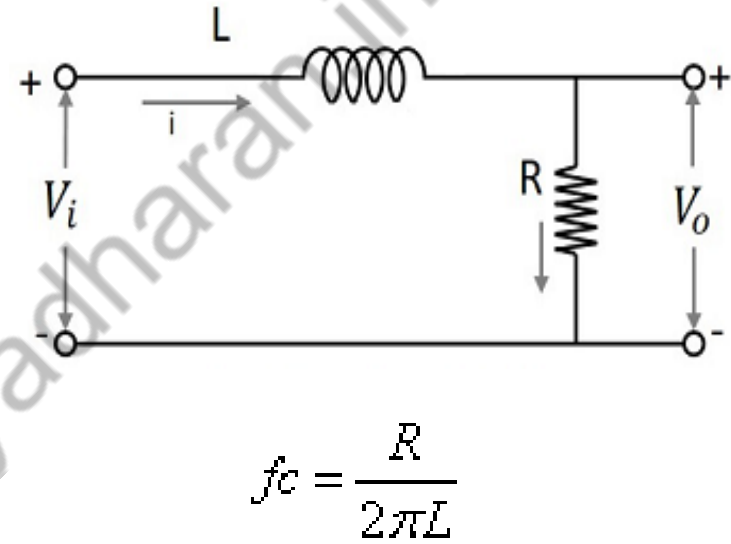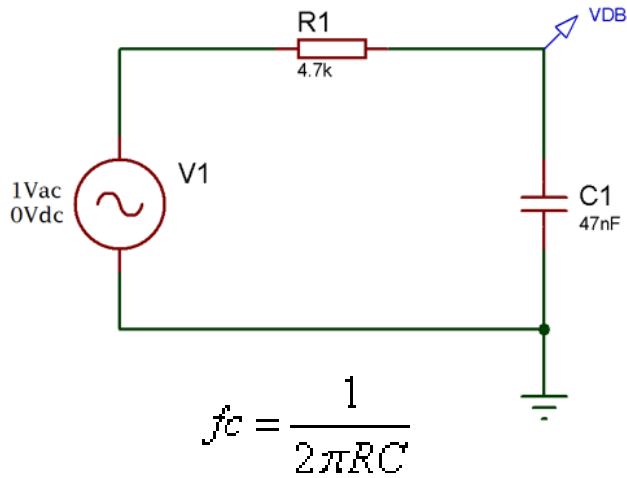

$L = 1 \text{ H}$

Demonstration in LT SPICE

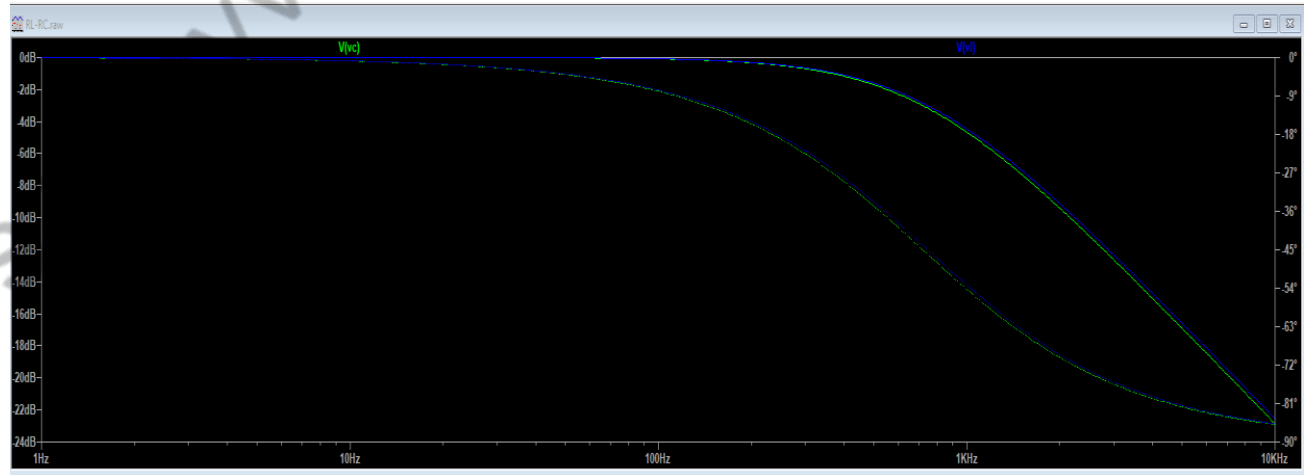

Example 7

Example: For a magnetic circuit, on no-load condition, core loss is, $P_c = 16 \text{ W}$; apparent power, $(VA)_{\text{rms}} = 20 \text{ VA}$, $E_{1_{\text{max}}} = 275 \text{ V}$, $N=200$ turns. Assuming a sinusoidal flux waveform, find:

- Power factor,
- Iron current, I_c
- Magnetizing current, I_m

(a) Core loss: $P_c = E_1 \cdot I_\phi \cdot \cos\theta_c$

$$pf = \cos\theta_c = \frac{P_c}{VA} = \frac{16}{20} = 0.8$$

(b) $P_c = E_1 I_\phi \cos\theta_c$, $E_{1_{\text{rms}}} = \frac{275}{\sqrt{2}} = 194.5 \text{ Volt}$

$$I_\phi = \frac{16}{(194.5)(0.8)} = 0.103 \text{ A}$$

$$I_c = I_\phi \cos\theta_c = (0.103)(0.8) = 0.082 \text{ A}$$

$$(c) I_m = I_\phi \sin\theta_c = (0.103) \sin(\cos^{-1}0.8) = 0.062 \text{ A}$$

Example 8

Example: A 50 Hz, two winding transformer is rated as 3 KVA, 220/110 Volt. This transformer is connected as a **step-up auto** transformer to deliver 330 V to a resistive load when the input is from a 220 V source. Assuming that the transformer is ideal find:

- a-) the value of the load resistance for which rated current will flow in each winding.
- b-) the power delivered by transformer ;

$$I_1 = \frac{3000}{220} = 13.65 \text{ Amp}$$

$$I_2 = \frac{3000}{110} = 27.3 \text{ Amp}$$

$$(a) R_L = \frac{330}{27.3} = 12.1 \Omega$$

$$(b) P_T = 13.65 \times 220 = 3000 \text{ Watt}$$

Example 9

A 460-V:2400-V transformer has a series leakage reactance of 37.2Ω as referred to the high-voltage side. A load connected to the low-voltage side is observed to be absorbing 25 kW, unity power factor, and the voltage is measured to be 450 V. Calculate the corresponding voltage and power factor as measured at the high-voltage terminals.

Secondary

$$I_2 = \frac{P_{load}}{V_{load}} = \frac{25000}{450} = 55.55 \text{ A} \quad \Rightarrow \quad \text{Primary current } I_1 = \frac{460}{2400} \times 55.55 = 10.65 \text{ A}$$

Primary voltage:

$$V_1 = j37.2 I_1 + V_2' \quad V_2' = \frac{2400}{460} \times 450 = 2347.8 \text{ V}$$

$$\Rightarrow V_1 = j37.2 I_1 + V_2' = j37.2 \times 10.65 + 2347.8 = 2347.8 + j396.18 = 2381.0 \angle 9.58^\circ \text{ V}$$

Power factor at primary terminals: $\cos(9.58^\circ) = 0.9861$ lagging

Thank you

sanjayvidhyadharan.in