



**BITS Pilani**

Hyderabad Campus

Department of Electrical Engineering



# Digital Design : 2020-21


## Lab 5

### Dataflow Modelling

### Implementation of Adders

### in Xilinx ISE

## By Dr. Sanjay Vidhyadharan

 


# New Concepts


- 1. Dataflow Modelling**
- 2. Initialization**

# VLSI Design Levels

## Common Abstraction Levels

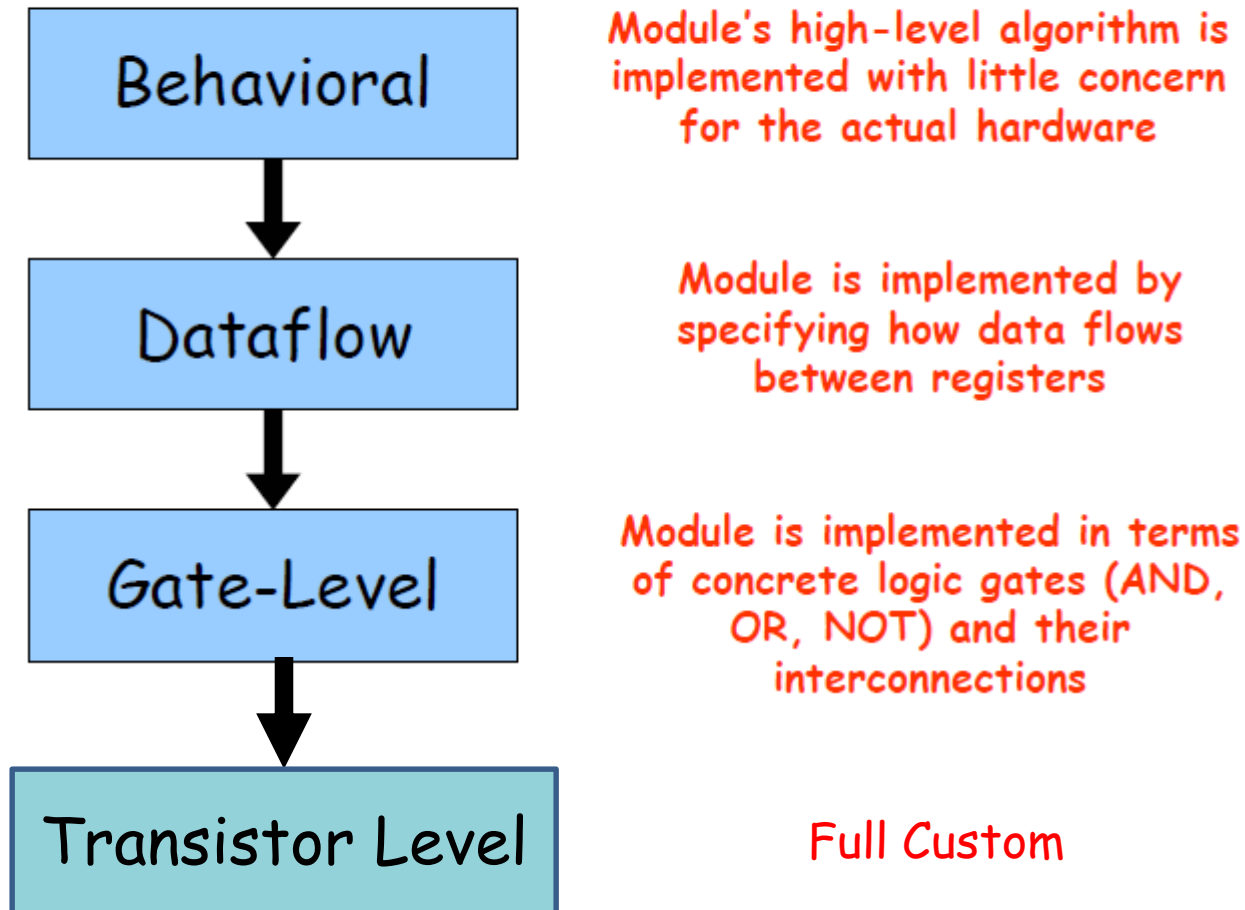


# Transistor Level

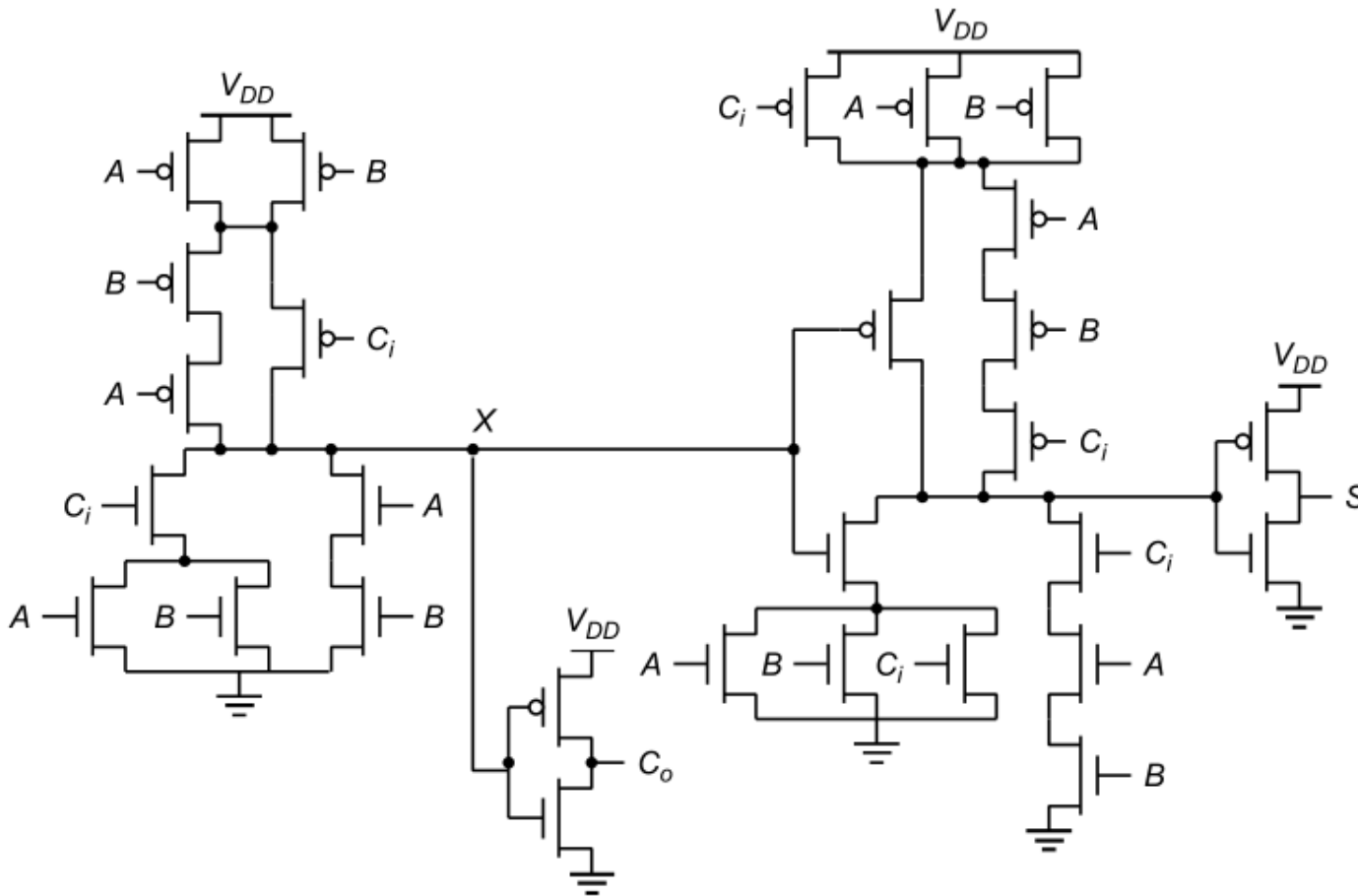


28 Transistors

# Transistor Level

 


# Gate Level Design

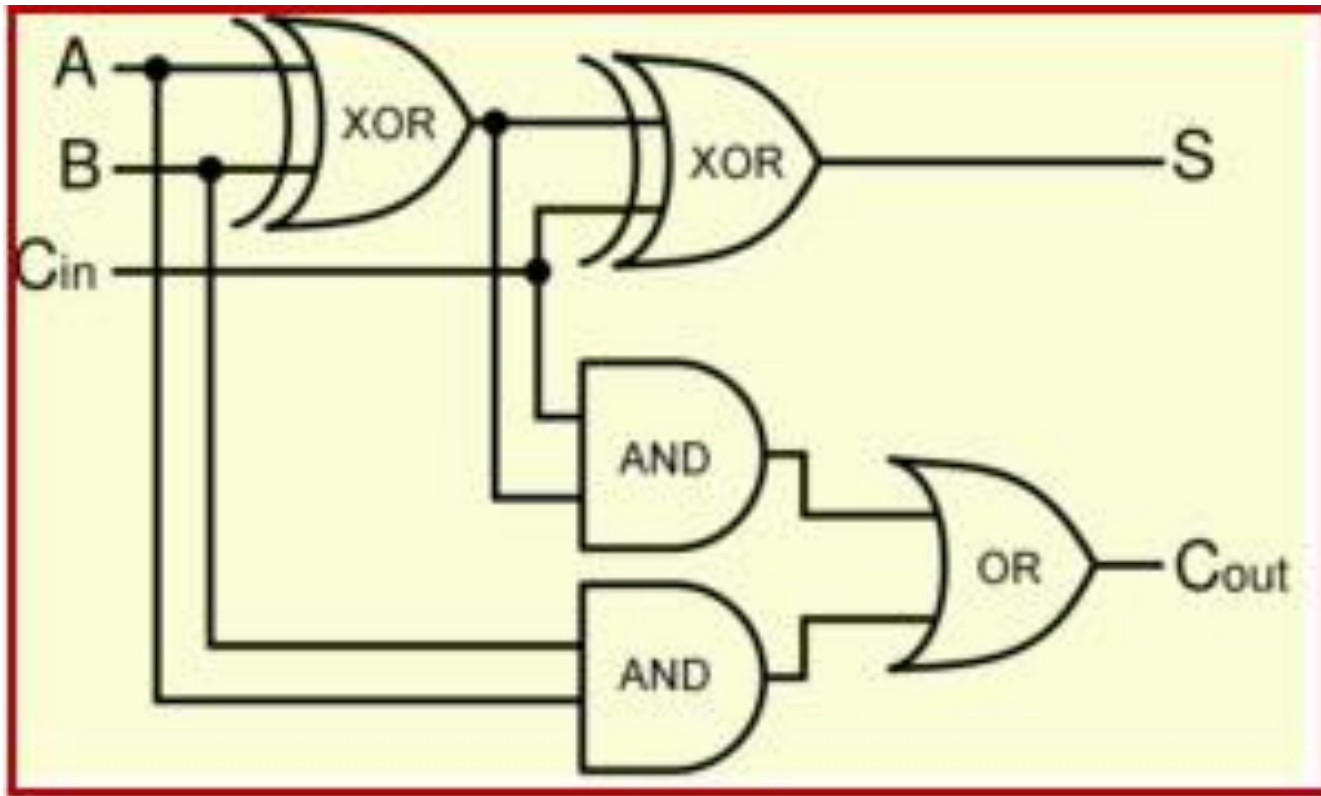

34 Transistors

# Dataflow Design

**GROW**

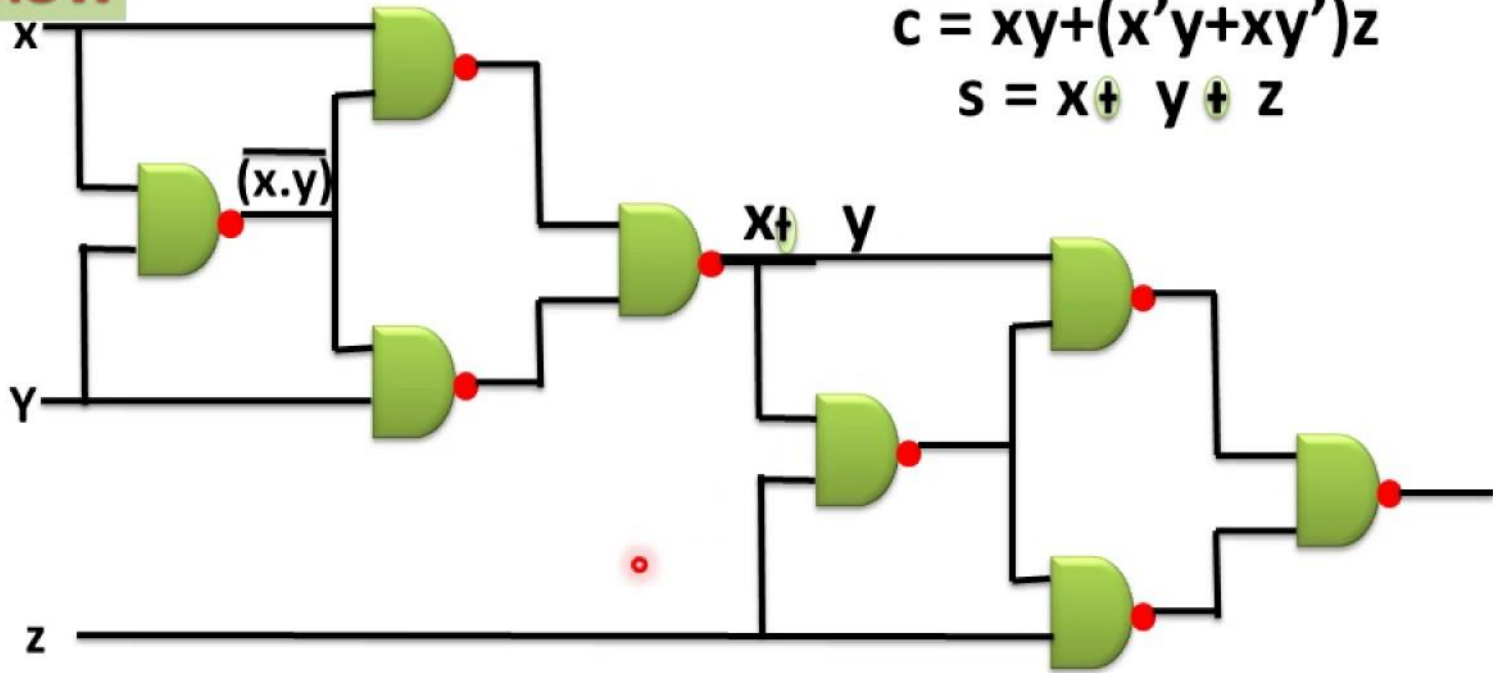

$$c = xy + (x'y + xy')z$$


$$s = x + y + z$$

**LEARN**

# Simple Circuit for Demonstration

## Gate Level Modelling

Simple Circuit to demonstrate HDL

 




# Simple Circuit for Demonstration

## Dataflow Modelling

Simple Circuit to demonstrate HDL

 

```
module Simple_circuit (input A,B,C, output x,y);
```

```
assign y=~C;
```

```
assign x=(A&B)|y;
```

```
endmodule
```

# Simple Circuit for Demonstration

## Verilog operators

Operator Token	Operator name
~	Bitwise negation (unary)
&	Bitwise and (binary)
&~	Bitwise nand (binary)
	Bitwise or (binary)
~	Bitwise nor (binary)
^	Bitwise exclusive or (binary)
^~ , ~^	Bitwise exclusive nor (binary)

# Simple Circuit for Demonstration

## Initialization:

$$F = (AB + \bar{C}) \cdot (CD + \bar{E})$$

```
module Simple_circuit (input A, input B,  
input C, output x, output y);  
wire w1;  
and g1 (w1,A,B); // and gate instance  
not g2 (y,C);  
or g3 (x,w1,y);  
endmodule
```

## Gate level modeling


```
module Simple_circuit2 (input A,B,C,D,E output F);  
wire w1,w2,w3,w4;  
  
Simple_circuit g1 (A,B,C,w1,w2);  
Simple_circuit g2 (C,D,E,w3,w4);  
and g3 (F,w1,w3);  
  
endmodule
```

# Problem Definition

## 1. Half Adder with dataflow modelling


```
module ha(  
    input a, b,  
    output c, s  
);
```

```
assign  
assign  
endmodule  
,
```

 


# Problem Definition
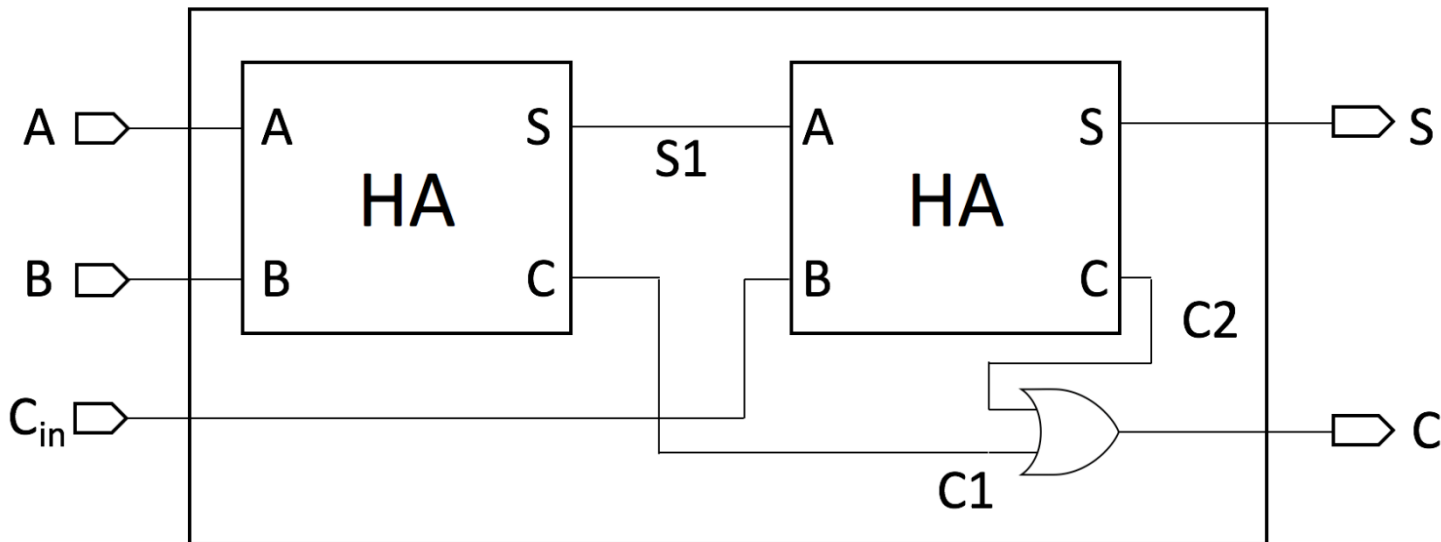
## 2. Full Adder using Half Adder with Gate level modeling



# Home Assignment

## 4-bit Parallel Adder

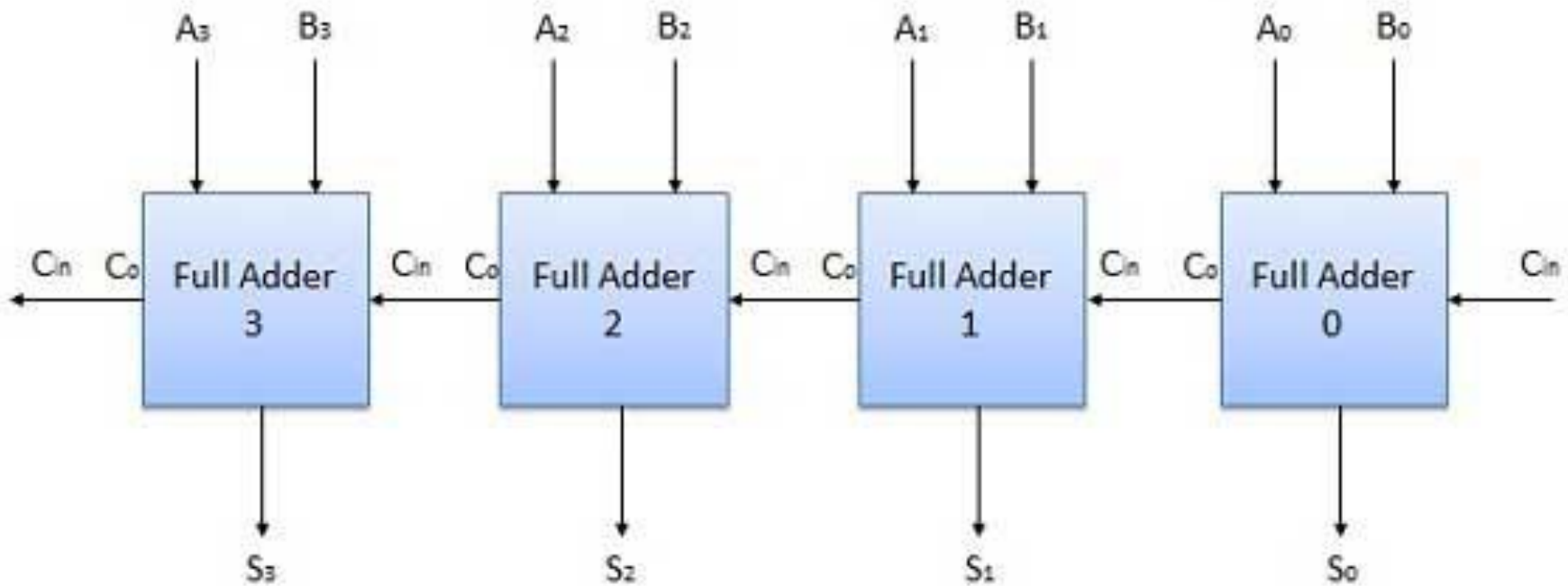



# Demonstration