



BITS Pilani

Hyderabad Campus

Department of Electrical Engineering



Digital Design : 2020-21

Lab 6


Dataflow Modelling

Implementation of 4-Bit Adder & BCD

Adder

in Xilinx ISE


By Dr. Sanjay Vidhyadharan

 

New Concepts

- 1. Handling multi-bit data**
- 2. Concatenation to group data {}**

Demonstration : 4-bit Adder

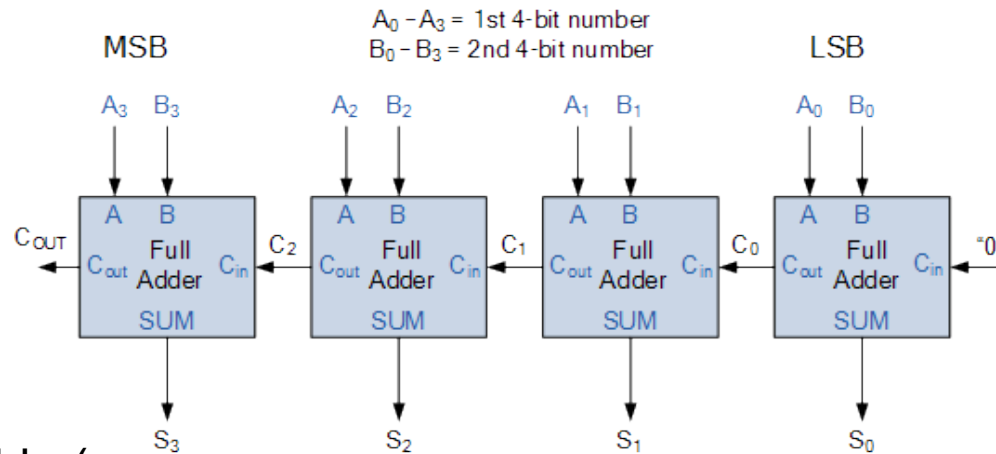

```

module Four_bit_adder(
    input [3:0] A,
    input [3:0] B,
    output [3:0] Sum,
    output Carry );

assign {Carry,Sum}=A+B;


endmodule
    
```

Remarks

[3:0] [MSB:LSB]


Concatenation

Problem 1: BCD Adder

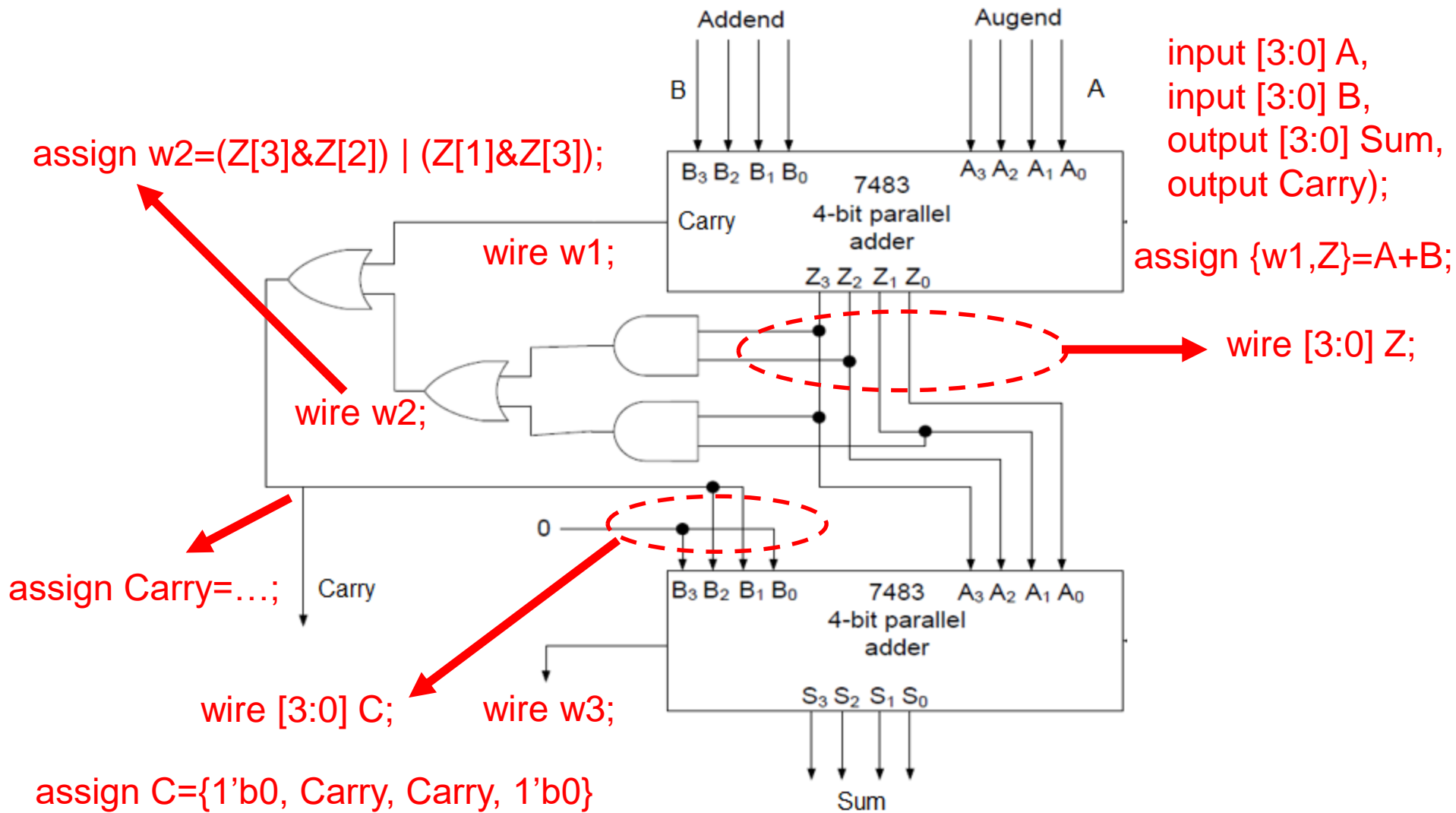

Additional Home Assignment

4-Bit Adder Subtractor

 

input [3:0] A,
input [3:0] B,
input M,
output [3:0] Sum,
output Carry,
output Overflow);

```
wire [3:0] X,Y,Z;
assign X= A&7; \\ (A& 4'b0111)
assign Y= (B^{M,M,M,M})&7;
assign Z=X+Y+M;
assign Overflow=Carry^Z[3];
```

```
assign {Carry,Sum} = A+(B^{M,M,M,M})+M;
```



Demonstration