



BITS Pilani

Hyderabad Campus

Department of Electrical Engineering




Digital Design : 2020-21

Lab 8


**Sequential Circuit Design using
D and JK Flipflops**

By Dr. Sanjay Vidhyadharan

 

The 74HCT74 D Flipflop

Connection Diagram

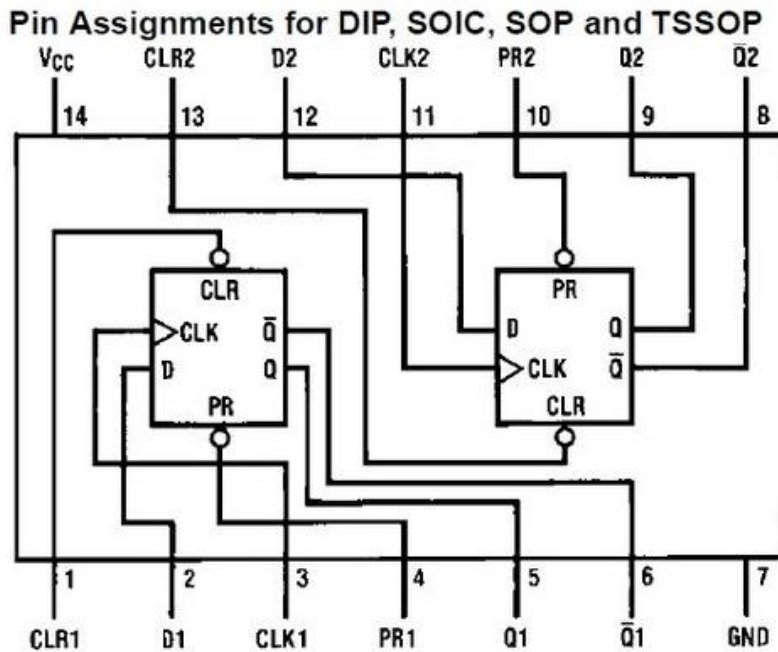

Truth Table


Inputs				Outputs	
PR	CLR	CLK	D	Q	\bar{Q}
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H (Note 1)	H (Note 1)
H	H	\uparrow	H	H	L
H	H	\uparrow	L	L	H
H	H	L	X	Q0	$\bar{Q}0$

Note: Q0 = the level of Q before the indicated input conditions were established.


Note 1: This configuration is nonstable; that is, it will not persist when pre-set and clear inputs return to their inactive (HIGH) level.

The 74HCT74 D Flipflop

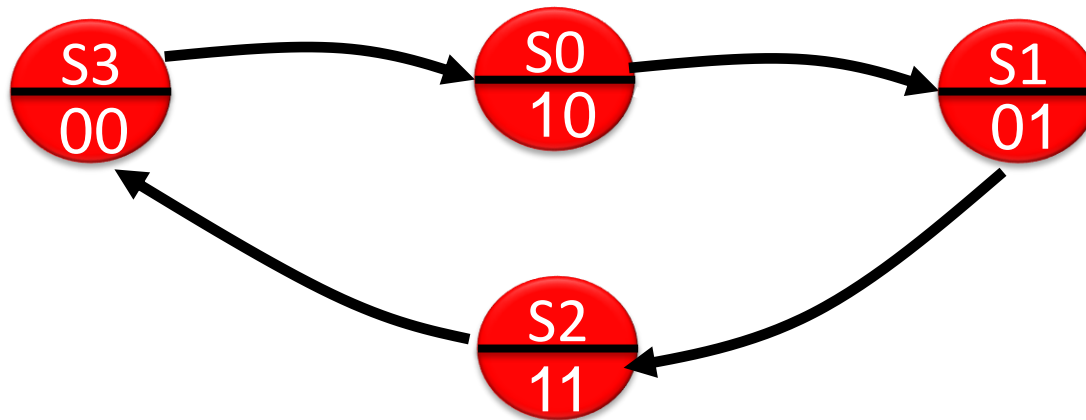Problem 1: Design a Counter using D-Flipflop as per state diagram given below:-



The 74HCT107 JK Flipflop

 


'LS107A
FUNCTION TABLE

INPUTS				OUTPUTS	
CLR̄	CLK	J	K	Q	Q̄
L	X	X	X	L	H
H	↓	L	L	Q ₀	Q̄ ₀
H	↓	H	L	H	L
H	↓	L	H	L	H
H	↓	H	H	TOGGLE	
H	H	X	X	Q ₀	Q̄ ₀

The 74HCT74 D Flipflop

 Problem 1: Design a Gray Counter using JK-Flipflop as per state diagram given below:-





Demonstration