



BITS Pilani

Hyderabad Campus

Department of Electrical Engineering




Digital Design : 2020-21

Lab 9

Combinational Circuit Design using Decoders and Multiplexers in Xilinx

By Dr. Sanjay Vidhyadharan

 

New Concepts

Conditional Statements

The Decoder

module

Decoder(a,b,c,d0,d1,d2,d3,d4,d5,d6,d7);

input a,b,c;

output d0,d1,d2,d3,d4,d5,d6,d7;

assign d0=(~a&~b&~c),

d1=(~a&~b&c),

d2=(~a&b&~c),

d3=(~a&b&c),


d4=(a&~b&~c),

d5=(a&~b&c),

d6=(a&b&~c),

d7=(a&b&c);

endmodule

 

The Conditional Statement

If statement in Verilog

```
if (sel == 1) f = a;  
else f = b;
```

Example : X is output of a Decoder, Y is output Function

```
begin  
    if (x[3] == 1'b1) y = 2'b11;  
    else if (x[2] == 1'b1) y = 2'b10;  
    else if (x[1] == 1'b1) y = 2'b01;  
    else y = 2'b00;  
end
```

The Decoder

```
module decoder (in,out);  
input [2:0] in;  
output [7:0] out;  
wire [7:0] out;  
assign out =  
(in == 3'b000 ) ? 8'b0000_0001 :  
(in == 3'b001 ) ? 8'b0000_0010 :  
(in == 3'b010 ) ? 8'b0000_0100 :  
(in == 3'b011 ) ? 8'b0000_1000 :  
(in == 3'b100 ) ? 8'b0001_0000 :  
(in == 3'b101 ) ? 8'b0010_0000 :  
(in == 3'b110 ) ? 8'b0100_0000 :  
(in == 3'b111 ) ? 8'b1000_0000 :  
8'h00;  
endmodule
```

The Decoder

Problem 1 : Design an Odd Parity Generator using a Decoder. Use Decoder as a verilog module.


```
module Parity(  
    input [2:0] A,  
    output F  
);
```

The Multiplexer

```

module m41 (out, a, b, c, d, s0, s1);
output out;
input a, b, c, d, s0, s1;
wire sobar, s1bar, T1, T2, T3, T4;
not (s0bar, s0), (s1bar, s1);
and (T1, a, s0bar, s1bar),
(T2, b, s0bar, s1),
(T3, c, s0, s1bar),
(T4, d, s0, s1);
or(out, T1, T2, T3, T4);
endmodule

```

 

The Multiplexer

```
module Mux(  
    input [7:0] I,  
    input [2:0] S,  
    output Y  
);  
assign Y = I[S];  
endmodule
```


The Multiplexer based FA

```
module FullAdder(  
    input A,  
    input B,  
    input C,  
    output Sum  
);  
wire [7:0] s;  
assign s = 8;  
Mux m1 (s,{A,B,C},Sum);  
endmodule
```

```
module Mux(  
    input [7:0] I,  
    input [2:0] S,  
    output Y  
);  
assign Y = I[S];  
endmodule
```

The Multiplexer based FA

Home Assignments

1. Parity Generator with Mux
2. Full Adder with Decoder