



**BITS Pilani**

Hyderabad Campus

Department of Electrical Engineering




# Digital Design : 2020-21

## Lab 2

# Parity Generator & Adders

**By Dr. Sanjay Vidhyadharan**

 

# Parity Generator




3-bit Message			Odd Parity Bit
X	Y	Z	
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

# Parity Generator

3-bit Message			Even Parity Bit
X	Y	Z	
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


# Parity Generator

## EX-OR Gate As Buffer and Inverter

   

Control	A	F	
0	0	0	} Pass
0	1	1	
1	0	1	} Invert
1	1	0	


# Parity Generator

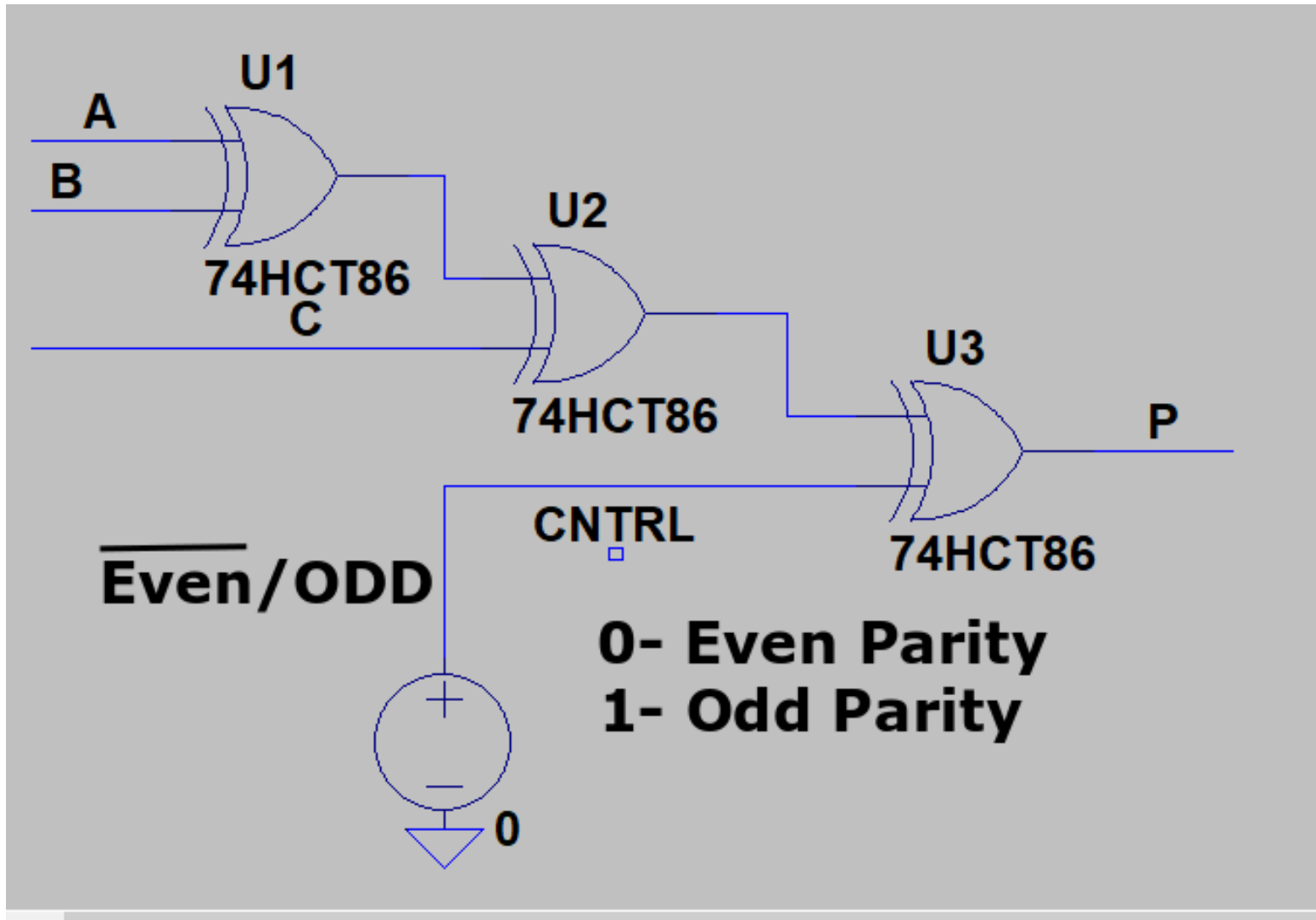

# Binary to Gray Converter

## Problem 1: Binary to Gray Converter

Decimal Number	4 bit Binary Number <u>ABCD</u>	4 bit Gray Code <u>G<sub>1</sub>G<sub>2</sub>G<sub>3</sub>G<sub>4</sub></u>
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

 

# Half Adder

## Problem 2: Half Adder



Truth Table

Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum}(S) = x \oplus y$$


$$\text{Carry}(C) = xy$$

Block Diagram

  

# Full Adder

## Problem 3: Full Adder

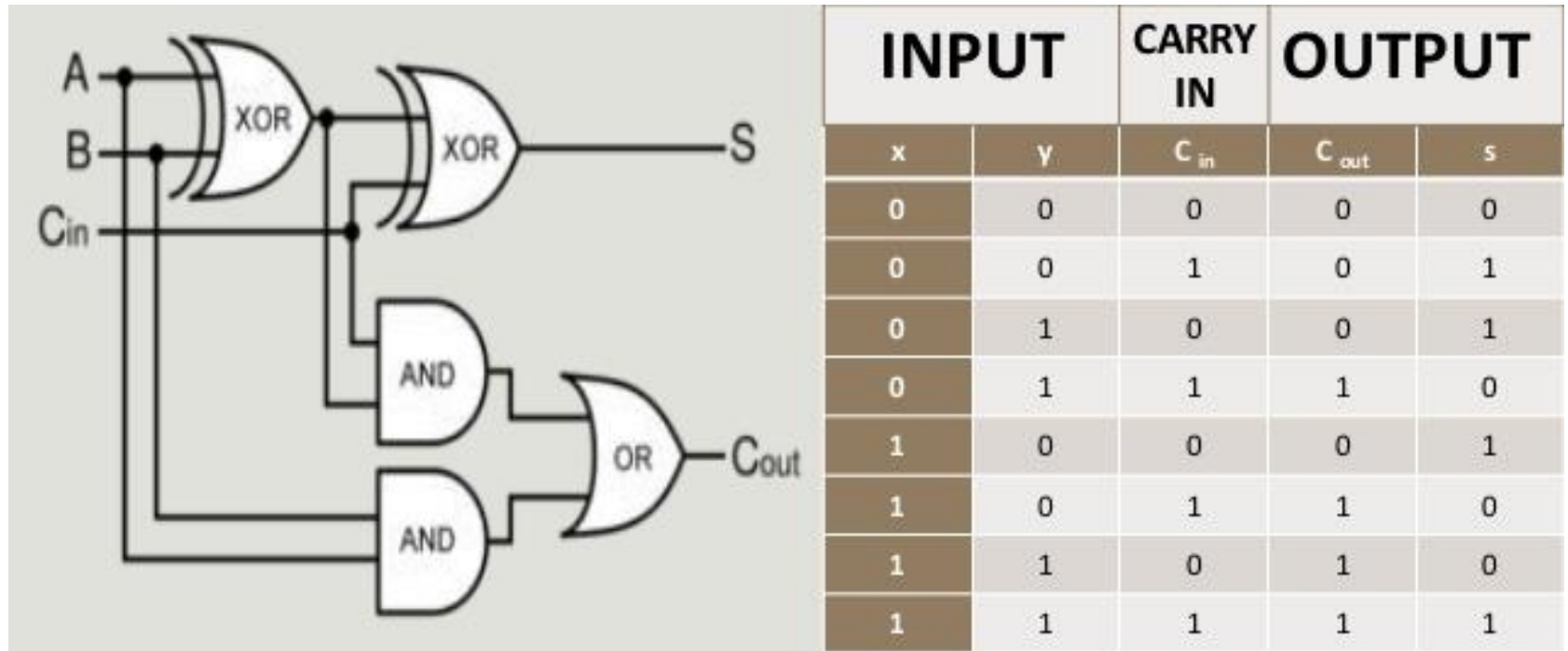

FULL ADDER CIRCUIT & TRUTH TABLE





# Demonstration