

Digital Electronics and Computer Organization

Digital Design

Lecture 15: Sequential Logic & SR Latch



Birla Institute of Technology & Science, Pilani
Hyderabad Campus

Innovate

achieve

lead



Sequential Circuits

Combinational circuits – The outputs are **entirely dependent on current inputs**

Sequential circuits



– The outputs are dependent on **current inputs as well as present state of storage elements**

Next state = external inputs + present state



Sequential Circuits

Classification

Synchronous Sequential circuits

Asynchronous Sequential circuits






Sequential Circuits

Asynchronous sequential circuits

The transition from one state to another is initiated by the change in the primary inputs there is **no external synchronization**

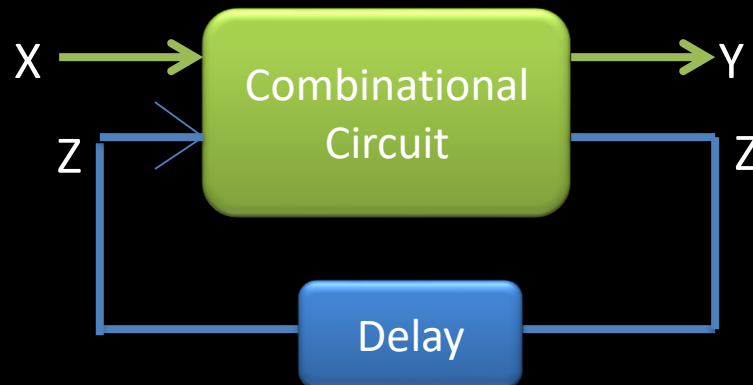The memory commonly used are **time-delayed devices**



May be regarded as **combinational circuits with feedback.**


May become **unstable**




Sequential Circuits

Synchronous sequential circuit

 Synchronous sequential circuits **change their states and output values at discrete instants of time**



 
Synchronization is achieved by a **timing device called clock generator**



Clock generator generates a clock signal having the form of a **periodic train of pulses**



Sequential Circuits

 

Clocked synchronous sequential circuit

Storage elements are **flip-flops**

Output value stored in flip-flop when clock occurs

Prior to the occurrence of the clock **the combinational output must be stable**

Speed of the **combinational logic is critical**




Storage elements

Maintains a binary state indefinitely until directed by an input signal to switch states

Latches

Storage elements that operate with signal levels (rather than signal transitions)

Latch active

 

Level Sensitive

Flip-Flops

Storage elements that are controlled by clock transitions

Edge Sensitive




Storage elements

Maintains a binary state indefinitely until directed by an input signal to switch states

Latches

Storage elements that operate with signal levels (rather than signal transitions)

Level Sensitive

 


Flip-Flops

Storage elements that are controlled by clock transitions

Edge Sensitive




Storage elements

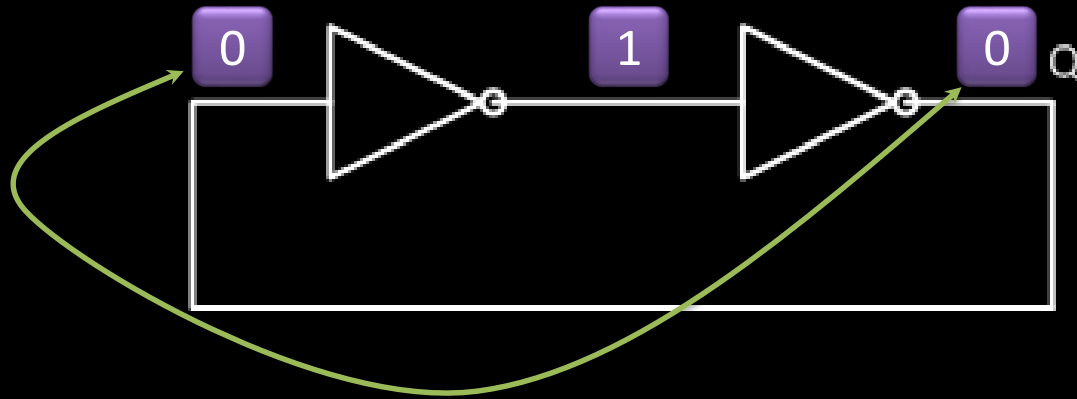

Storing 0



Storage elements


 


Storing 0

Is there any way to control the storage value ?




NOR - NAND

  



Latches

SR Latch

 

Reset = 0, Set = 0


No change in outputs

New state = Old state



Latches

SR Latch

 


Reset = 1, Set = 0 $Q = 0$ and $Q' = 1$

Reset operation



Latches

SR Latch

 


Reset = 0, Set = 1 $Q = 1$ and $Q' = 0$

Set operation



Latches

SR Latch

 

Reset = 1, Set = 1 $Q = 0$ and $Q' = 0$ But

Reset = 0, Set = 0

Cant predict output - > metastable state



Latches

SR Latch

Cant predict output - \rightarrow metastable state


Set = 1, reset = 1 is thus forbidden state

S	R	Q	Q'	
0	0	Q	Q'	No change
0	1	0	1	Reset
1	0	1	0	set
1	1	0	0	Forbidden



Latches

S'R' Latch

 



Latches

S'R' Latch

S	R	Q	Q'
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q	Q'

Forbidden

Set


Reset

No change



Latches

S'R' Latch

 

$Reset' = 1, Set' = 1$


No change in outputs

New state = Old state



Latches

S'R' Latch

 


Reset' = 1, Set' = 0 $Q = 1$ and $Q' = 0$

set operation



Latches

SR Latch

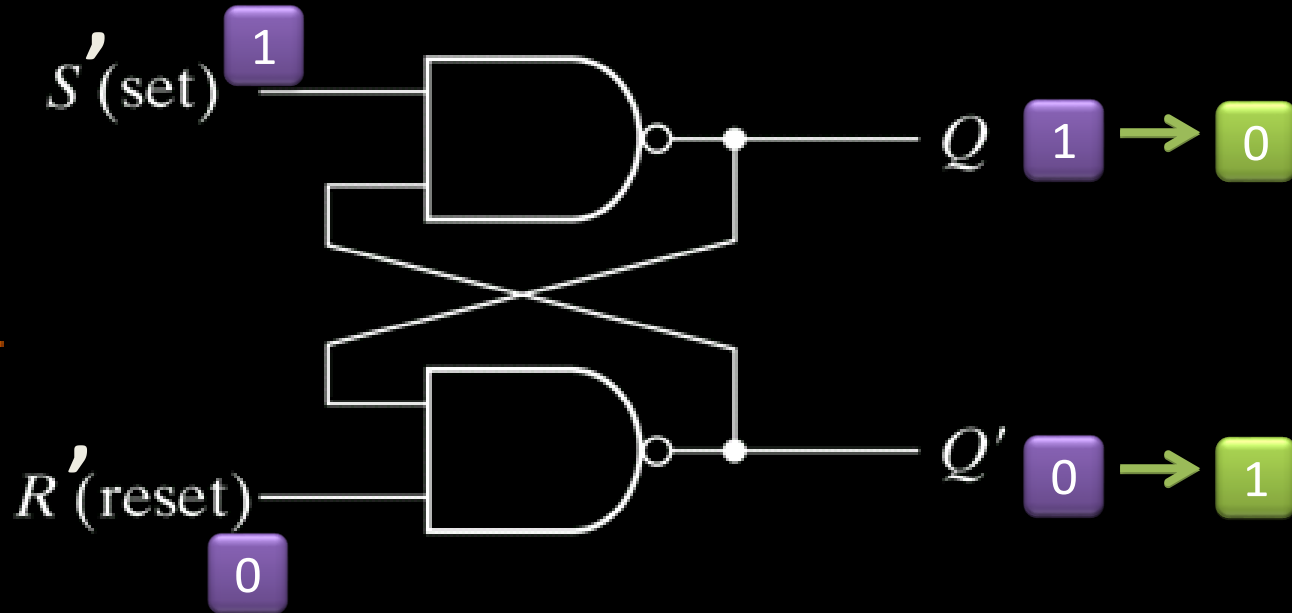


Reset' = 0, Set' = 1 $Q = 0$ and $Q' = 1$

Reset operation



Latches

SR Latch

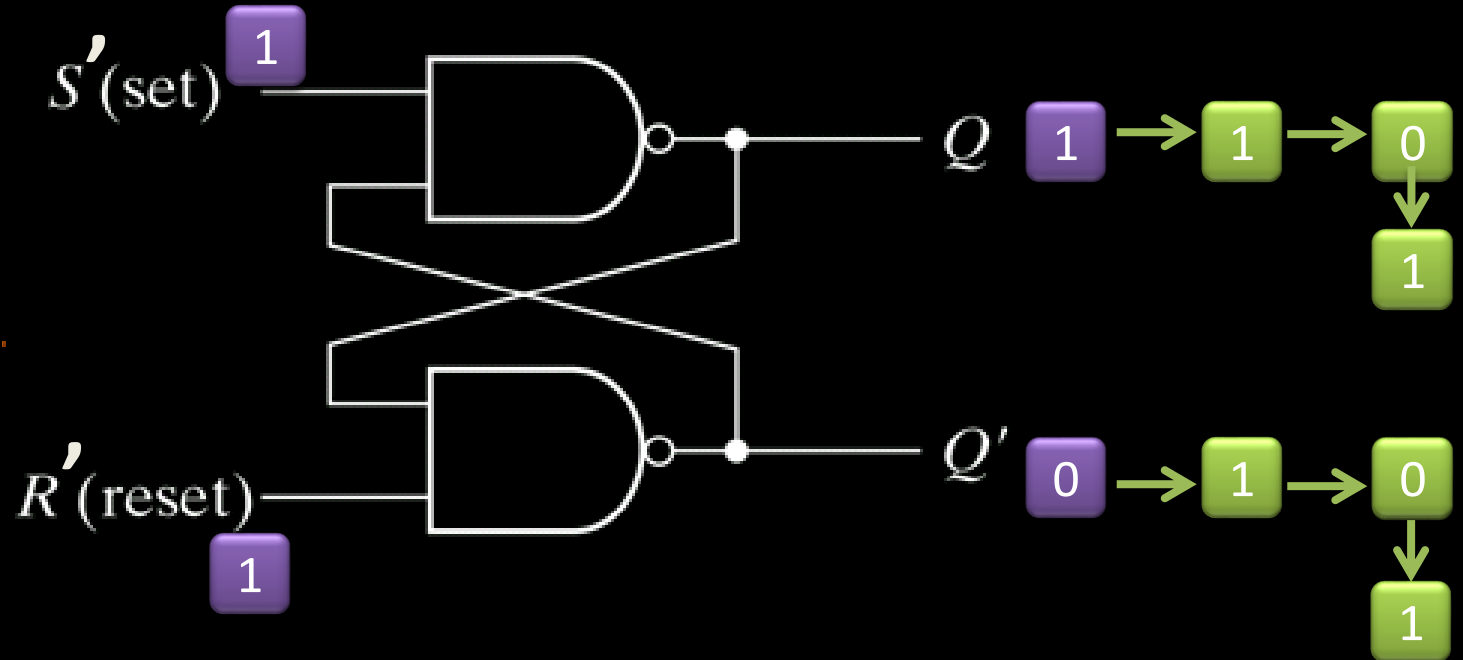

$Reset' = 0, Set' = 0$ $Q = 1$ and $Q' = 1$ But

$Reset' = 1, Set' = 1$

Cant predict output - > metastable state



Latches


S'R' Latch

S	R	Q	Q'	
0	0	1	1	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q	Q'	No change



Latches


SR Latch with enable

 



Latches

SR Latch with enable

 



Thank You
