

Digital Electronics and Computer Organization

Digital Design

Lecture 16 : D-Latches and D-Flipflops



Birla Institute of Technology & Science, Pilani
Hyderabad Campus

2020

Innovate

achieve

1


lead



Latches



SR Latch with Enable

 



Latches



D Flip-flop circuit





Latches



D Latch with Enable

En	D	Q	Q'	
0	X	Q	Q'	No change
1	0	0	1	Reset
1	1	1	0	Set

$D = 0$ makes $S = 0$ and $R = 1$


$D = 1$ makes $S = 1$ and $R = 0$



Latches



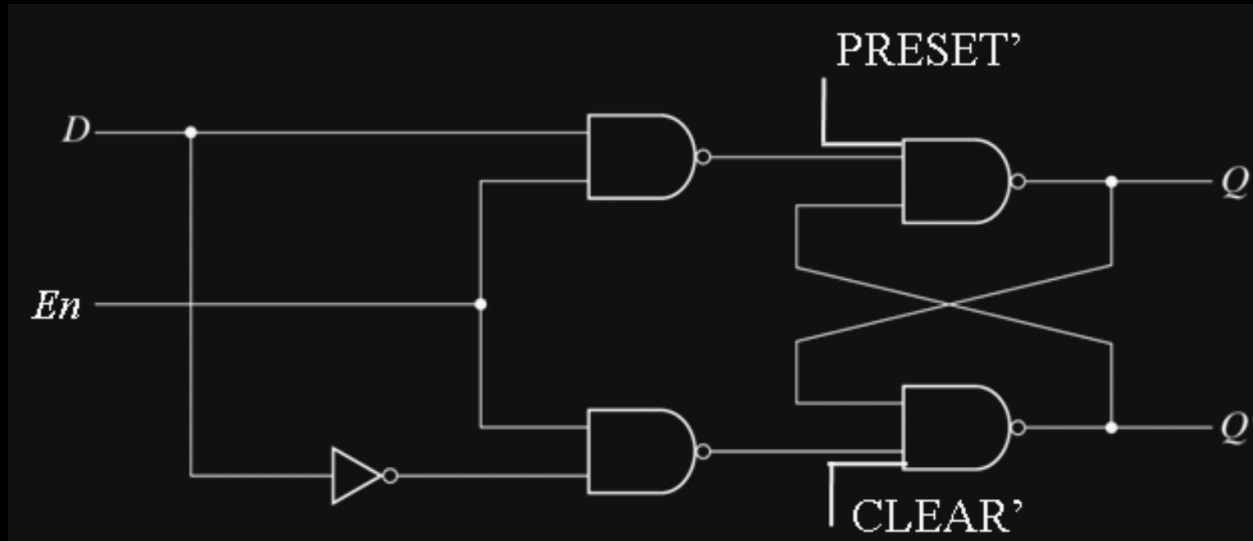D Latch with Asynchronous PRESET and CLEAR



Activating PRESET' (i.e. 0) makes $Q=1$. This in turn maintains $Q'=0$


Activating CLEAR' (i.e. 0) makes $Q'=1$. This in turn maintains $Q=0$




Latches




Graphic Symbols

 

SR Latch

 

S'R' Latch

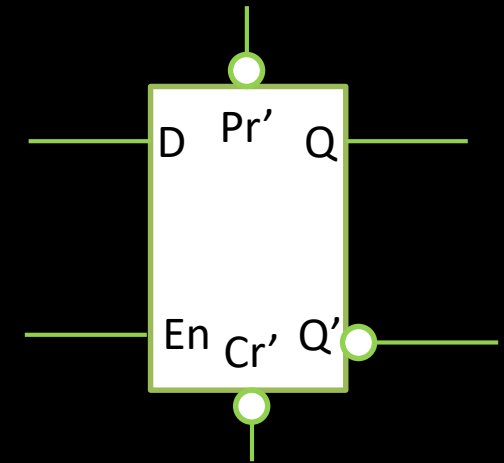


D Latch




Sequential Circuits

 Latch – Responds to change in level of clock pulse




 The key to the proper operation of a flip flop is to trigger it only during signal transition.





Race around in Latches

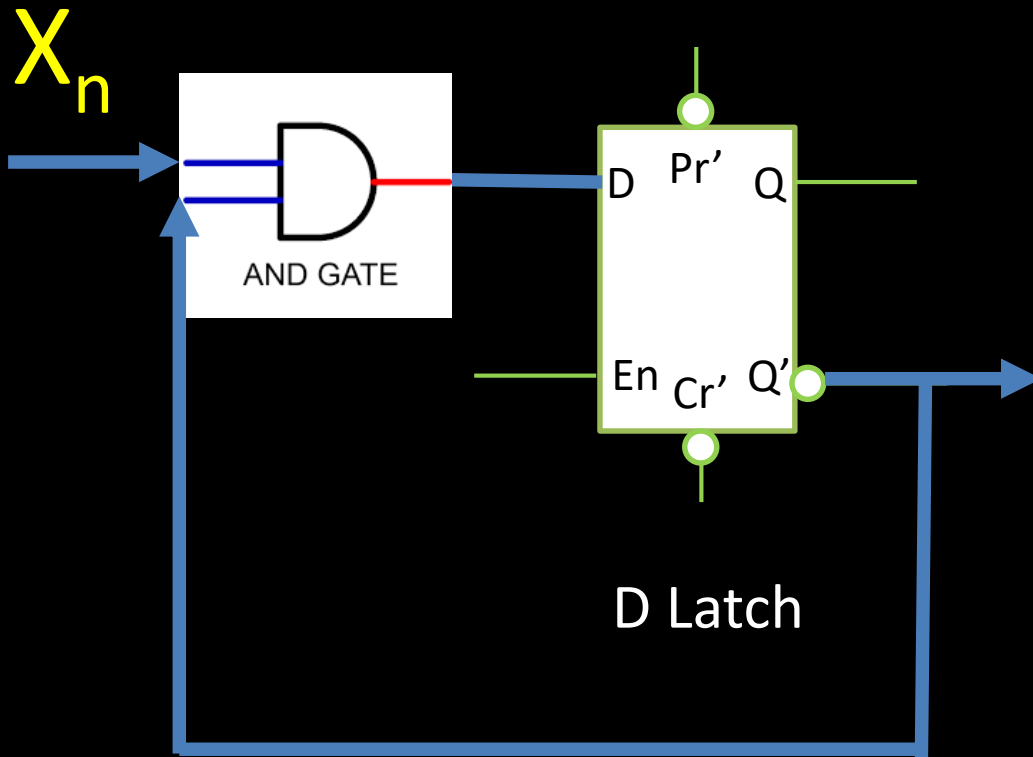

$$Y_n = X_n \cdot X_{n-1}$$



Flip-Flops



Two ways to build a flip flop

Special configuration of two latches to isolate the output of flip-flop

Gate based design which triggers only during signal transition of clock and is disabled during rest of clock pulse



Master Slave Flip-flop

  

If D changes

Y will be affected and not Q

If D changes

Y remains unaffected and Q stable


-ve Edge Triggered



Edge Triggered D Flip-Flops



Master Slave Flip-flop

 

CLK




D





Edge Triggered D Flip-Flops


Master Slave Flip-flop

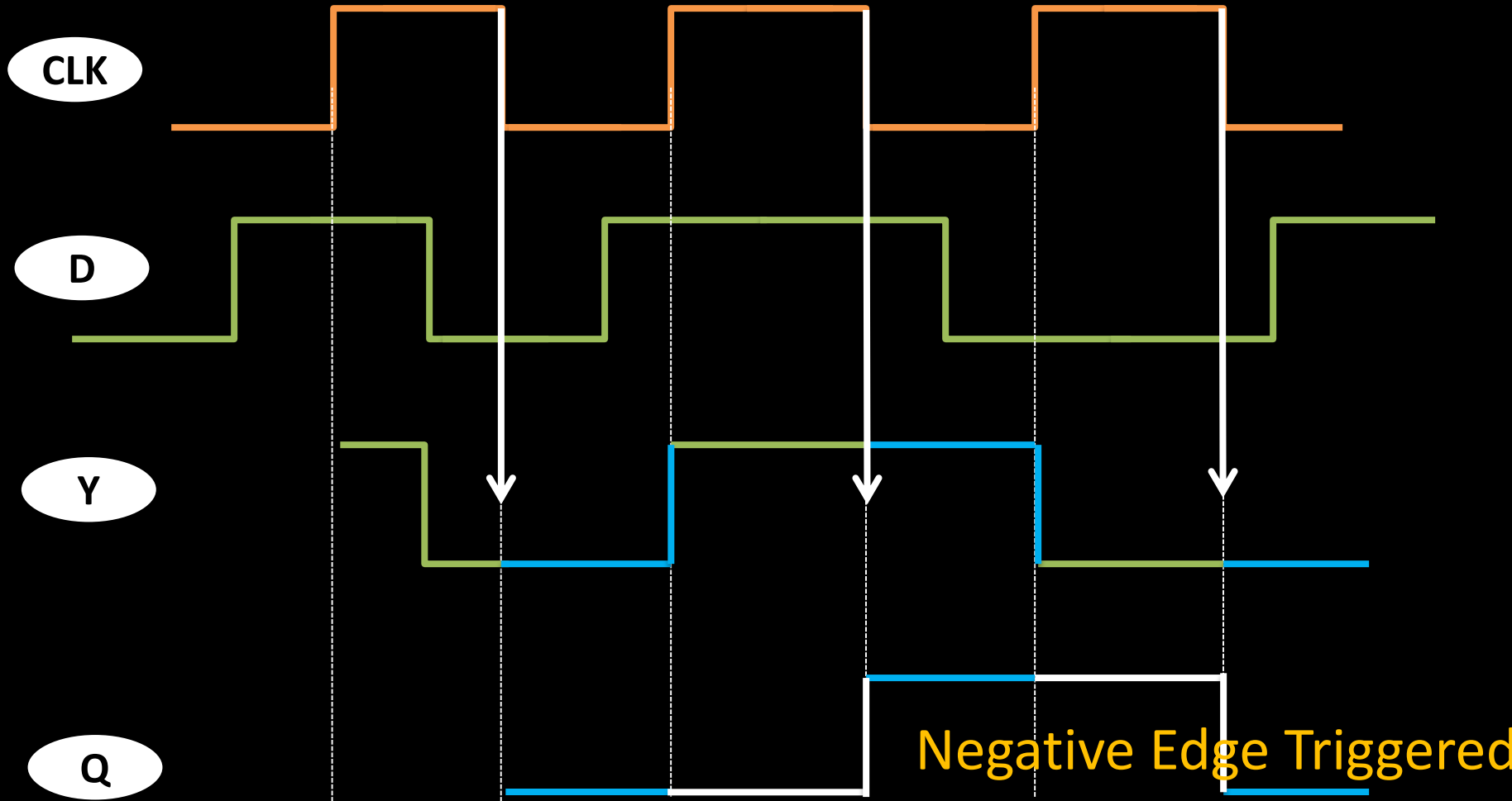



Edge Triggered D Flip-Flops

D-type positive edge triggered

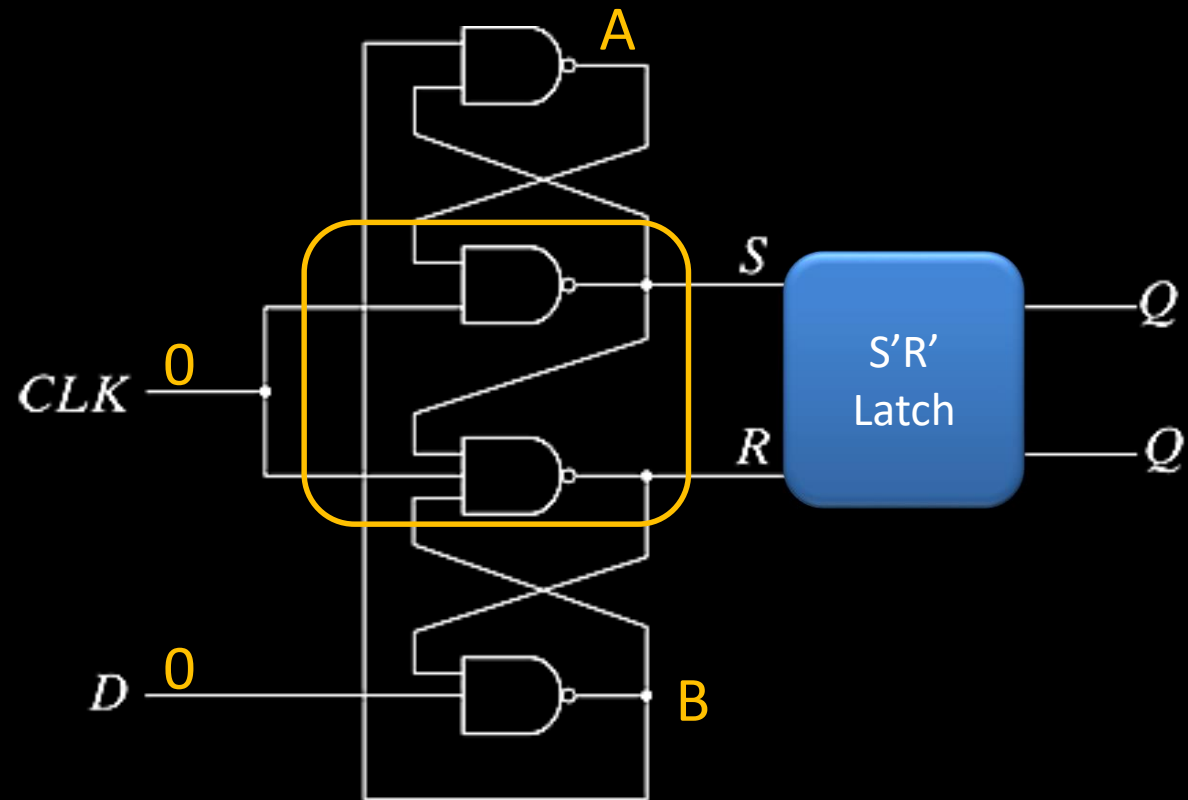

Case 2:

$CLK = 1, D=0, S=1, R=0$

$B=1, A=0$

$D \rightarrow 0 \rightarrow 1 \rightarrow 0$

$B = 1$ Since $R=0$

Case 3:

$CLK = 1, D=1, S=0, R=1$

$B=0, A=1$

$D \rightarrow 1 \rightarrow 0 \rightarrow 0$

$B \rightarrow 0 \rightarrow 1 \rightarrow 0$

$R=1$ Since $S=0$


$A=1$ Since $S=0$

Hence Initial state of Q and Q' is maintained



Edge Triggered D Flip-Flops

D-type positive edge triggered

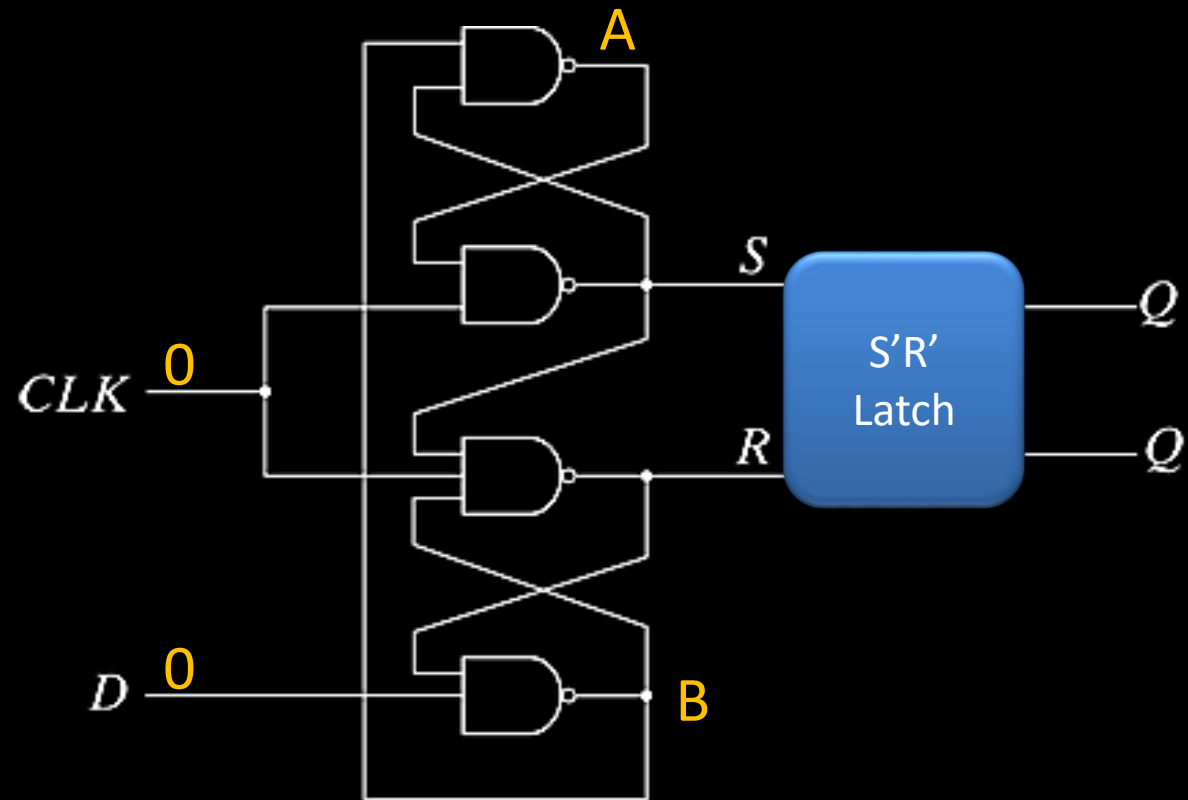

Case 4:

CLK = 0 , D=0, S=1, R=0

B=1, A=1, Q=0

D ->1

B=0

CLK->1

R=1

A=1


S=0

Q=1



Edge Triggered D Flip-Flops

D-type positive edge triggered

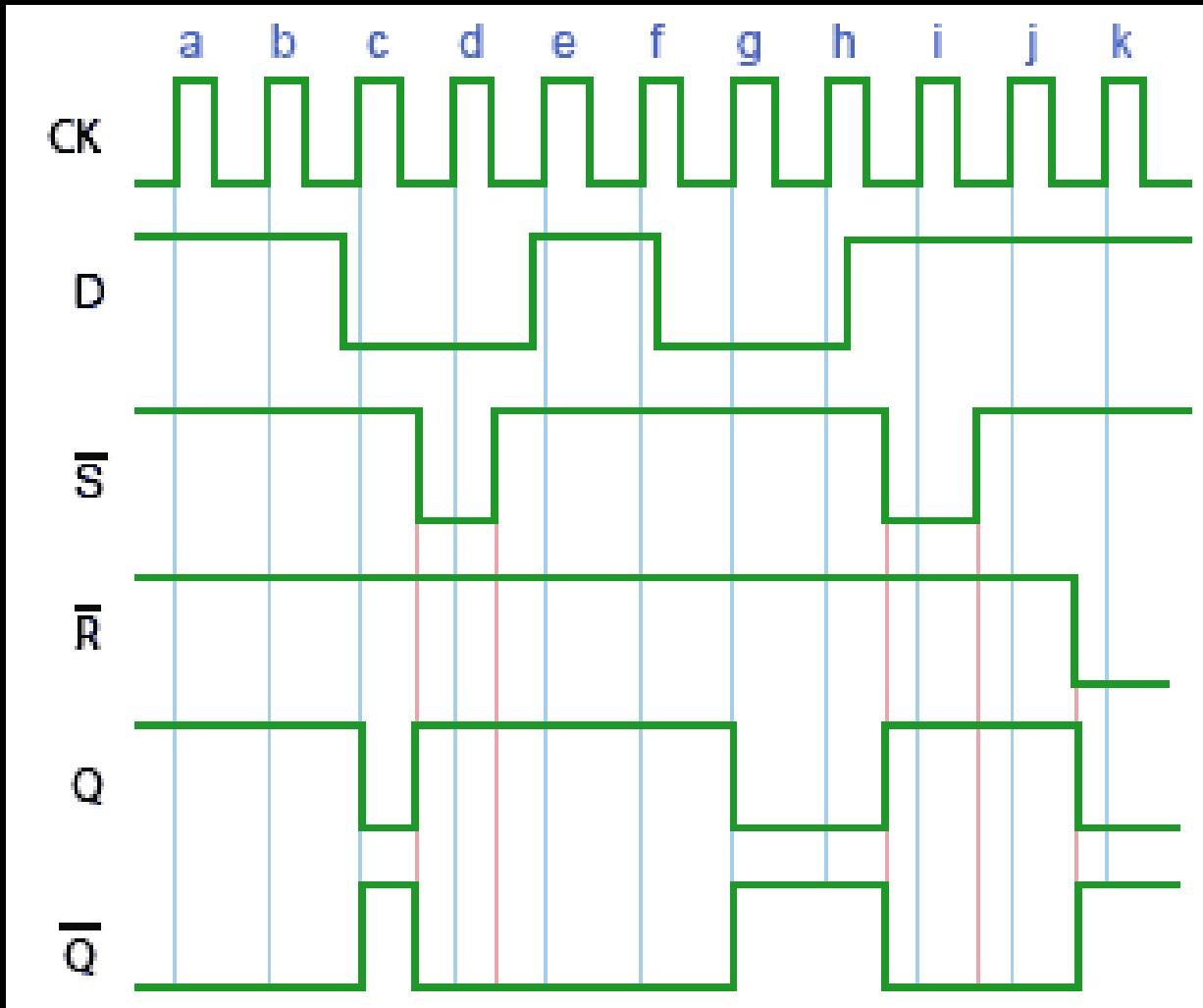



Thank You