

# Digital Electronics and Computer Organization

## Digital Design

### Lecture 17: T & JK Flip-Flops



**Birla Institute of Technology & Science, Pilani**  
Hyderabad Campus

10/3/2020





## Flip-Flops interconnection of gates

Edge Triggered D Flip-flop – Most efficient and economical (less number of gates)


## Other Flip-flops

JK Flip-flop


T Flip-flop



# Other Flip-Flops

 

JK Flip-flop

 


T Flip-flop



# Other Flip-Flops

## JK Flip-flop

### Characteristic Table

 


J	K	Q(t+1)	
0	0	Q(t)	No Change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Toggle/ Complement

### Characteristic Equation??

$$Q(t+1) = JQ' + K'Q$$

# Edge Triggered JK Flip-Flops



Positive Edge triggered

 



# Other Flip-Flops

## JK Flip-flop

  

Design J-K Flip-flop using D flip-flop

$$Q(t+1) = D$$

$$Q(t+1) = JQ' + K'Q$$


Analyze



# Other Flip-Flops

## JK Flip-flop

### Characteristic Table

 

J	K	Q(t+1)	
0	0	Q(t)	No Change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Toggle

Characteristic Equation??

$$Q(t+1) = JQ' + K'Q$$

$$Q(t+1) = J'K'.Q + J'K.0 + JK'.1 + JKQ'$$


$$Q(t+1) = J'K'.Q + JK'Q + JK'Q' + JKQ'$$

$$Q(t+1) = K'Q(J' + J) + JQ'(K + K')$$



# Other Flip-Flops

## T Flip-flop

 

## Characteristic Table

T	Q(t+1)
0	Q(t)
1	Q'(t)



No Change      Toggle

Characteristic Equation??

$$Q(t+1) = T \oplus Q$$

# Other Flip-Flops

## T Flip-flop

  

Design T Flip-flop using JK flip-flop


$$Q(t+1) = JQ' + K'Q$$

$$Q(t+1) = T \oplus Q = TQ' + T'Q$$





# Edge Triggered T Flip-Flops

Positive Edge triggered

 

# Other Flip-Flops

## T Flip-flop

  


Design T Flip-flop using D flip-flop

$$Q(t+1) = D$$

$$Q(t+1) = T \oplus Q$$
 
# Models of sequential circuits


Mealy Model – output depends on present state and input



Outputs change if the inputs change during the clock cycle
 
# Models of sequential circuits


Moore Model – output depends only on present state only



Outputs synchronized with clock





# Counter

 



# Asynchronous Counter

  



# Thank You