

# Digital Electronics and Computer Organization

## Digital Design

### Lecture 18: Sequential Circuit Design



**Birla Institute of Technology & Science, Pilani**  
Hyderabad Campus

11/6/2020

Innovate

achieve

1

lead



# Sequential Circuits

## Design Steps

1. Derive State diagram →
2. State table →
3. State Equations →
4. Circuit




# Design of Sequential Circuits

## Design

2-bit synchronous counter

Common clock for all the Flip-flops

## State Diagram

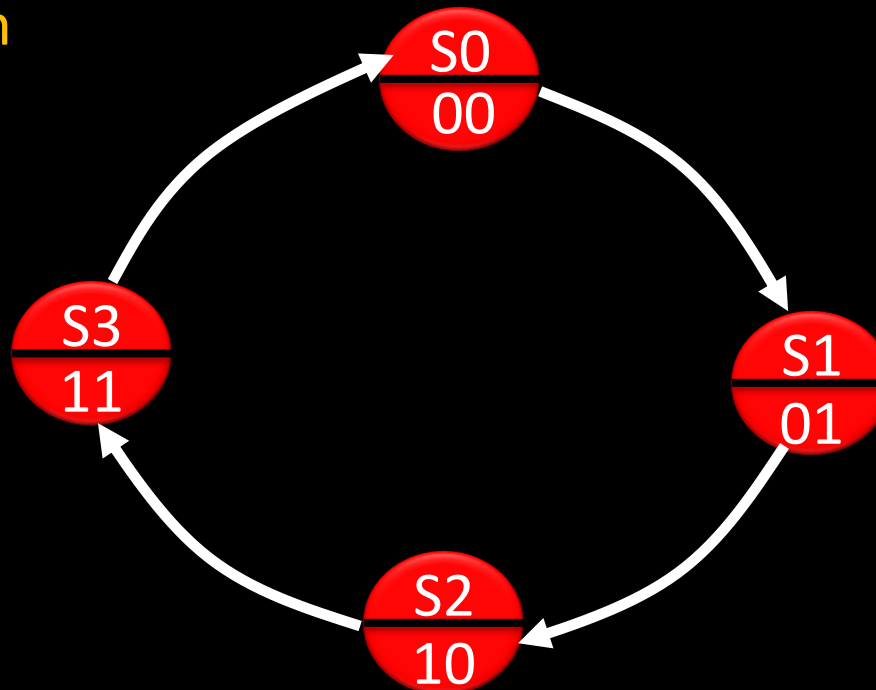



# Sequential Circuits

## State Table

Present State			Next State		
	$Q_B$	$Q_A$		$Q_B(t+1)$	$Q_A(t+1)$
S0	0	0	S1	0	1
S1	0	1	S2	1	0
S2	1	0	S3	1	1
S3	1	1	S0	0	0



# Excitation Tables

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

Characteristic Table

Q(t)	Q(t+1)	J	K	
0	0	0	X	(0 0) (0 1)
0	1	1	X	(1 0) (1 1)
1	0	X	1	(1 1) (0 1)
1	1	X	0	(1 0) (0 0)

Excitation Table



# Sequential Circuits

## State Table

## JK Flip-flop implementation

Present State			Next State		Flip-flop Inputs		Flip-flop Inputs		
	$Q_B$	$Q_A$		$Q_B(t+1)$	$Q_A(t+1)$	$J_B$	$K_B$	$J_A$	$K_A$
S0	0	0	S1	0	1	0	X	1	X
S1	0	1	S2	1	0	1	X	X	1
S2	1	0	S3	1	1	X	0	1	X
S3	1	1	S0	0	0	X	1	X	1

## State Equations

$$J_B = Q_A$$

$$K_B = Q_A$$

$$J_A = 1$$

$$K_A = 1$$



# Sequential Circuits


## State Equations

$$J_B = Q_A$$

$$K_B = Q_A$$

$$J_A = 1$$

$$K_A = 1$$

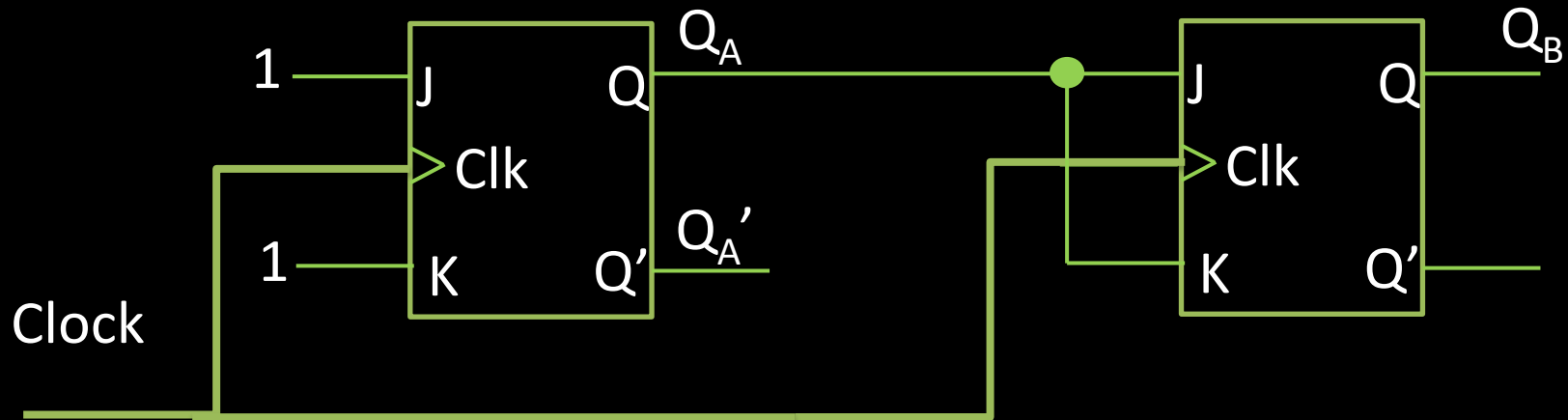



# Design of Clocked sequential Circuits

D	Q(t+1)
0	0
1	1

Characteristic Table

T	Q(t+1)
0	Q(t)
1	Q'(t)

Characteristic Table

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Excitation Table

Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table





# Sequential Circuits

## State Table

## D Flip-flop implementation

Present State			Next State			Flip-flop Inputs	
	$Q_B$	$Q_A$		$Q_B(t+1)$	$Q_A(t+1)$	$D_B$	$D_A$
S0	0	0	S1	0	1	0	1
S1	0	1	S2	1	0	1	0
S2	1	0	S3	1	1	1	1
S3	1	1	S0	0	0	0	0

## State Equations

$$Q_B(t+1) = D_B = Q_A \oplus Q_B$$

$$Q_A(t+1) = D_A = Q_A'$$




# Sequential Circuits

## State Equations


$$Q_B(t+1) = D_B = Q_A \oplus Q_B$$

$$Q_A(t+1) = D_A = Q_A'$$

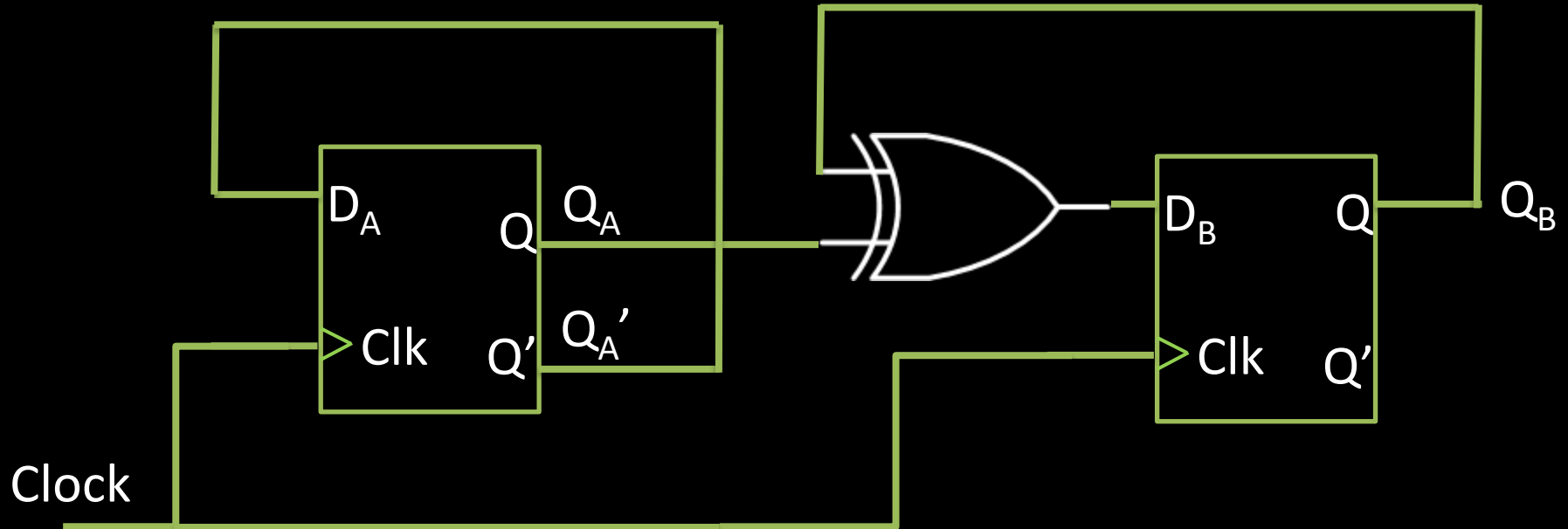




# Design Mod 3 synchronous counter

 


Present states		Next states		Flip-flop Inputs			
$Q_B$	$Q_A$	$Q_{B+1}$	$Q_{A+1}$	$J_B$	$K_B$	$J_A$	$K_A$
0	0	0	1	0	X	1	X
0	1	1	0	1	X	X	1
1	0	0	0	X	1	0	X
1	1	0	0	X	1	X	1

 




# Design Mod 3 synchronous counter

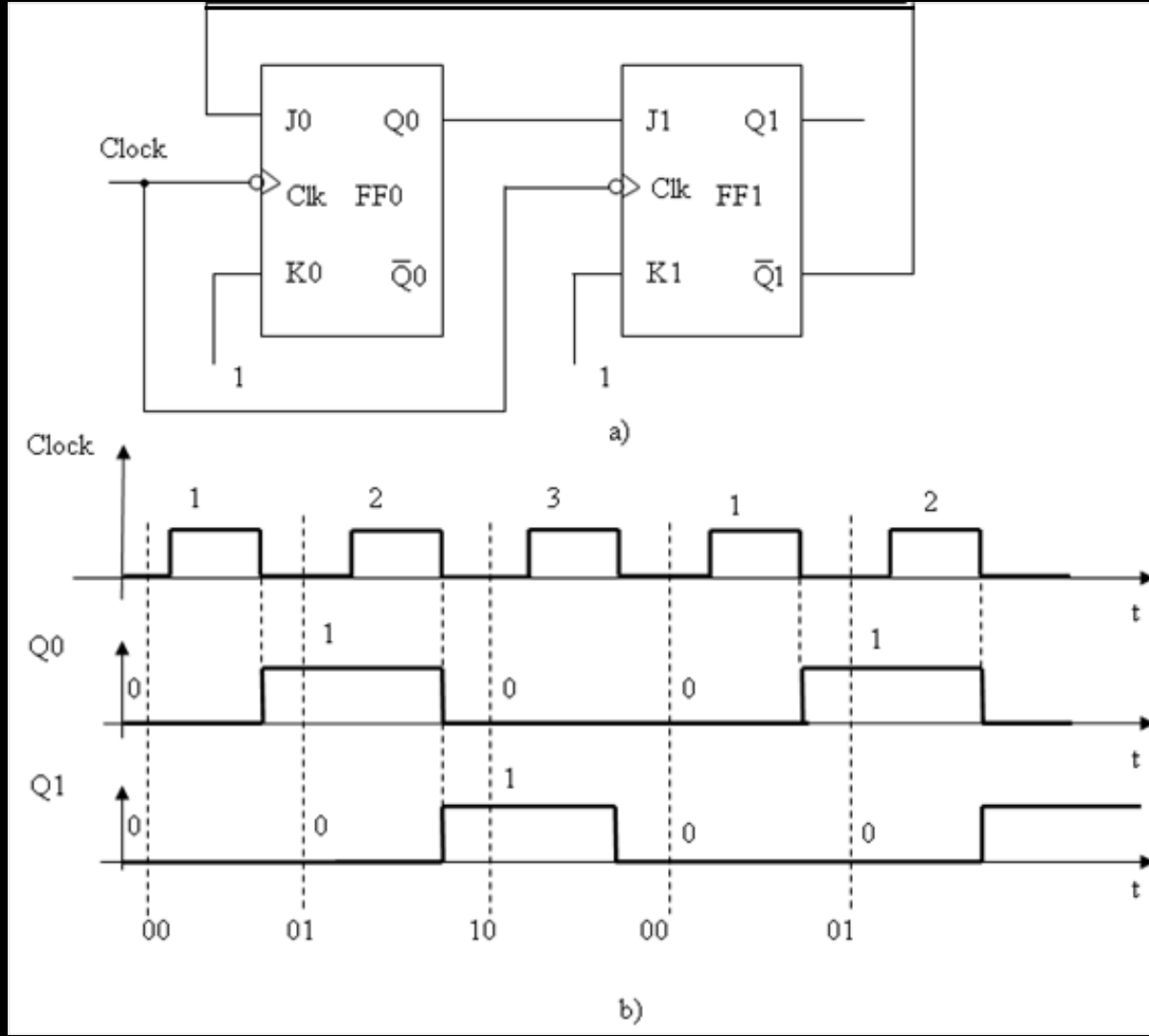




# Design Mod 5 Asynchronous counter

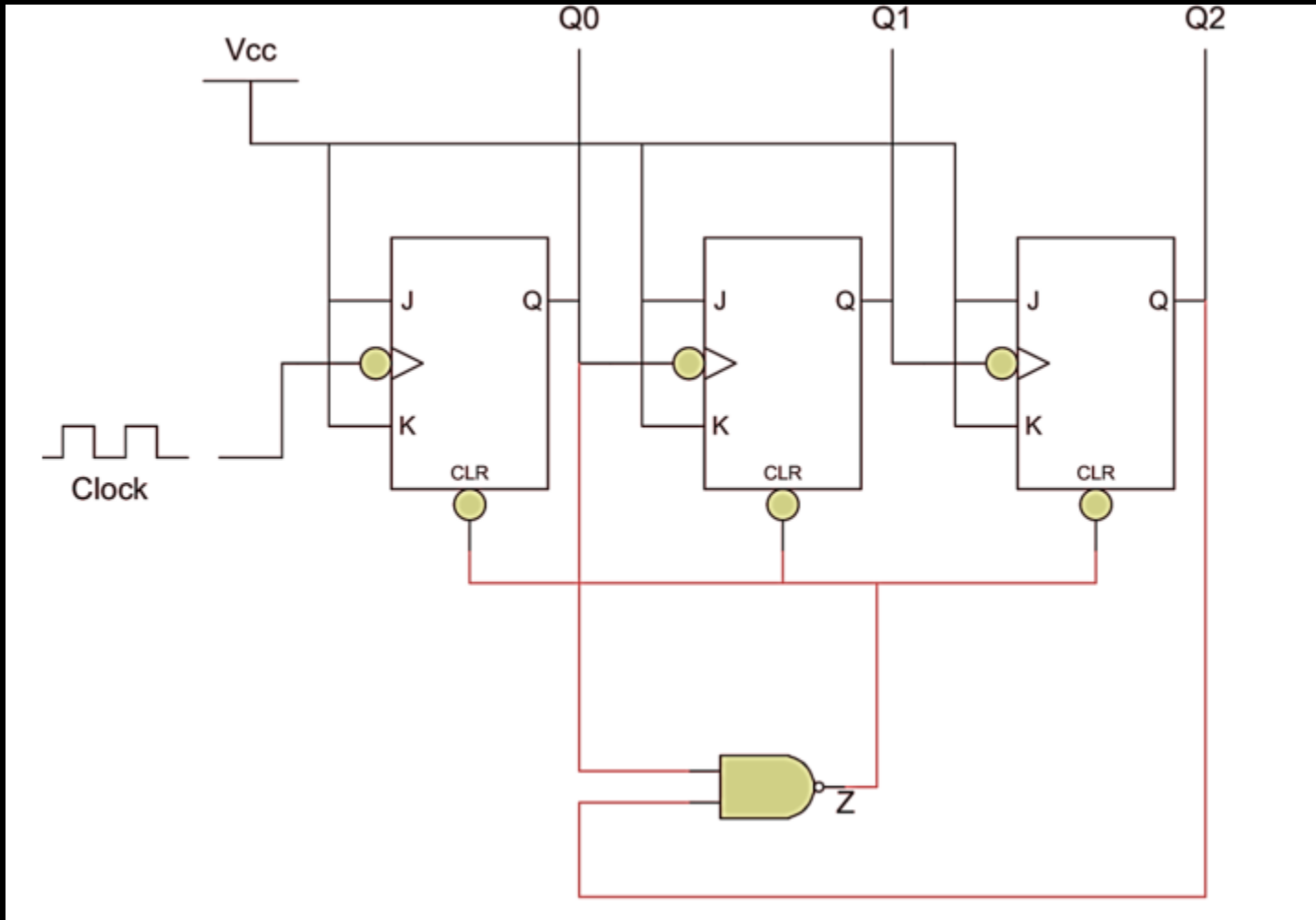



# Design Mod 5 Asynchronous counter

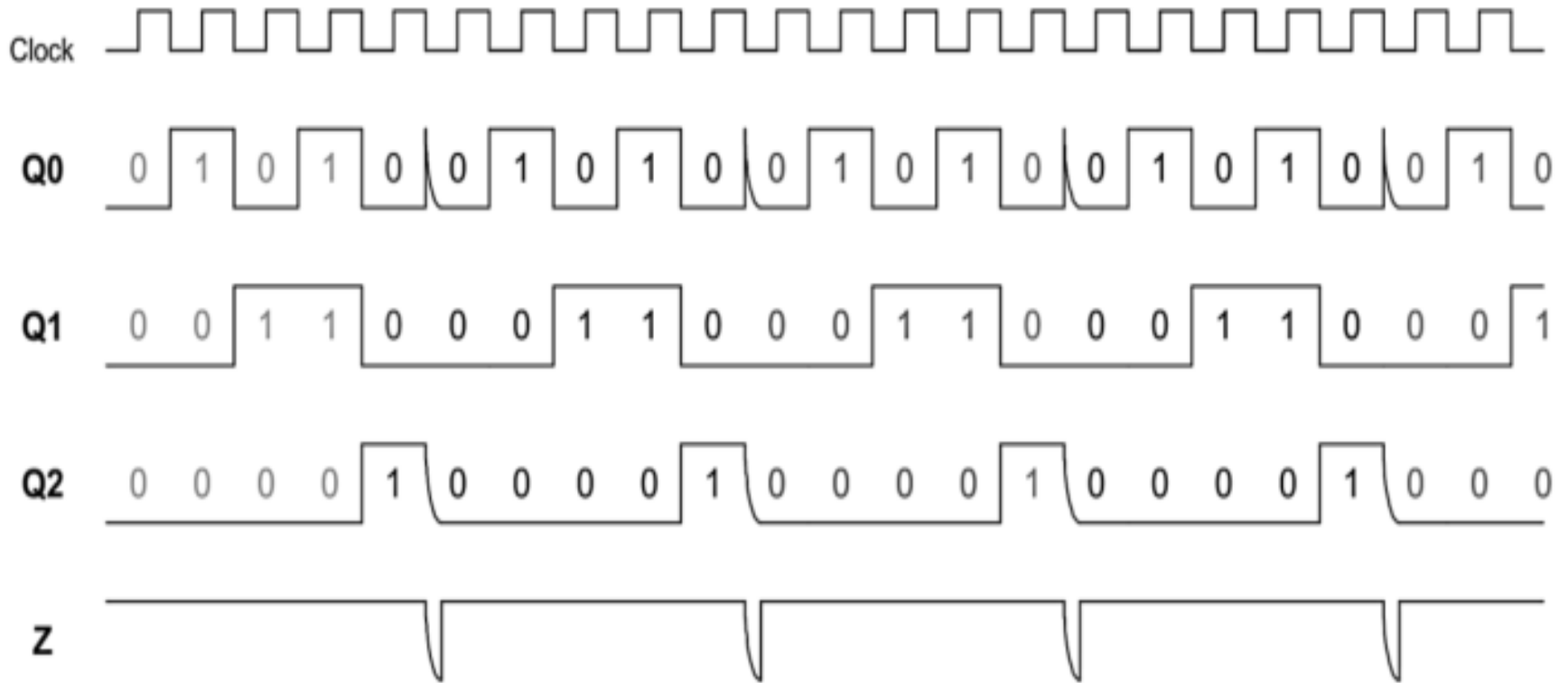



Thank You