

# Digital Electronics and Computer Organization

## Digital Design

### Lecture 25: Memory



**Birla Institute of Technology & Science, Pilani**  
Hyderabad Campus

2020

Innovate

achieve

1

lead



# Types of memory used in digital systems

## RAM (Random Access Memory)

- Can perform both Read and Write Operations
- Stored information is lost when power is turned off

## ROM (Read Only Memory)

- Can perform only Read operations
- Suitable information already stored and can be retrieved at any time
- Binary information “Programmed” in to ROM by embedded hardware

## Hard Disks

Read / Write Non-volatile

Magnetic      SSD




# Read-Only Memory

8 bit data is called Byte, 16 bit is called Word

A block diagram of a ROM is shown below. It consists of  $k$  address inputs and  $n$  data outputs.

The number of words in a ROM is determined from the fact that  $k$  address input lines are needed to specify  $2^k$  words.


$n$  represents the output data length

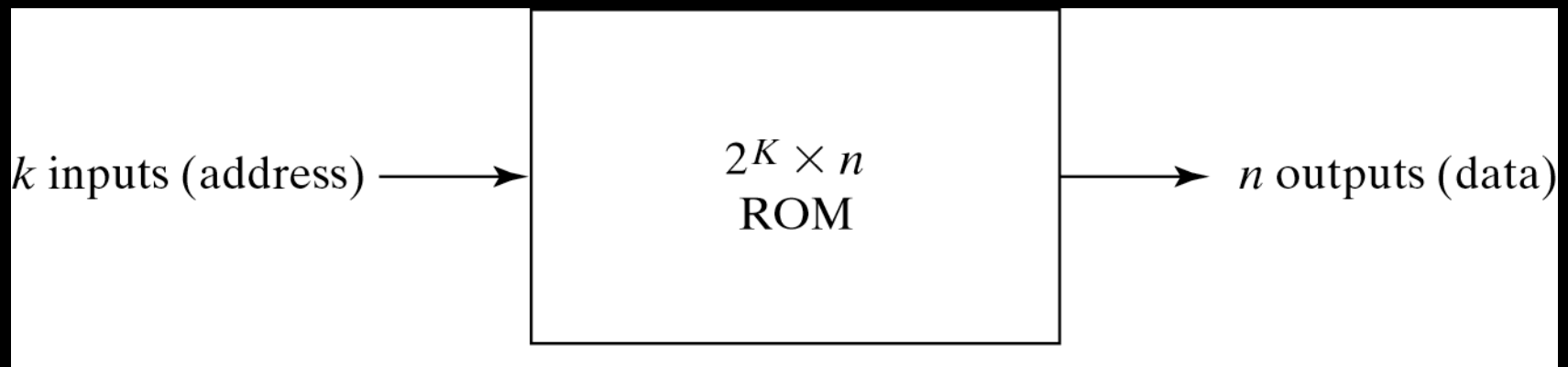



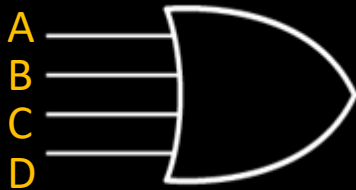
## ROMs

- May have 100s of million gates interconnected through 100s of thousands of internal path
- To show internal logic of such a device – employ a special gate symbology applicable to array logic



(a) Conventional symbol

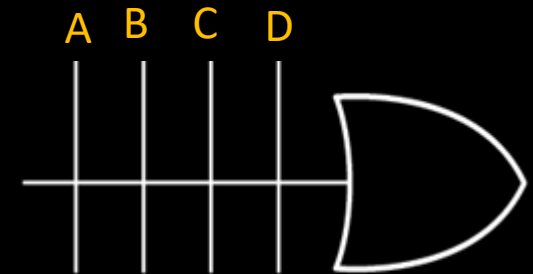


(b) Array logic symbol



# Read Only Memory

Internal Logic 32 X 8 ROM

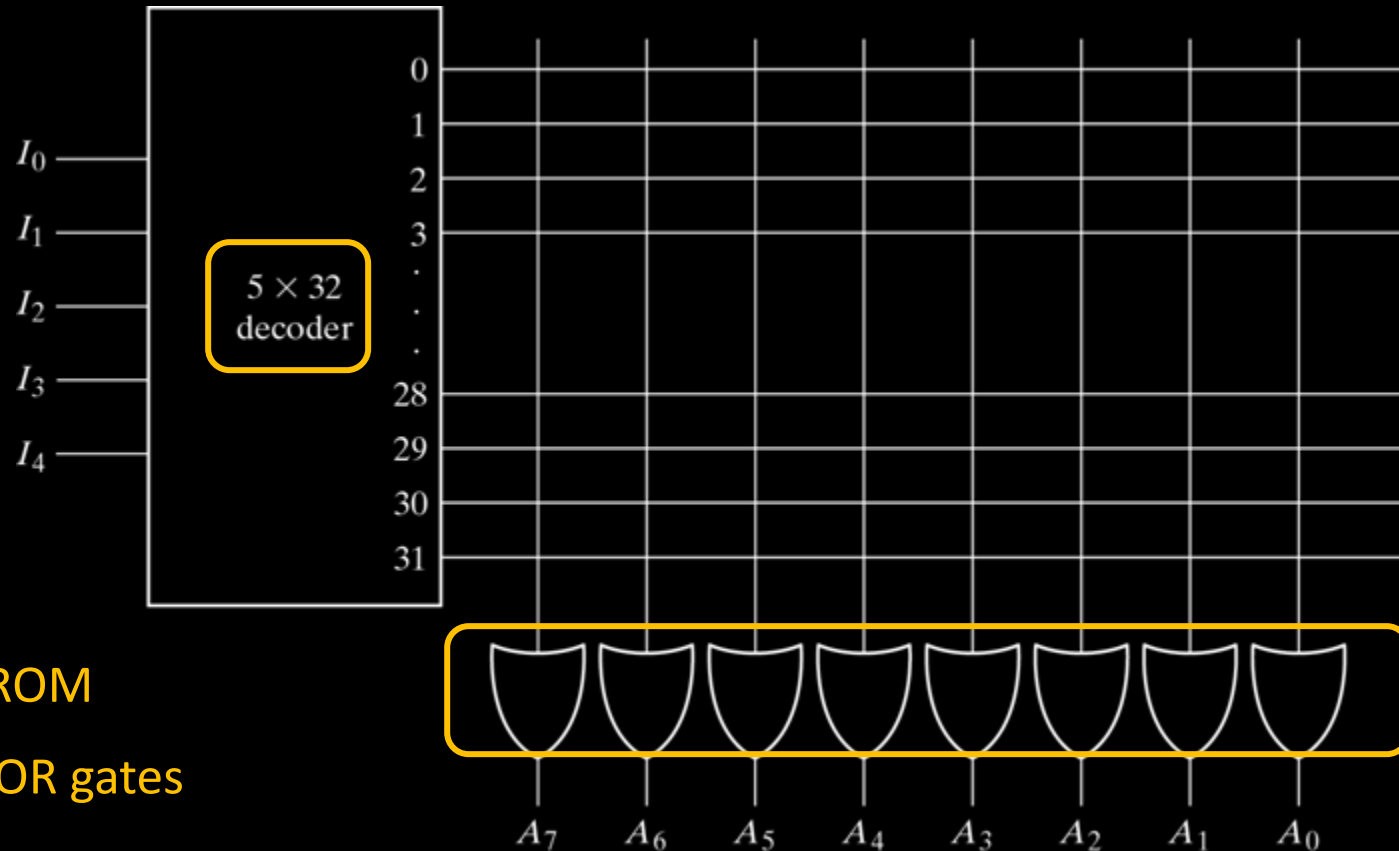

In General for  $2^k \times n$  ROM


$k \times 2^k$  Decoder and  $n$  OR gates

Each OR gate has  $2^k$  inputs


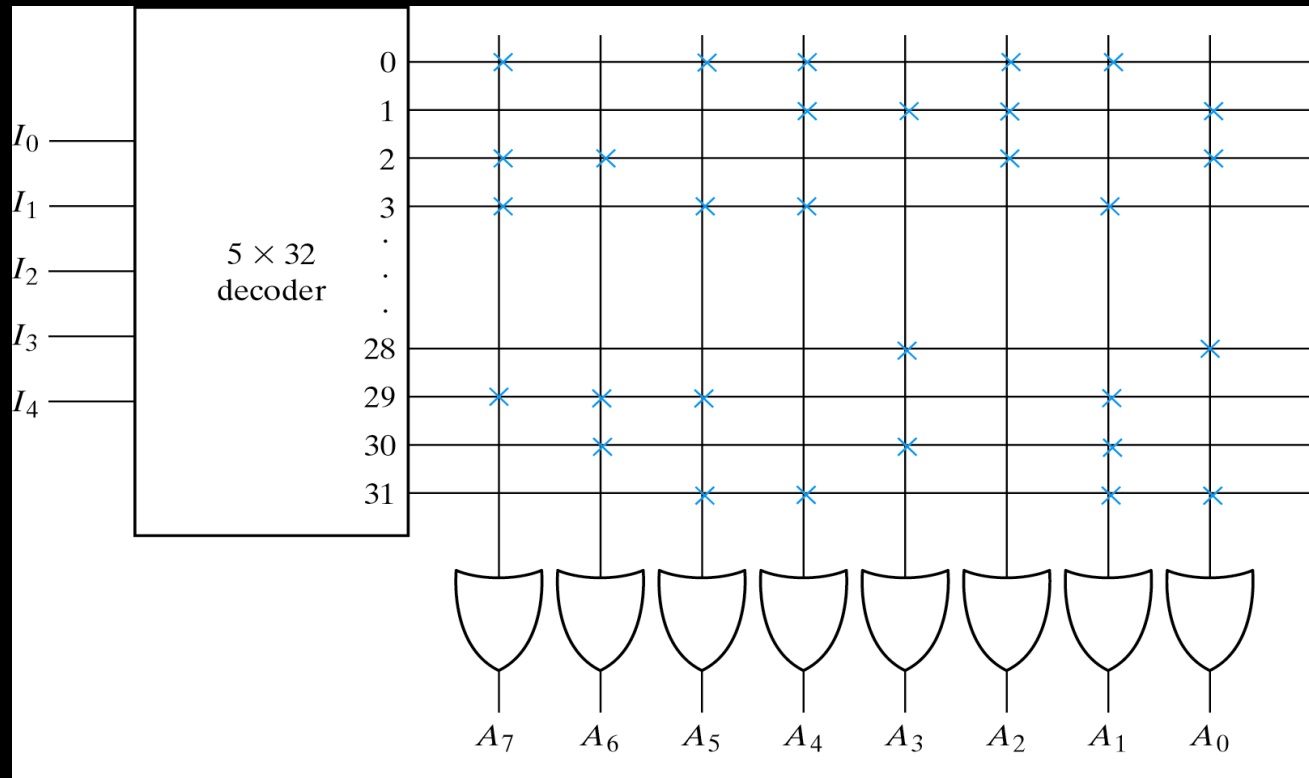
# Programming the ROM


Address 3 = 10110010 is permanent storage using fuse link



X : means connection

# Programming the ROM


## 1. Masking During Metallization

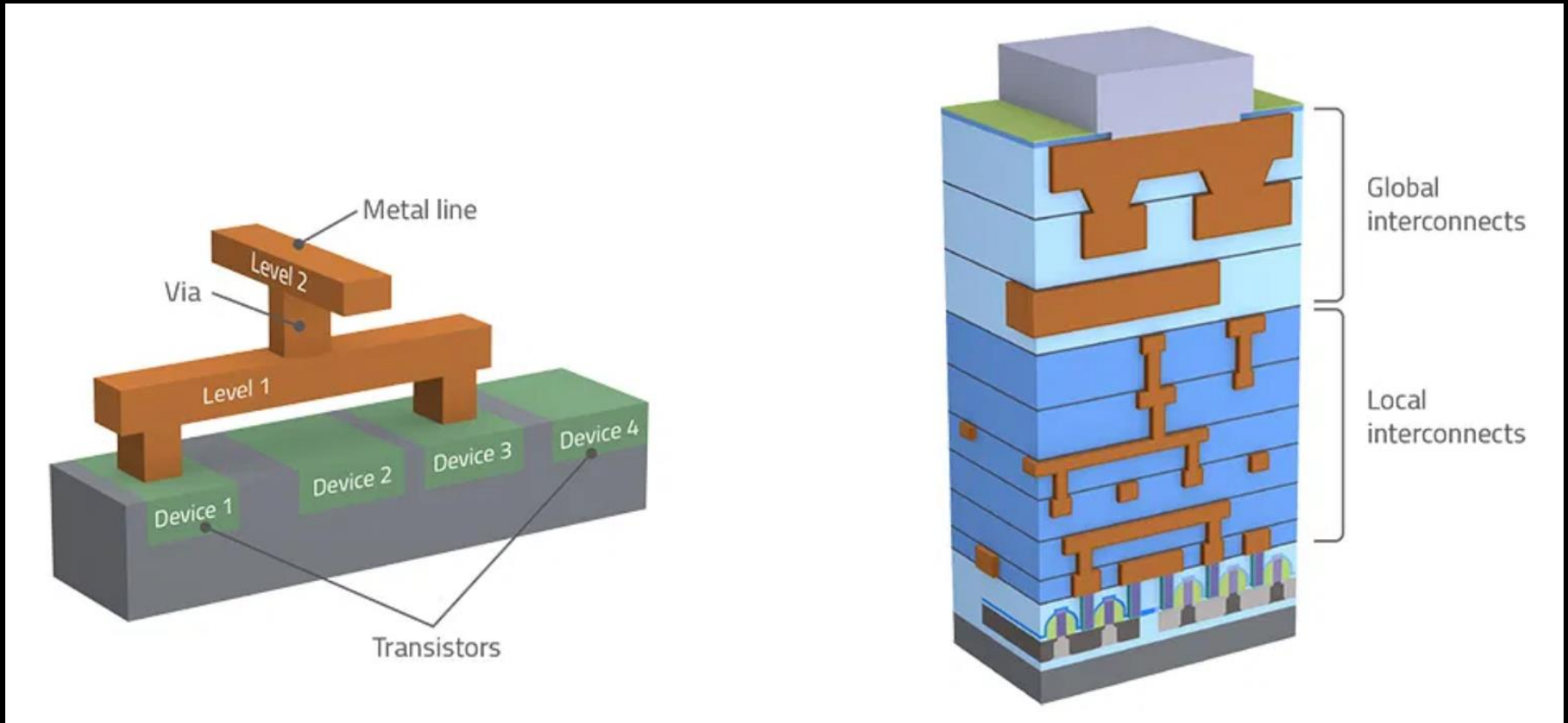



# Programming the ROM
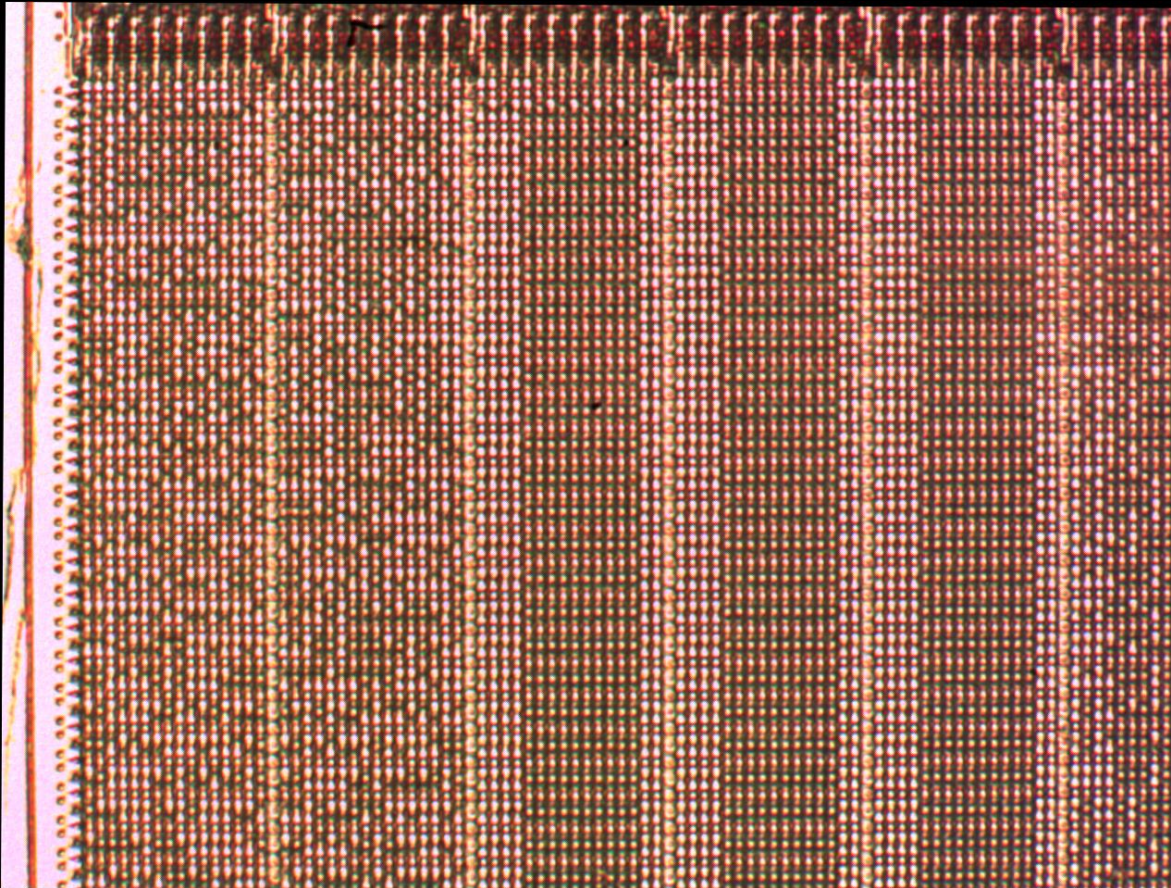
## 1. Masking During Metallization (PROM)








# Programming the ROM


## 2. Fuse (PROM)

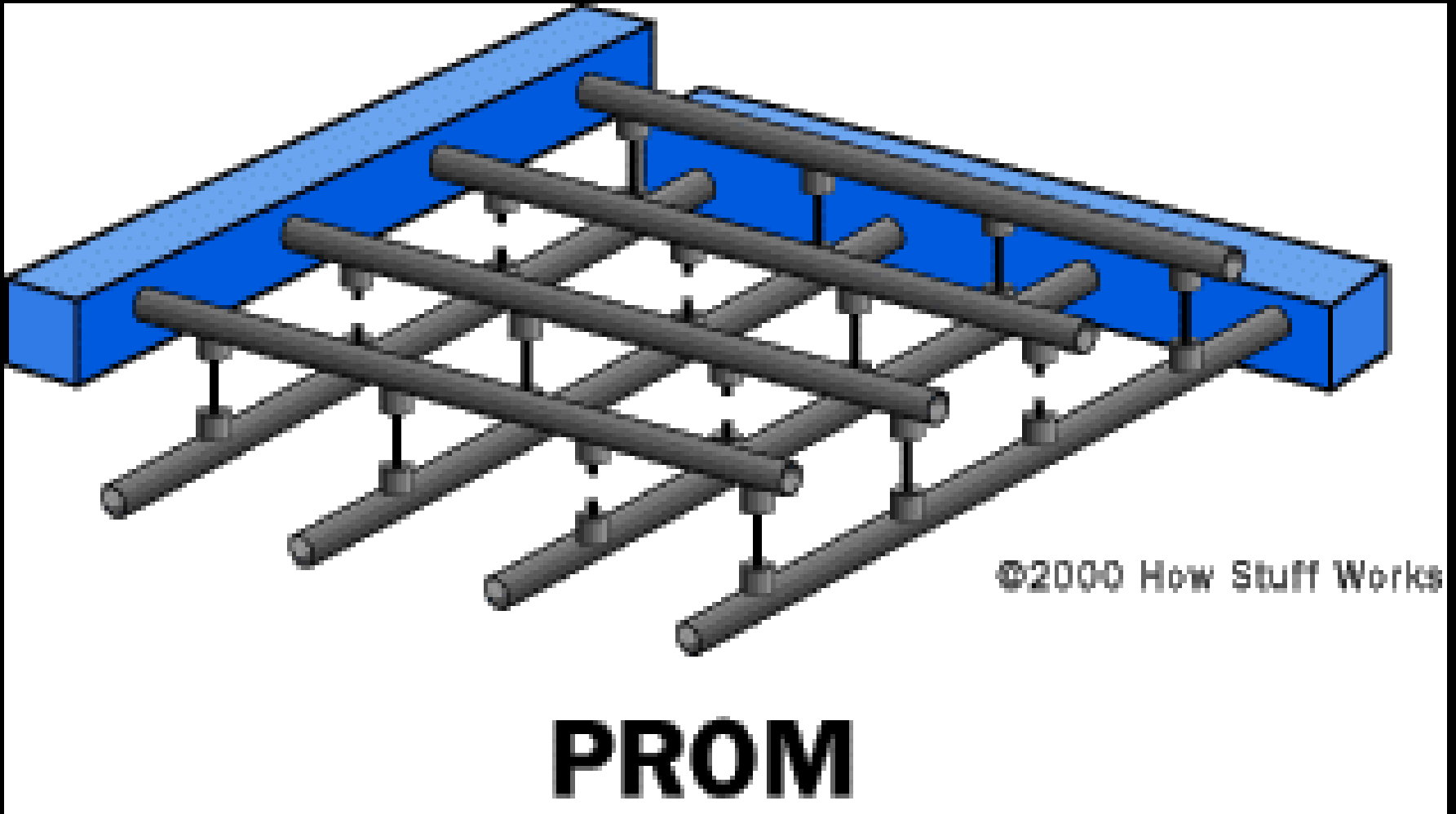



# Programming the ROM


## 2. Fuse (PROM)

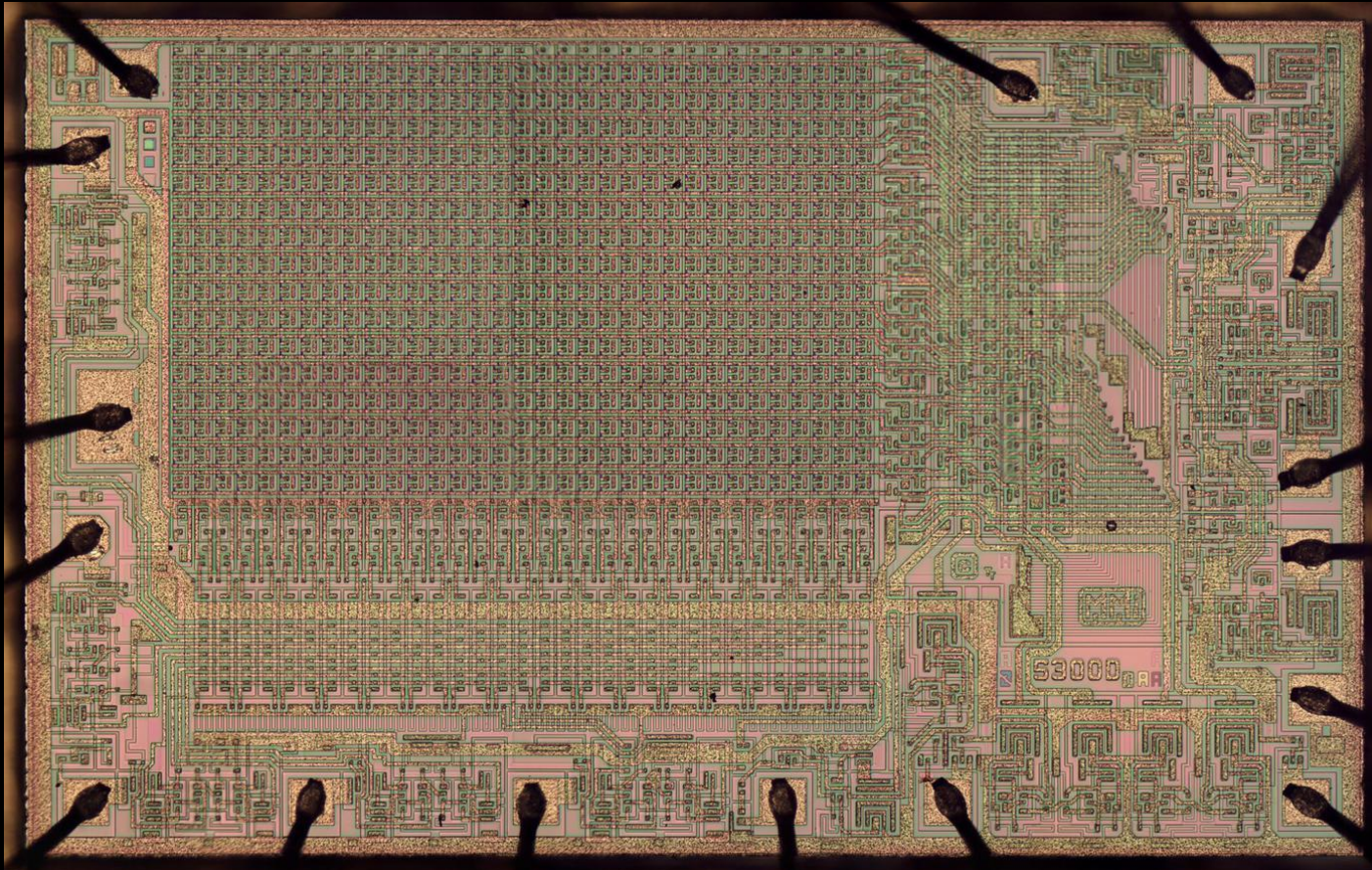



# Programming the ROM


## 3. EPROM

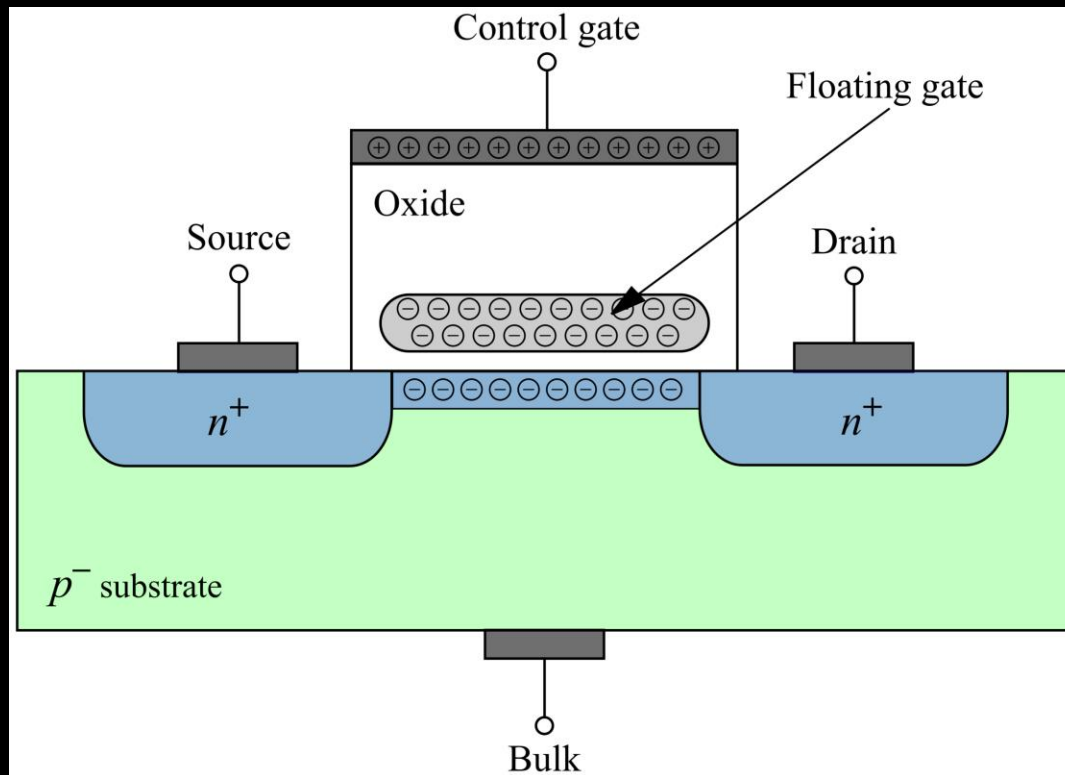




# Programming the ROM

## 3. EPROM

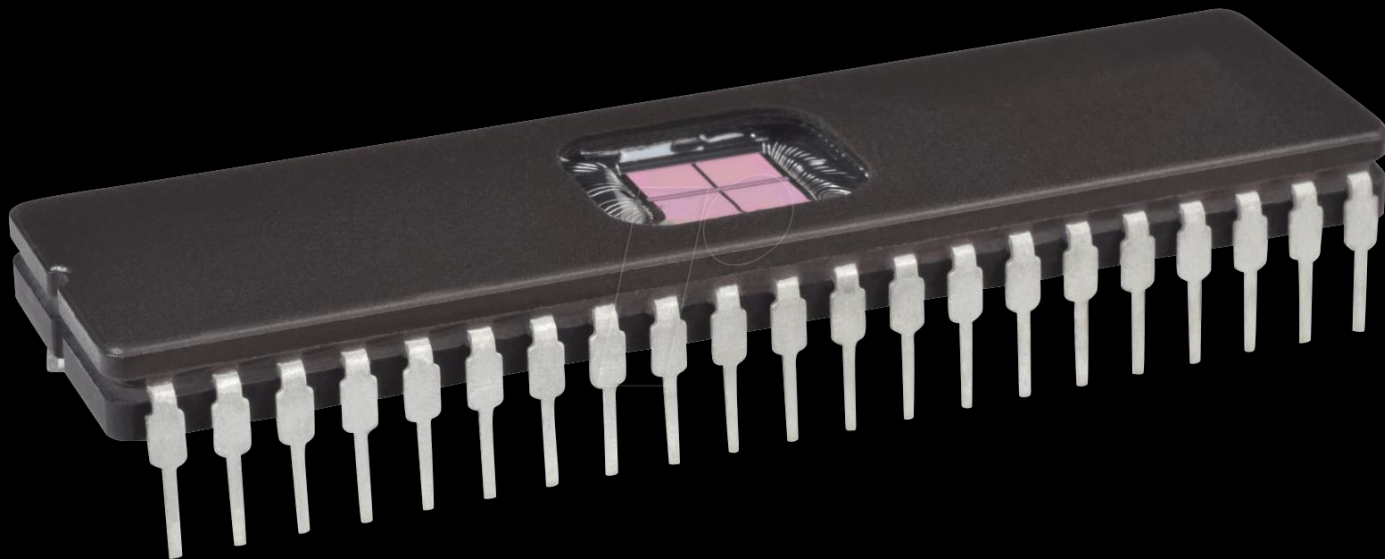

# Programming the ROM

## 4. EEPROM

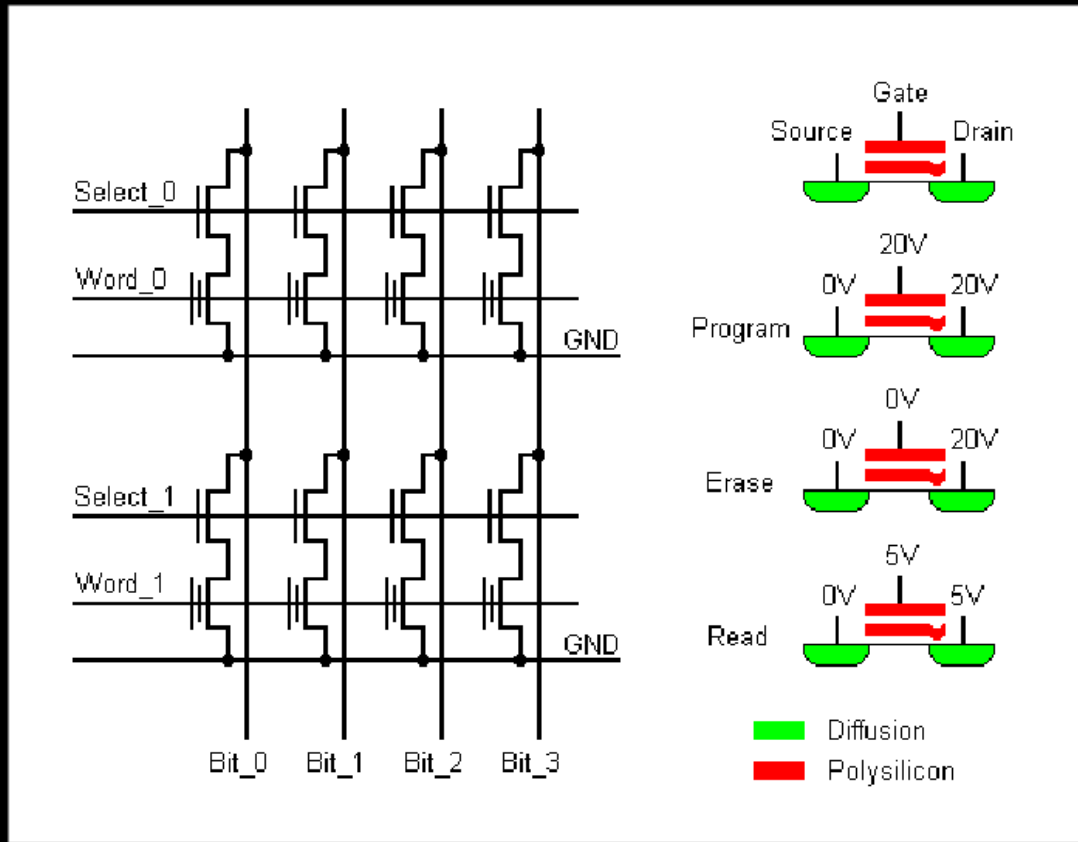




# Programming the ROM

- E.g., Implement the 3-input logics  $f_0 = \Sigma (0,1,5,7)$ ,  $f_1 = \Sigma (0,1,2,6)$  and  $f_2 = \Sigma (2,3,4)$  using a ROM.

$a$	$b$	$c$	$f_2$	$f_1$	$f_0$
0	0	0	0	1	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	0	0	1
1	1	0	0	1	0
1	1	1	0	0	1

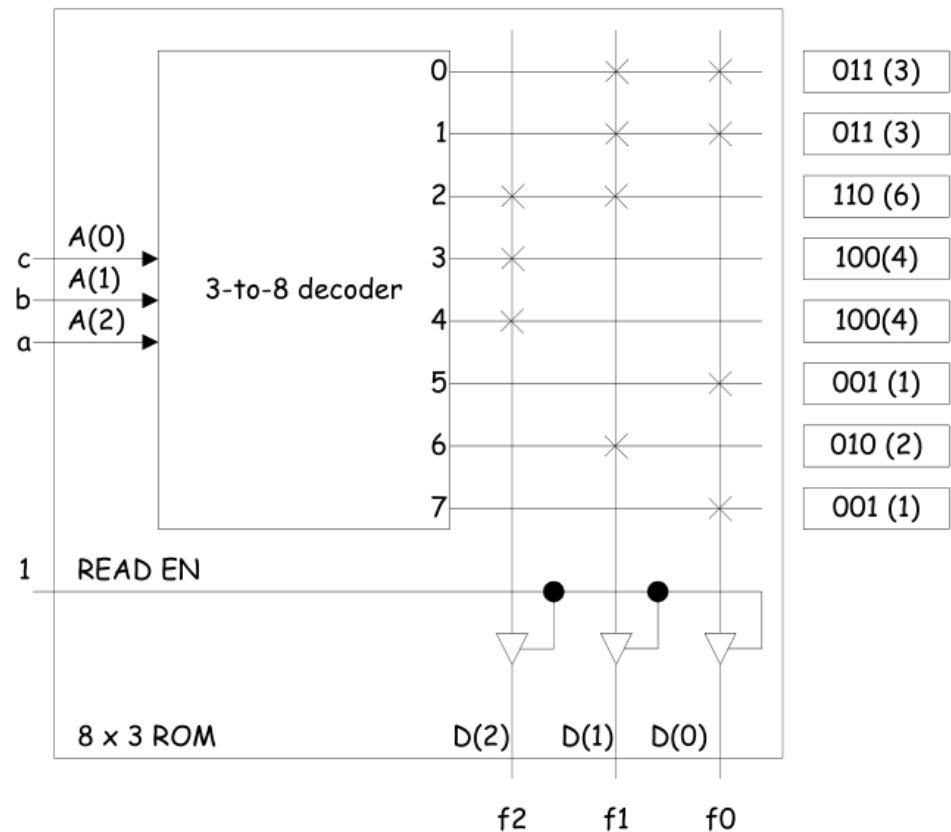



# Programming the ROM


Example: Design a combinational circuit using a ROM. The circuit accepts a 3-bit number and generates an output binary number equal to the square of the input number.

Inputs			Outputs						Decimal
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49



# Programming the ROM

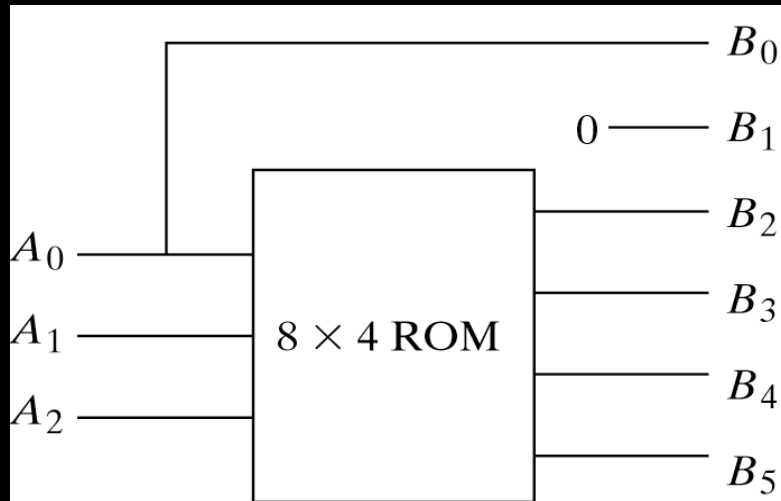Example: Design a combinational circuit using a ROM. The circuit accepts a 3-bit number and generates an output binary number equal to the square of the input number.



(a) Block diagram

$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table





Thank You