

Digital Electronics and Computer Organization

Digital Design

Lecture 26: Programmable Logic Devices



Birla Institute of Technology & Science, Pilani
Hyderabad Campus

2020

Innovate

achieve

1

lead



Types of PLD

Programmable Logic Array (PLA)

Programmable Array Logic Array (PAL)

Simple Programmable Logic Device (SPLD)

Complex Programmable Logic Device (CPLD)

Field Programmable Gate Arrays (FPGAs)



PLA

Programmable device capable of implementing functions expressed in SOP.

- Consists of input buffers and inverters followed by:
- Programmable AND plane, followed by
- Programmable OR plane.
- Can implement m logic functions of n variables. Limit is the number of product terms that can be generated inside of the device.




PLA

FIGURE 9-29

PLA with Three Inputs, Five Product Terms, and Four Outputs


© Cengage Learning 2014

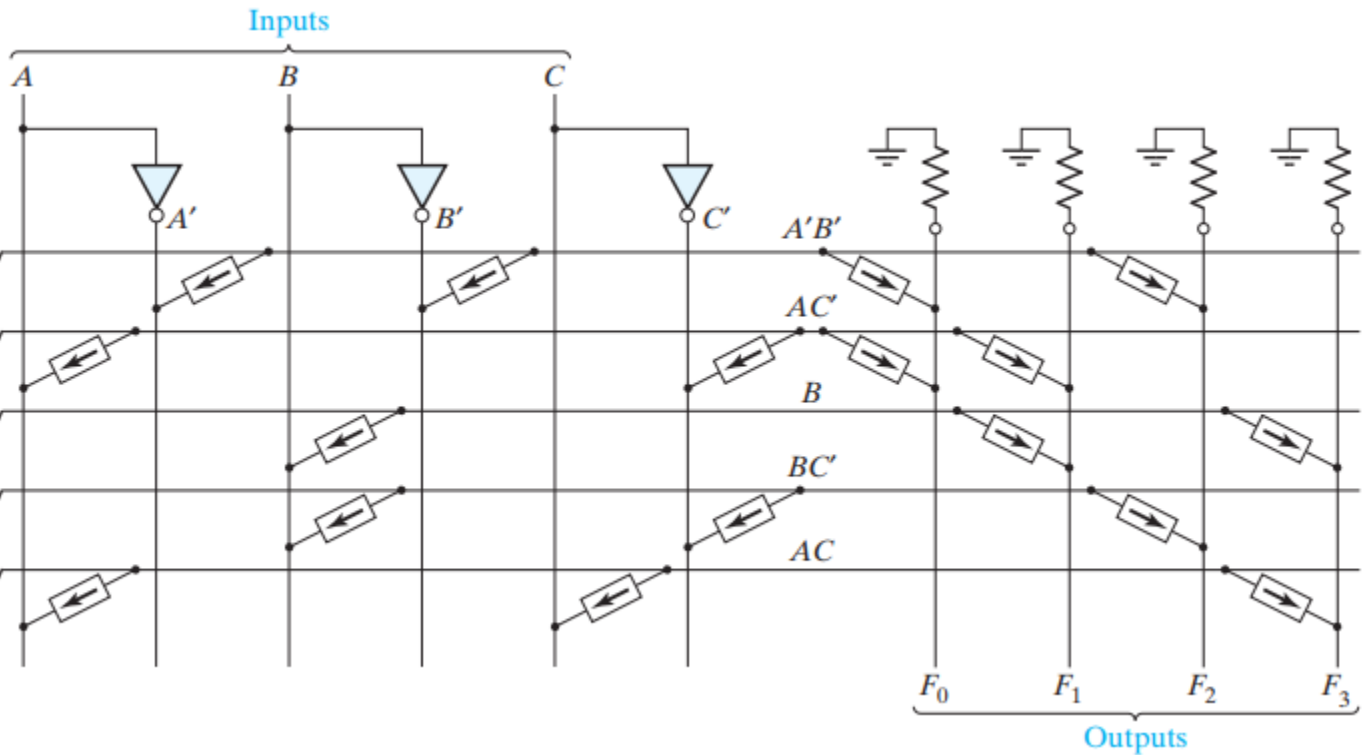



PLA

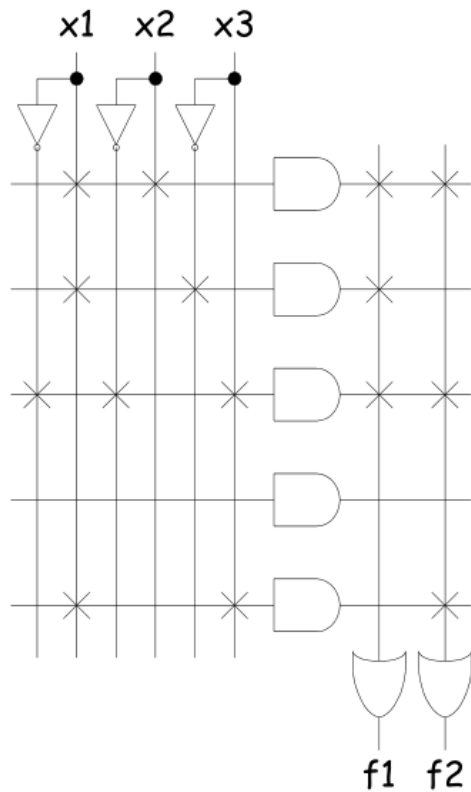□ Example implementing 2 logic functions of 3 inputs using a 3-5-2 PLA.



$$f_1 = x_1x_2 + x_1\bar{x}_3 + \bar{x}_1\bar{x}_2x_3$$

$$f_2 = x_1x_2 + \bar{x}_1\bar{x}_2x_3 + x_1x_3$$




PAL

- Similar to a PLA, but only has a programmable AND plane.
 - The OR plane is fixed.
- Not as flexible as a PLA since only certain AND gates feed each OR gate, but has fewer things that need programming.



PAL

□ Example of a PAL:

 


$$f_1 = x_1x_2 + x_1\bar{x}_3$$

$$f_2 = \bar{x}_2x_3 + x_1x_3$$

PAL

Programming a PAL

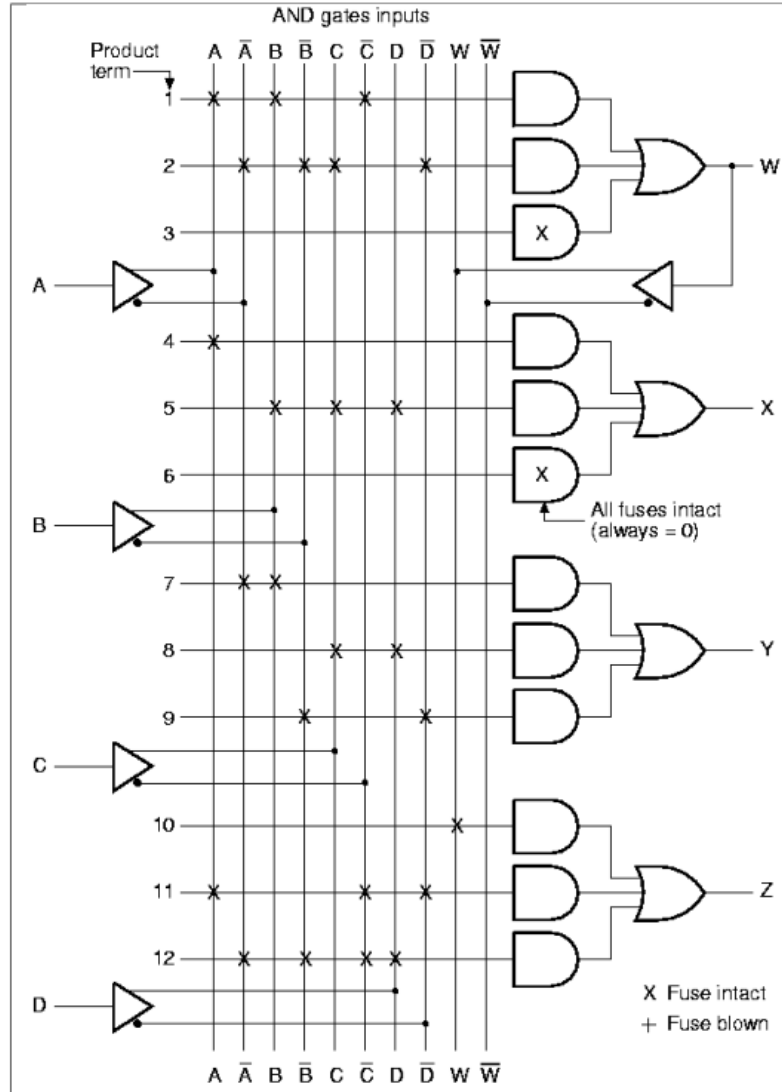



Programmable Array Logic

Example

$$W(A, B, C, D) = \sum (2, 12, 13)$$

$$X(A, B, C, D) = \sum (7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$Y(A, B, C, D) = \sum (1, 2, 8, 12, 13)$$

$$W(A, B, C, D) = ABC' + A'B'CD'$$

$$X(A, B, C, D) = A + BCD$$

$$\begin{aligned} Y(A, B, C, D) &= ABC' + A'B'CD' + AC'D' + A'B'C'D \\ &= W + AC'D' + A'B'C'D \end{aligned}$$



Programmable Array Logic

Example

$$W(A, B, C, D) = ABC' + A'B'CD'$$

$$X(A, B, C, D) = A + BCD$$

$$Y(A, B, C, D) = W + AC'D' + A'B'C'D$$

Product	AND Inputs					Outputs
	A	B	C	D	w	
1	1	1	0	--	--	$W = ABC' + A'B'CD'$
2	0	0	1	0	--	
3	--	--	--	--	--	
4	1	--	--	--	--	$X = A + BCD$
5	--	1	1	1	--	
6	--	--	--	--	--	
7	--	--	--	--	1	$Y = W + AC'D' + A'B'C'D$
8	1	--	0	0	--	
9	0	0	0	1	--	



Section 1

Section 2

Section 3



Programmable Array Logic

 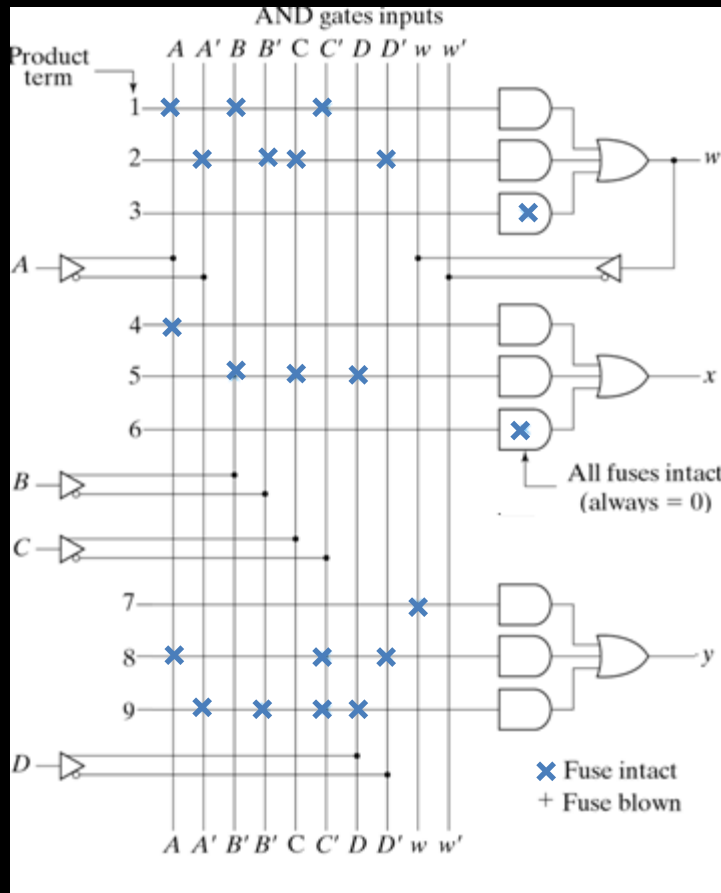

Example


$$W(A, B, C, D) = ABC' + A'B'CD'$$

$$X(A, B, C, D) = A + BCD$$

$$Y(A, B, C, D) = W + AC'D' + A'B'C'D$$


Simple Programmable Logic Device (SPLD)

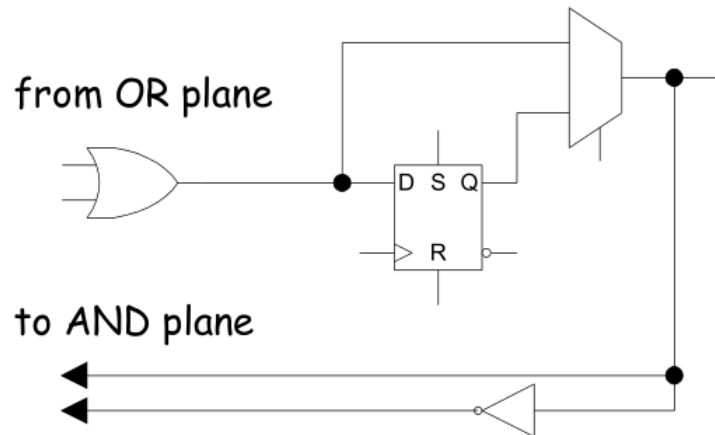- ❑ To implement sequential circuits, take a PAL and add some flip-flops at the output of the OR plane.
- ❑ For example...



- ❑ Above circuit (plus SOP from the AND plane and OR gate) form a **MacroCell**.
- ❑ Several **MacroCells** together in the same IC is called an SPLD.

Registered (Sequential) PAL:

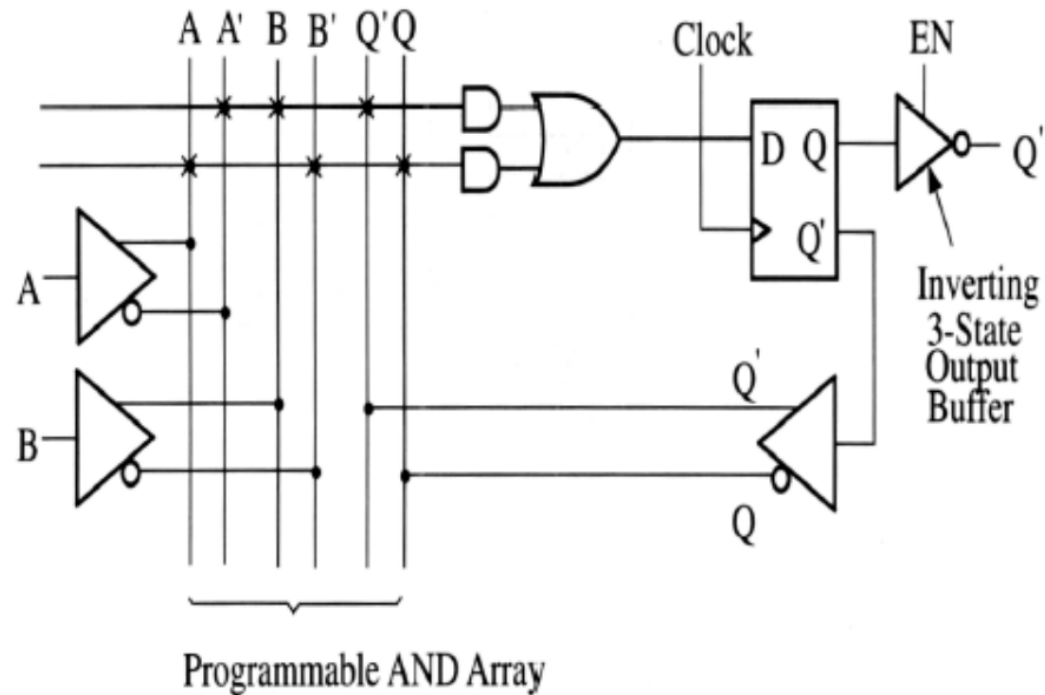

$$Q^+ = D = A'BQ' + AB'Q$$



Complex Programmable Logic Device (CPLD)


- PLA, PAL and SPLD typically contain small number of outputs (e.g., 16 outputs) with many inputs (e.g., 36 inputs) and a fair number of product terms.
 - Therefore only good for simple circuits where each equation has a wide fanin.

- Using a **Complex Programmable Logic Device (CPLD)** is the "next step" if we have a large complicated circuit...

- CLPD consists of many SPLD connected together by a **Programmable Routing Fabric** all in the **same IC**.


Complex Programmable Logic Device (CPLD)

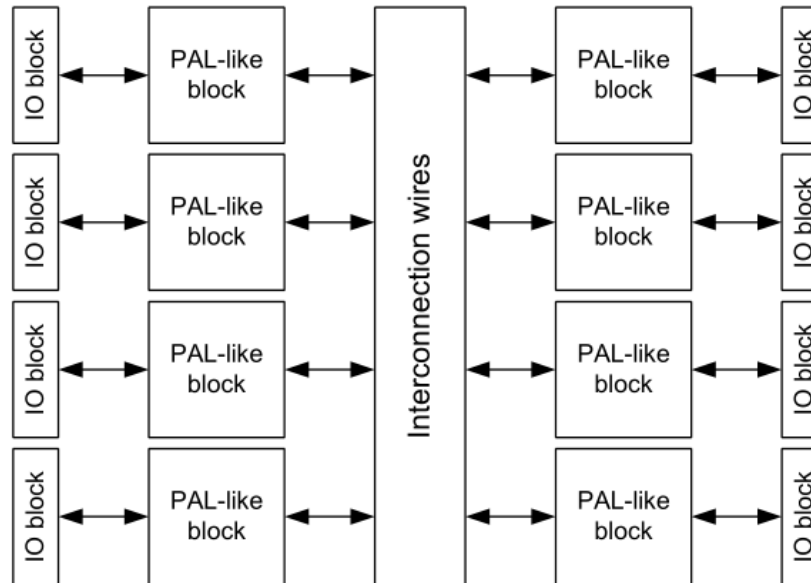- Typical architecture (each PAL-like block has many inputs - e.g., 36 - , many product terms - e.g., 80 - and several outputs - e.g., 16).





Field Programmable Gate Array (FPGA)

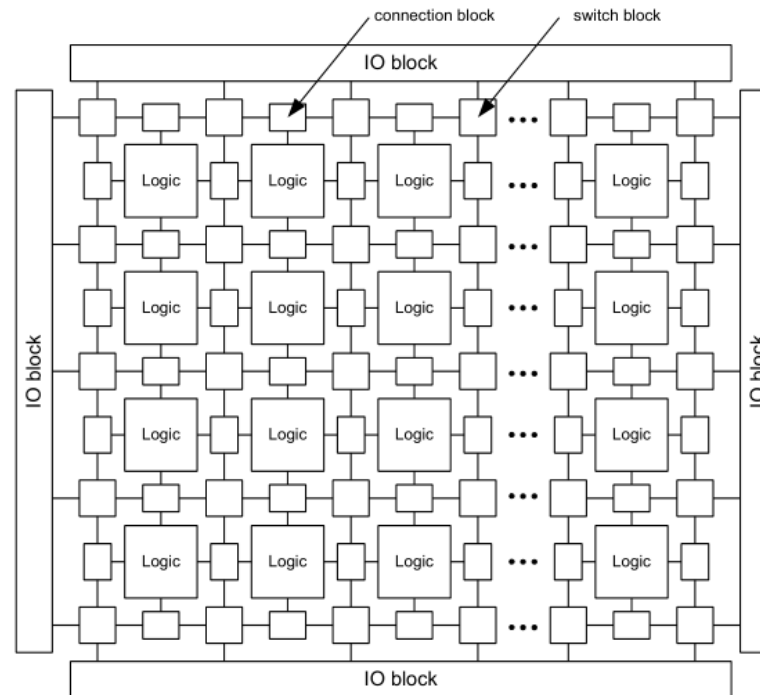- Typical FPGA consists of many small logic blocks interconnected by programmable routing resources.





SRAM

  



Thank You