

Digital Design

Revision for T2



Birla Institute of Technology & Science, Pilani
Hyderabad Campus

3/2020

Innovate

achieve

1

lead




NAND Implementation

AB \ CD	00	01	11	10
00	0	0	1	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

Annotations: A box around the '1' in row 00, column 11 is labeled $B'CD$. A box around the entire bottom two rows (11 and 10) is labeled A .

$$F = A + B'CD$$

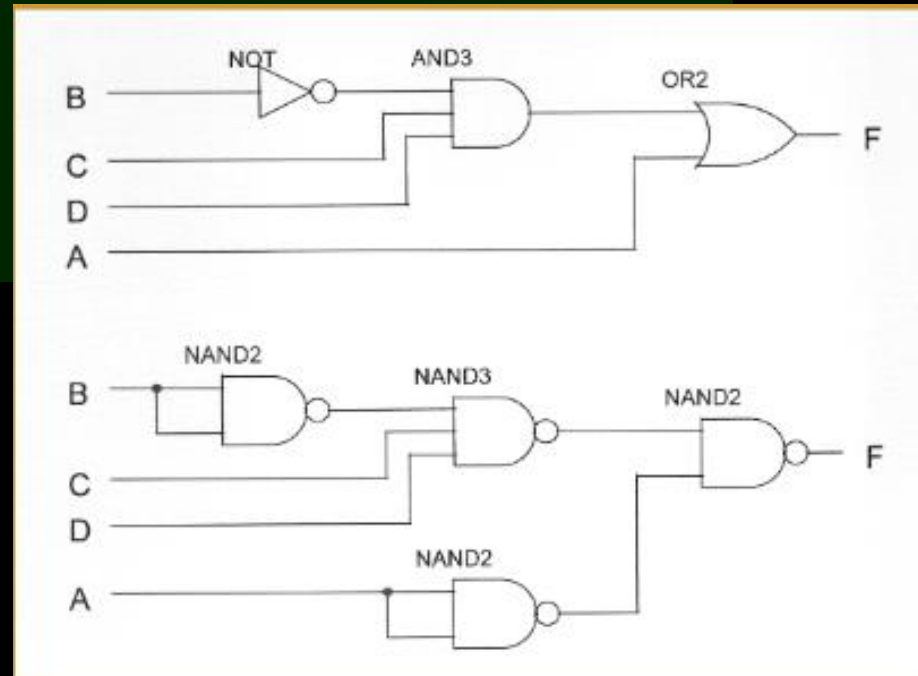

NOR Implementation

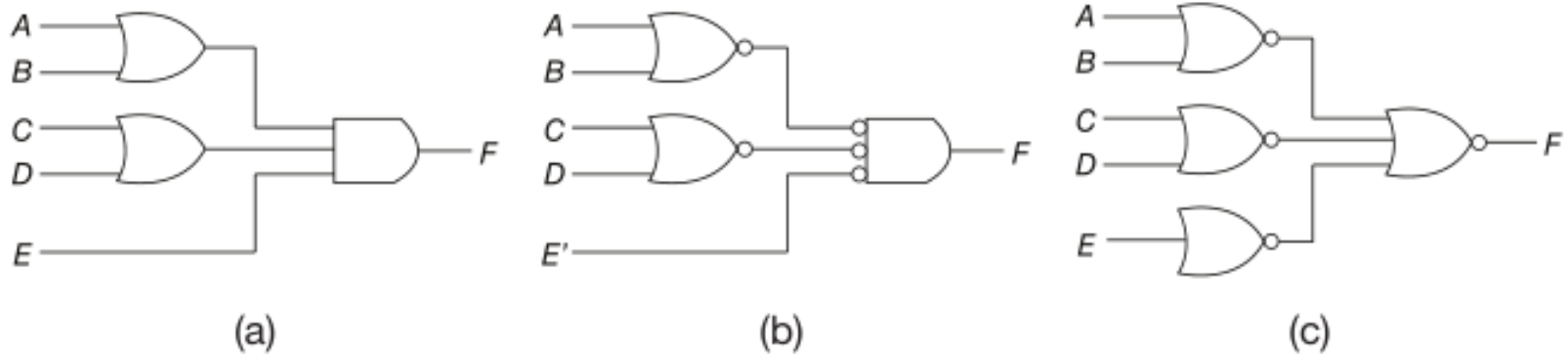



Figure 3.20 Three ways to implement $F = (A + B)(C + D)E$

Minimization of Boolean Expression by 5 Variable K-Map (SOP form)

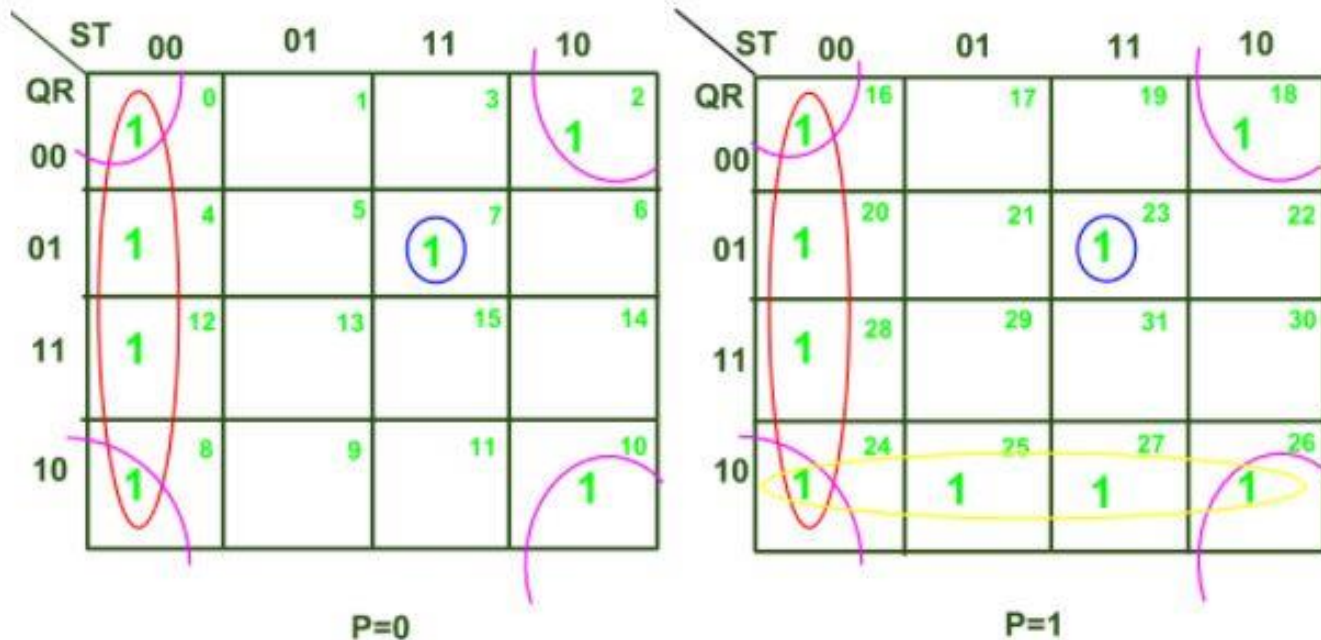I. Solving SOP function -

For clear understanding, let us solve the example of SOP function minimization of 5 Variable K-Map using the following expression :

$$\sum m(0, 2, 4, 7, 8, 10, 12, 16, 18, 20, 23, 24, 25, 26, 27, 28)$$




$$F(PQRST) = S'T' + Q'RST + PQR' + R'T'$$

Minimization of Boolean Expression by 5 Variable K-Map (POS form)

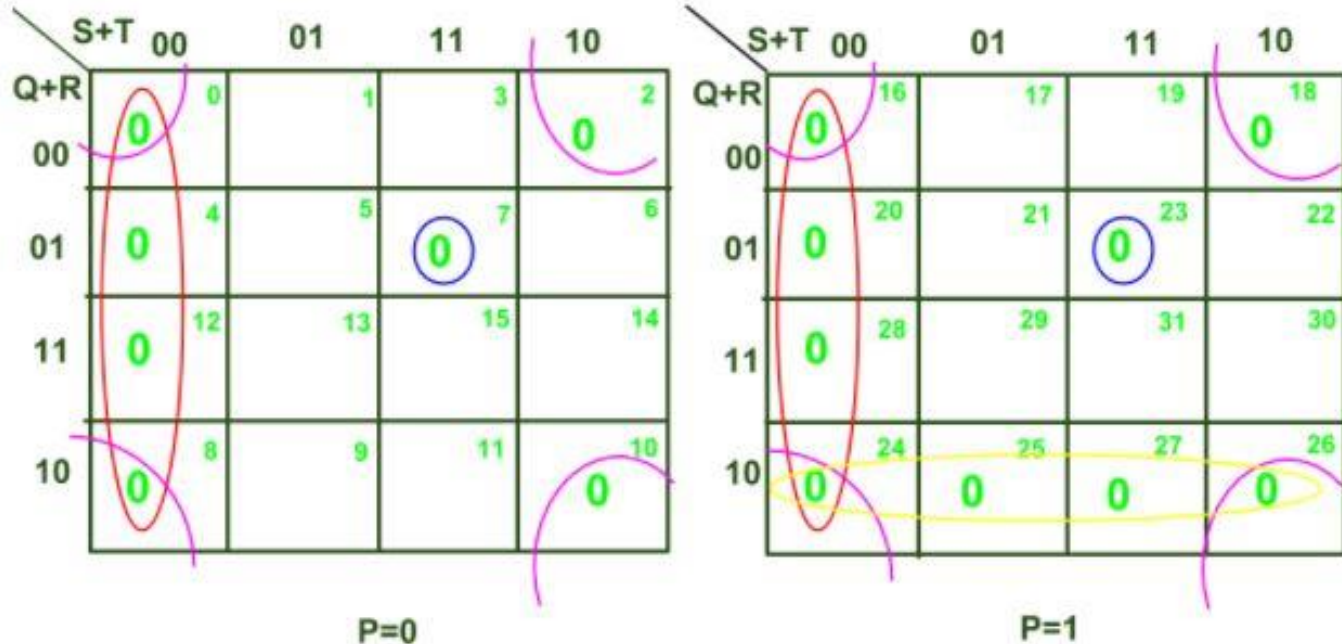II. Solving POS function -

Now, let us solve the example of POS function minimization of 5 Variable K-Map using the following expression :


$$\prod M(0, 2, 4, 7, 8, 10, 12, 16, 18, 20, 23, 24, 25, 26, 27, 28)$$



$$f(PQRST) = (S+T) \cdot (R+T) \cdot (Q+R'+S'+T') \cdot (P'+Q'+R)$$


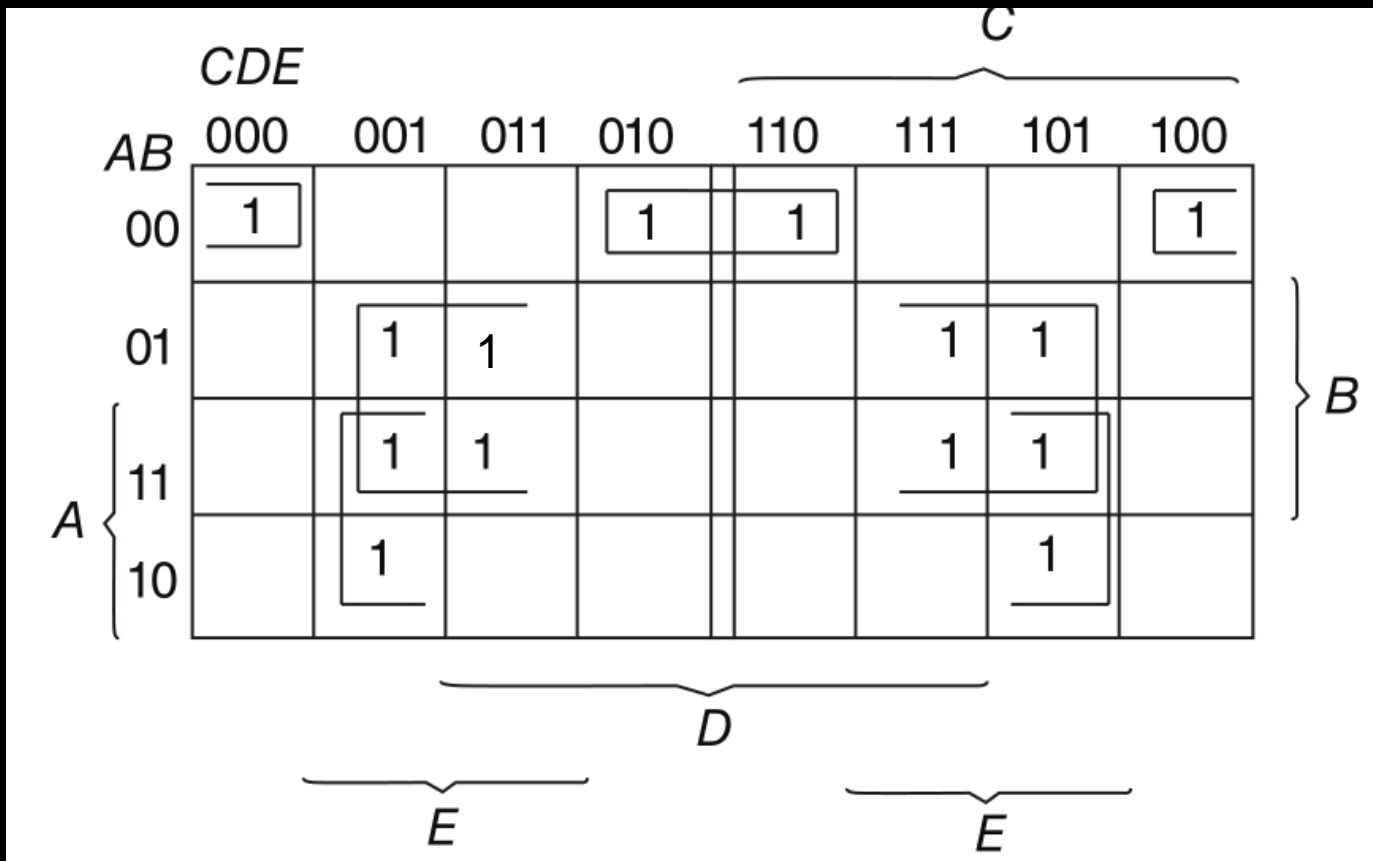
$$F(A, B, C, D, E) = \sum(0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 29, 31)$$



$$BE + AD'E + A'B'E'$$



Prime Implicants

Column I

Column II

Column III

group 0	<u>0 0000</u> ✓
group 1	1 0001✓
	2 0010✓
	8 1000✓
group 2	<u>5 0101</u> ✓
	6 0110✓
	9 1001✓
	<u>10 1010</u> ✓
group 3	7 0111✓
	14 1110✓

0,1	000-	✓
0,2	00-0	✓
0,8	-000	✓
<hr/>		
1,5	0-01	← A = w'y'z
1,9	-001	✓
2,6	0-10	✓
2,10	-010	✓
8,9	100-	✓
8,10	10-0	✓
5,7	01-1	← B = w'xz
6,7	011-	← C = w'xy
6,14	-110	✓
10,14	1-10	✓

0,1,8,9	-00-	← D = x'y'
0,2,8,10	-0-0	← E = x'z'
<u>2,6,10,14</u>	--10	← F = yz'

A, B, C, D, E, F are Prime Implicants



Essential Prime Implicants

2. Find Essential Prime Implicants

The Minterms 9 and 14 are covered by single terms

		Minterms									
		0	1	2	5	6	7	8	9	10	14
Prime Implicants	(1,5) $A=w'y'z$		X		X						
	(5,7) $B=w'xz$				X		X				
	(6,7) $C=w'xy$					X	X				
	(0,1,8,9) $D=x'y'$	X	X					X	X		
	(0,2,8,10) $E=x'z'$	X		X				X		X	
	(2,6,10,14) $F=yz'$			X		X				X	X

$$f(w, x, y, z) = \sum(0,1,2,5,6,7,8,9,10,14)$$

yz' and $x'y'$

Essential Prime Implicants



Static Glitch Elimination

	bc	00	01	11	10
a	0	0	1	0	0
1	0	0	1	1	1

$$f=ab+b'c + ac$$

The extra product term does not include the changing input variable, and therefore serves to prevent possible momentary output glitches due to this variable.



Multi-Output Circuit Optimization

		F1				F2				F3			
		CD				CD				CD			
		00	01	11	10	00	01	11	10	00	01	11	10
AB	00	1	1					1				1	
	01	1	1					1				1	
	11					1	1	1	1	1	1	1	
	10											1	1
		3 Gates- I/p-7				3 Gates- I/p-7				2 Gates- I/p-4			



Full Adder

Two level logic

Output delay

$A, B, C_{in} \rightarrow \text{Sum}$


Delay through 2 xor gates

$$t_s = 2 t_{xor}$$

$A, B, C_{in} \rightarrow \text{Cout}$

Delay through an AND gate
and an OR gate


$$t_{Cout} = t_{and} + t_{or}$$

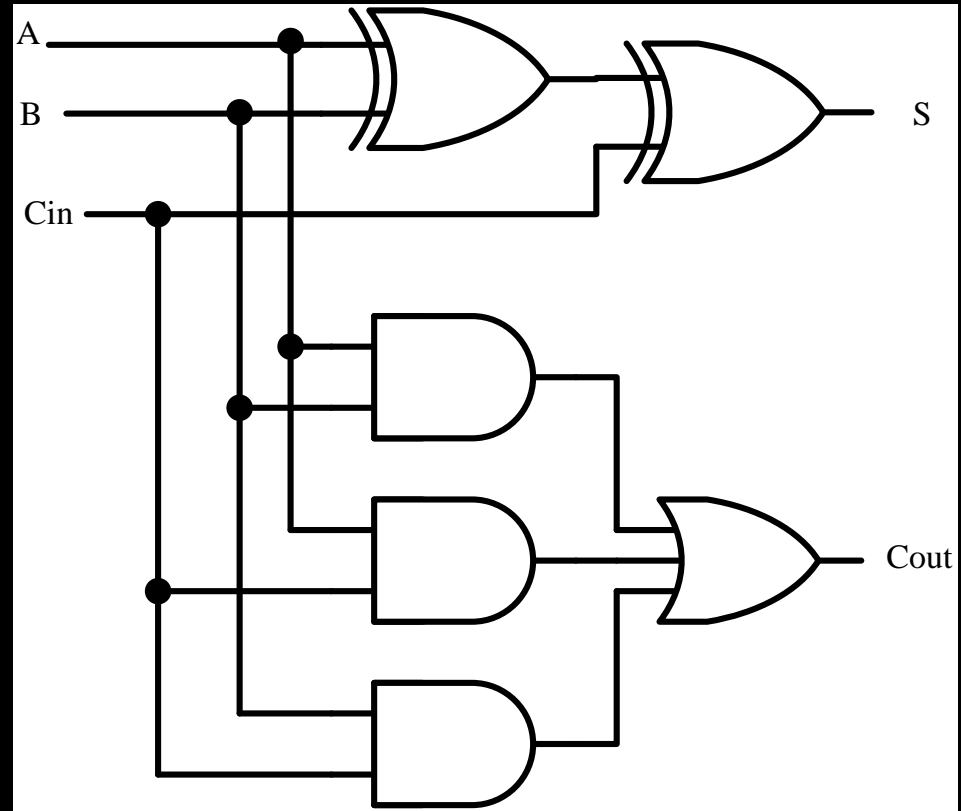



Ripple Carry Adder

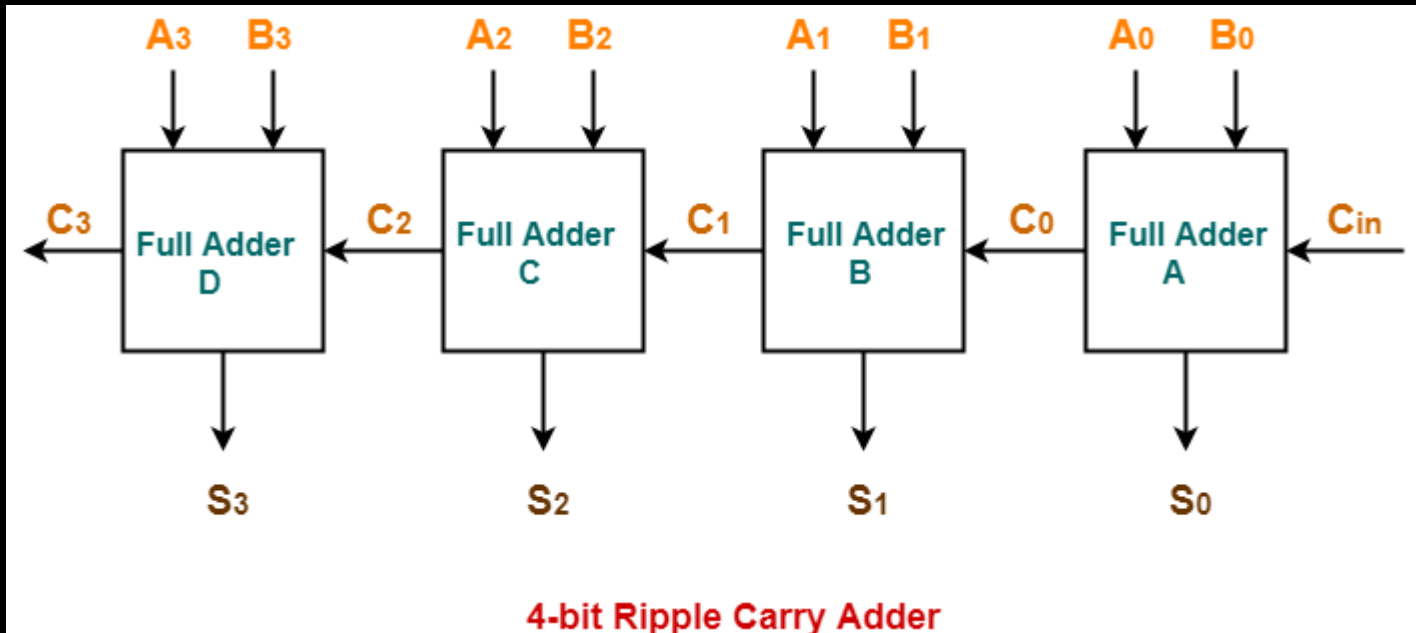This is called Ripple Carry Adder, because of the construction with full adders are connected in cascade.




Delay = 4 X Full Adder Delay



Carry Look-Ahead Adder

1-bit CLA

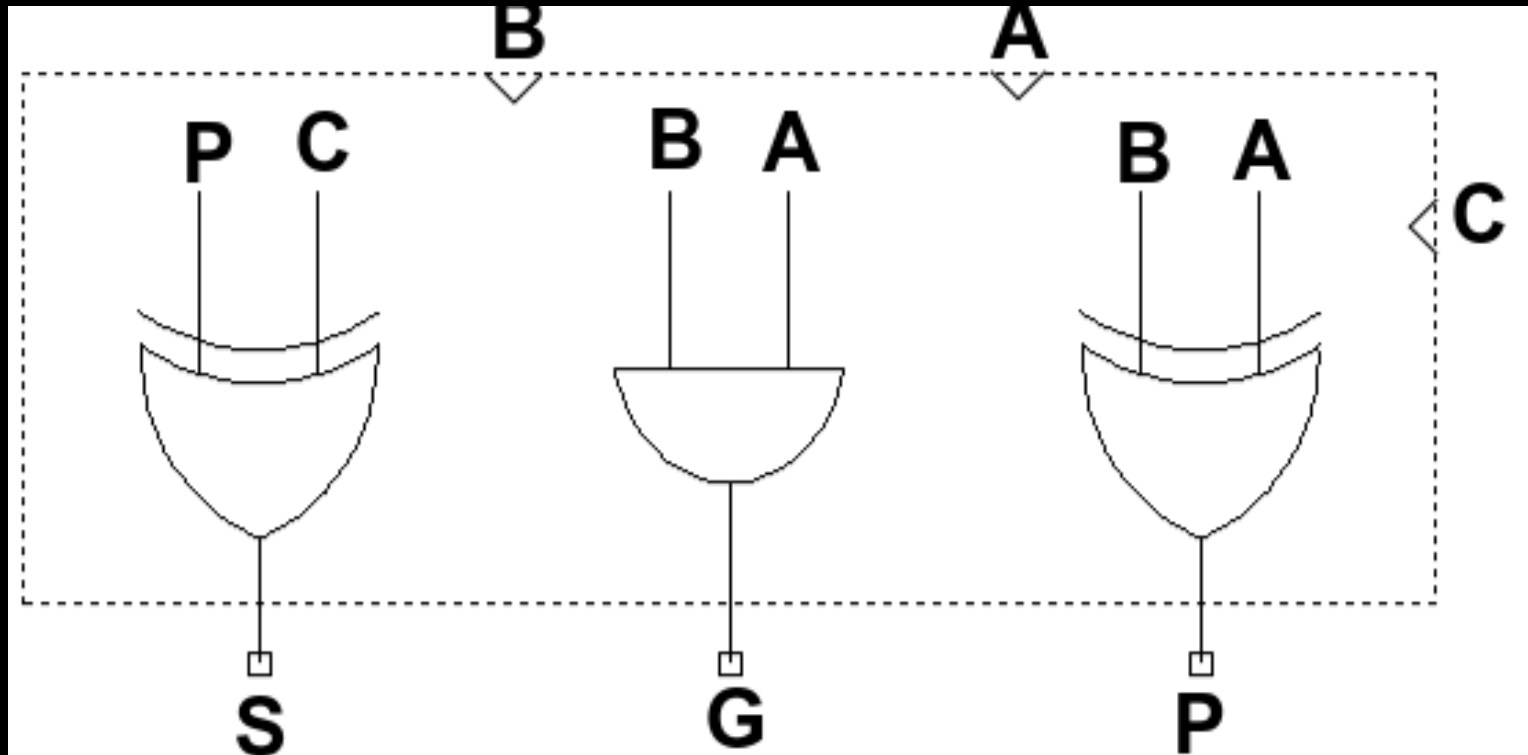





Carry Look-Ahead Adder

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$
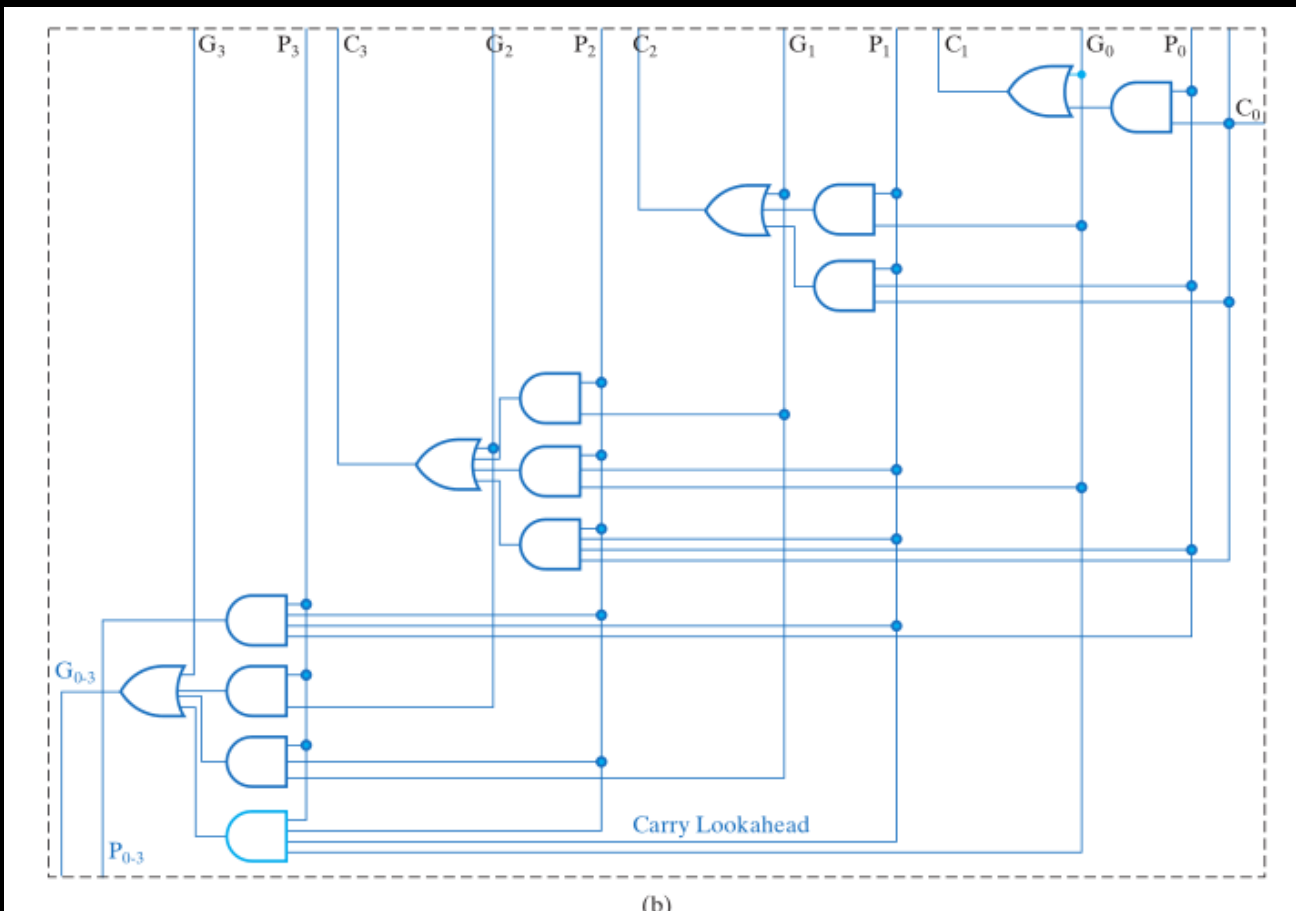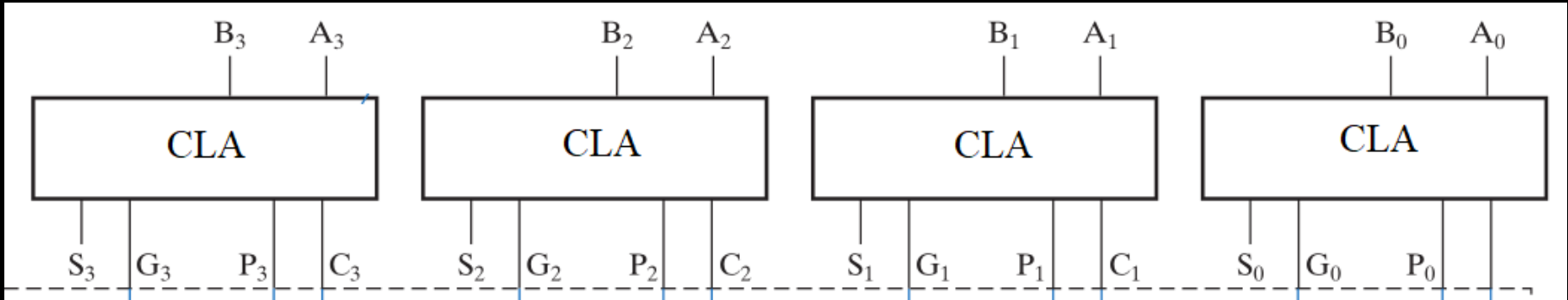
$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$



(b)




Binary Multiplier

A_3B_3 A_3B_2 A_3B_1 A_3B_0

A_2B_3 A_2B_2 A_2B_1 A_2B_0


A_1B_3 A_1B_2 A_1B_1 A_1B_0

A_0B_3 A_0B_2 A_0B_1 A_0B_0

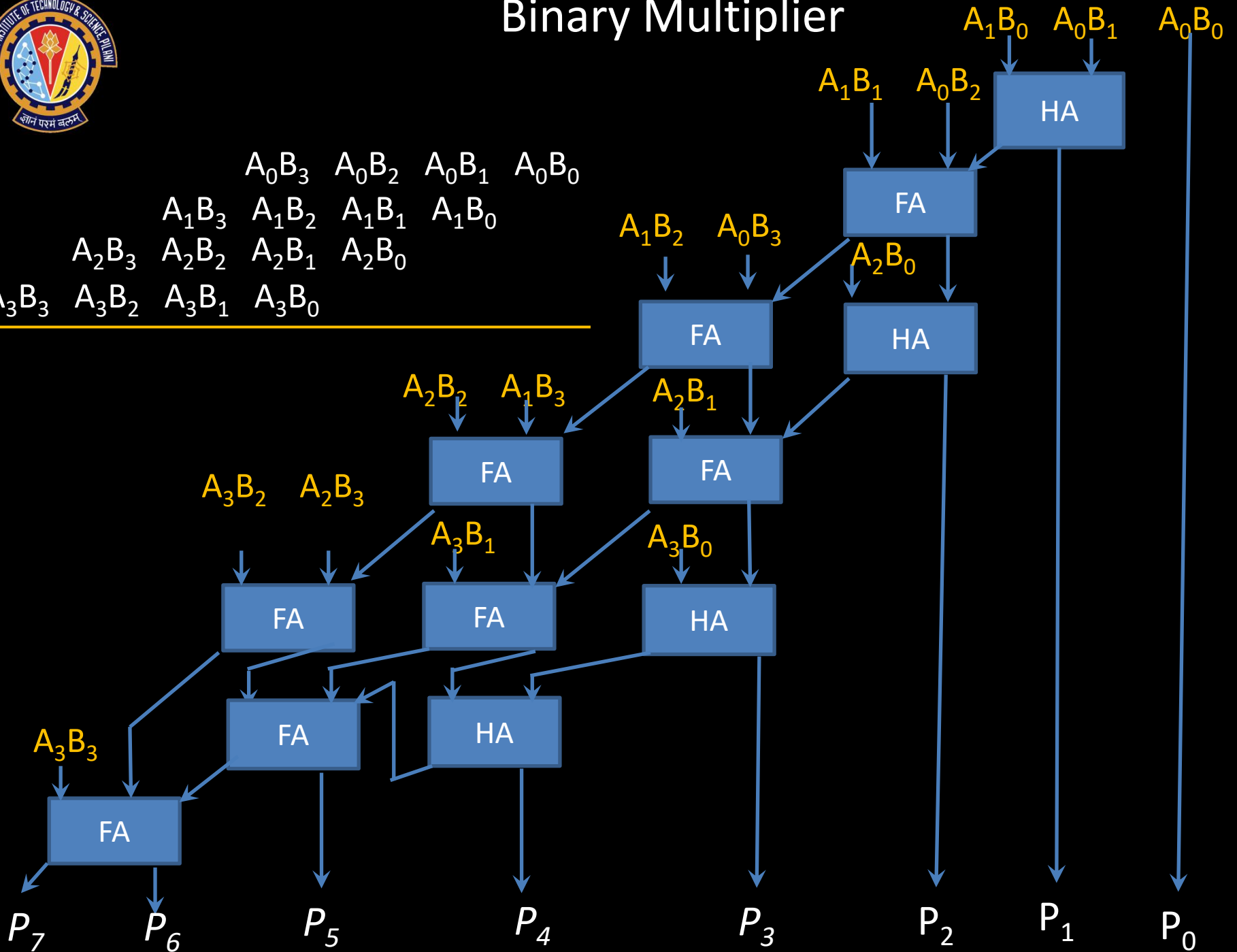



Decoder

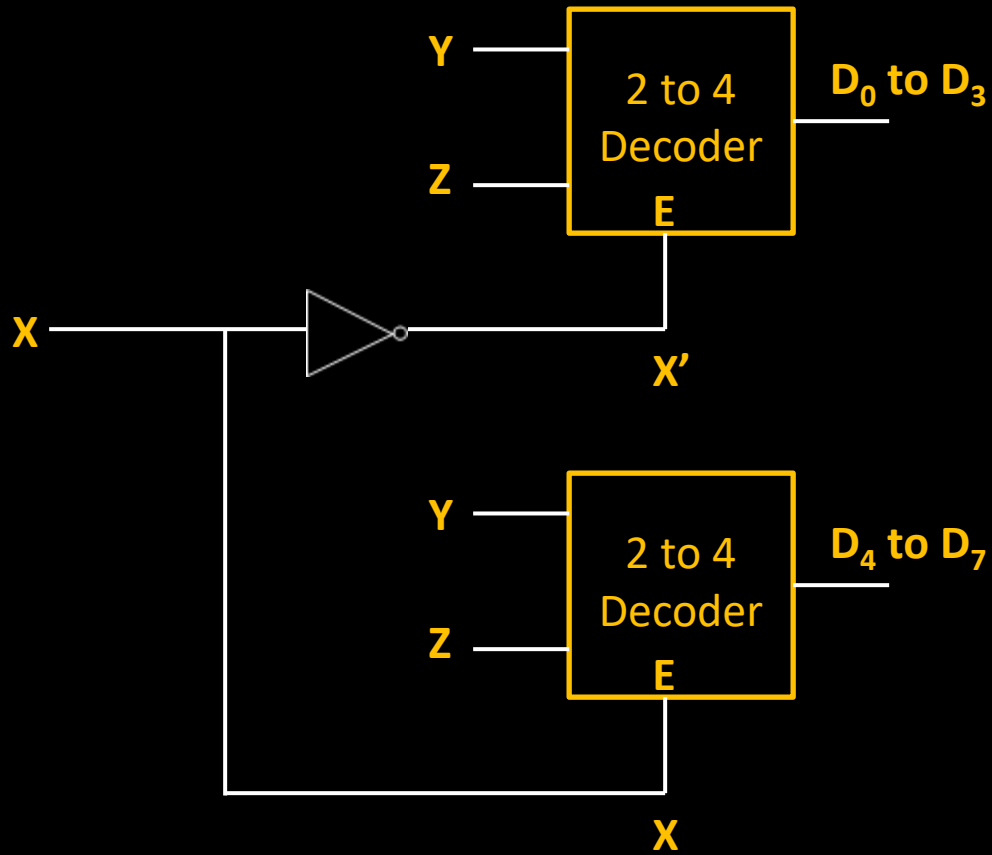





Decoder

Implementing function using Decoders
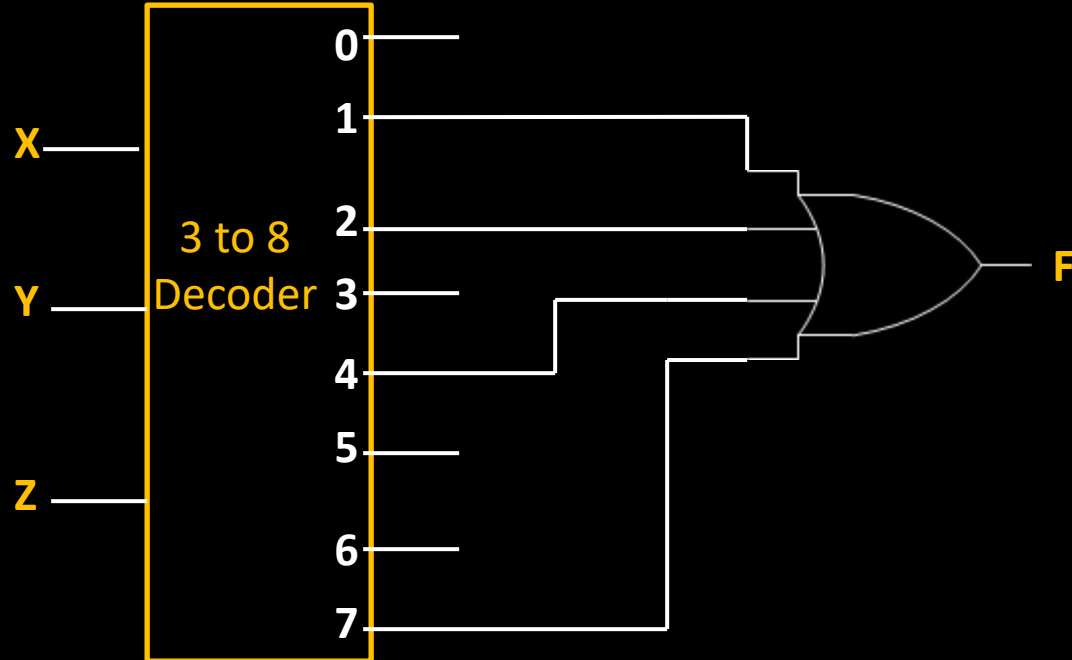
$$F = \sum (1, 2, 4, 7) = X'Y'Z + X'YZ' + XY'Z' + XYZ$$



Binary to Gray Using Encoder-Decoder

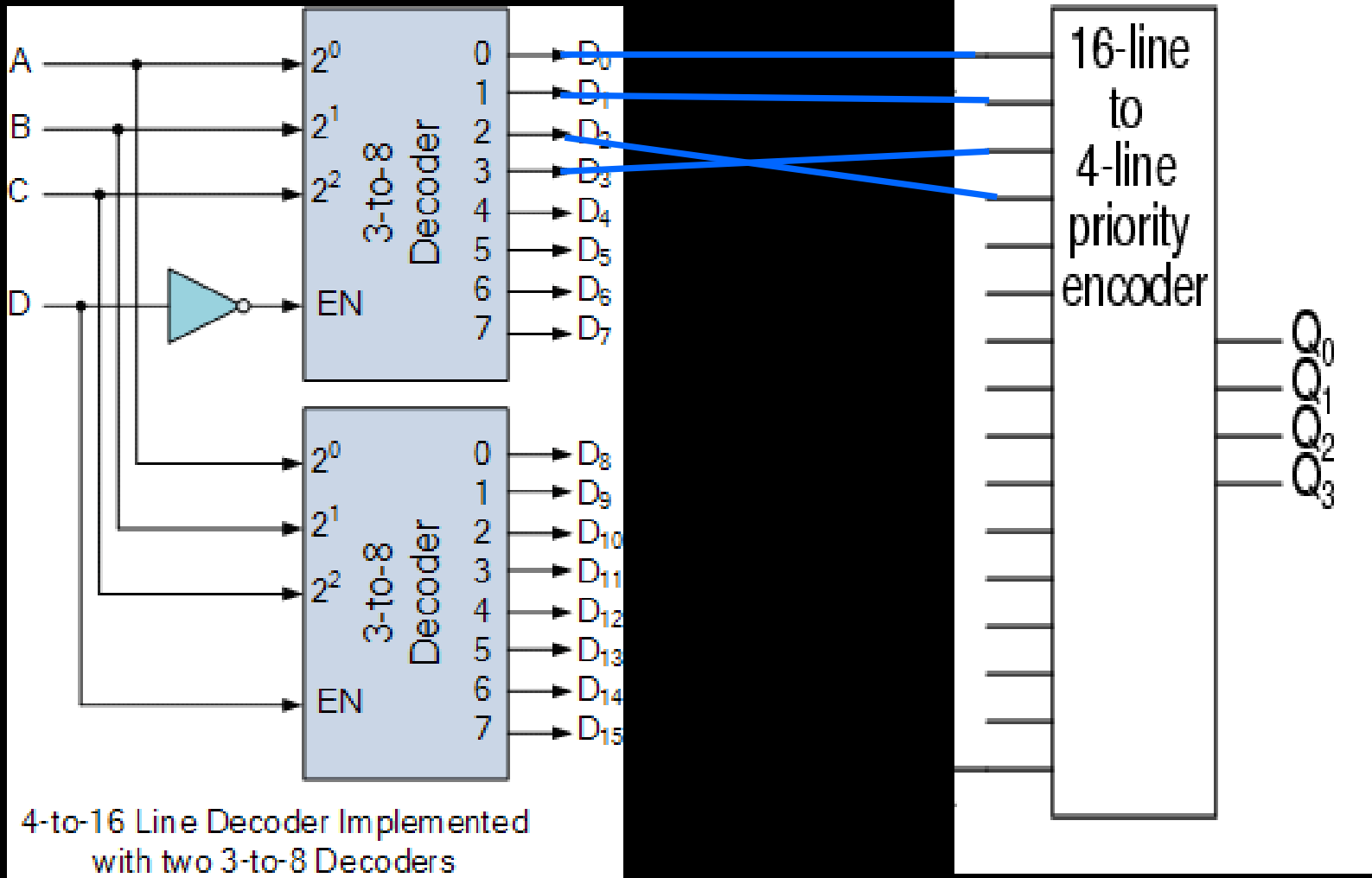




Multiplexers

Boolean Function implementation

$$F(X, Y, Z) = \sum(1, 2, 6, 7)$$

X	Y	Z	F	
0	0	0	0	$F = Z$
0	0	1	1	
0	1	0	1	$F = Z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

4:1
Multiplexer

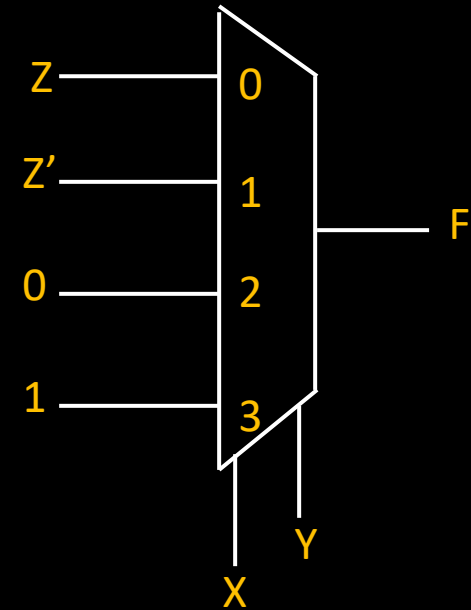



Multiplexers

Boolean Function implementation


$$F(X, Y, Z) = \sum(1, 2, 6, 7)$$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$F = Y \oplus Z$$

$$F = Y$$


2:1
Multiplexer

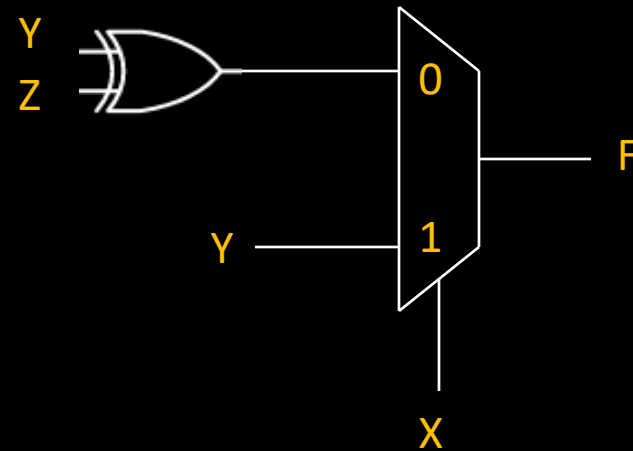



Latches


SR Latch with enable

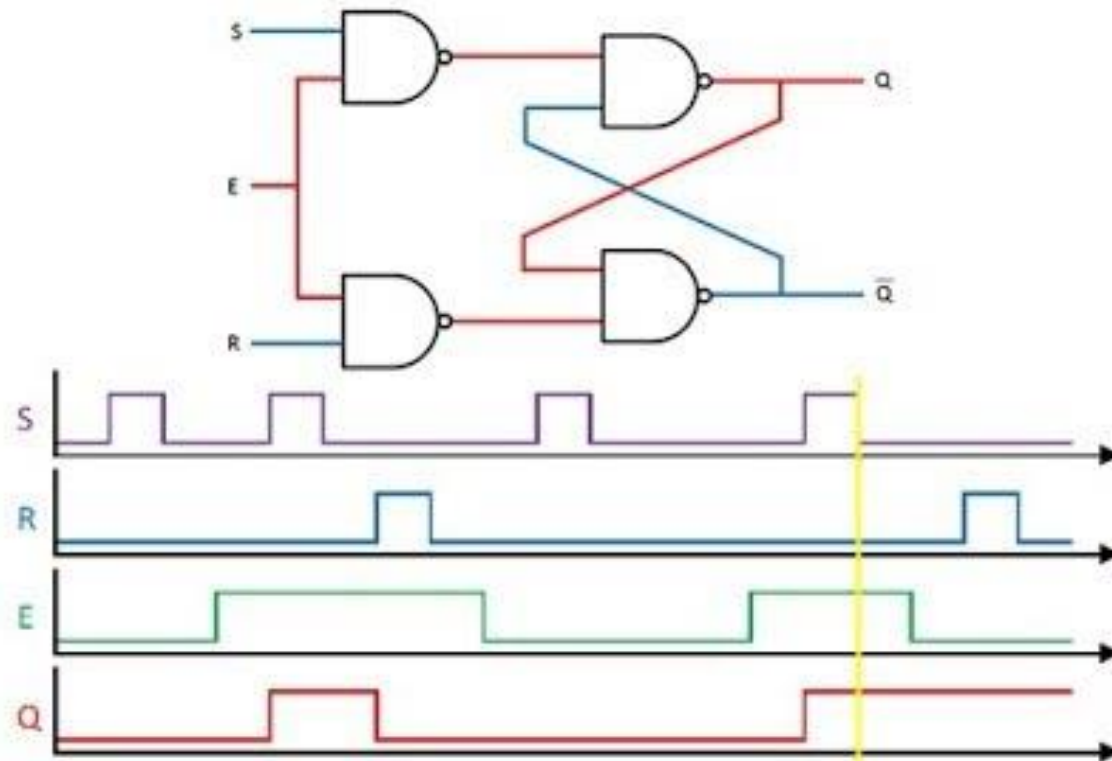



Edge Triggered D Flip-Flops


D-type positive edge triggered

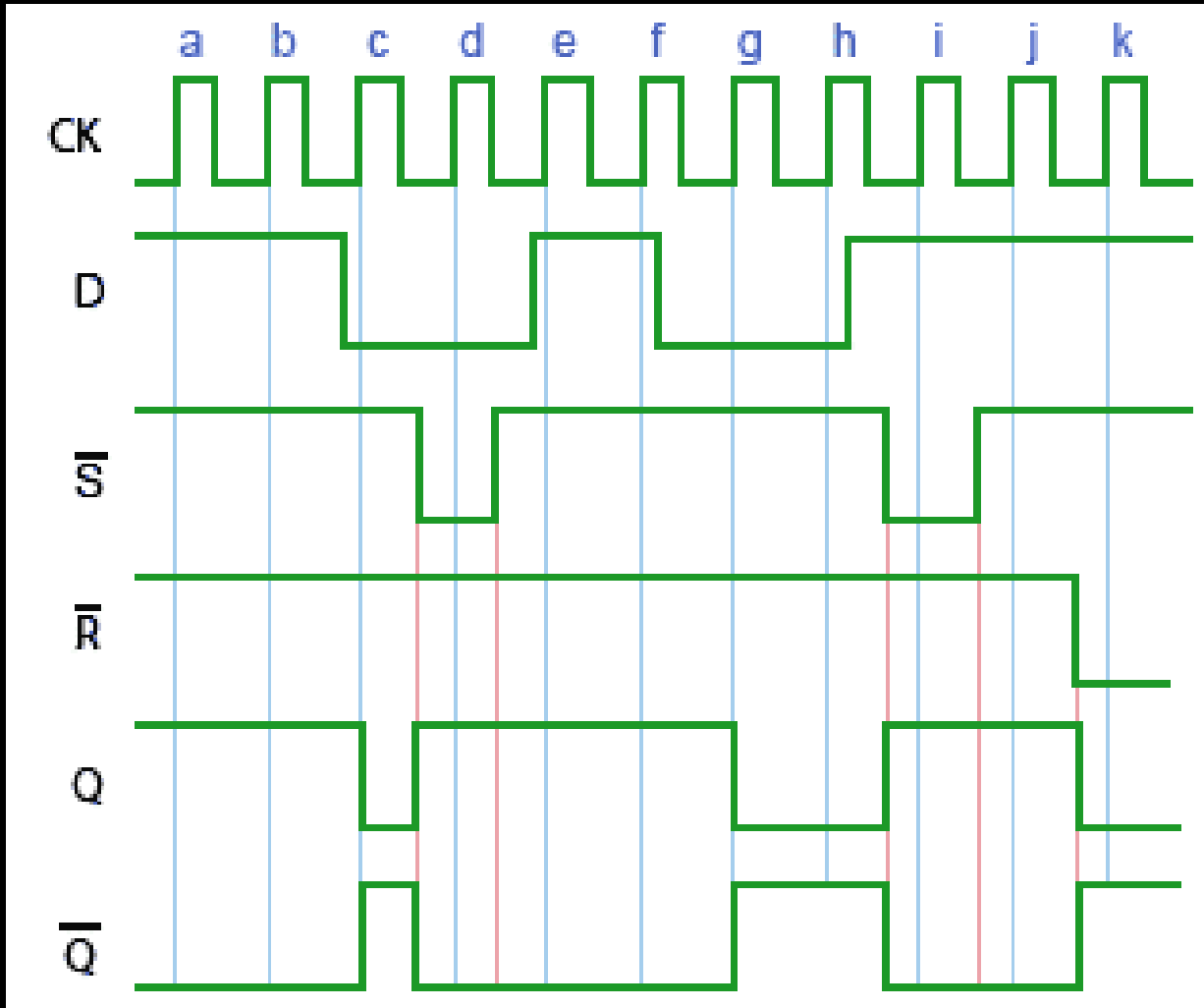



Other Flip-Flops

JK Flip-flop

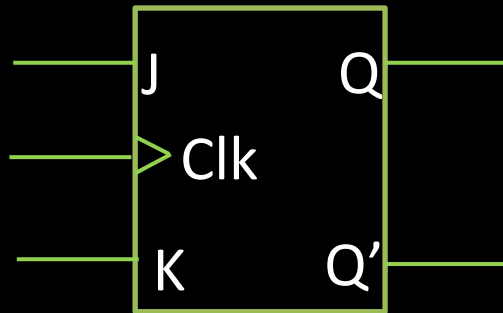

Characteristic Table

J	K	Q(t+1)	
0	0	Q(t)	No Change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Toggle/ Complement


Characteristic Equation??

$$Q(t+1) = JQ' + K'Q$$



Edge Triggered JK Flip-Flops


Positive Edge triggered

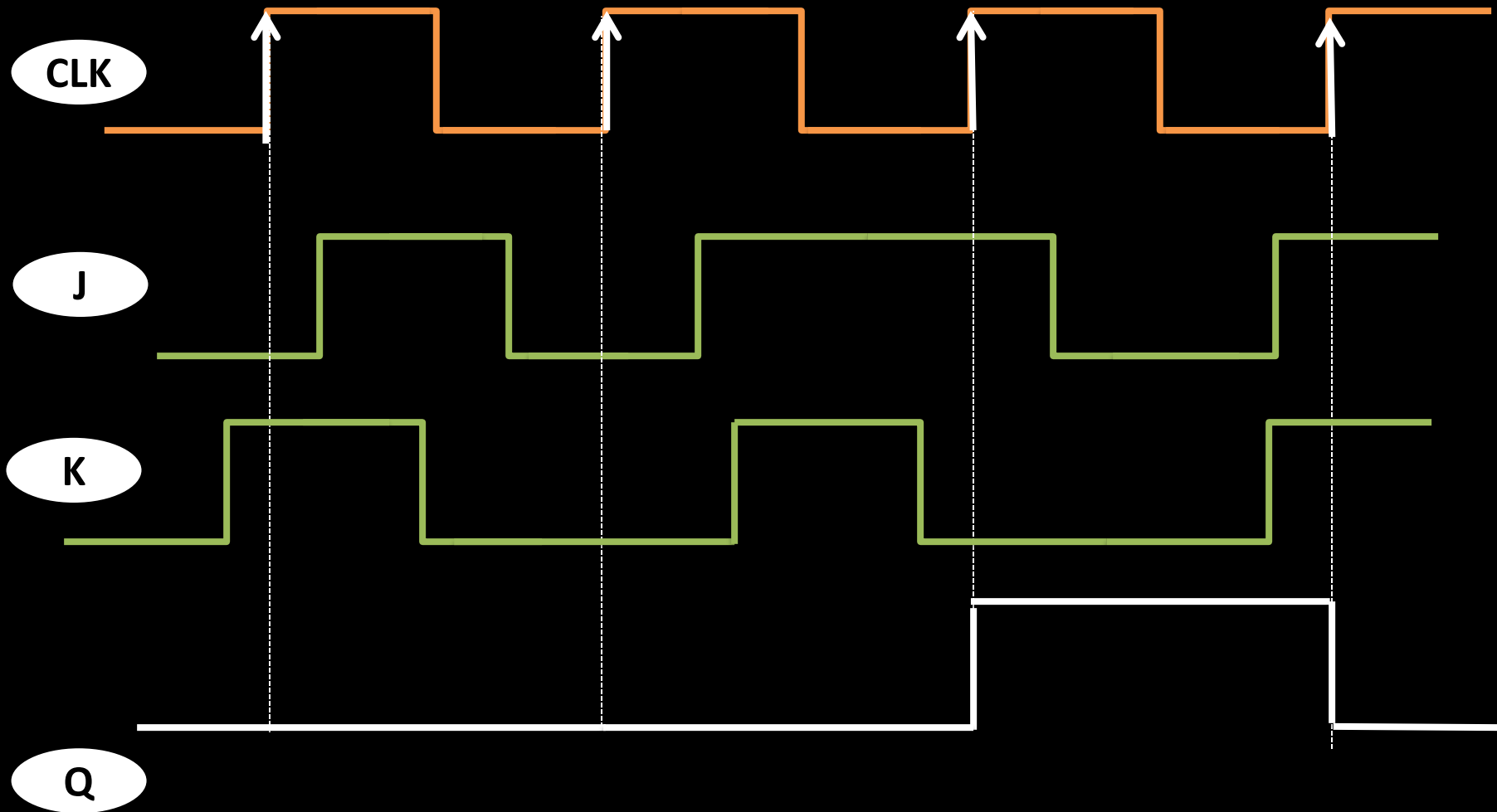



Other Flip-Flops

T Flip-flop

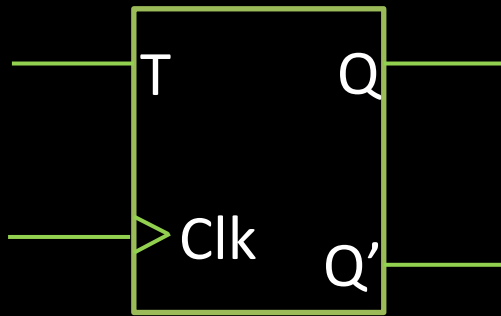

Characteristic Table

T	Q(t+1)	
0	Q(t)	No Change
1	Q'(t)	Toggle

Characteristic Equation??

$$Q(t+1) = T \oplus Q$$



Edge Triggered T Flip-Flops

Positive Edge triggered

