



**BITS Pilani**

Hyderabad Campus

Department of Electrical Engineering



# Digital Design


## First Semester 2020-21

### Tutorial : 10

## State Table Reduction

# Digital Design Tutorial : 10

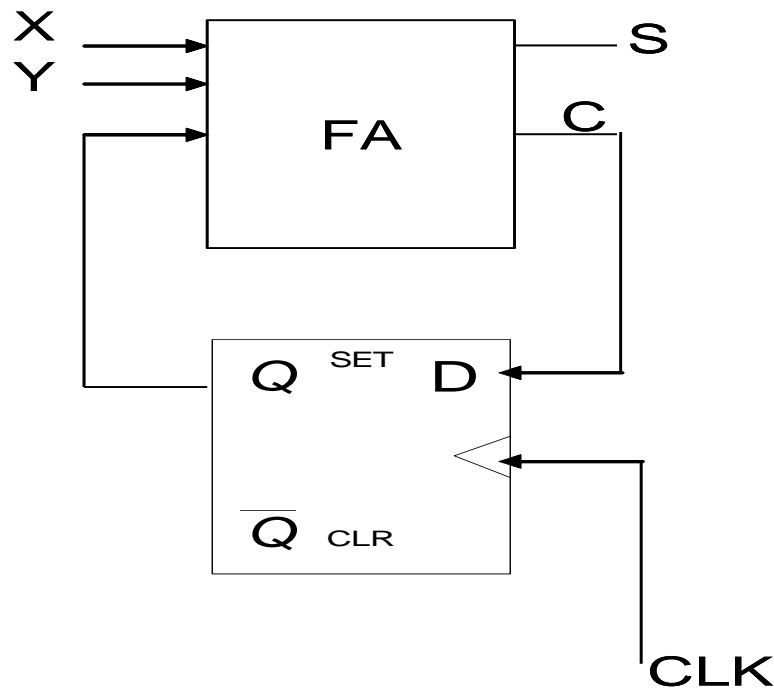1. A sequential circuit has one flip-flop Q, two inputs x and y, and one output S. It consists of a full-adder circuit connected to a D flip-flop, as shown. Derive the state table and state diagram of the sequential circuit.



# Digital Design Tutorial : 10

2. Reduce the number of states in the following table and tabulate the reduced state table.

PRESENT STATE	NEXT STATE		OUTPUT	
	X=0	X=1	X=0	X=1
a	f	b	0	0
b	d	c	0	0
c	f	b	0	0
d	g	a	1	0
f	f	b	1	1
g	g	d	0	1

# Digital Design Tutorial : 10

## 3. Optimize using Implication Table .

**State Table to be Reduced.**

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	d	a	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	d	1	0
f	c	b	0	0
g	a	e	1	0