



BITS Pilani

Hyderabad Campus

Department of Electrical Engineering



Digital Design

First Semester 2020-21

Tutorial : 09

Sequence Detector

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.