



**BITS Pilani**

Hyderabad Campus

Department of Electrical Engineering



# Digital Design

## First Semester 2020-21

### Tutorial : 09

# Sequence Detector

# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

## Step 1

We are designing a sequence detector for a 5-bit sequence, so we need 5 states. We label these states A, B, C, D, and E. State A is the initial state.

## Step 2

Characterize Each State by What has been Input and What is Expected State


State	Has	Awaiting
A	--	11011
B	1	1011
C	11	011
D	110	11
E	1101	1

# Digital Design Tutorial : 09

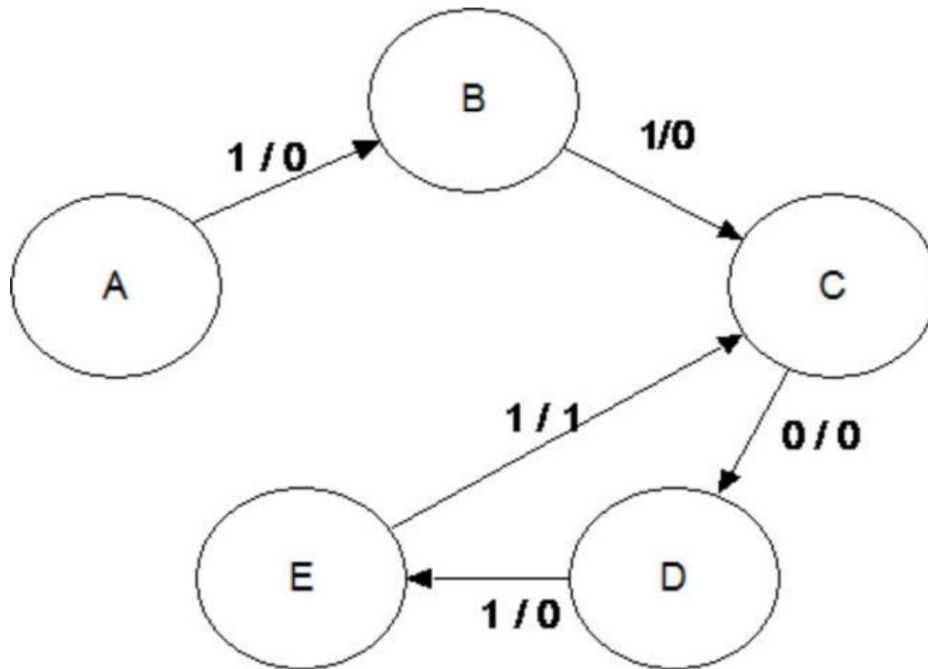1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 3


Do the Transitions for the Expected Sequence



# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 4 Complete the State Diagram

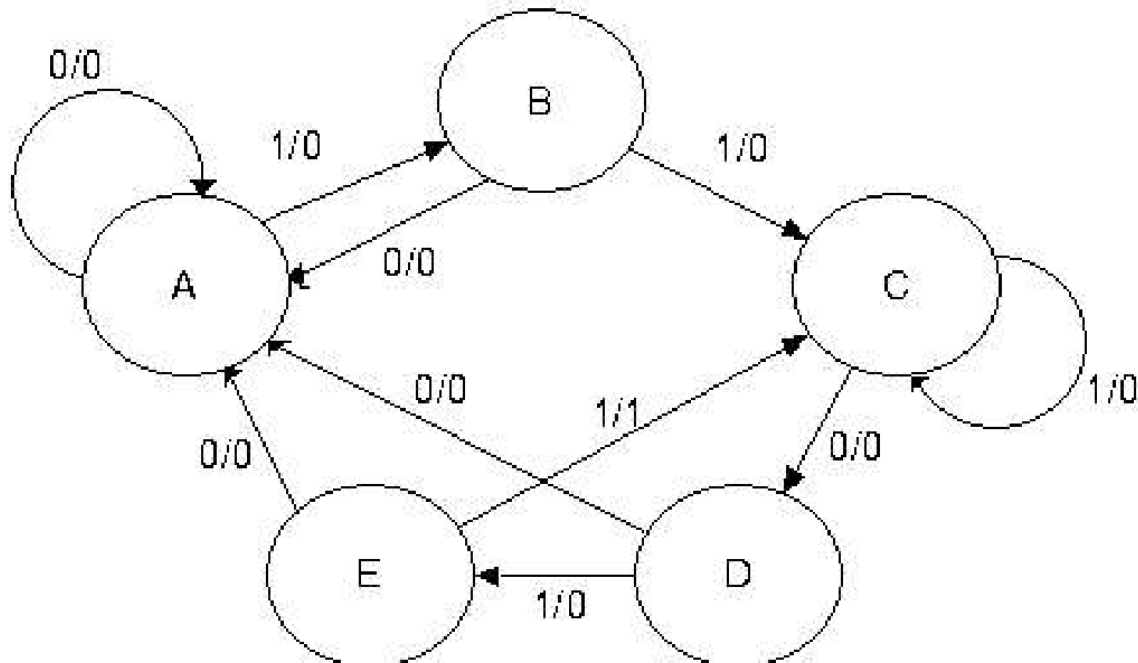

# Digital Design Tutorial : 09

1. Design a 11011sequence detector using JK flip-flops. Allow overlap.

Step 5 Make State Table

Present State	Next State / Output	
	X = 0	X = 1
A	A / 0	B / 0
B	A / 0	C / 0
C	D / 0	C / 0
D	A / 0	E / 0
E	A / 0	C / 1

# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 6 – Determine the Number of Flip-Flops Required

We have 5 states, so  $N = 5$ . We solve the equation  $2^{P-1} < 5 \leq 2^P$  by inspection, noting that it is solved by  $P = 3$ . So we need three flip-flops.

Step 7 – Assign a unique P-bit binary number (state vector) to each state.

The simplest way is to make the following assignments

A = 000

B = 001

C = 011 Note that states 010, 110, and 111 are not used.

D = 100

E = 101

Occasionally, a better assignment can be detected by inspection of the next state table. I note that the next states in the table cluster into two disjoint sets for  $X = 0$  and  $X = 1$ . For  $X = 0$  the possible next states are A and D For  $X = 1$  the possible next states are B, C, and E. For this reason, I elect to give even number assignments to states A and D, and to give odd number assignments to states B, C, and E.

# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 8 – Generate the Transition Table With Output

Present State		Next State / Output	
		X = 0	X = 1
	$Y_2Y_1Y_0$	$Y_2Y_1Y_0 / Z$	$Y_2Y_1Y_0 / Z$
A	0 0 0	0 0 0 / 0	0 0 1 / 0
B	0 0 1	0 0 0 / 0	0 1 1 / 0
C	0 1 1	1 0 0 / 0	0 1 1 / 0
D	1 0 0	0 0 0 / 0	1 0 1 / 0
E	1 0 1	0 0 0 / 0	0 1 1 / 1



# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 9 – Separate the Transition Table into Three Tables, One for Each Flip-Flop

Y2			Y1			Y0		
PS	Next State		PS	Next State		PS	Next State	
$Y_2Y_1Y_0$	$X = 0$	$X = 1$	$Y_2Y_1Y_0$	$X = 0$	$X = 1$	$Y_2Y_1Y_0$	$X = 0$	$X = 1$
000	0	0	000	0	0	000	0	1
001	0	0	001	0	1	001	0	1
011	1	0	011	0	1	011	0	1
100	0	1	100	0	0	100	0	1
101	0	0	101	0	1	101	0	1

Match     $Y_1$      $Y_2 \cdot Y_0'$     0     $Y_0$     0    1

# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 10 – Separate the Transition Table into Three Tables, One for Each Flip-Flop

Y2			Y1			Y0		
PS	Next State		PS	Next State		PS	Next State	
$Y_2Y_1Y_0$	$X = 0$	$X = 1$	$Y_2Y_1Y_0$	$X = 0$	$X = 1$	$Y_2Y_1Y_0$	$X = 0$	$X = 1$
0 0 0	0	0	0 0 0	0	0	0 0 0	0	1
0 0 1	0	0	0 0 1	0	1	0 0 1	0	1
0 1 1	1	0	0 1 1	0	1	0 1 1	0	1
1 0 0	0	1	1 0 0	0	0	1 0 0	0	1
1 0 1	0	0	1 0 1	0	1	1 0 1	0	1
Match	$Y_1$	$Y_2 \cdot Y_0'$	0	$Y_0$		0	1	

$$D2 = X' \cdot Y1 + X \cdot Y2 \cdot Y0'$$


$$D1 = X \cdot Y0$$

$$D0 = X$$

# Digital Design Tutorial : 09

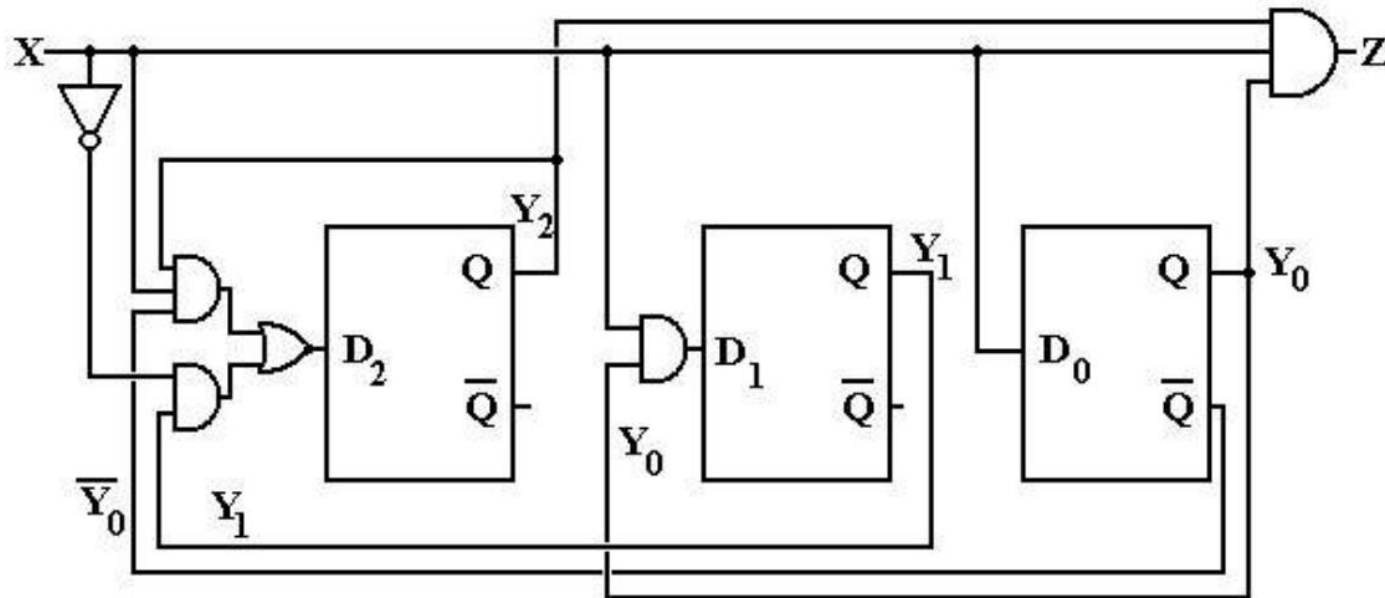1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 11 – design implemented with D flip-flops



$$D_2 = X' \cdot Y_1 + X \cdot Y_2 \cdot Y_0'$$

$$D_1 = X \cdot Y_0$$

$$D_0 = X$$

# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 12 – Derive an Input Table for Each JK Flip-Flop using its Excitation Table  
And Produce the Input Equations for Each Flip-Flop

$Y_2Y_1Y_0$	$X = 0$			$X = 1$		
	$Y_2$	$J_2$	$K_2$	$Y_2$	$J_2$	$K_2$
<b>0 0 0</b>	0	0	d	0	0	d
<b>0 0 1</b>	0	0	d	0	0	d
<b>0 1 1</b>	1	1	d	0	0	d
<b>1 0 0</b>	0	d	1	1	d	0
<b>1 0 1</b>	0	d	1	0	d	1

$$X = 0$$

$$J_2 = Y_1$$

$$K_2 = 1$$

$$X = 1$$

$$J_2 = 0$$

$$K_2 = Y_0$$

$$\text{thus, } J_2 = X' \cdot Y_1$$

$$\text{thus, } K_2 = X' + X \cdot Y_0 = X' + Y_0.$$

# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 13 – Derive an Input Table for Each JK Flip-Flop using its Excitation Table  
And Produce the Input Equations for Each Flip-Flop

Y <sub>2</sub> Y <sub>1</sub> Y <sub>0</sub>	X = 0			X = 1		
	Y <sub>1</sub>	J <sub>1</sub>	K <sub>1</sub>	Y <sub>1</sub>	J <sub>1</sub>	K <sub>1</sub>
0 0 0	0	0	d	0	0	d
0 0 1	0	0	d	1	1	d
0 1 1	0	d	1	1	d	0
1 0 0	0	0	d	0	0	d
1 0 1	0	0	d	1	1	d

$$X = 0$$

$$J_1 = 0$$

$$K_1 = 1$$

$$X = 1$$

$$J_1 = Y_0$$

$$K_1 = 0$$

thus  $J_1 = X \cdot Y_0$  and  $K_1 = X'$ .

# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 14 – Derive an Input Table for Each JK Flip-Flop using its Excitation Table  
And Produce the Input Equations for Each Flip-Flop

Y <sub>2</sub> Y <sub>1</sub> Y <sub>0</sub>	X = 0			X = 1		
	Y <sub>0</sub>	J <sub>0</sub>	K <sub>0</sub>	Y <sub>0</sub>	J <sub>0</sub>	K <sub>0</sub>
0 0 0	0	0	d	1	1	d
0 0 1	0	d	1	1	d	0
0 1 1	0	d	1	1	d	0
1 0 0	0	0	d	1	1	d
1 0 1	0	d	1	1	d	0

$$X = 0$$

$$J_0 = 0$$

$$K_0 = 1$$

$$X = 1$$

$$J_0 = 1$$


$$K_0 = 0$$

thus  $J_0 = X$  and  $K_0 = X'$ , as expected.

# Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 15 – Draw Circuit

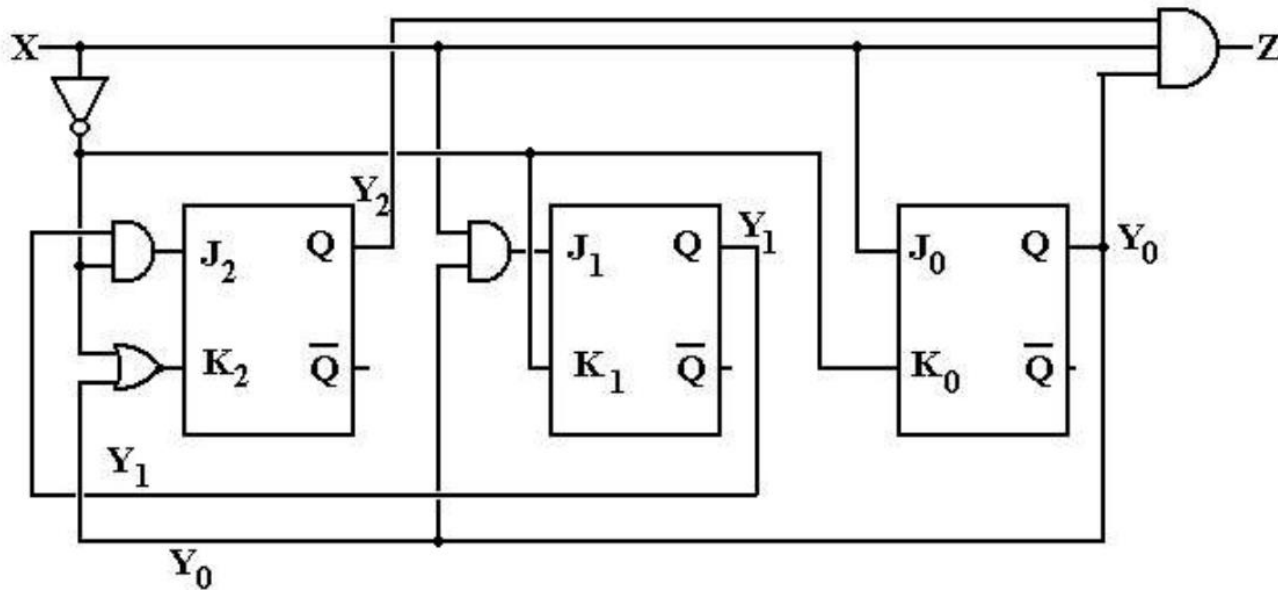

The equations implemented in this design are:

$$Z = X \cdot Y_2 \cdot Y_0$$

$$J_2 = X' \cdot Y_1$$

$$J_1 = X \cdot Y_0$$

$$J_0 = X$$

$$K_2 = X' + Y_0$$

$$K_1 = X'$$

$$K_0 = X'$$