




Digital Design : 2020-21


Lab 3

4-Bit Parallel Adder & BCD Adder

By Dr. Sanjay Vidhyadharan

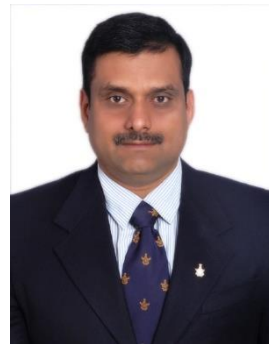

4-Bit Adder

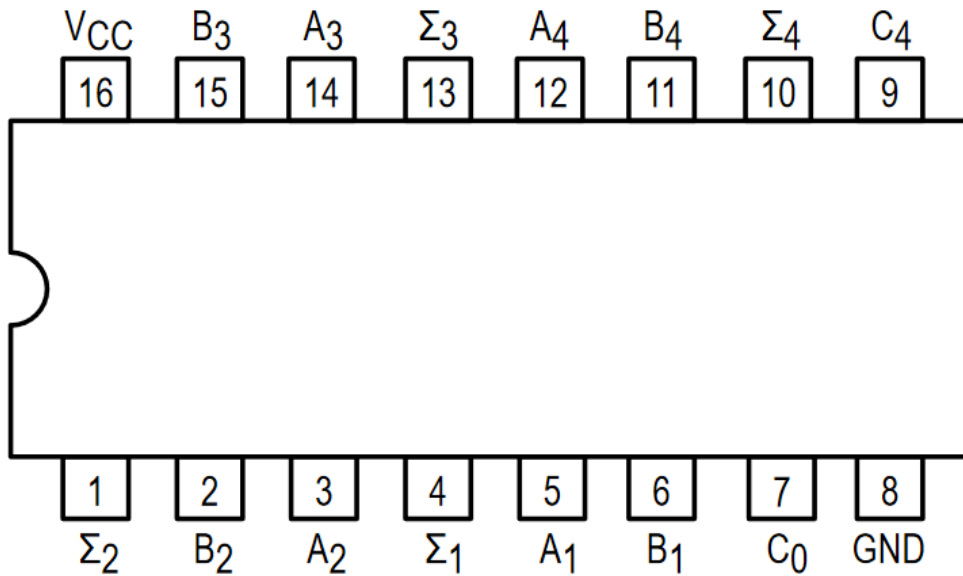


74283

Sanjay

4-Bit Adder

LOGIC DIAGRAM

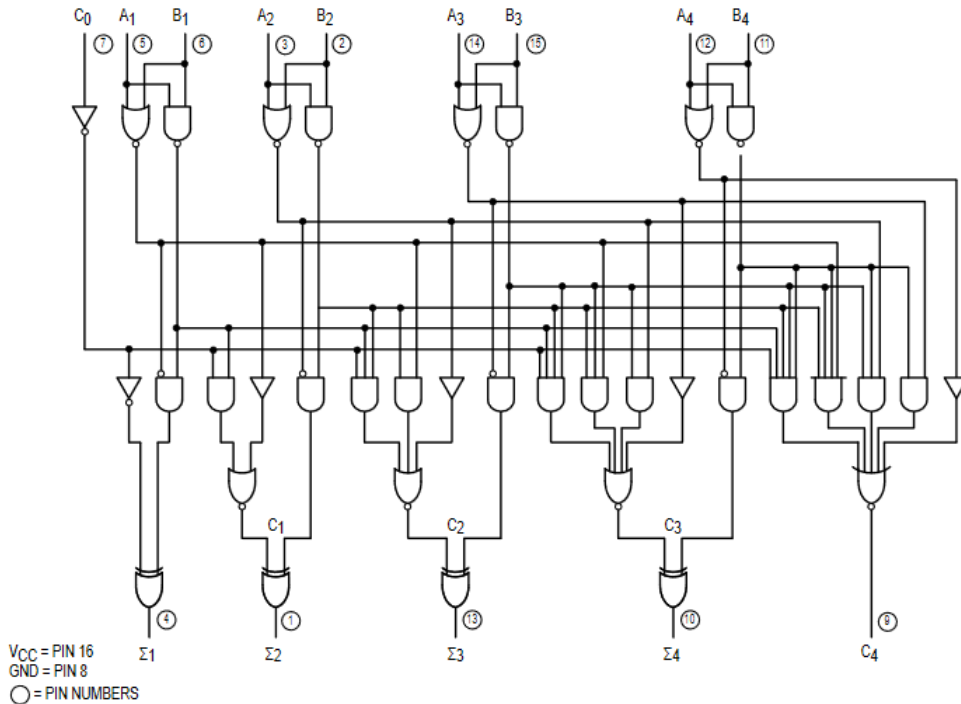


4-BIT BINARY FULL ADDER WITH FAST CARRY

The SN54/74LS283 is a high-speed 4-Bit Binary Full Adder with internal carry lookahead. It accepts two 4-bit binary words (A_1-A_4 , B_1-B_4) and a Carry Input (C_0). It generates the binary Sum outputs ($\Sigma_1-\Sigma_4$) and the Carry Output (C_4) from the most significant bit. The LS283 operates with either active HIGH or active LOW operands (positive or negative logic).


4-Bit Parallel Addder

Demo

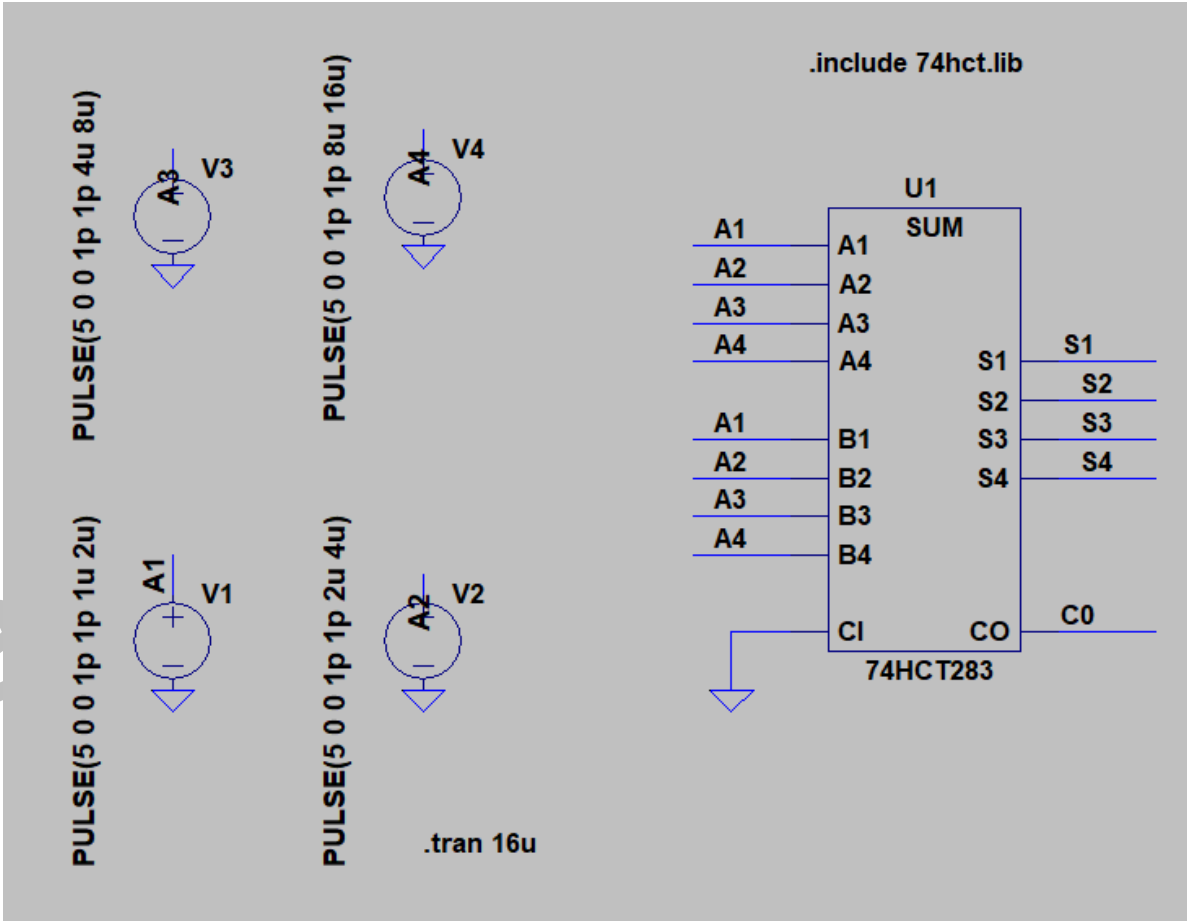

4-Bit Adder Subtractor

Problem 1

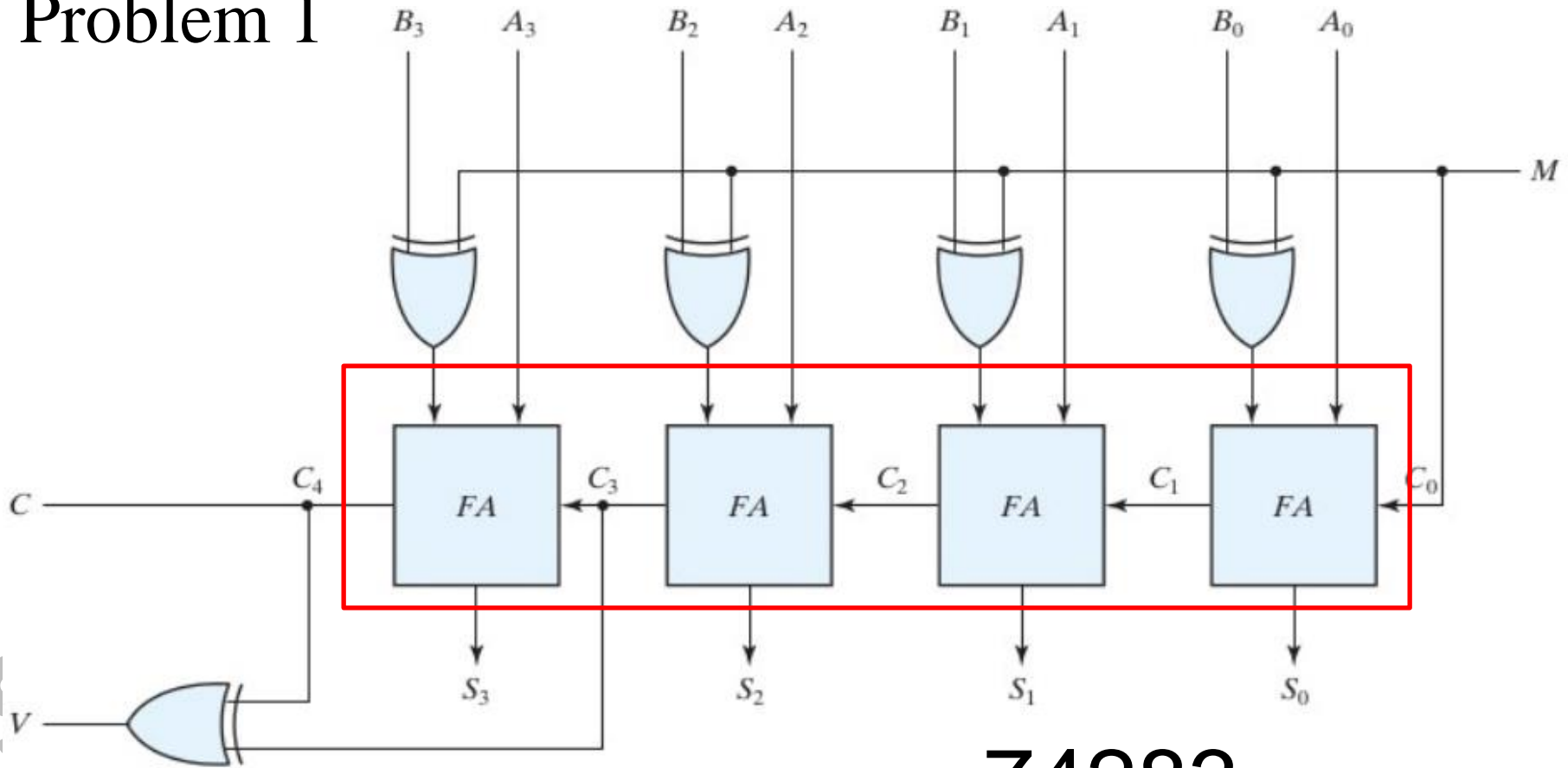

74283

4-Bit Adder Subtractor

Problem 1


| Signed 2's compl (n=4) | decimal value |
|------------------------|-----------------|
| 0000 | 0 |
| 0001 | 1 |
| 0010 | 2 |
| 0011 | 3 |
| 0100 | 4 |
| 0101 | 5 |
| 0110 | 6 |
| 0111 | $7=2^{n-1} - 1$ |
| 1000 | $-8=-2^{n-1}$ |
| 1001 | -7 |
| 1010 | -6 |
| 1011 | -5 |
| 1100 | -4 |
| 1101 | -3 |
| 1110 | -2 |
| 1111 | -1 |

ran.in

Sanjay


4-Bit Adder Subtractor

| A | B | M | Sum | Remarks |
|----|---|---|-----|----------|
| 0 | 4 | 0 | | |
| 1 | 4 | 0 | | |
| 2 | 4 | 0 | | |
| 3 | 4 | 0 | | |
| 4 | 4 | 0 | | Overflow |
| 5 | 4 | 0 | | Overflow |
| 6 | 4 | 0 | | Overflow |
| 7 | 4 | 0 | | Overflow |
| -8 | 4 | 0 | | |
| -7 | 4 | 0 | | |
| -6 | 4 | 0 | | |
| -5 | 4 | 0 | | |
| -4 | 4 | 0 | | |
| -3 | 4 | 0 | | |
| -2 | 4 | 0 | | |
| -1 | 4 | 0 | | |

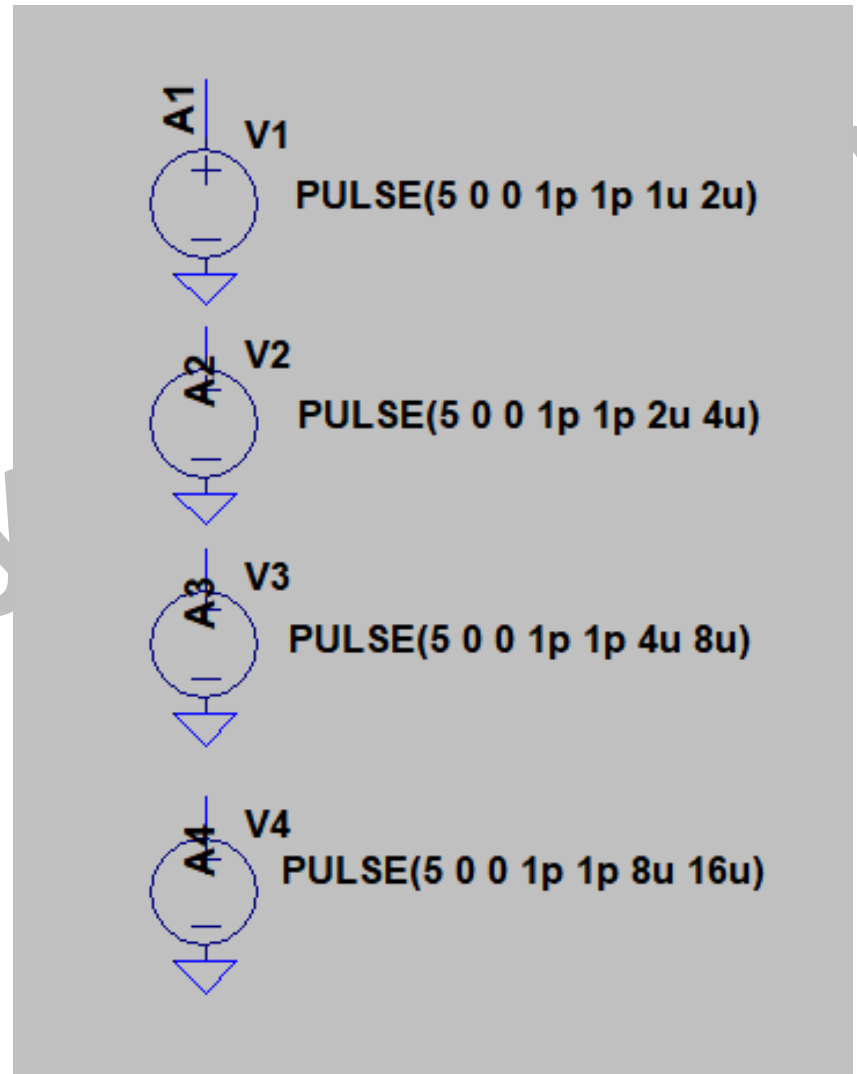


4-Bit Adder Subtractor


| A | B | M | Sum | Remarks |
|----|---|---|-----|----------|
| 0 | 4 | 1 | | |
| 1 | 4 | 1 | | |
| 2 | 4 | 1 | | |
| 3 | 4 | 1 | | |
| 4 | 4 | 1 | | |
| 5 | 4 | 1 | | |
| 6 | 4 | 1 | | |
| 7 | 4 | 1 | | |
| -8 | 4 | 1 | | Overflow |
| -7 | 4 | 1 | | Overflow |
| -6 | 4 | 1 | | Overflow |
| -5 | 4 | 1 | | Overflow |
| -4 | 4 | 1 | | |
| -3 | 4 | 1 | | |
| -2 | 4 | 1 | | |
| -1 | 4 | 1 | | |

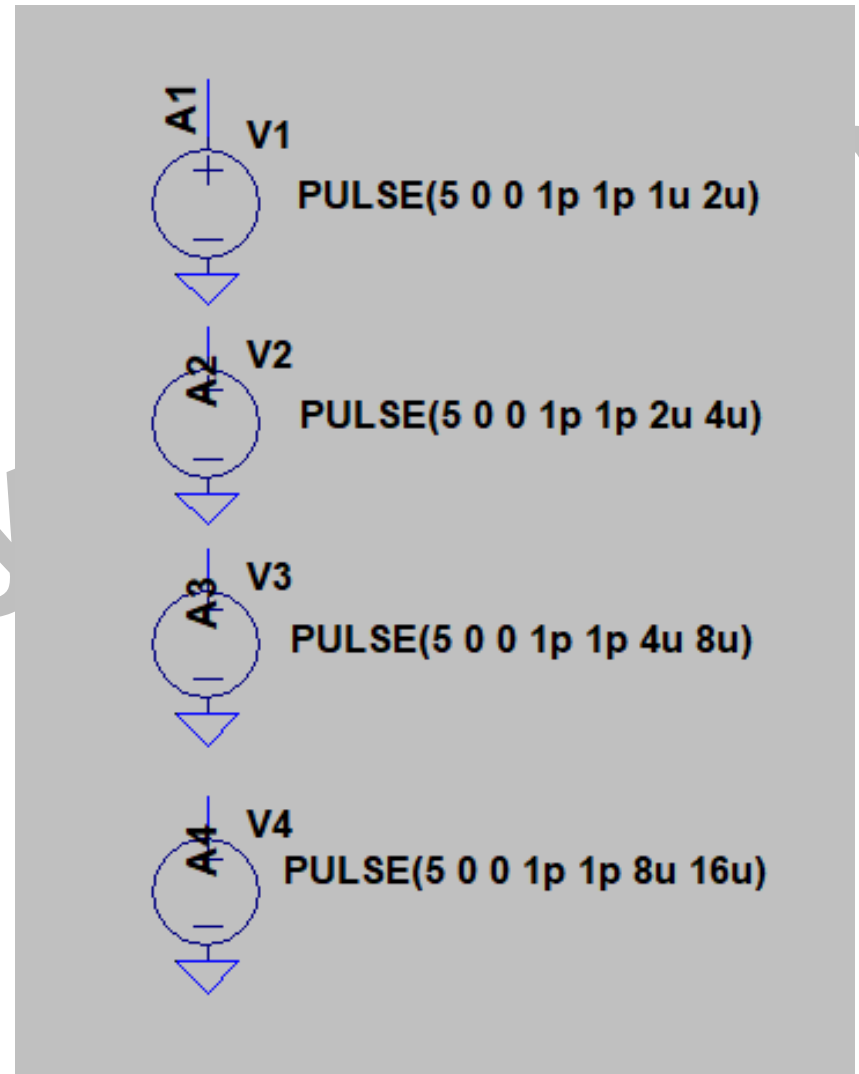

4-Bit Adder Subtractor

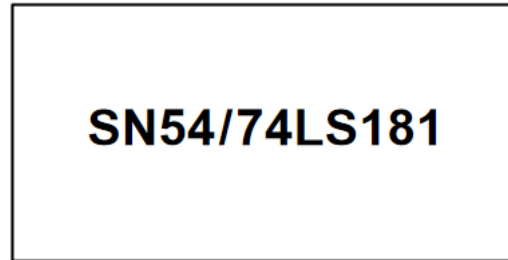


CONNECTION DIAGRAM DIP (TOP VIEW)

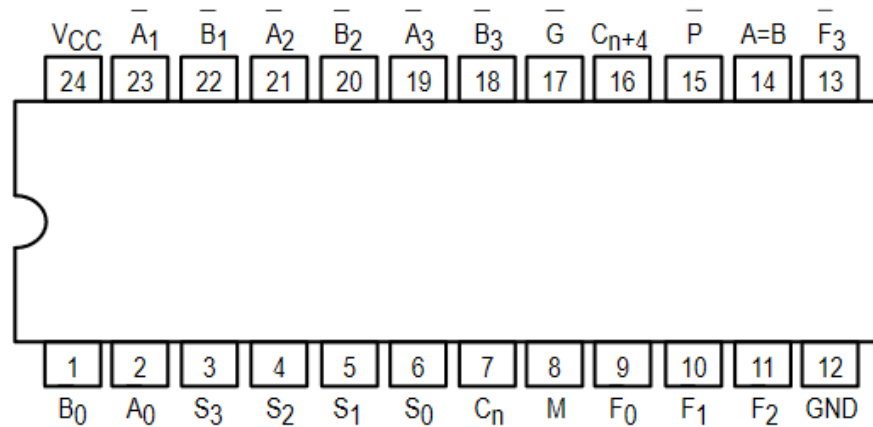

NOTE:
The Flatpak version
has the same pinouts
(Connection Diagram) as
the Dual In-Line Package.

BCD Adder


Problem 2

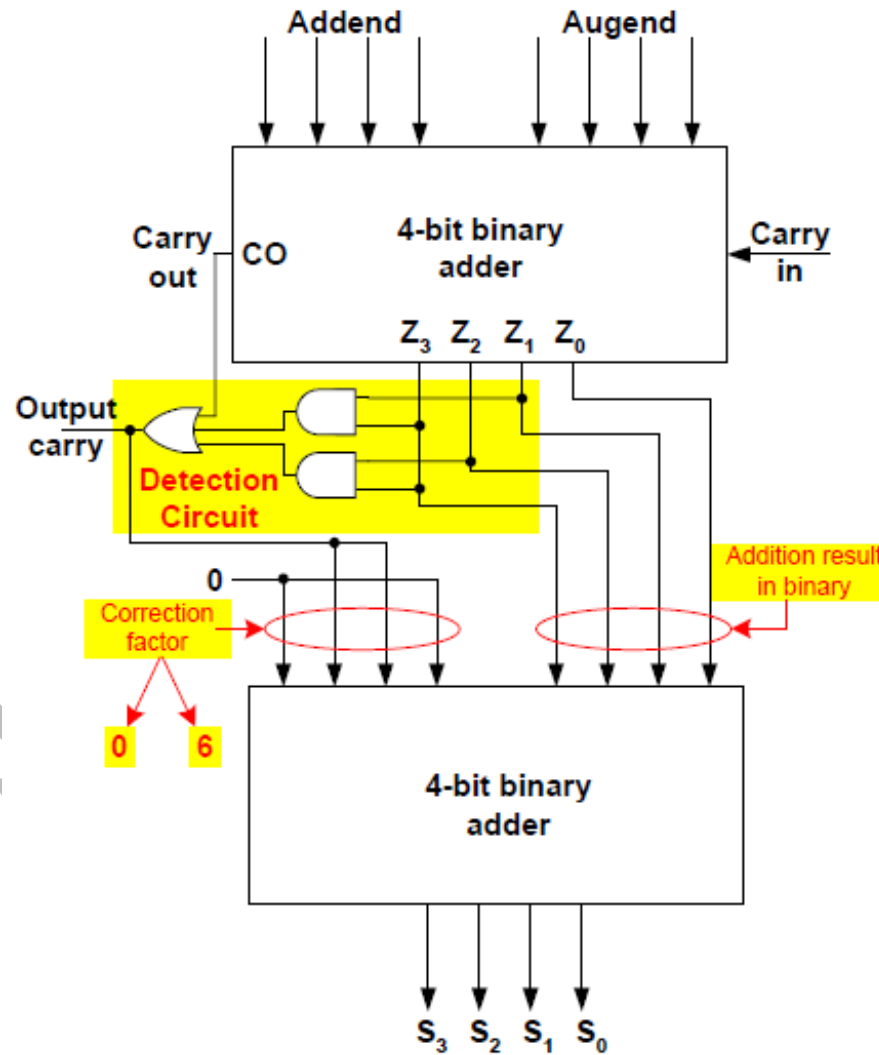

BCD Adder

| A | B | Carry | Sum |
|---|---|-------|-----|
| 0 | 0 | | |
| 1 | 1 | | |
| 2 | 2 | | |
| 3 | 3 | | |
| 4 | 4 | | |
| 5 | 5 | | |
| 6 | 6 | | |
| 7 | 7 | | |
| 8 | 8 | | |
| 9 | 9 | | |

Trans : 9u

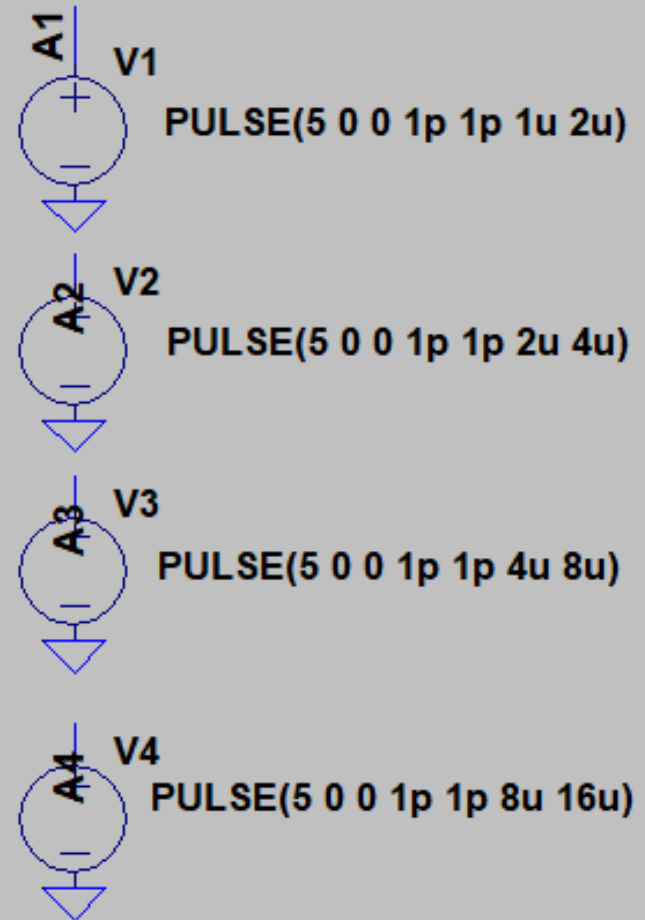



Demonstration