



Digital Design

First Semester 2020-21

Tutorial : 12


CMOS Implementation

CMOS Device Structure


For every CMOS device, there are essentially **two** separate circuits:

- 1) *The Pull-Up Network*
- 2) *The Pull-Down Network*

The basic **CMOS** structure is:

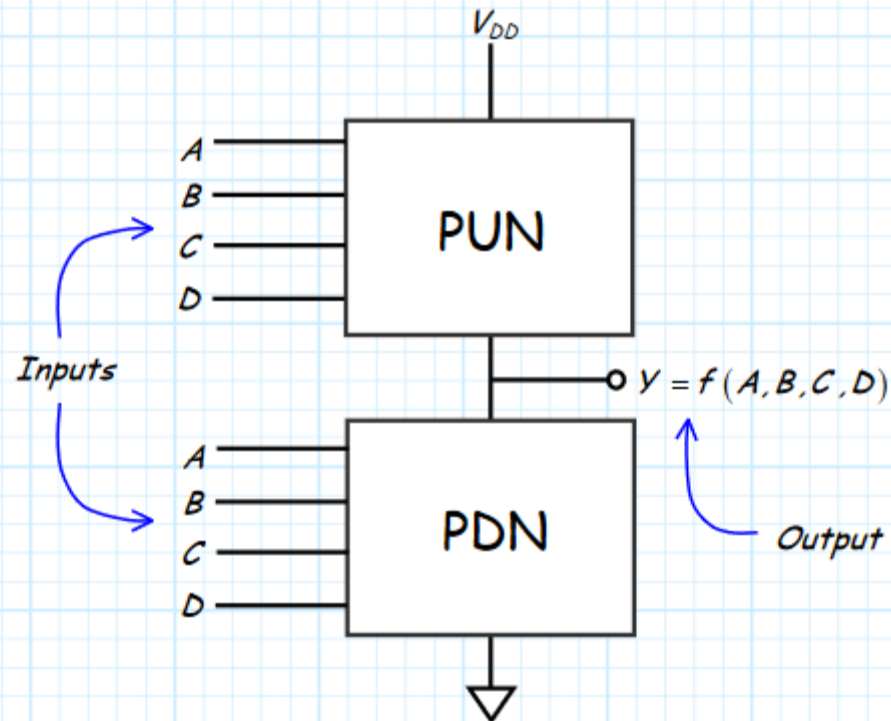


 State 1: PUN is **open** and PDN is **conducting**.




In this state,
the output is
LOW (i.e., $Y=0$).

 State 2: PUN is **conducting** and PDN is **open**.




In this state,
the output is
HIGH (i.e., $Y=1$).

 Thus, the PUN and the PDN essentially act as **switches**, connecting the output to **either** V_{DD} or to ground:




- * Note that the key to proper operation is that **one** switch must be closed, while the **other** must be open.
- * **Both** switches closed or **both** switches open would cause an **ambiguous** digital output!
- * To prevent this from occurring, the PDN and PUN must be **complementary** circuits.

 For example, consider the **CMOS inverter**:



For more **complex** digital CMOS gates (e.g., a 4-input OR gate), we find:

 - 1) The PUN will consist of **multiple** inputs, therefore requires a circuit with **multiple PMOS** transistors.
- 2) The PDN will consist of **multiple** inputs, therefore requires a circuit with **multiple NMOS** transistors.




PDN Design Synthesis


1. If the PDN is **conducting**, then the **output** will be **low**.
Thus, we must find a Boolean expression for the **complemented output** \bar{Y} .


In turn, the PDN can only be conducting if **one or more** of the NMOS devices are **conducting**—and NMOS devices will be conducting (i.e., **triode mode**) when the **inputs are high** ($V_{GSN} = V_{DD}$).

Thus, we **must** express \bar{Y} in terms of **un-complemented inputs** A, B, C , etc (i.e., $\bar{Y} = f(A, B, C)$).

e.g., $\rightarrow \bar{Y} = A + BC$

 

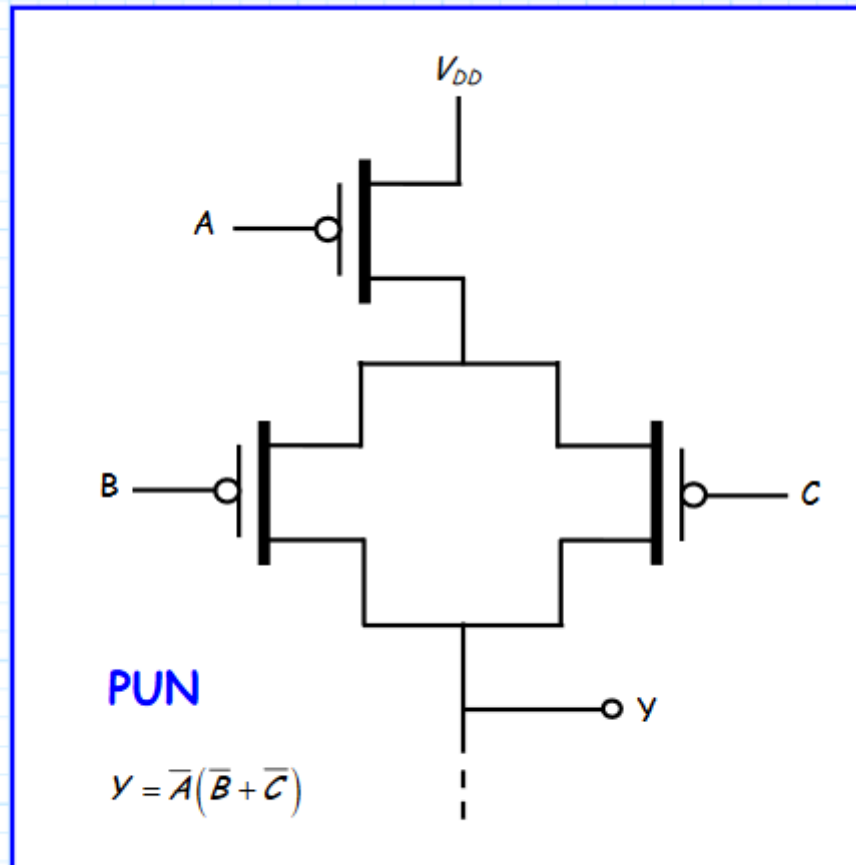

 

Problem 1


1. Realize the following logic function with AOI gates and CMOS Transistors

$$f = \overline{x_1 x_2 + x_3 x_4 + x_5}.$$

Problem 1


1. Realize the following logic function with AOI gates and CMOS Transistors

$$f = \overline{x_1x_2 + x_3x_4 + x_5}.$$

 

Problem 1


1. Realize the following logic function with AOI gates and CMOS Transistors $f = \overline{x_1x_2 + x_3x_4 + x_5}$.

 

Problem 2

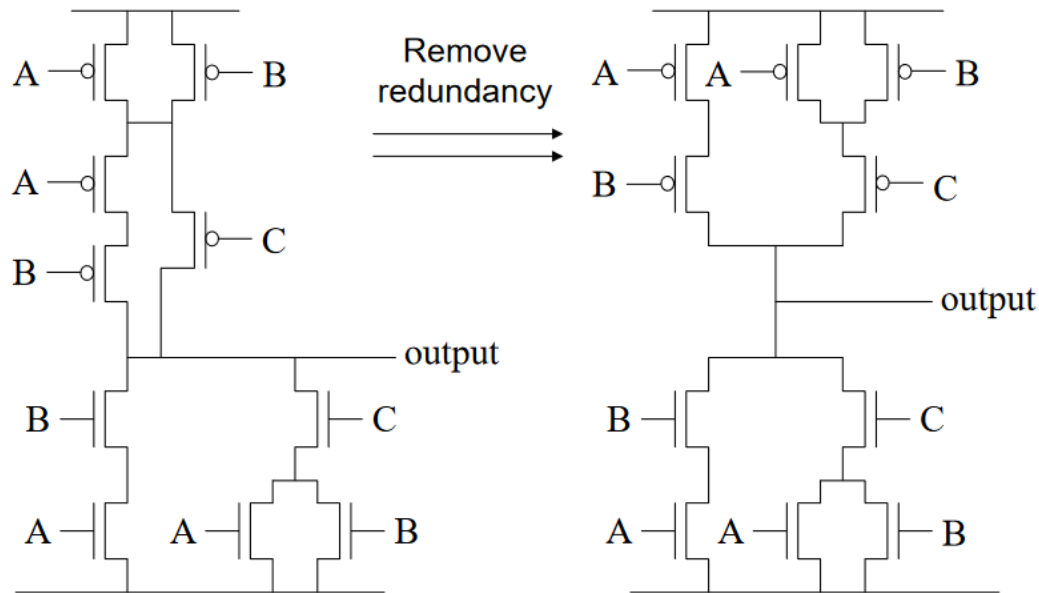2. Realize Full Adder with CMOS Transistors

$$F = \overline{((A.B) + C.(A+B))} = \text{carry}$$




Symmetrical !

Problem 2

2. Realize Full Adder with CMOS Transistors


$$F = \overline{(ABC + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C})} = \overline{\text{sum}}$$

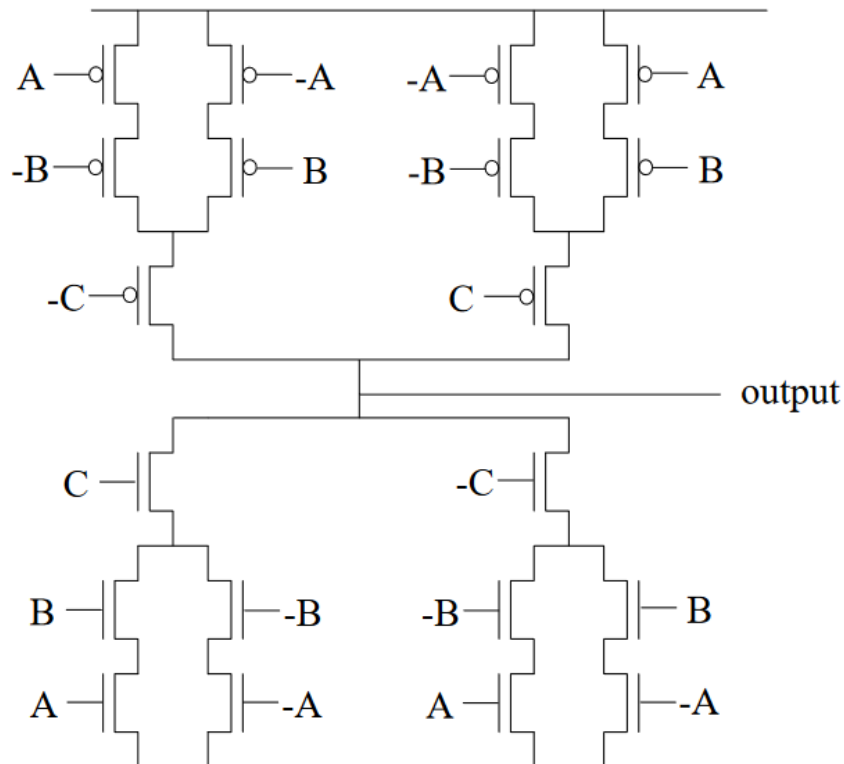

Problem 2

2. Realize Full Adder with CMOS Transistors


$$F = \overline{(ABC + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C})} = \overline{\text{sum}}$$

 

Problem 2

2. Realize Full Adder with CMOS Transistors

Full Adder Circuit

 

Problem 2

2. Realize Full Adder with CMOS Transistors

Full Adder Circuit

