




Digital Design
First Semester 2020-21
Tutorial : 06

**Design using Decoders and
Multiplexers**

SanjayVidhyadaran.in

Digital Design Tutorial : 06

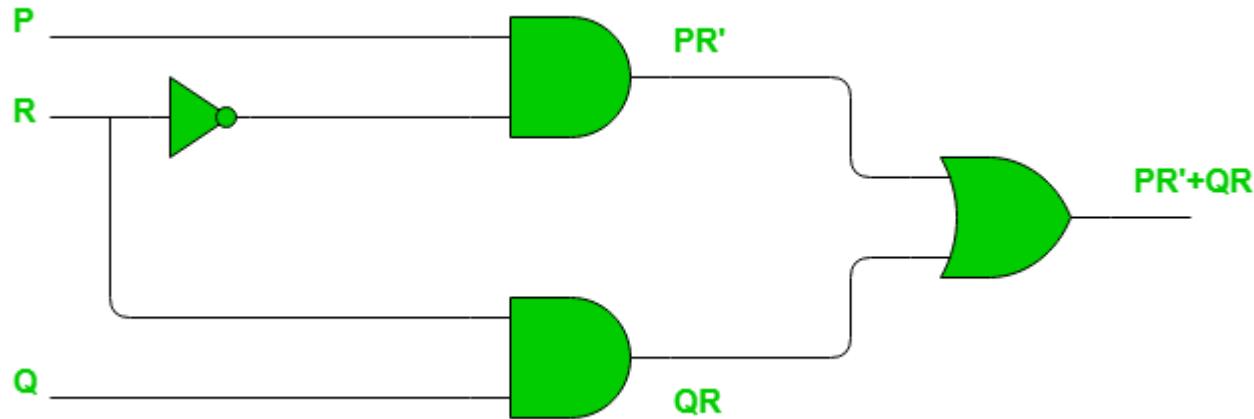
1. Identify hazard in the circuit and eliminate it



Digital Design Tutorial : 06

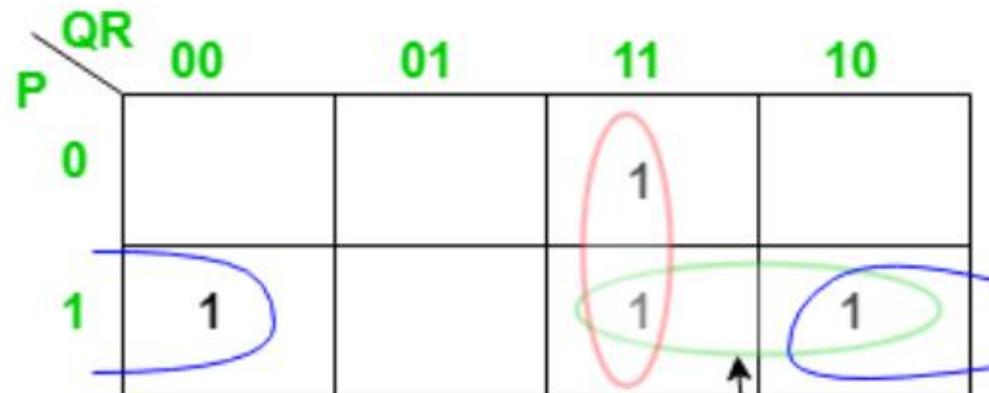1. Identify hazard Free circuit for

$$F(P, Q, R) = QR + P\bar{R} = \sum m\{3, 4, 6, 7\}$$




These 1's are not inside one group
This may cause static-1 hazard

Digital Design Tutorial : 06

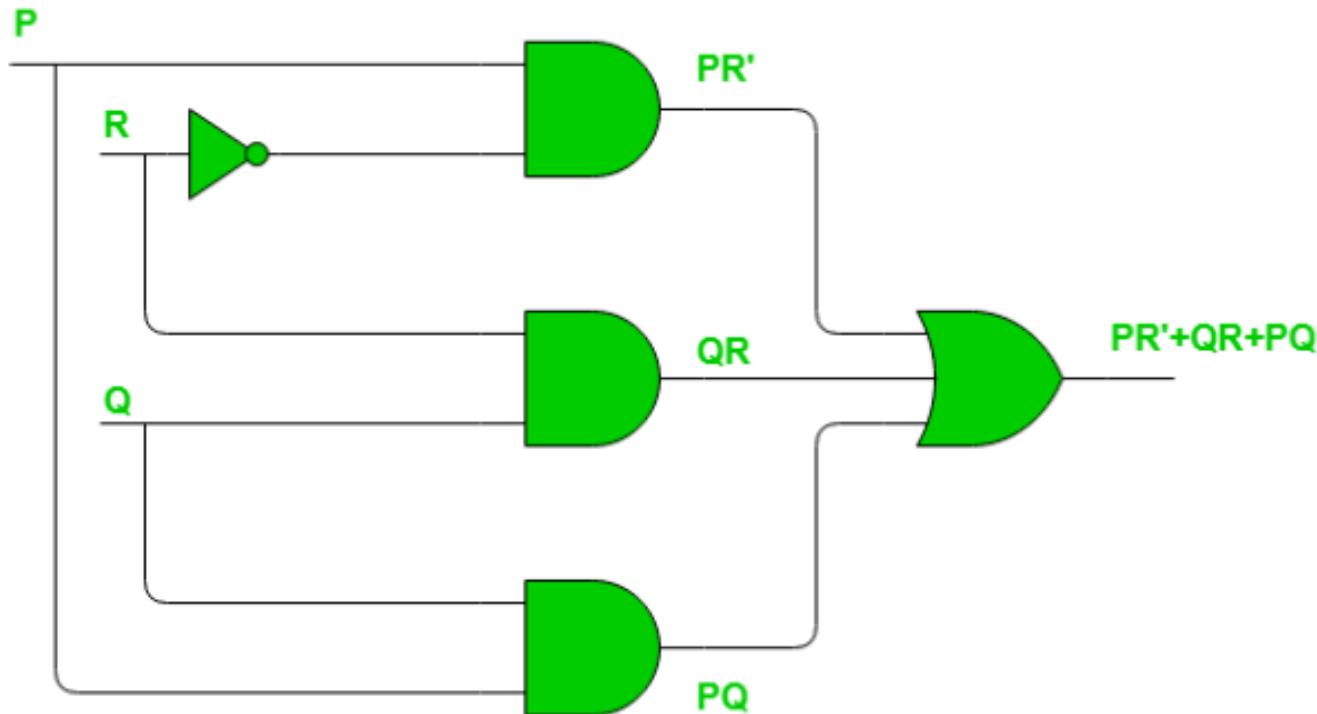1. Identify hazard Free circuit for

$$F(P, Q, R) = QR + P\bar{R} = \sum m\{3, 4, 6, 7\}$$



Digital Design Tutorial : 06

2 .


Problem: Implement the function $f(w_1, w_2, w_3) = \sum m(0, 1, 3, 4, 6, 7)$ by using a 3-to-8 binary decoder and an OR gate.

SanjayVidhyadharan... ↗

Digital Design Tutorial : 06

2 .

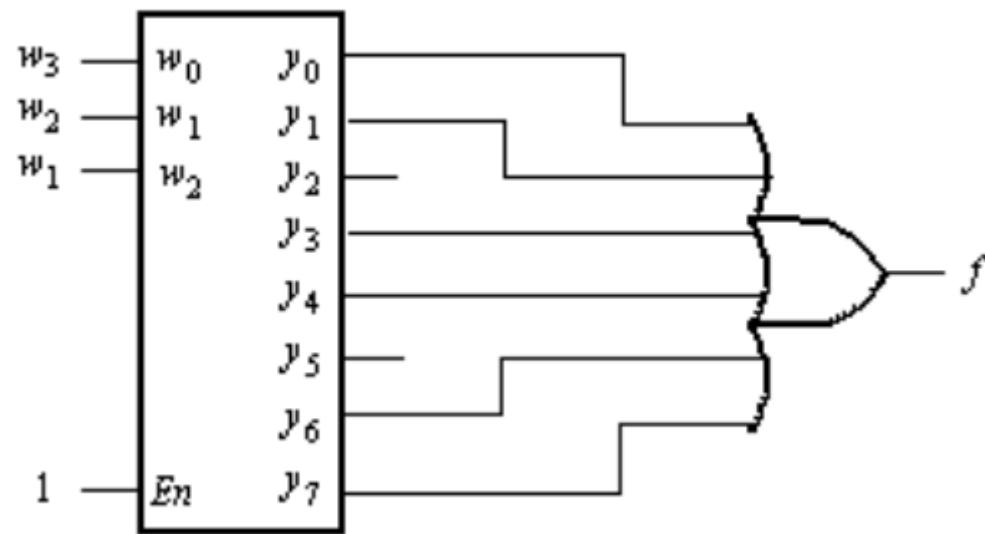Problem: Implement the function $f(w_1, w_2, w_3) = \sum m(0, 1, 3, 4, 6, 7)$ by using a 3-to-8 binary decoder and an OR gate.



Digital Design Tutorial : 06


3. Implement Full Adder Using Decoder

SanjayVidhyadharan.in

Digital Design Tutorial : 06

3. Implement Full Adder Using Decoder

2 to 4 Decoder

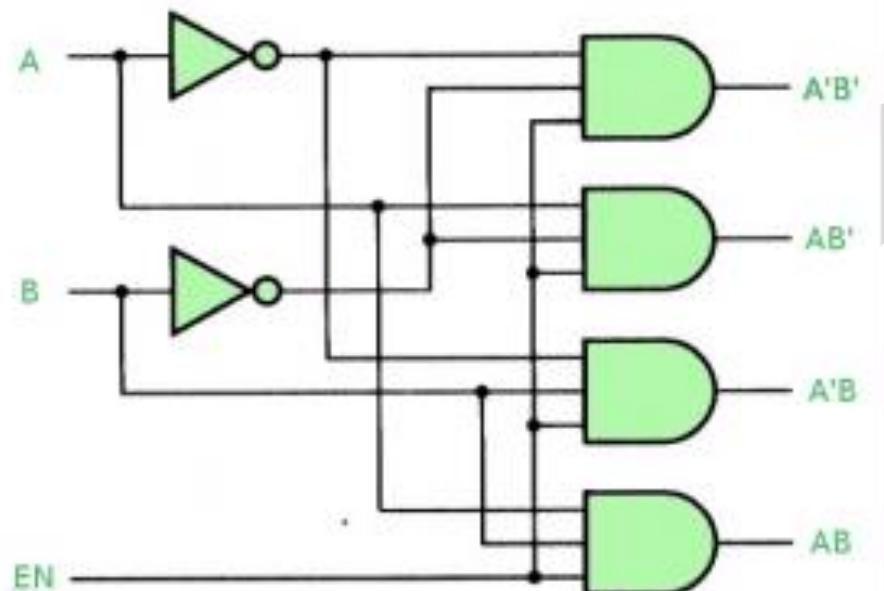


Truth Table-

| E | A | B | D_0 | D_1 | D_2 | D_3 |
|---|---|---|-------|-------|-------|-------|
| 0 | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

Digital Design Tutorial : 06

3. Implement Full Adder Using Decoder

| x | y | z | S | C |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

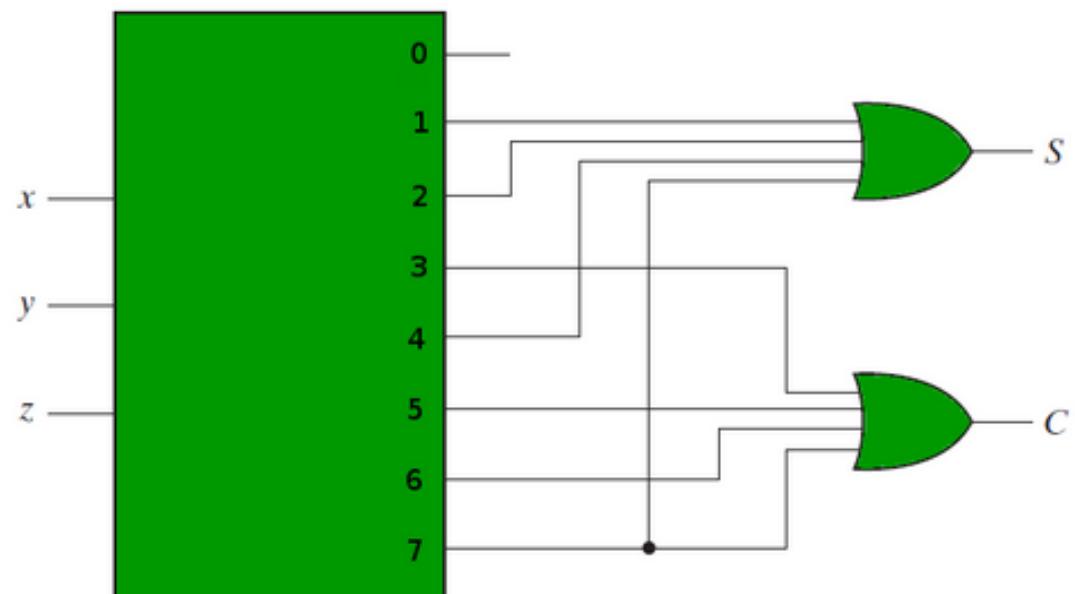

Therefore we have-

$$S = \sum(1, 2, 4, 7)$$

$$C = \sum(3, 5, 6, 7)$$

Digital Design Tutorial : 06


4. Implement $F = X'YZ' + XY'Z + XYZ'$ with an 8:1 MUX

SanjayVidhyadharan.in

Digital Design Tutorial : 06

4. Implement $F = X'YZ' + XY'Z + XYZ'$ with an 8:1 MUX

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |

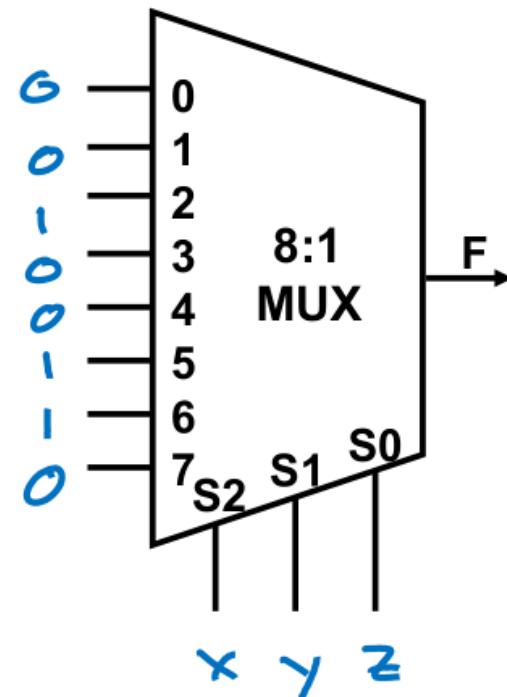

Digital Design Tutorial : 06

5. Implement $F = X'YZ' + XY'Z + XYZ'$ with a 4:1 MUX

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |

