



Digital Design

First Semester 2020-21

Tutorial : 09

Sequence Detector

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

SanjayVidhyadharan.in

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 1

We are designing a sequence detector for a 5-bit sequence, so we need 5 states. We label these states A, B, C, D, and E. State A is the initial state.

Step 2

Characterize Each State by What has been Input and What is Expected State


State	Has	Awaiting
A	--	11011
B	1	1011
C	11	011
D	110	11
E	1101	1

Digital Design Tutorial : 09

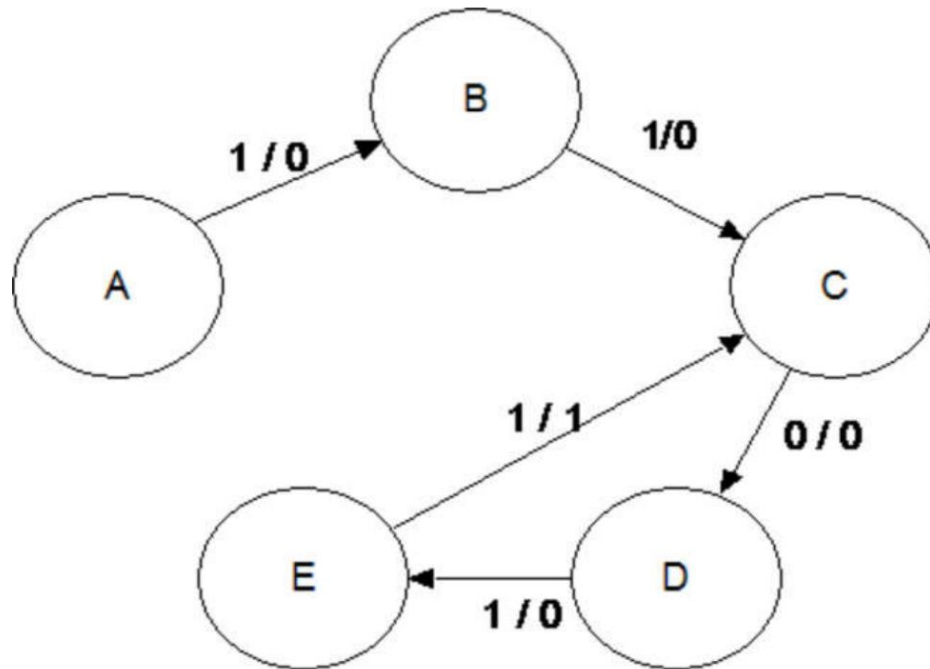1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 3


Do the Transitions for the Expected Sequence



Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 4 Complete the State Diagram

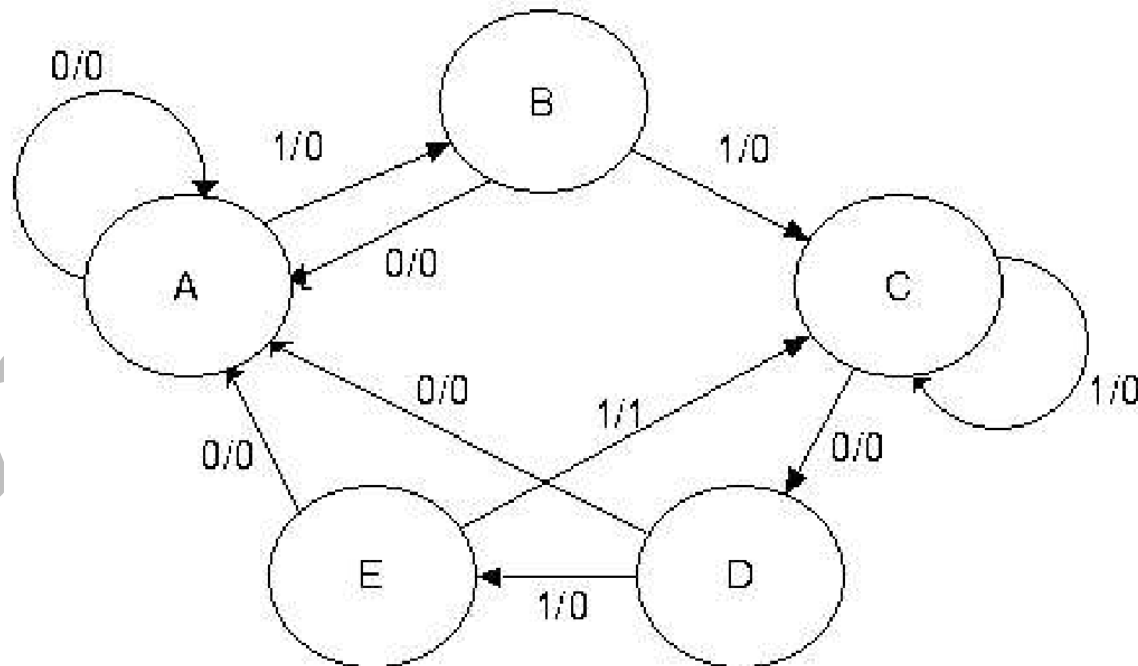

Digital Design Tutorial : 09

1. Design a 11011sequence detector using JK flip-flops. Allow overlap.

Step 5 Make State Table

Present State	Next State / Output	
	X = 0	X = 1
A	A / 0	B / 0
B	A / 0	C / 0
C	D / 0	C / 0
D	A / 0	E / 0
E	A / 0	C / 1

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 6 – Determine the Number of Flip-Flops Required

We have 5 states, so $N = 5$. We solve the equation $2^{P-1} < 5 \leq 2^P$ by inspection, noting that it is solved by $P = 3$. So we need three flip-flops.

Step 7 – Assign a unique P-bit binary number (state vector) to each state.

The simplest way is to make the following assignments

A = 000

B = 001

C = 011 Note that states 010, 110, and 111 are not used.

D = 100

E = 101

Occasionally, a better assignment can be detected by inspection of the next state table. I note that the next states in the table cluster into two disjoint sets for $X = 0$ and $X = 1$. For $X = 0$ the possible next states are A and D For $X = 1$ the possible next states are B, C, and E. For this reason, I elect to give even number assignments to states A and D, and to give odd number assignments to states B, C, and E.

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 8 – Generate the Transition Table With Output

Present State		Next State / Output	
		X = 0	X = 1
	$Y_2Y_1Y_0$	$Y_2Y_1Y_0 / Z$	$Y_2Y_1Y_0 / Z$
A	0 0 0	0 0 0 / 0	0 0 1 / 0
B	0 0 1	0 0 0 / 0	0 1 1 / 0
C	0 1 1	1 0 0 / 0	0 1 1 / 0
D	1 0 0	0 0 0 / 0	1 0 1 / 0
E	1 0 1	0 0 0 / 0	0 1 1 / 1

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 9 – Separate the Transition Table into Three Tables, One for Each Flip-Flop

Y2			Y1			Y0		
PS	Next State		PS	Next State		PS	Next State	
Y ₂ Y ₁ Y ₀	X = 0	X = 1	Y ₂ Y ₁ Y ₀	X = 0	X = 1	Y ₂ Y ₁ Y ₀	X = 0	X = 1
0 0 0	0	0	0 0 0	0	0	0 0 0	0	1
0 0 1	0	0	0 0 1	0	1	0 0 1	0	1
0 1 1	1	0	0 1 1	0	1	0 1 1	0	1
1 0 0	0	1	1 0 0	0	0	1 0 0	0	1
1 0 1	0	0	1 0 1	0	1	1 0 1	0	1
Match	Y ₁	Y ₂ ·Y ₀ '	0	Y ₀	0	1		

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 10 – Separate the Transition Table into Three Tables, One for Each Flip-Flop

Y2			Y1			Y0		
PS	Next State		PS	Next State		PS	Next State	
Y ₂ Y ₁ Y ₀	X = 0	X = 1	Y ₂ Y ₁ Y ₀	X = 0	X = 1	Y ₂ Y ₁ Y ₀	X = 0	X = 1
0 0 0	0	0	0 0 0	0	0	0 0 0	0	1
0 0 1	0	0	0 0 1	0	1	0 0 1	0	1
0 1 1	1	0	0 1 1	0	1	0 1 1	0	1
1 0 0	0	1	1 0 0	0	0	1 0 0	0	1
1 0 1	0	0	1 0 1	0	1	1 0 1	0	1

Match Y₁ Y₂·Y₀' 0 Y₀ 0 1

$$D2 = X' \cdot Y1 + X \cdot Y2 \cdot Y0'$$


$$D1 = X \cdot Y0$$

$$D0 = X$$

Digital Design Tutorial : 09

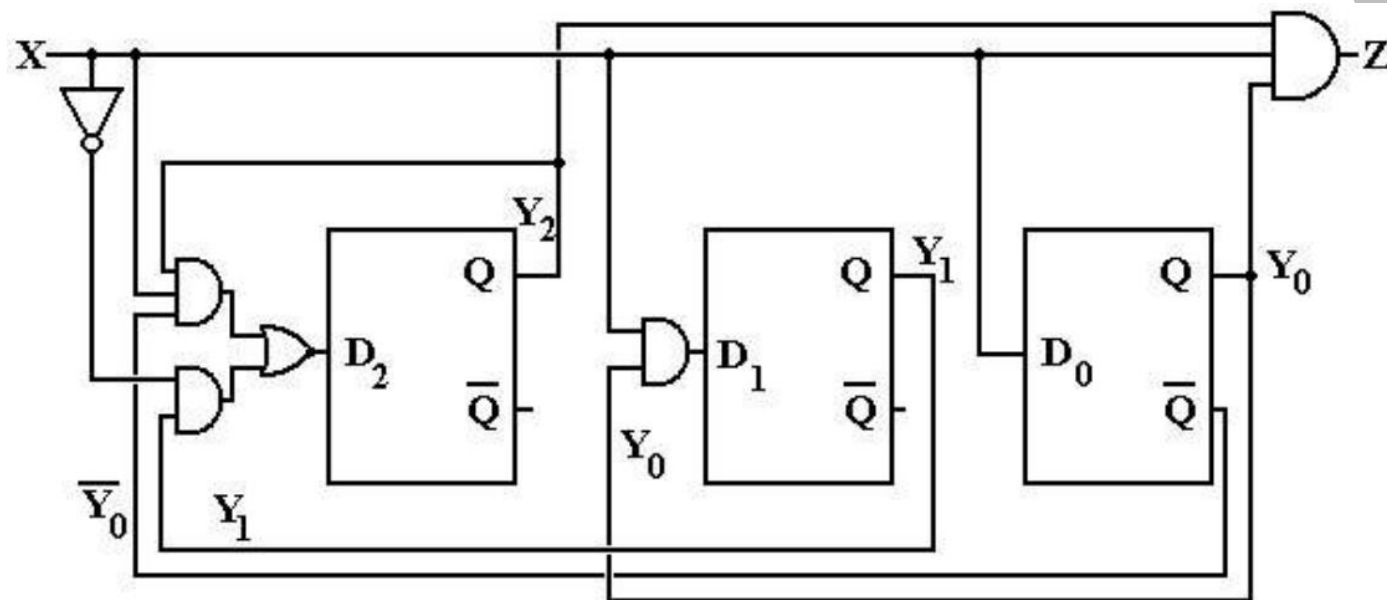1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 11 – design implemented with D flip-flops



$$D_2 = X' \cdot Y_1 + X \cdot Y_2 \cdot Y_0'$$

$$D_1 = X \cdot Y_0$$

$$D_0 = X$$

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 12 – Derive an Input Table for Each JK Flip-Flop using its Excitation Table
And Produce the Input Equations for Each Flip-Flop

$Y_2Y_1Y_0$	$X = 0$			$X = 1$		
	Y_2	J_2	K_2	Y_2	J_2	K_2
0 0 0	0	0	d	0	0	d
0 0 1	0	0	d	0	0	d
0 1 1	1	1	d	0	0	d
1 0 0	0	d	1	1	d	0
1 0 1	0	d	1	0	d	1

$X = 0$

$J_2 = Y_1$

$K_2 = 1$

$X = 1$

$J_2 = 0$

$K_2 = Y_0$

thus, $J_2 = X' \cdot Y_1$

thus, $K_2 = X' + X \cdot Y_0 = X' + Y_0$.

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 13 – Derive an Input Table for Each JK Flip-Flop using its Excitation Table
And Produce the Input Equations for Each Flip-Flop

$Y_2Y_1Y_0$	$X = 0$			$X = 1$		
	Y_1	J_1	K_1	Y_1	J_1	K_1
0 0 0	0	0	d	0	0	d
0 0 1	0	0	d	1	1	d
0 1 1	0	d	1	1	d	0
1 0 0	0	0	d	0	0	d
1 0 1	0	0	d	1	1	d

$$X = 0$$

$$J_1 = 0$$

$$K_1 = 1$$

$$X = 1$$

$$J_1 = Y_0$$

$$K_1 = 0$$

thus $J_1 = X \cdot Y_0$ and $K_1 = X'$.

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 14 – Derive an Input Table for Each JK Flip-Flop using its Excitation Table And Produce the Input Equations for Each Flip-Flop

$Y_2Y_1Y_0$	$X = 0$			$X = 1$		
	Y_0	J_0	K_0	Y_0	J_0	K_0
0 0 0	0	0	d	1	1	d
0 0 1	0	d	1	1	d	0
0 1 1	0	d	1	1	d	0
1 0 0	0	0	d	1	1	d
1 0 1	0	d	1	1	d	0

$$\begin{aligned}X &= 0 \\J_0 &= 0 \\K_0 &= 1\end{aligned}$$


$$\begin{aligned}X &= 1 \\J_0 &= 1 \\K_0 &= 0\end{aligned}$$

thus $J_0 = X$ and $K_0 = X'$, as expected.

Digital Design Tutorial : 09

1. Design a 11011 sequence detector using JK flip-flops. Allow overlap.

Step 15 – Draw Circuit

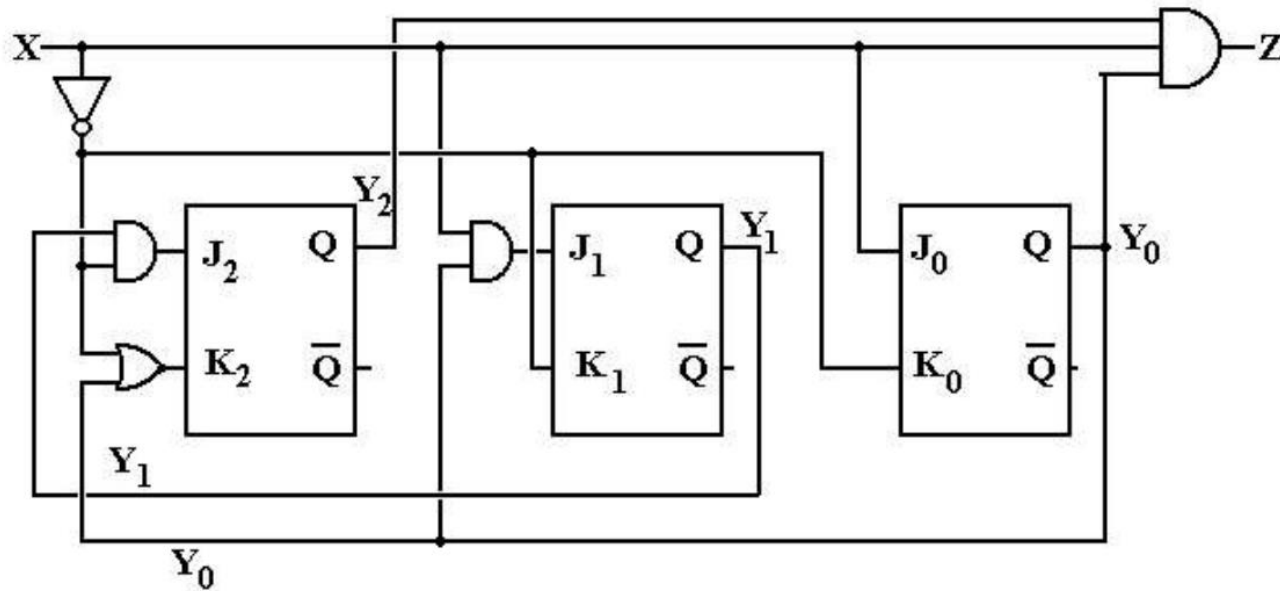

The equations implemented in this design are:

$$Z = X \cdot Y_2 \cdot Y_0$$

$$J_2 = X' \cdot Y_1$$

$$J_1 = X \cdot Y_0$$

$$J_0 = X$$

$$K_2 = X' + Y_0$$

$$K_1 = X'$$

$$K_0 = X'$$