



Digital Design

Lecture 15: Sequential Logic & SR Latch

sanjayvidhyadharan.in

Sequential Circuits

Combinational circuits – The outputs are **entirely dependent on current inputs**

Sequential circuits



– The outputs are dependent on **current inputs as well as present state of storage elements**

Next state = external inputs + present state

Sequential Circuits

Classification

Synchronous Sequential circuits

Asynchronous Sequential circuits


sanjayvidhyadharan.in

Sequential Circuits

Asynchronous sequential circuits

The transition from one state to another is initiated by the change in the primary inputs there is **no external synchronization**

 The memory commonly used are **time-delayed devices**




May be regarded as **combinational circuits with feedback.**

May become **unstable**

Sequential Circuits

Synchronous sequential circuit

 Synchronous sequential circuits **change their states and output values at discrete instants of time**




Synchronization is achieved by a **timing device called clock generator**



Clock generator generates a clock signal having the form of a **periodic train of pulses**

Sequential Circuits

 

Clocked synchronous sequential circuit

Storage elements are **flip-flops**

Output value stored in flip-flop when clock occurs

Prior to the occurrence of the clock **the combinational output must be stable**

Speed of the **combinational logic is critical**


Storage elements

Maintains a binary state indefinitely until directed by an input signal to switch states

Latches

Storage elements that operate with signal levels (rather than signal transitions)

Latch active

 

Level Sensitive

Flip-Flops

Storage elements that are controlled by clock transitions

Edge Sensitive

Storage elements

Maintains a binary state indefinitely until directed by an input signal to switch states

Latches


Storage elements that operate with signal levels (rather than signal transitions)

Level Sensitive


Flip-Flops

Storage elements that are controlled by clock transitions

Edge Sensitive

 


Storage elements

 

Storing 0

Storage elements

 

Storing 0


Is there any way to control the storage value ?

NOR -NAND



Latches

SR Latch

 


Reset = 0, Set = 0

No change in outputs

New state = Old state

Latches

SR Latch

 


Reset = 1, Set = 0 $Q = 0$ and $Q' = 1$

Reset operation

Latches

SR Latch

 


Reset = 0, Set = 1 $Q = 1$ and $Q' = 0$

Set operation

Latches

SR Latch

 

Reset = 1, Set = 1 $Q = 0$ and $Q' = 0$ But

Reset = 0, Set = 0

Cant predict output - > metastable state

Latches

SR Latch

Cant predict output - > metastable state

Set = 1, reset = 1 is thus forbidden state

S	R	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	0	0

No change


Reset

set

Forbidden

Latches

S'R' Latch

 

Latches

S'R' Latch

S	R	Q	Q'
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q	Q'

Forbidden

Set

Reset


No change

sanjayvidnyan.com

sanjayvidnyan.in

Latches

S'R' Latch

 


Reset' = 1, Set' = 1

No change in outputs

New state = Old state

Latches

S'R' Latch

 


Reset' = 1, Set' = 0 $Q = 1$ and $Q' = 0$

set operation

Latches

SR Latch

 


Reset' = 0, Set' = 1 $Q = 0$ and $Q' = 1$

Reset operation

Latches

SR Latch

 

Reset' = 0, Set' = 0 $Q = 1$ and $Q' = 1$ But

Reset' = 1, Set' = 1

Cant predict output - > metastable state

Latches

S'R' Latch

S	R	Q	Q'
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q	Q'

Forbidden

Set

Reset


No change

sanjayvidnyan.com

sanjayvidnyan.in


Latches

SR Latch with enable

 

Latches

SR Latch with enable

 

Thank You

sanjayvidhyadharan.in