



Electrical Science: 2021-22

Lecture 11



Second Order Circuits

By Dr. Sanjay Vidhyadharan

sanjayvidhyadharan.in

Second Order Circuit

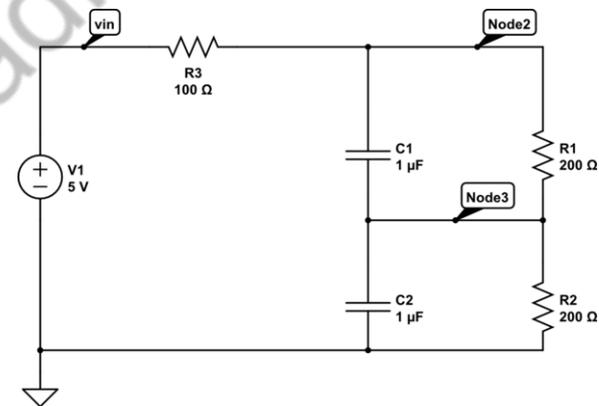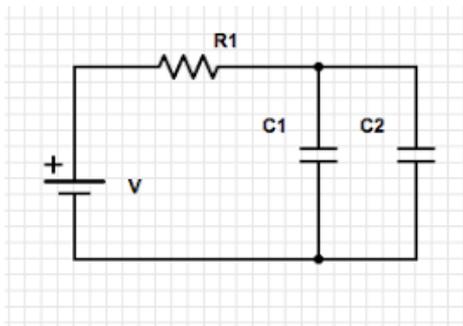- **First Order Circuit:** Any circuit with a **single energy storage element**, an **arbitrary number of sources**, and an **arbitrary number of resistors** is a circuit of **order 1**.




- **Second Order Circuit:**
 - 2nd -order circuit responses are described by 2nd - order differential equations

Second Order Circuit

- **Second Order Circuit:**

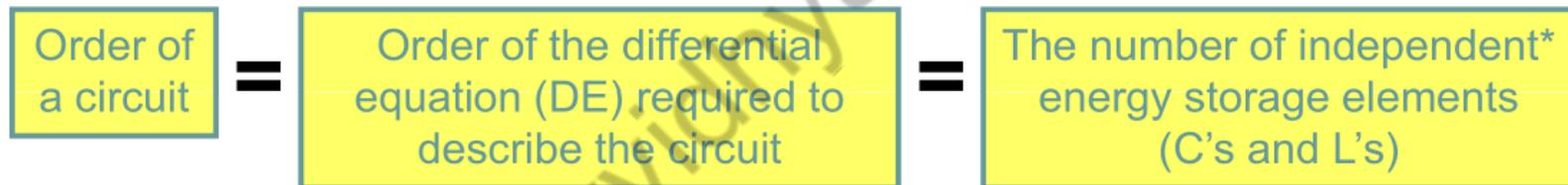- 2nd -order circuit responses are described by 2nd - order differential equations






* C's and L's are independent if they cannot be combined with other C's and L's (in series or parallel, for example)


Second Order Circuits

- Second Order Circuit:**

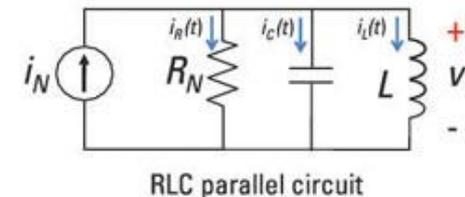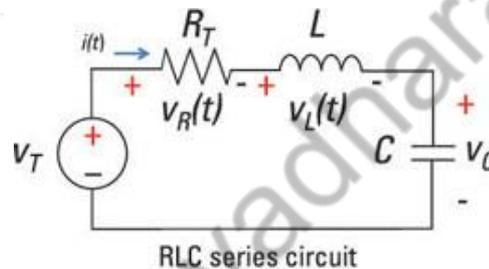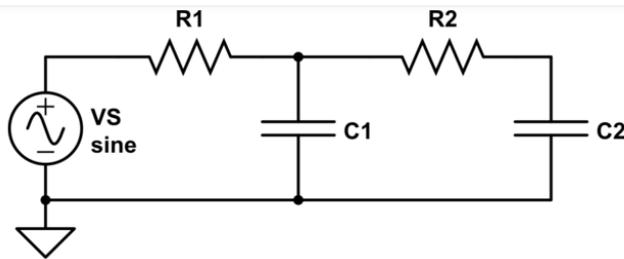- 2nd -order circuit responses are described by 2nd -order differential equations


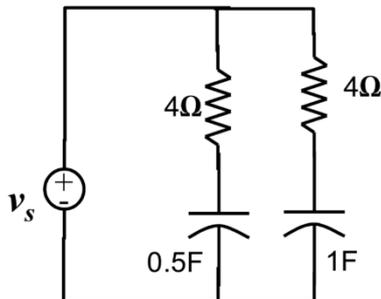
$$\frac{dV_{C1}}{dt} = \frac{dV_{C2}}{dt} + R_2 C_2 \frac{d^2 V_{C2}}{dt^2}$$




$$Z_1 = R_1 + \frac{1}{sC_1} = \frac{sC_1 R_1 + 1}{sC_1}$$

$$Z_2 = R_2 + \frac{1}{sC_2} = \frac{sC_2 R_2 + 1}{sC_2}$$

$$Z_1 || Z_2 = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{C_1 C_2 R_1 R_2 s^2 + (C_1 R_1 + C_2 R_2) s + 1}{C_1 C_2 (R_1 + R_2) s^2 + (C_1 + C_2) s}$$


Applications of Second Order Circuits

Application of RC/RL/RLC

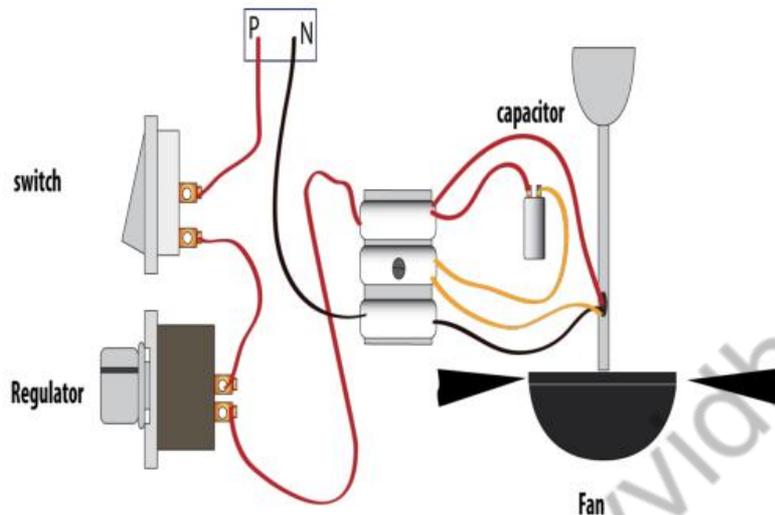


Electric Fan Circuit

Electric Fan

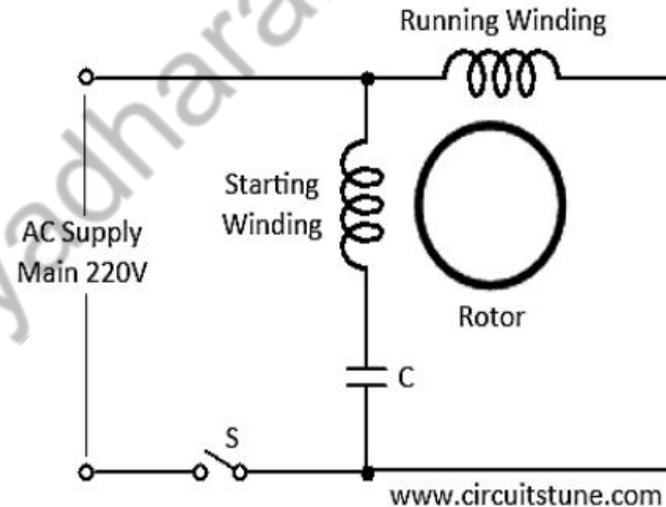


Ceiling fan wiring diagram

Applications of Second Order Circuits

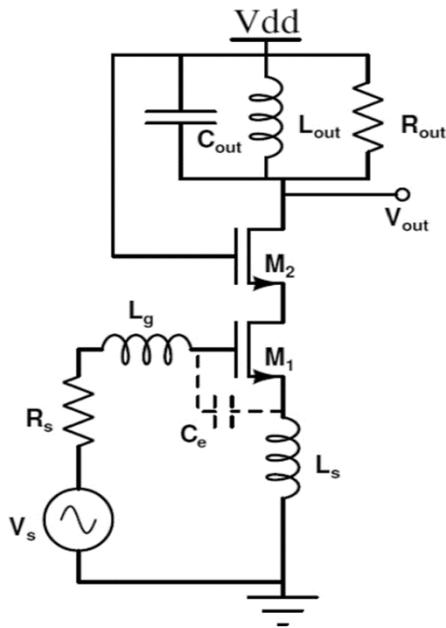

Tuned Circuits

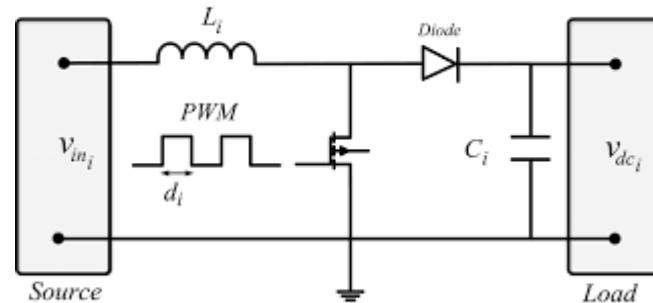

DC Boost Converters

Response of a Series RLC Circuit

$$v_c + Ri + L \frac{di}{dt} = 0$$


Inserting $i = C \frac{dv}{dt}$;

$$v_c + RC \frac{dv}{dt} + LC \frac{d^2v}{dt^2} = 0$$

$$\gg \frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$\gg \frac{d^2y(t)}{dt^2} + 2\alpha \frac{dy(t)}{dt} + \omega_n^2 y(t) = 0$$
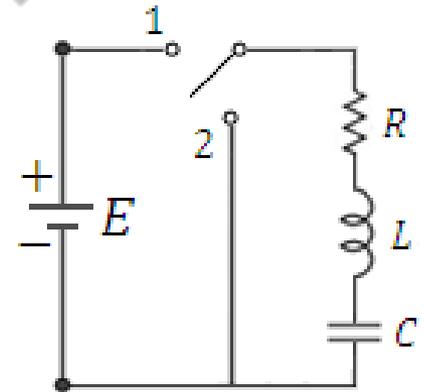
$$\alpha = \frac{R}{2L}; \quad \omega_n = \frac{1}{\sqrt{LC}};$$



Response of a Series RLC Circuit

$$\gg \frac{d^2y(t)}{dt^2} + 2\alpha \frac{dy(t)}{dt} + \omega_n^2 y(t) = 0$$

$$s^2 + 2\alpha s + \omega_n^2 = 0$$

By Quadratic formula

$$s = \frac{-2\alpha \pm \sqrt{4\alpha^2 - 4\omega_n^2}}{2} = -\alpha \pm \sqrt{\alpha^2 - \omega_n^2}$$


The two values of s

$$s_1 = -\alpha - \sqrt{\alpha^2 - \omega_n^2}$$

$$s_2 = -\alpha + \sqrt{\alpha^2 - \omega_n^2}$$

$$y(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

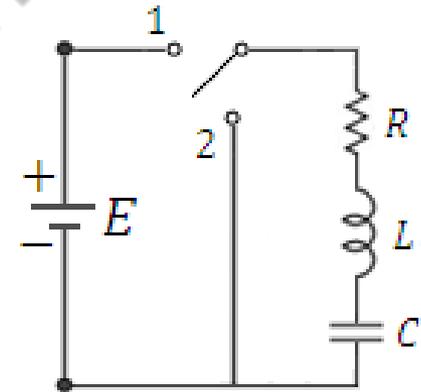(A_1 and A_2 are arbitrary constants and are determined from the initial conditions)



$$\alpha = \frac{R}{2L}; \quad \omega_n = \frac{1}{\sqrt{LC}};$$

Response of a Series RLC Circuit

$$y(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

(A_1 and A_2 are arbitrary constants and are determined from the initial conditions)

Three types of solutions are inferred:

1. If $\alpha > \omega_n$, we have the over-damped case.
2. If $\alpha = \omega_n$, we have the critically-damped case.
3. If $\alpha < \omega_n$, we have the under-damped case.

- **Overdamped Case ($\alpha > \omega_0$)**

$$\alpha > \omega_0 \text{ implies } R^2 > 4L/C$$

$$\alpha = \frac{R}{2L}; \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha = \frac{R}{2L}; \quad \omega_n = \frac{1}{\sqrt{LC}};$$



When this happens, both roots s_1 and s_2 are negative and real.

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

The response is given as,

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

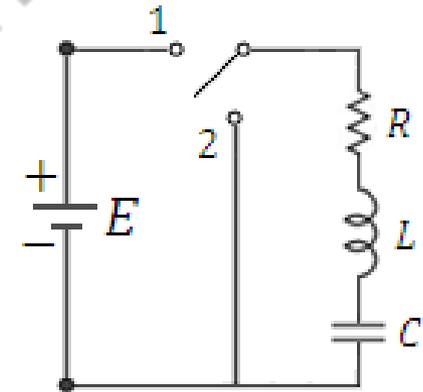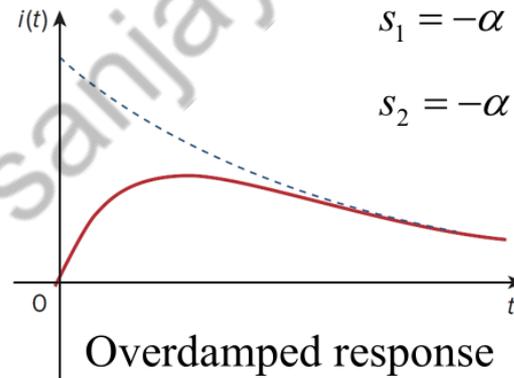

Response of a Series RLC Circuit

$$y(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

(A_1 and A_2 are arbitrary constants and are determined from the initial conditions)

Three types of solutions are inferred:



1. If $\alpha > \omega_n$, we have the over-damped case.
2. If $\alpha = \omega_n$, we have the critically-damped case.
3. If $\alpha < \omega_n$, we have the under-damped case.

- **Critically Damped Case ($\alpha = \omega_0$)**

$\alpha = \omega_0$ implies $R^2 = 4L/C$

Thus $s_1 = s_2 = -\alpha = -\frac{R}{2L}$

$i = (A_1 t + A_2) e^{-\alpha t}$

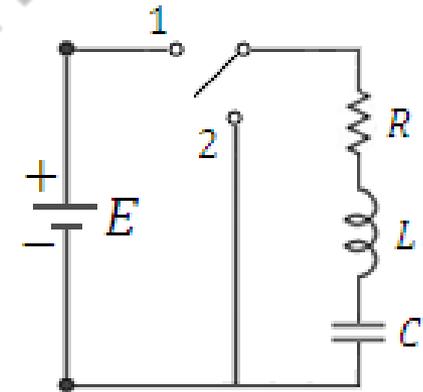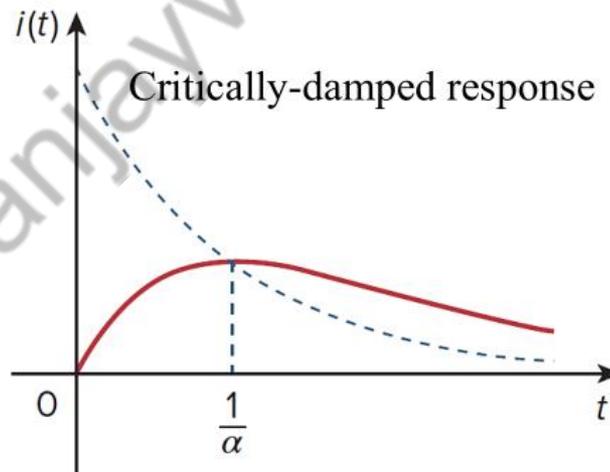

$$\alpha = \frac{R}{2L}; \quad \omega_n = \frac{1}{\sqrt{LC}}$$

Response of a Series RLC Circuit

Three types of solutions are inferred:

1. If $\alpha > \omega_0$, we have the over-damped case.
2. If $\alpha = \omega_0$, we have the critically-damped case.
3. If $\alpha < \omega_0$, we have the under-damped case.

- **Underdamped Case ($\alpha < \omega_0$)**

$\alpha < \omega_0$ implies $R^2 < 4L/C$. The roots may be written

$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\omega_d$$

$$s_2 = -\alpha - \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha - j\omega_d$$

where, $j = \sqrt{-1}$; $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$


$$i(t) = A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t}$$

$$= e^{-\alpha t} (A_1 e^{-j\omega_d t} + A_2 e^{j\omega_d t})$$


$$i(t) = e^{-\alpha t} [A_1 (\cos \omega_d t + j \sin \omega_d t) + A_2 (\cos \omega_d t - j \sin \omega_d t)]$$

$$= e^{-\alpha t} [(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t]$$

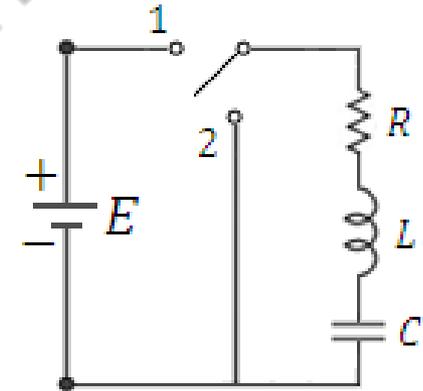
$$i(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$


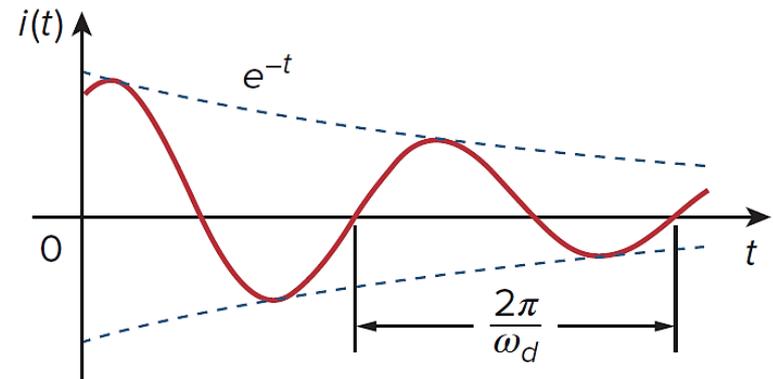
$$\alpha = \frac{R}{2L}; \quad \omega_n = \frac{1}{\sqrt{LC}}$$




Response of a Series RLC Circuit

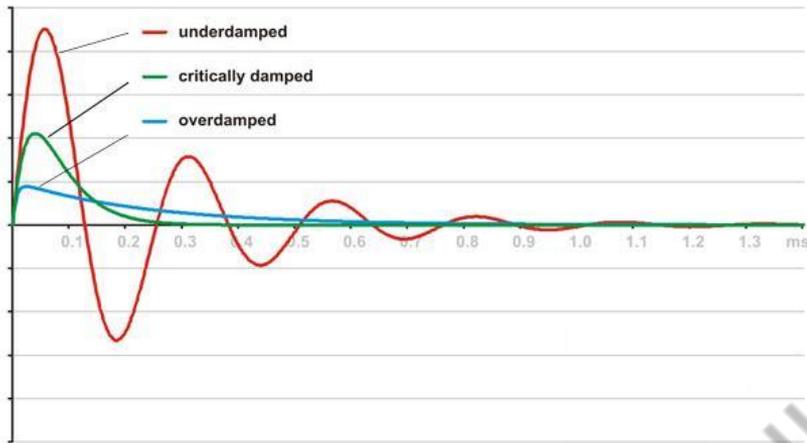

$$\alpha = \frac{R}{2L}; \quad \omega_n = \frac{1}{\sqrt{LC}};$$

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$
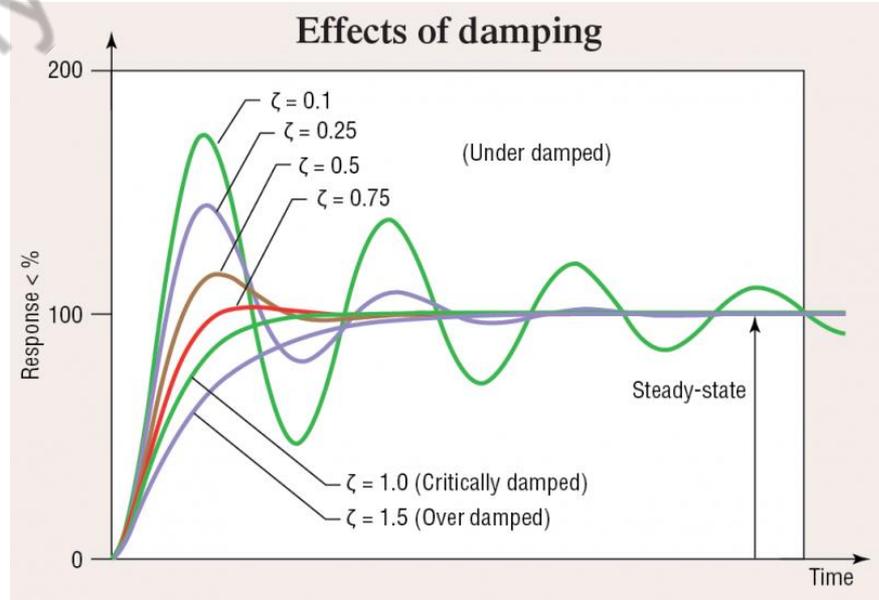
$$\text{Damping Ratio} = \frac{\text{Damping factor } (\alpha)}{\text{Natural Frequency } (\omega_n)}$$




Response of a Series RLC Circuit

Special case if $R=0$

Kirchhoff: $V_C + V_L = 0$
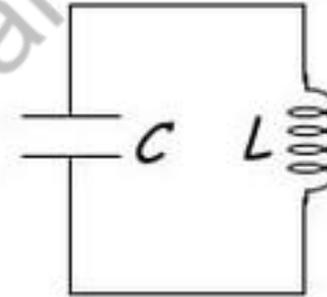
$$\frac{Q}{C} + L \frac{dI}{dt} = 0$$
$$\frac{Q}{C} + L \frac{d^2Q}{dt^2} = 0$$
$$\frac{d^2Q}{dt^2} + \frac{1}{LC} Q = 0$$



This is the SHM equation!!

$$\frac{d^2Q}{dt^2} + \omega^2 Q = 0 \quad \text{with} \quad \omega = \frac{1}{\sqrt{LC}}$$

Solution:

$$Q = Q_0 \cos(\omega t + \varphi)$$

Response of a Series RLC Circuit

Special case if $R=0$

$$Q = Q_0 \cos(\omega t + \varphi)$$

$$I = -Q_0 \omega \sin(\omega t + \varphi)$$

$$V_c = \frac{Q}{C} = \frac{Q_0}{C} \cos(\omega t + \varphi)$$


$$V_L = L \frac{dI}{dt} = -LQ_0 \omega^2 \cos(\omega t + \varphi)$$

$$U_c = \frac{Q^2}{2C} = \frac{Q_0^2}{2C} \cos^2(\omega t + \varphi)$$

$$U_L = \frac{1}{2} L I^2 = \frac{1}{2} L Q_0^2 \omega^2 \sin^2(\omega t + \varphi)$$

$$= \frac{Q_0^2}{2C} \sin^2(\omega t + \varphi)$$
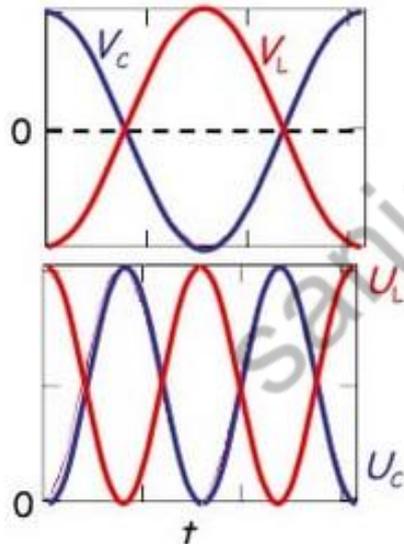
$$\frac{LQ_0^2 \omega^2}{2} = \frac{LQ_0^2}{2} \frac{1}{LC} = \frac{Q_0^2}{2C}$$



Energy is continuously transformed:
electric \leftrightarrow magnetic

Compare to mass and spring (SHM):
kinetic \leftrightarrow potential

Response of a Parallel RLC Circuit

Assume initial inductor current I_0 and initial capacitor voltage V_0 ,

Three elements are in parallel, they have the same voltage v across them.

Applying KCL at the top node gives,


$$\frac{v}{R} + \frac{1}{L} \int_{-\infty}^0 v(\tau) d\tau + C \frac{dv}{dt} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$s_{1,2} = \frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$
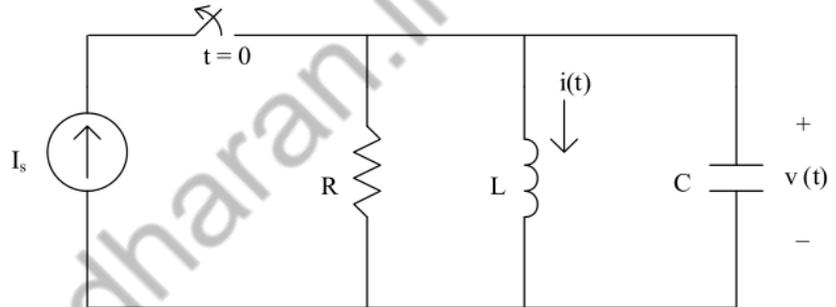
$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}, \quad \alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$



Response of a Parallel RLC Circuit

Assume initial inductor current I_0 and initial capacitor voltage V_0 ,

Three elements are in parallel, they have the same voltage v across them.

Applying KCL at the top node gives,


$$\frac{v}{R} + \frac{1}{L} \int_{-\infty}^0 v(\tau) d\tau + C \frac{dv}{dt} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$s_{1,2} = \frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

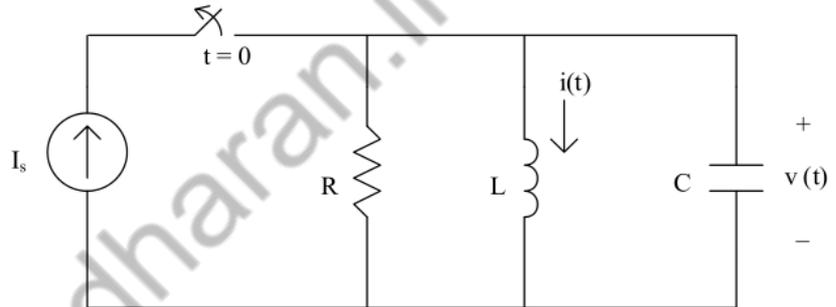
$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}, \quad \alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$



Response of a Parallel RLC Circuit

$$s_{1,2} = \frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$
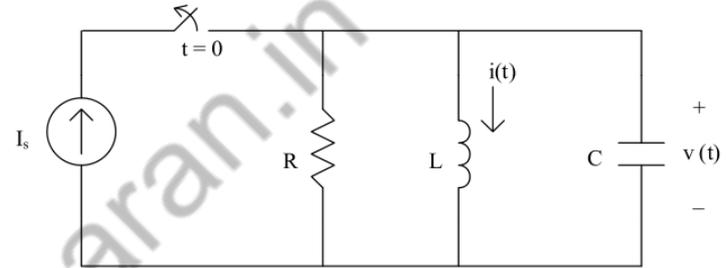
$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}, \quad \alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$



Overdamped Case ($\alpha > \omega_0$)

$\alpha > \omega_0 \Rightarrow L/C > 4R^2$. The roots of the characteristic equation are real and negative. The response is,


$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$



Critically Damped Case ($\alpha = \omega_0$)

$\alpha = \omega_0 \Rightarrow L/C = 4R^2$. The roots are real and equal so that the response is,


$$v(t) = (A_1 + A_2 t) e^{-\alpha t}$$

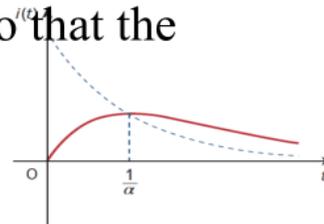

Underdamped Case ($\alpha < \omega_0$)

$\alpha < \omega_0 \Rightarrow L/C < 4R^2$. In this case the roots are complex conjugates expressed as $s_{1,2} = -\alpha \pm j\omega_d$; $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$
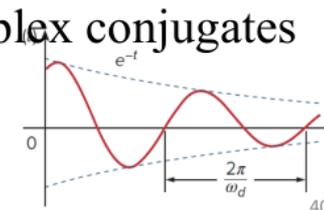
$$v(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$



Thank you

sanjayvidhyadharan.in