



# **Electrical Science: 2021-22**

## **Lecture 1**

### **Power Sources**


**By Dr. Sanjay Vidhyadharan**

sanjayvidhyadharan.in

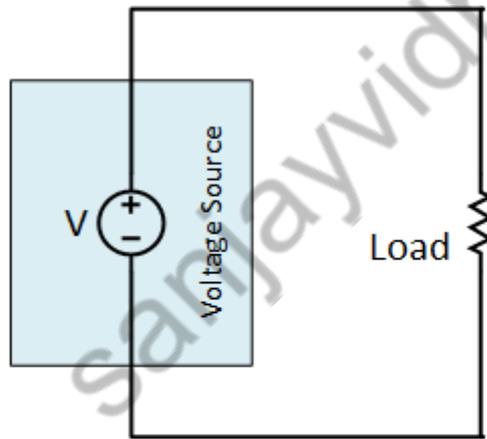
# Ideal vs. Practical Voltage Sources

An imaginary voltage source, which can provide a constant voltage to load ranging from zero to infinity. Such voltage source is having zero internal resistance, and is called an **Ideal Voltage Source**. Practically it is not possible to build a voltage source with no internal resistance and constant voltage for that long-range of the load.

Practical voltage sources always have some resistance value in series with an ideal voltage source. And because of that series resistance, voltage drops when current passes through it. So, **Practical Voltage Source has internal resistance and slightly variable voltage**.




Ideal Voltage  
Source

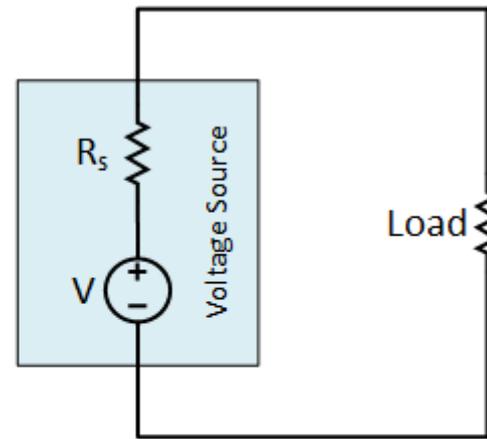

Practical Voltage  
Source


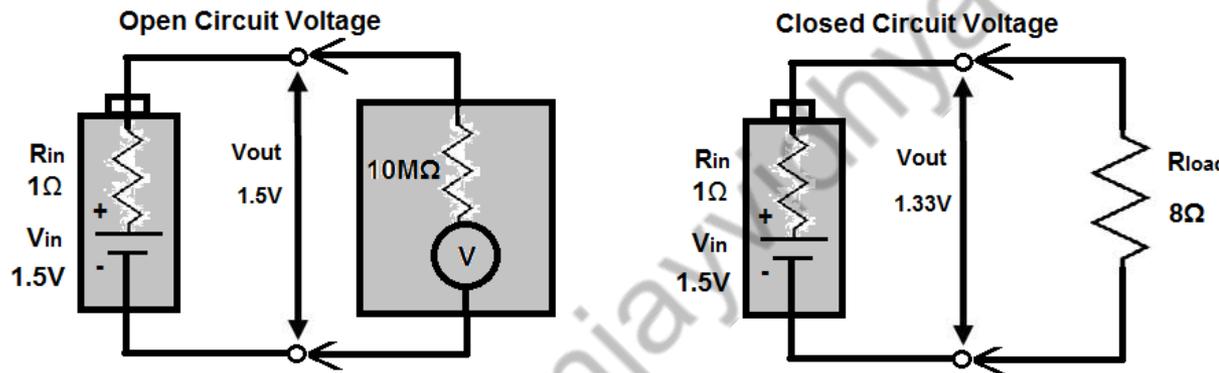
# Battery Internal Resistance

Batteries have internal resistance because the elements that make it up aren't perfect conductors. The electrodes and electrolytes aren't 100% conductive. So, they will have some resistance (internal resistance) in them.




Battery	Internal Resistance
9-V zinc carbon	35Ω
9-V lithium	16Ω to 18Ω
9-V alkaline	1Ω to 2Ω
AA alkaline	0.15Ω
AA NiMH	0.02Ω
D Alkaline	0.1Ω
D NiCad	0.009Ω
D SLA	0.006Ω
AC13 zinc-air	5Ω
76 silver	10Ω
675 mercury	10Ω
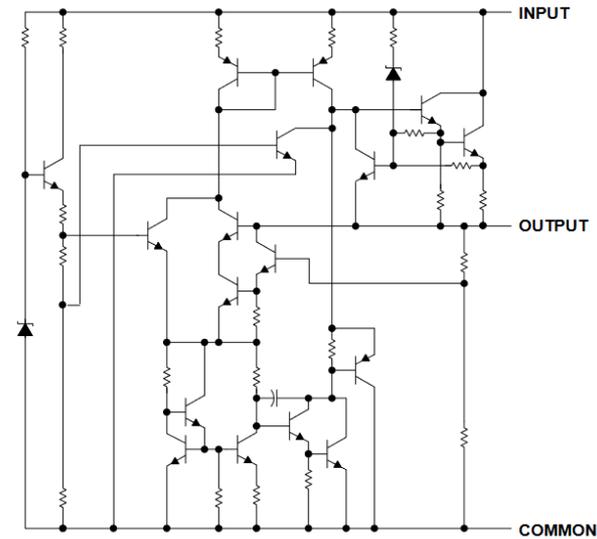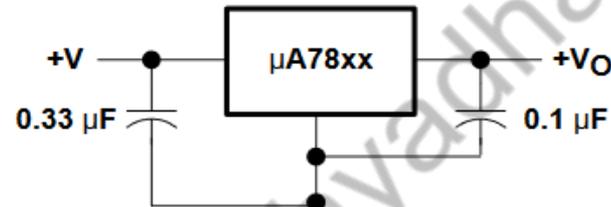
# Internal Resistance of Regulated Voltage Sources







		MIN	MAX	UNIT	
$V_I$	Input voltage	$\mu A7805C$	7	25	V
		$\mu A7808C$	10.5	25	
		$\mu A7810C$	12.5	28	
		$\mu A7812C$	14.5	30	
		$\mu A7815C$	17.5	30	
		$\mu A7824C$	27	38	
$I_O$	Output current		1.5	A	
$T_J$	Operating virtual junction temperature	$\mu A7800C$ series	0	125	$^{\circ}C$
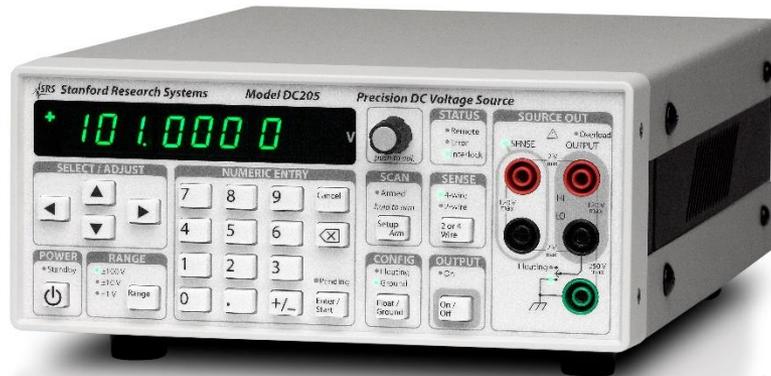
# Internal Resistance of Regulated Voltage Sources




The DC205 low-noise, high-resolution DC voltage source is the right tool when a precision bias source is needed. Its bipolar, four-quadrant output delivers up to 100 V with 1  $\mu$ V resolution and up to 50 mA of current.

# Ideal vs. Practical Current Sources

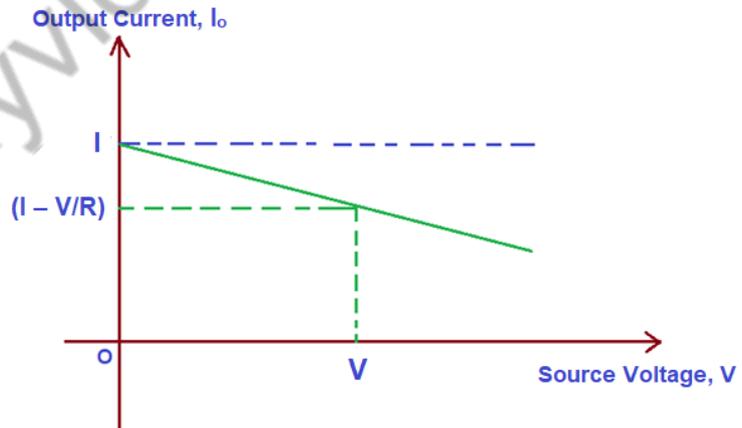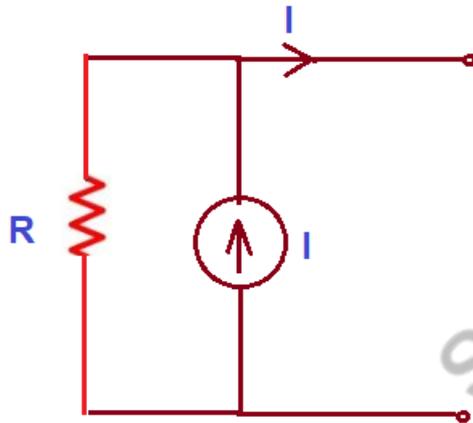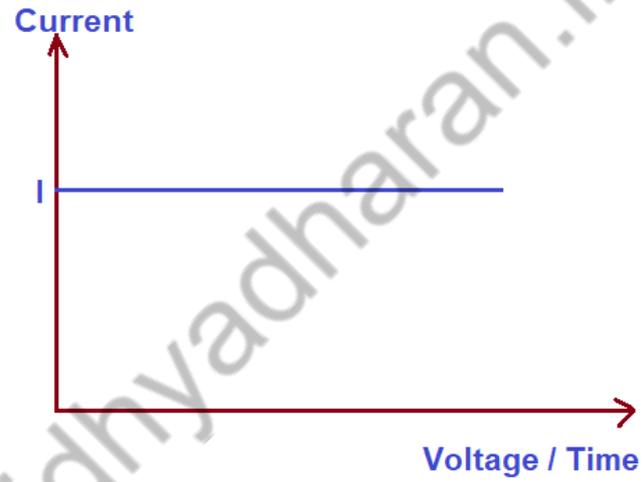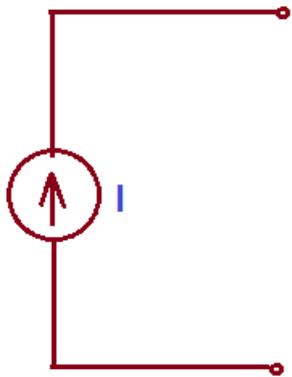

# Classification of Power Sources

## Classification

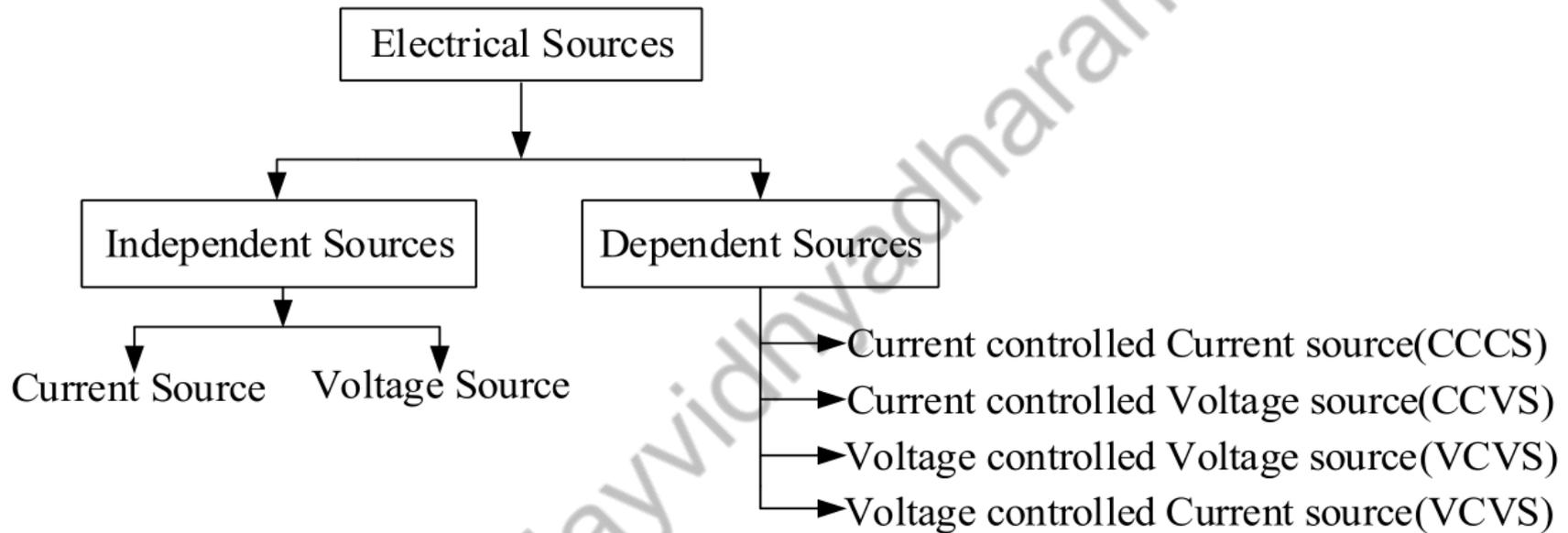


Sources in which the voltage is completely independent of the current, or the current is completely independent of the voltage; these are termed independent sources.

Special kinds of sources for which either the source voltage or current, depends upon a current or voltage elsewhere in the circuit; such sources are referred to as dependent sources.

# Classification of Power Sources

## Independent Voltage Sources

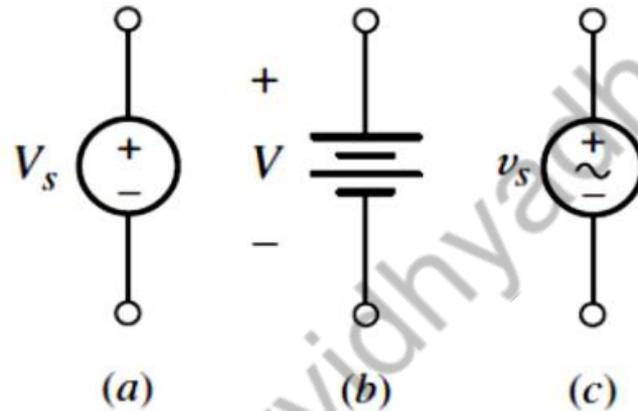


(a) DC voltage source; (b) battery symbol; (c) AC voltage source symbol

**The terminal voltage is completely independent of the current through it.**

# Classification of Power Sources


## Independent Voltage Sources

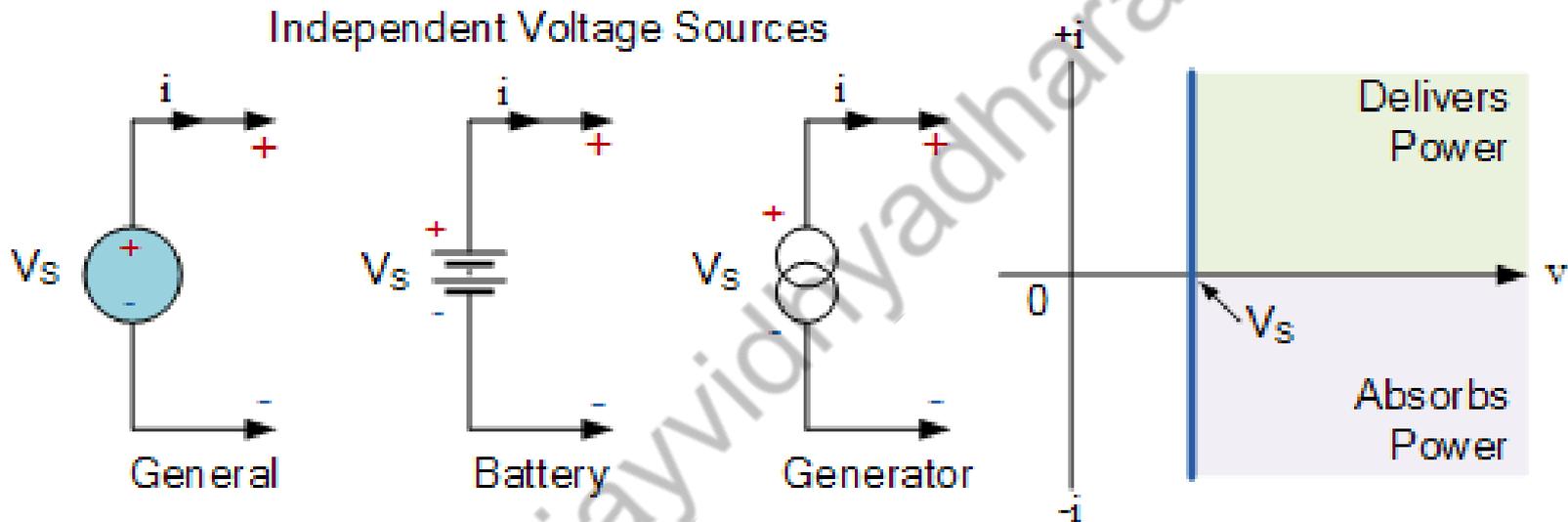

The terminal voltage is completely independent of the current through it.

# Classification of Power Sources






## Independent Current Sources

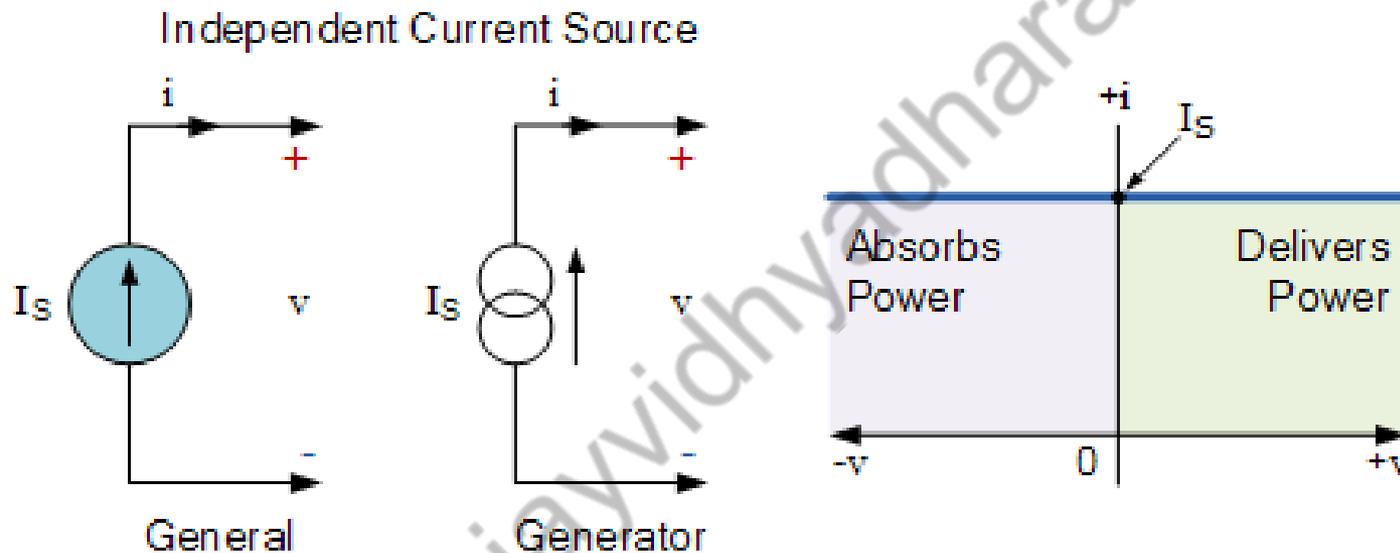

The terminal current is completely independent of the voltage across it.


# Classification of Power Sources

## Dependent Power Sources

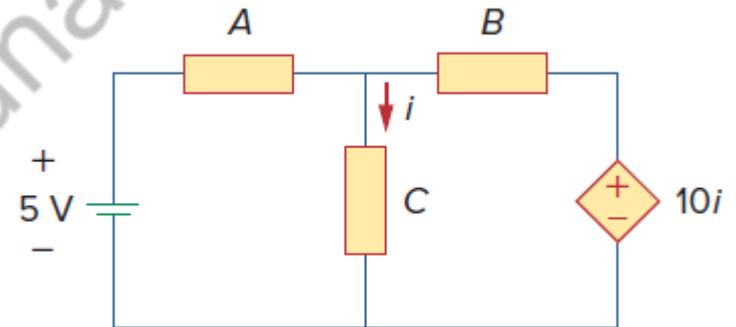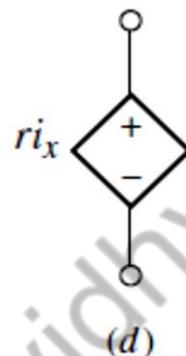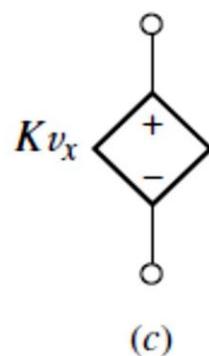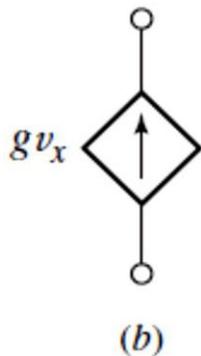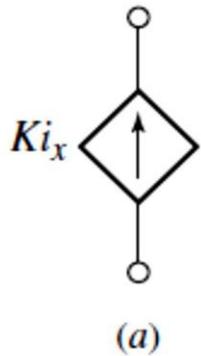

Current-controlled voltage source

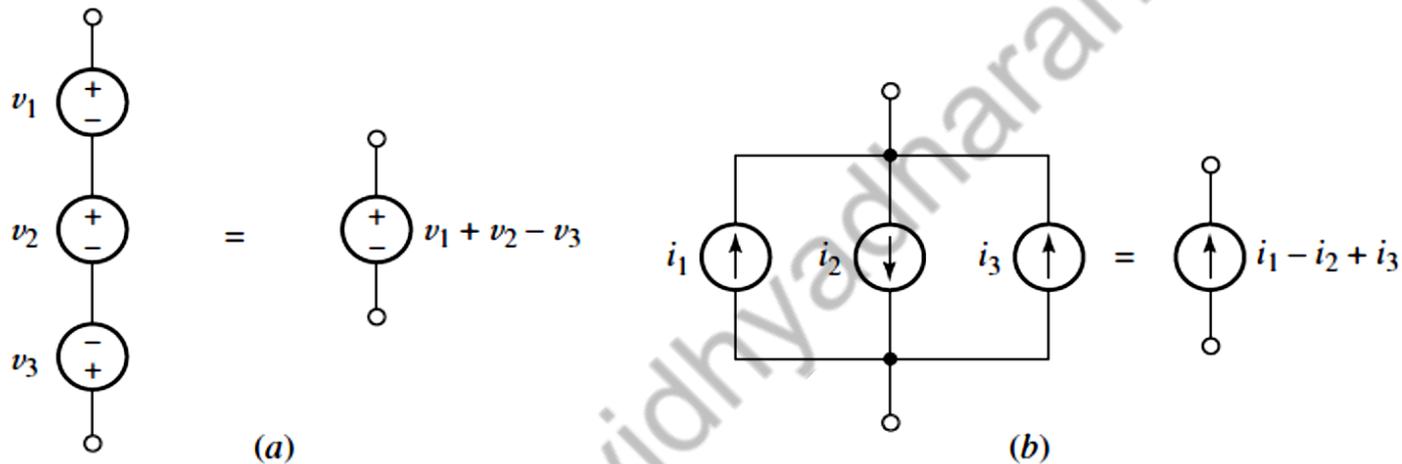
# SERIES AND PARALLEL CONNECTION OF SOURCES



- (a) Series-connected voltage sources can be replaced by a single source.  
(b) Parallel current sources can be replaced by a single source.

# SERIES AND PARALLEL CONNECTION OF SOURCES


## Voltage Sources in Parallel

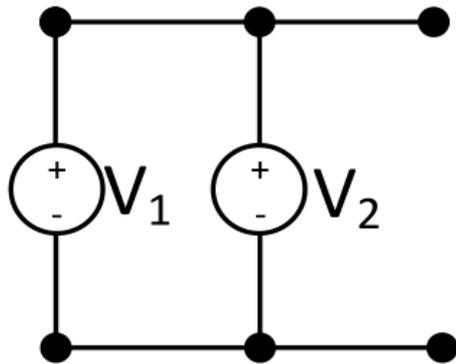


$$V_1 = V_2$$



$$V_1 \neq V_2$$


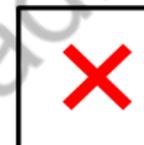


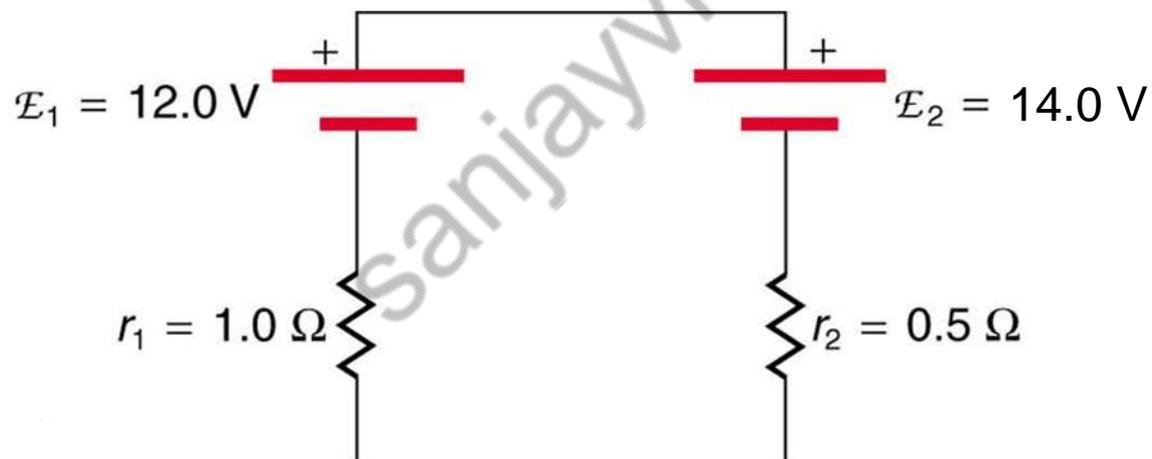Why to connect Voltage Sources in Parallel ?




# SERIES AND PARALLEL CONNECTION OF SOURCES

## Current Sources in Series

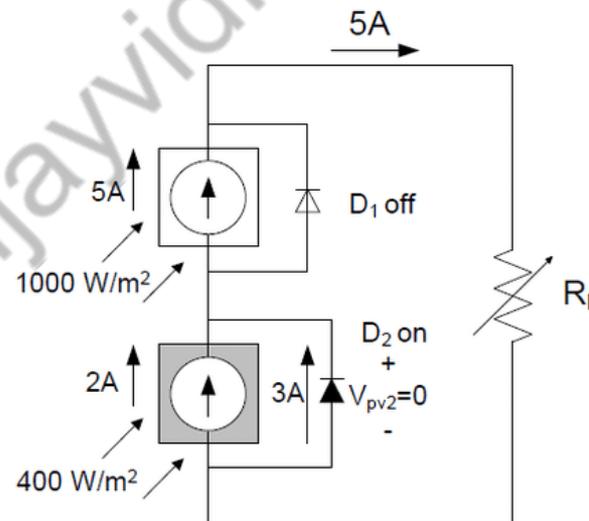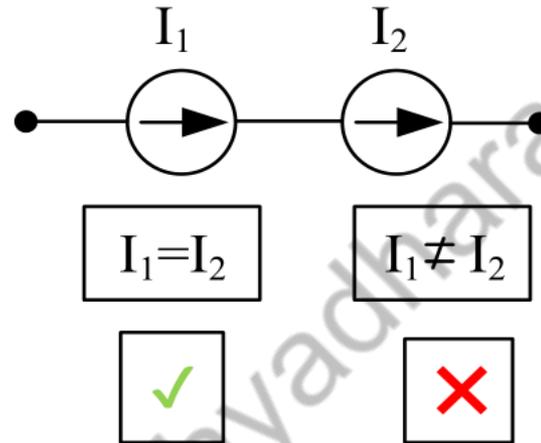

# SOURCE TRANSFORMATION

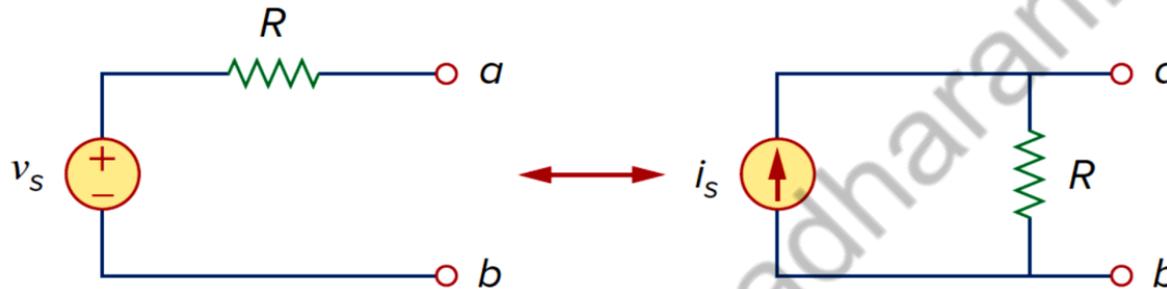

Transformation of independent sources. **Provided**,  $v_s = i_s \times R$  or  $i_s = \frac{v_s}{R}$

A source transformation is the process of replacing a voltage source  $V_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with a resistor  $R$ , or vice versa.

Thevenin and Norton equivalents

**Thank you**

sanjayvidhyadharan.in