



Electrical Science: 2021-22

Lecture 8


Capacitors

By Dr. Sanjay Vidhyadharan

sanjayvidhyadharan.in

Capacitors

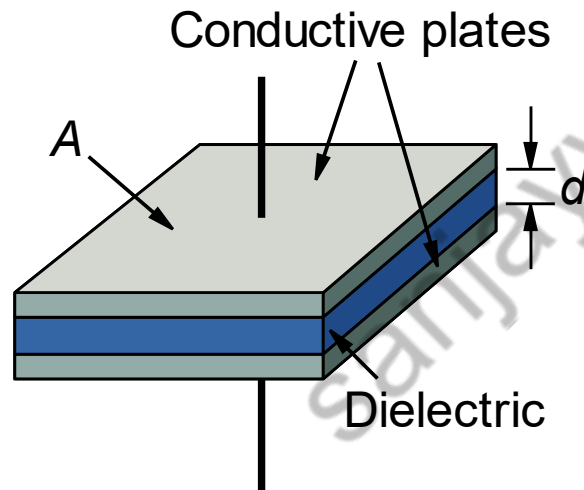- A capacitor is a device which can store electrical charge.
- Capacitor consists of a pair of conducting plates separated by an insulator. The insulator is called a dielectric and is often air, paper or oil.





$$C = \frac{Q}{V}$$

C = capacitance (unit farad (F))


Q = the magnitude of the charge on one plate (unit coulombs (C))

V = the p.d. between the plates (unit volts (V))

Types of Capacitors

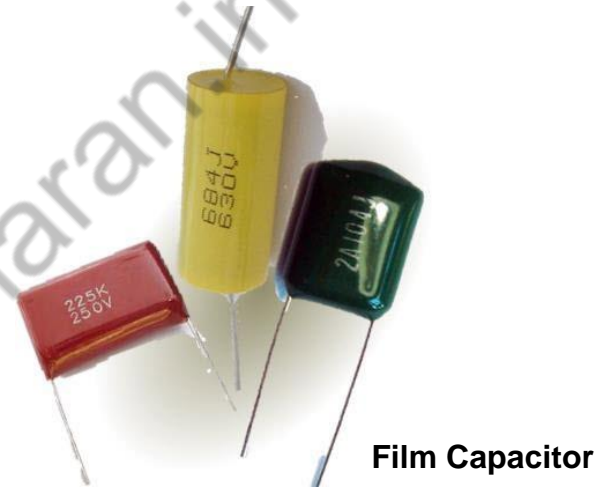
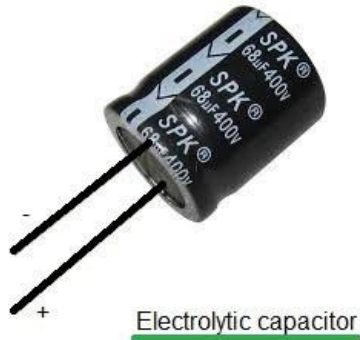


Ceramic capacitors

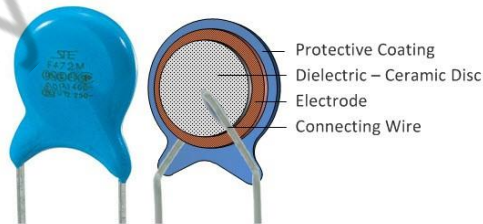


The multilayer ceramic capacitors are prepared by using the surface mounted (SMD) technology and they are smaller in size, therefore, it is used widely. The values of the ceramic capacitors are typically between the 1nF and 1 μ F and the values are up to 100 μ F are possible.

Charge Stored in a Capacitor

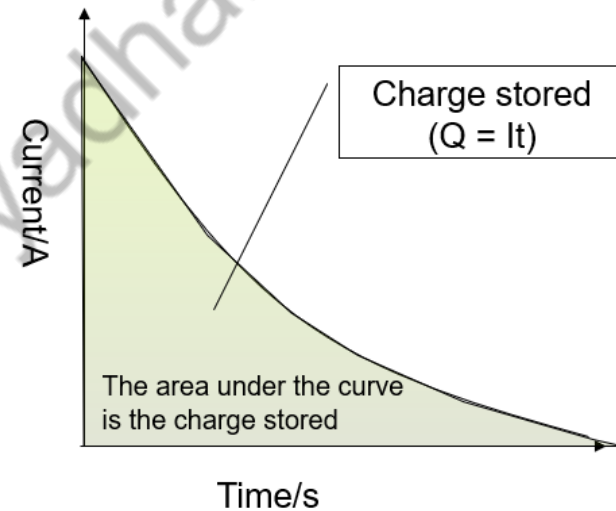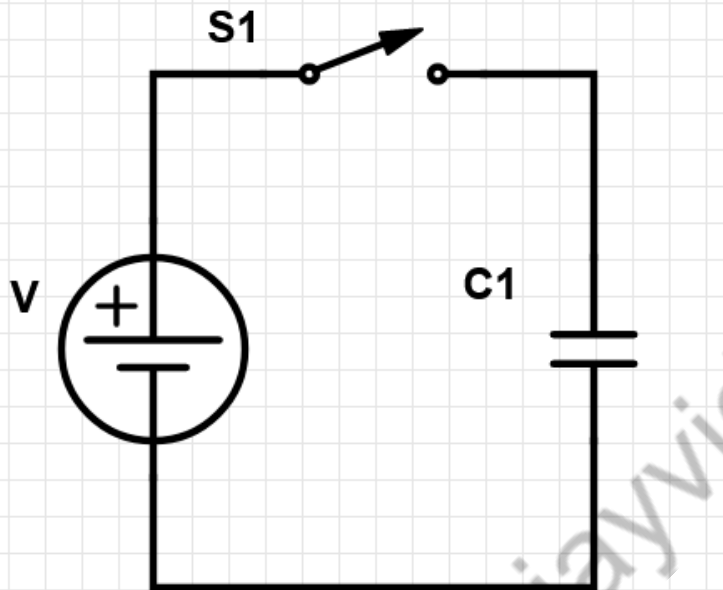

sanjayvidhyacharan.in

Charging a Capacitor

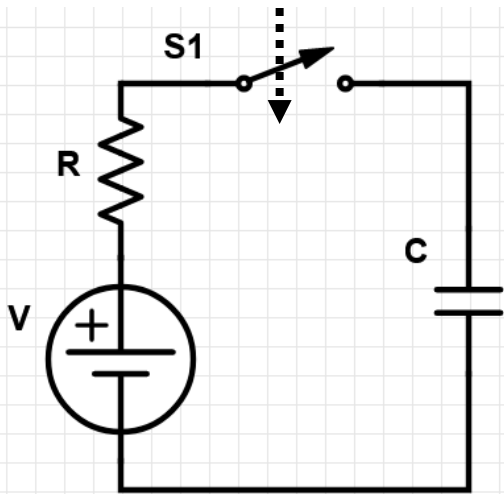

$$V - iR - q/C = 0$$

$$\frac{dq}{dt} = \frac{V}{R} - \frac{q}{RC}$$

$$\frac{dq}{q - CV} = -\frac{dt}{RC}$$


$$\int_0^q \frac{dq}{q - CV} = -\int_0^t \frac{dt}{RC}$$

$$\ln\left(\frac{q - CV}{-CV}\right) = -\frac{t}{RC}$$


$$q = CV(1 - e^{-t/RC})$$

$$i = \frac{V}{R} e^{-t/RC}$$


$$i = I_0 e^{-t/RC}$$

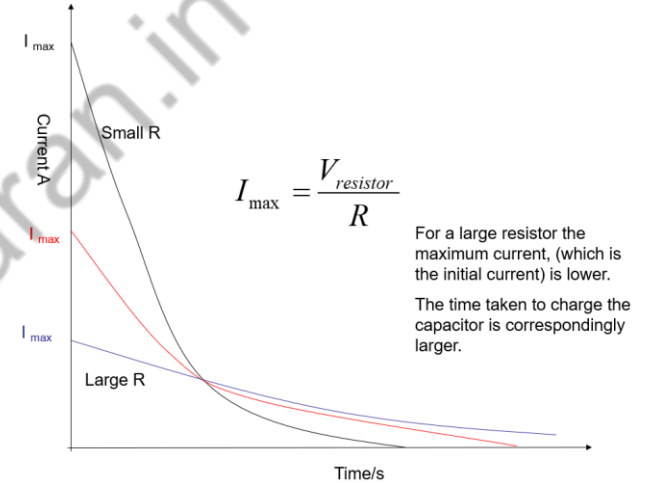

$$V_c = \frac{q}{C} = V(1 - e^{-t/RC})$$

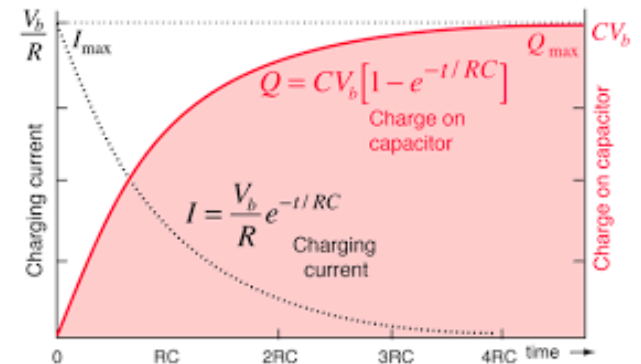


Charging a Capacitor

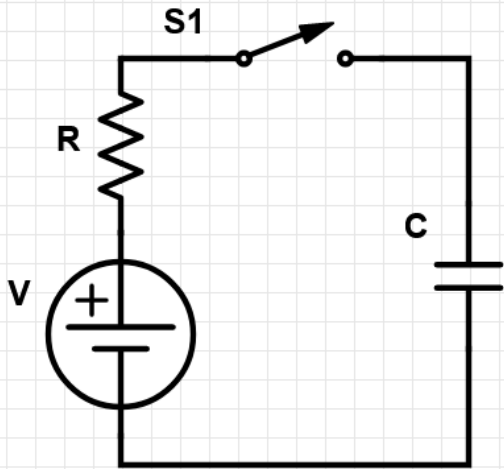


$$V_c = V (1 - e^{-t/RC})$$

Time Constant $T = RC$

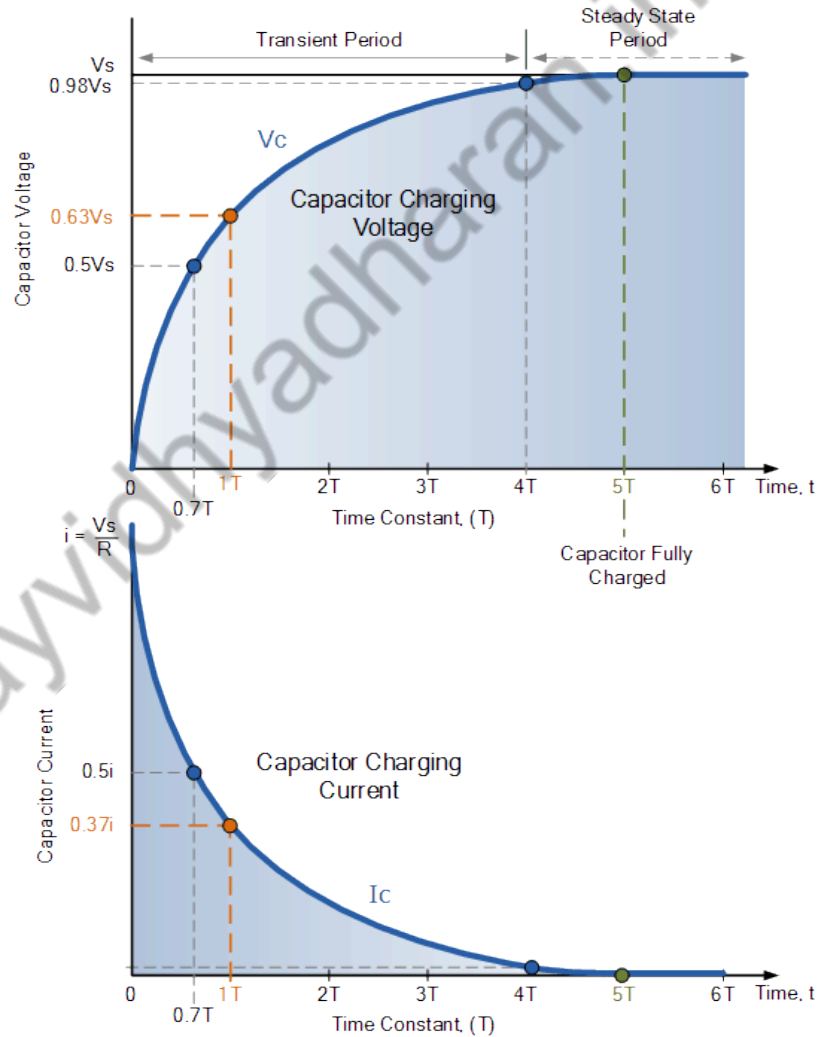


Charging a Capacitor

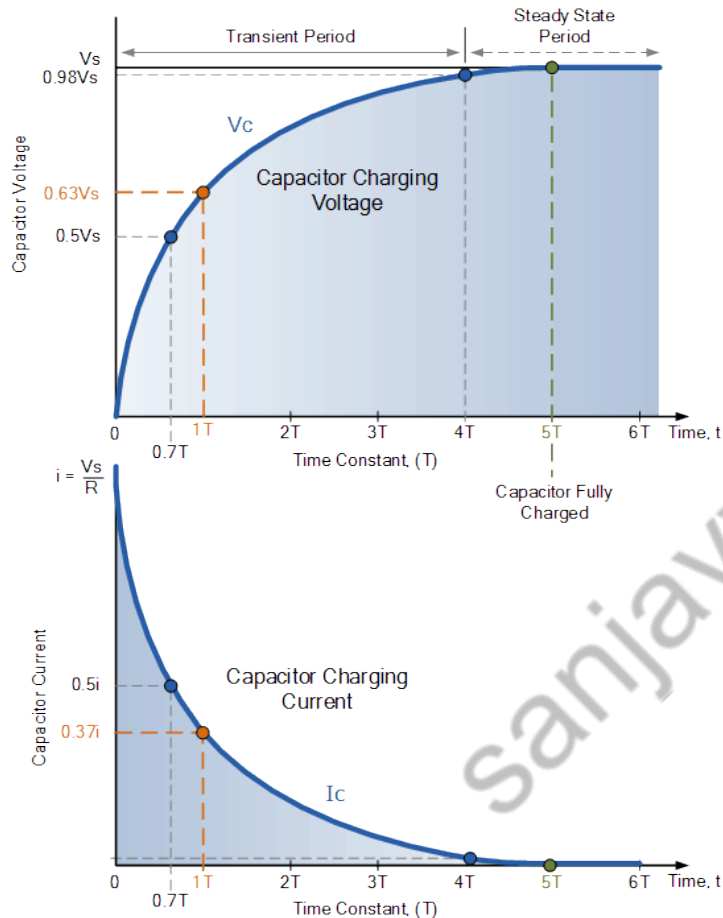

$$V_c = V (1 - e^{-t/RC})$$

Time Constant	RC Value	Percentage of Maximum	
		Voltage	Current
0.5 time constant	$0.5T = 0.5RC$	39.3%	60.7%
0.7 time constant	$0.7T = 0.7RC$	50.3%	49.7%
1.0 time constant	$1T = 1RC$	63.2%	36.8%
2.0 time constants	$2T = 2RC$	86.5%	13.5%
3.0 time constants	$3T = 3RC$	95.0%	5.0%
4.0 time constants	$4T = 4RC$	98.2%	1.8%
5.0 time constants	$5T = 5RC$	99.3%	0.7%


Charging a Capacitor

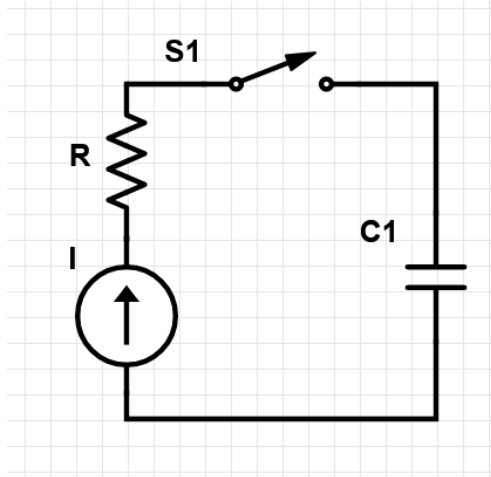



$$I = \frac{dq}{dt} = C \frac{dV_c}{dt}$$

$$dV_c = \frac{I}{C} dt$$

$$V_c = \frac{I}{C} t$$

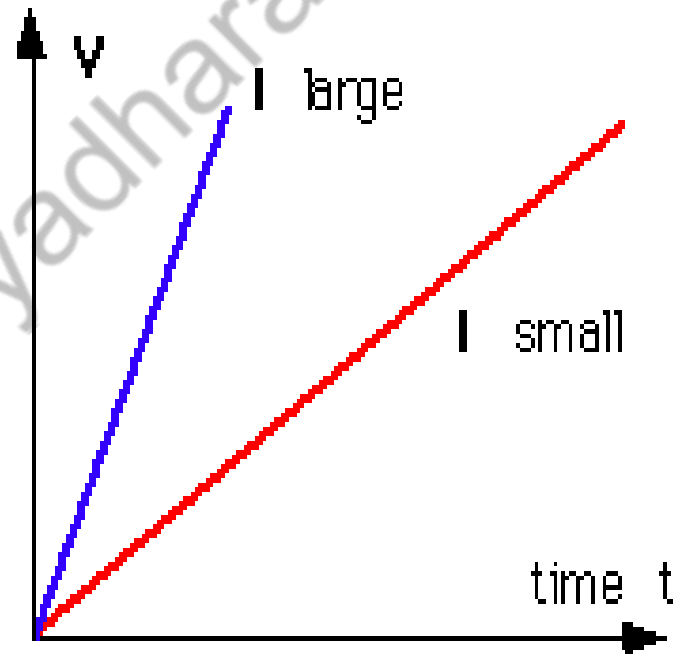

Discharging a Capacitor

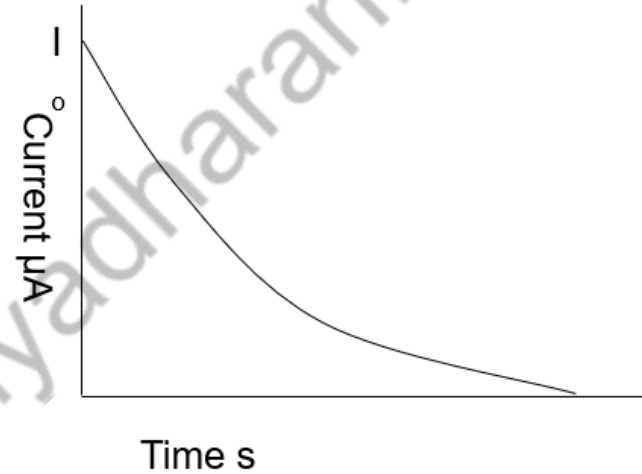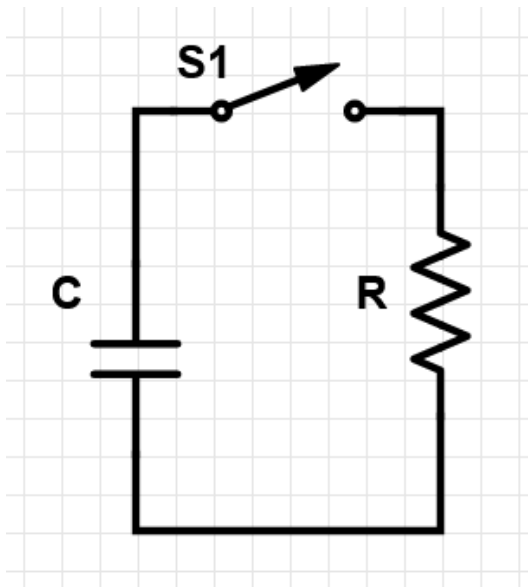

$$I = I_0 e^{-\frac{t}{CR}}$$

$$I_0 = \frac{V_0}{R}$$

$$V_C = V e^{-t/RC}$$

Note that the only variable on the right is t.

When $t=CR$

$e = 2.718$ so $1/e = 0.368$

$$I = 0.368I_0$$

Series Capacitors


$$V_1 = \frac{Q}{C_1} \quad V_2 = \frac{Q}{C_2} \quad V_3 = \frac{Q}{C_3}$$

$$V_1 + V_2 + V_3 = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$


$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

A single capacitor which has the same effect is: $V = \frac{Q}{C}$
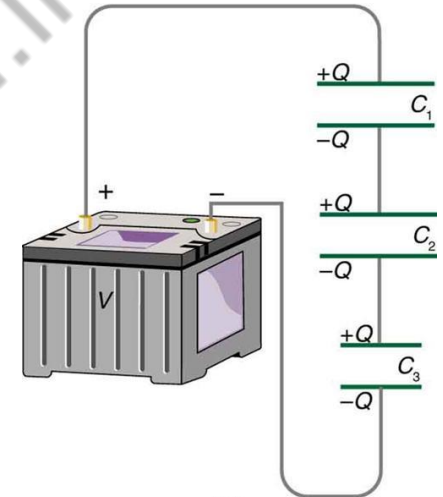
$$\text{So: } \frac{1}{C} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$




(a)

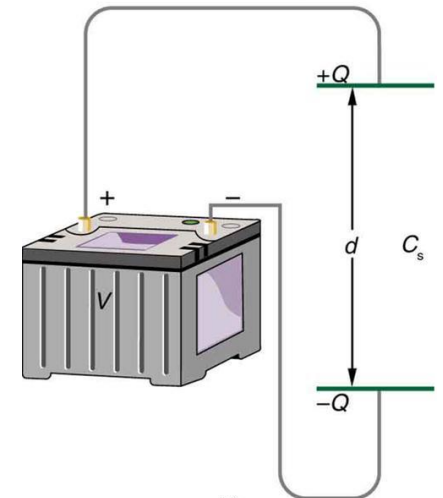

(b)

Parallel Capacitors

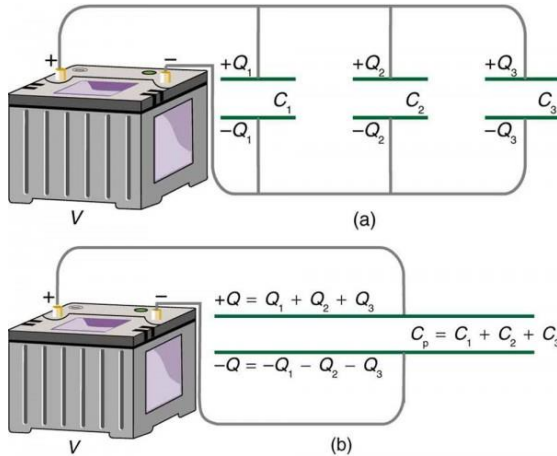

$$Q_1 = C_1V \quad Q_2 = C_2V \quad Q_3 = C_3V$$

$$Q_1 + Q_2 + Q_3 = C_1V + C_2V + C_3V$$


$$Q_1 + Q_2 + Q_3 = (C_1 + C_2 + C_3)V$$

$$Q = CV$$

$$\text{So } C = C_1 + C_2 + C_3$$

	capacitors	resistors
Series connection	$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$	$R = R_1 + R_2 + R_3$
Parallel connection	$C = C_1 + C_2 + C_3$	$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$

Energy Stored in Capacitor

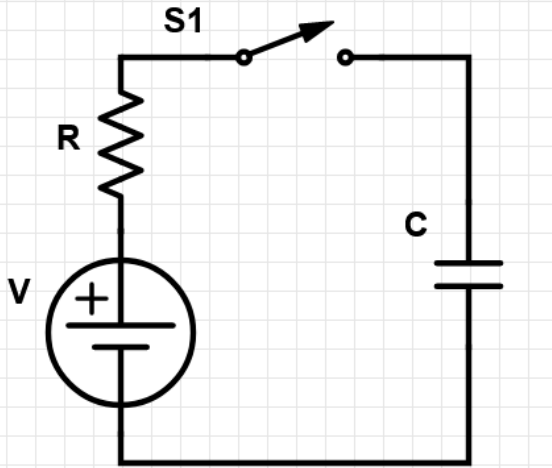


$$\text{Energy stored in } C = \int_0^V V_C \cdot C dV_C = \frac{1}{2} V^2 * C$$

$$\text{Energy consumed from power supply} = V_{DD} \int_0^T i(t) dt = V_{DD} \cdot Q_{CL} = V_{DD}^2 \cdot C_L$$

$$\text{Energy dissipated in Resistor during charging} = \frac{1}{2} \cdot V_{DD}^2 \cdot C_L$$

Energy Stored in Capacitor

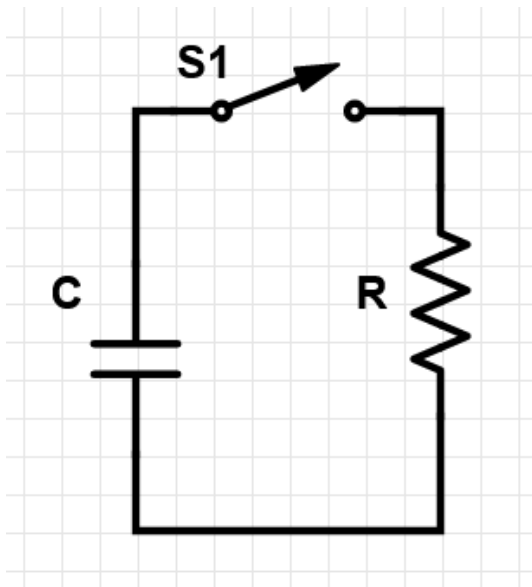

Energy **stored** in C during charging = $\int_0^V V_c \cdot C dV_c = \frac{1}{2} V^2 * C$


Energy **dissipated** in Resistor during discharging = $\frac{1}{2} V^2 * C$

Applications of Capacitors

1. Energy storage
2. Power conditioning
3. RF coupling and decoupling applications
4. LPF, HPF. BPF Filters
5. Oscillators
6. Noise Filters

sanjayvidhyadharan.in

Energy Stored in Capacitor

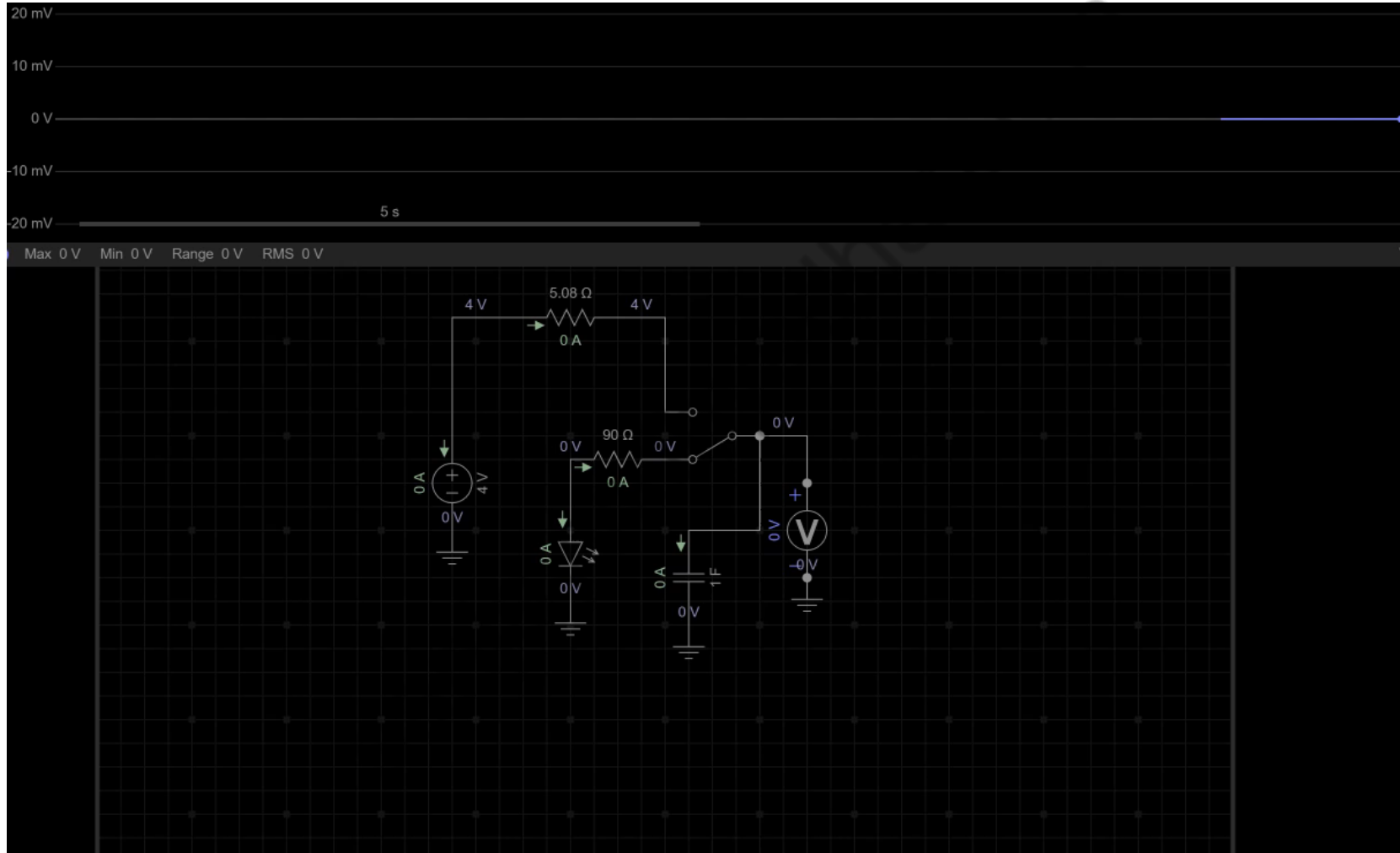

Thank you

sanjayvidhyadharan.in