



# **Electrical Science: 2021-22**

## **Lecture 9**

### **Inductors**


**By Dr. Sanjay Vidhyadharan**

sanjayvidhyadharan.in


# Inductors

- An Inductor is a device which can store energy.
- Inductance is the property of a conductor to **oppose a change in current**.


Inductor symbols

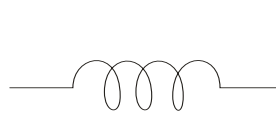


Air core

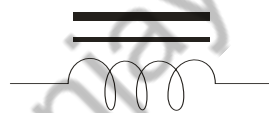

Iron core

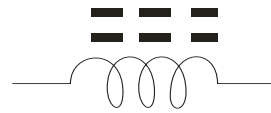

Ferrite core

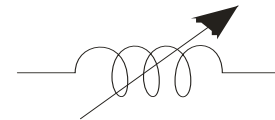

Variable

# Types of Inductors



# Self Inductance of a Coil

- Self inductance of a circuit element (a coil, wire, resistor or whatever) as

$$L = F_B / I$$

- From this we have  $F_B = LI$  and so


$$dF_B / dt = L dI / dt$$

- and Faraday's law gives


$$E = - L dI / dt$$

- Since this emf opposes changes in the current (in the component) it is often called the “back emf”.
- From now on “inductance” means self-inductance.


# Inductance Formula

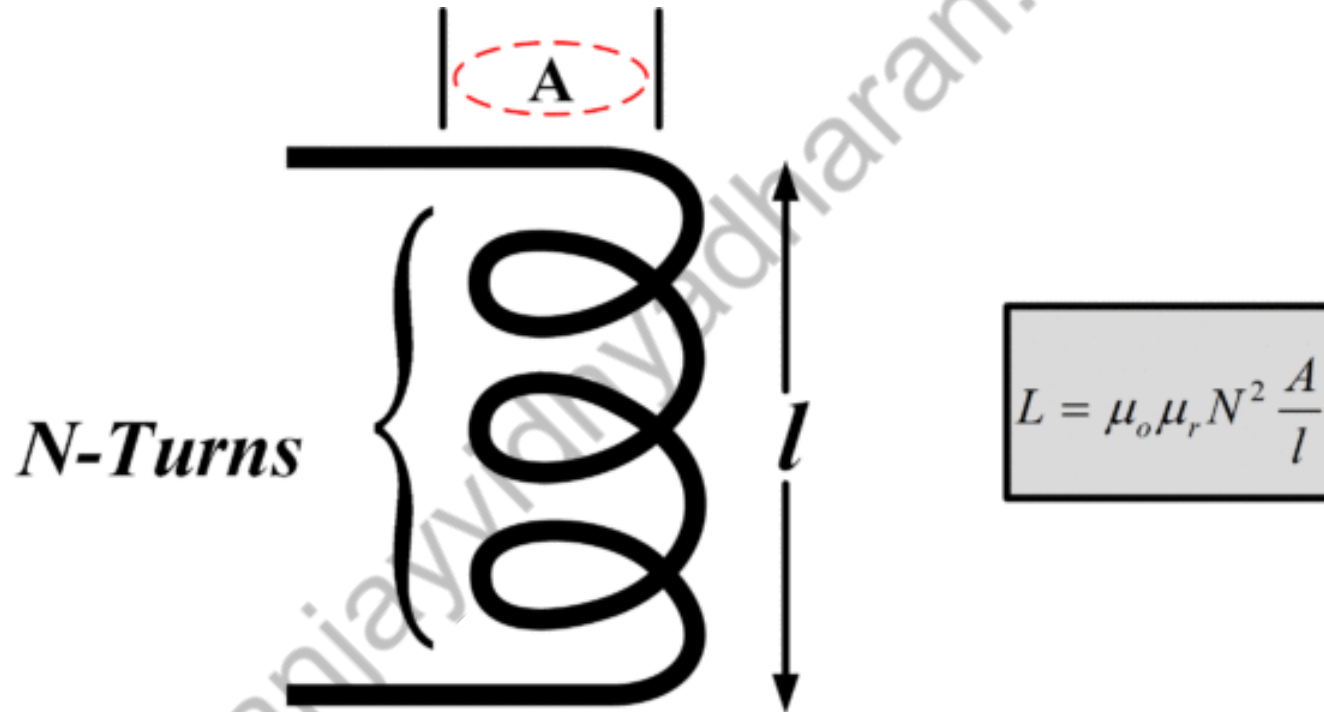

# Steady State Current in an Inductor

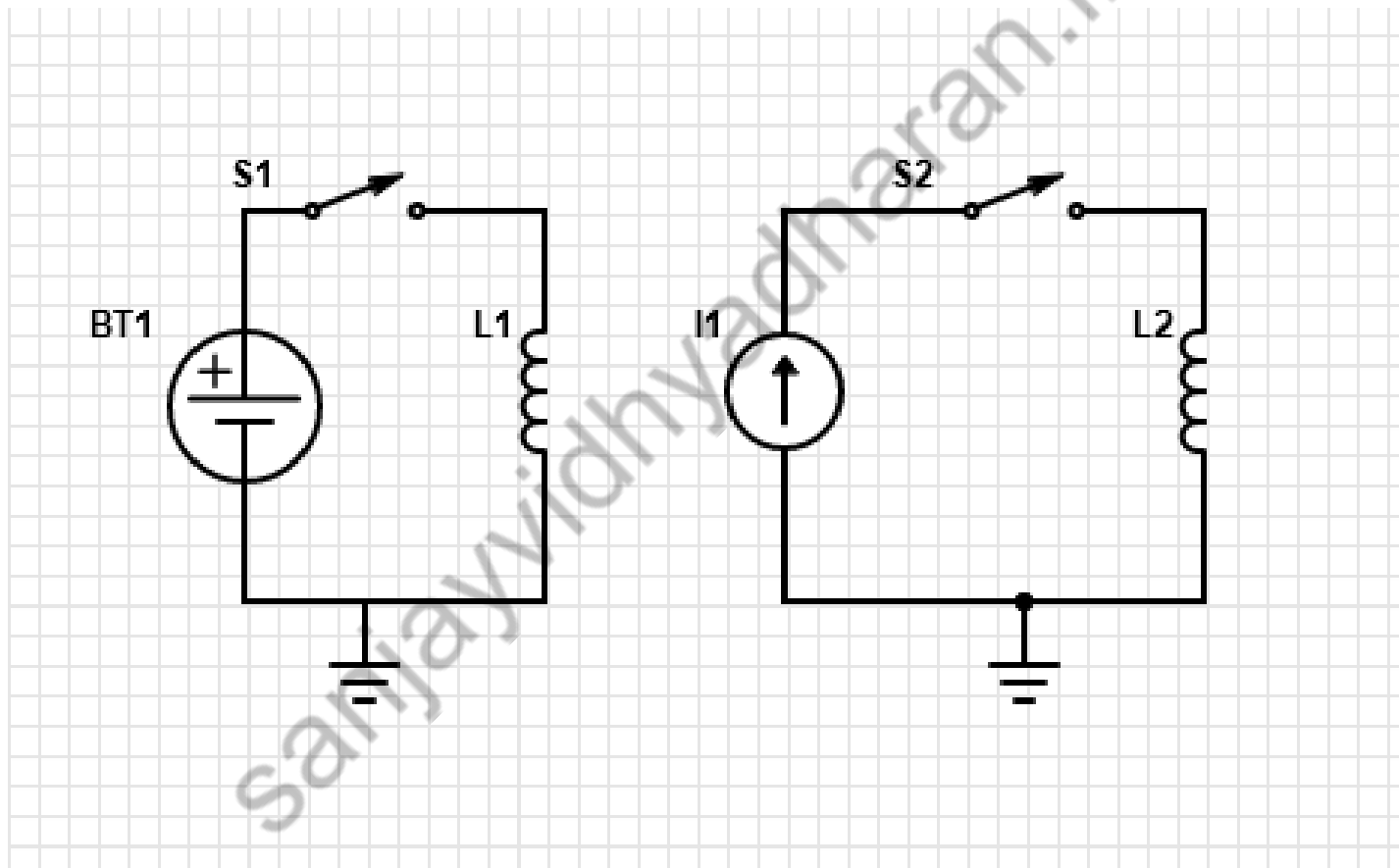

# Current in an Inductor

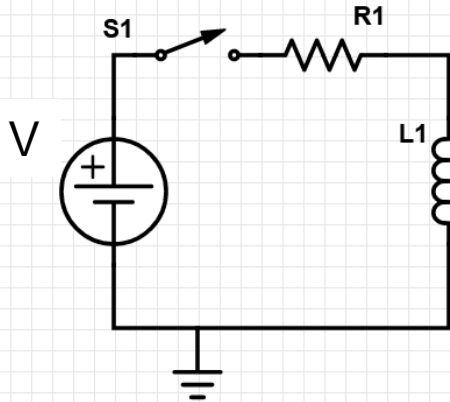

Switch Open : No Current


When Switch is closed

Current  $I$  flows, growing gradually, and a 'back emf'  $E_L$  is generated in inductor.

The emf  $E_L$  opposes the current  $I$


$$\Rightarrow E_L = -L \frac{dI}{dt}$$

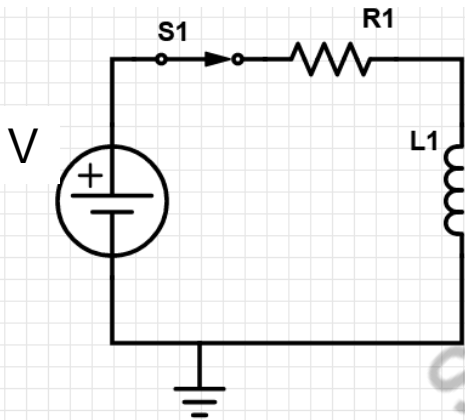After a certain time the current ( $V/R$ ) becomes steady. Then  $E_L$  is zero.



# Current in an Inductor

$$V_c = V (1 - e^{-t/RC})$$



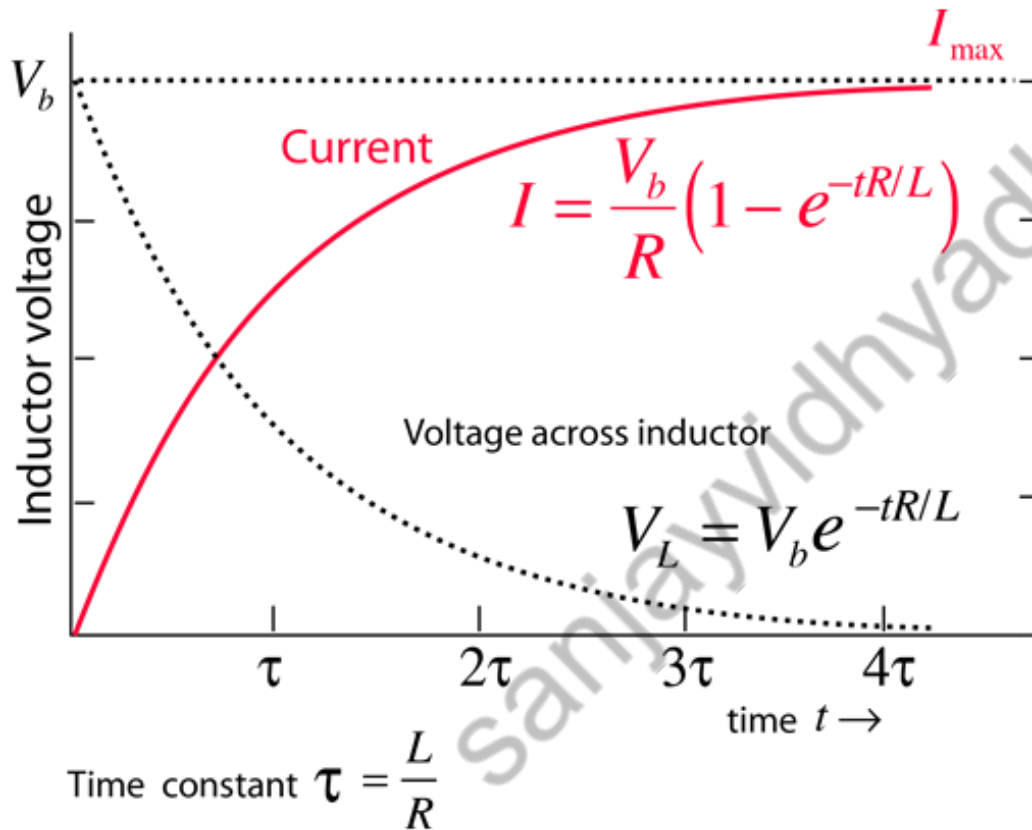


Current through inductor

TIME CONSTANT ( $\tau$ )	% ULTIMATE VALUE
0.1	10
0.5	40
0.7	50
0.9	60
1	63.2
2	86.5
3	95.1
4	98.2
5	99.3





# Current in an Inductor

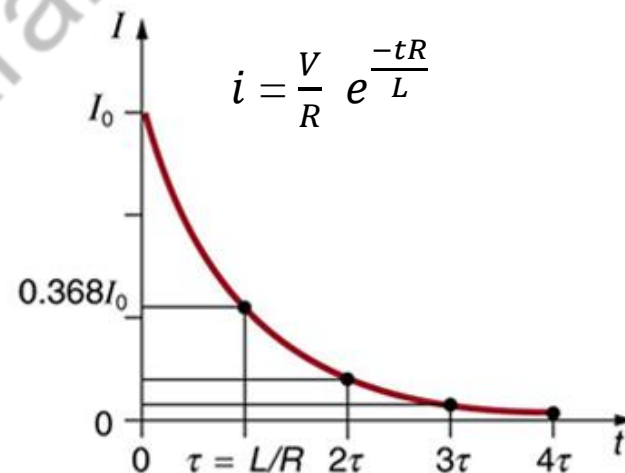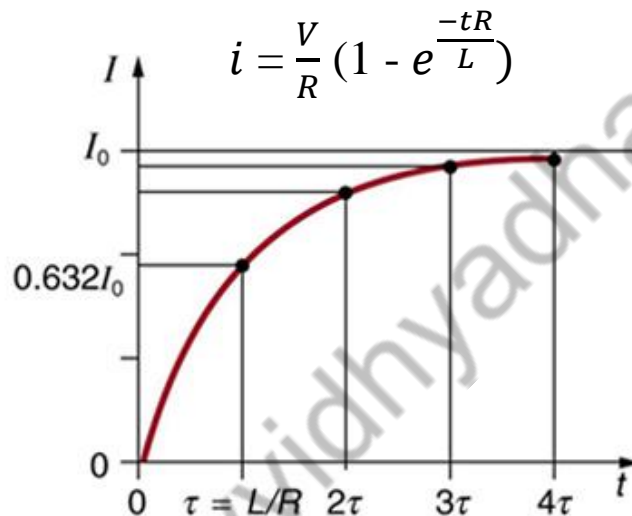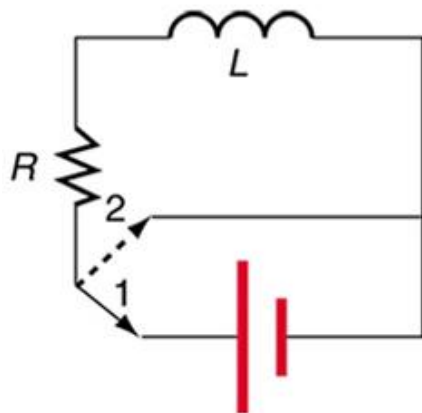

sanjayvidhyadharan.in

# Current in an Inductor

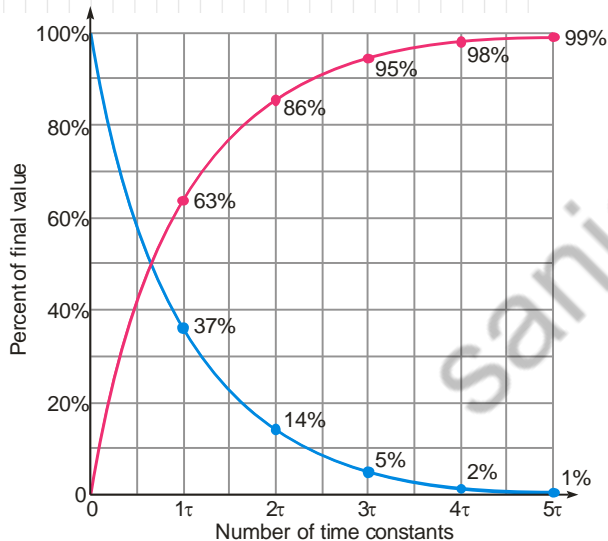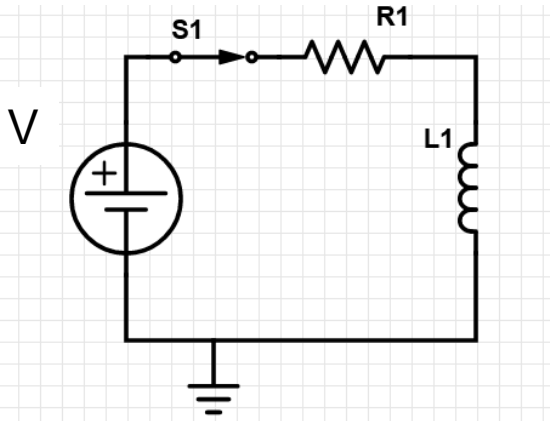

$$V - iR + E_L = 0$$

$$V - iR - L \frac{di}{dt} = 0$$

$$\frac{di}{V - iR} = \frac{dt}{L}$$


$$\int_0^i \frac{di}{V - iR} = \int_0^t \frac{dt}{L}$$

$$\frac{-1}{R} [\ln(V - iR)]_0^i = \frac{t}{L} \Big|_0^t$$

$$i = \frac{V}{R} (1 - e^{-\frac{tR}{L}})$$

$$V_c = V (1 - e^{-t/RC})$$

# Series Inductors

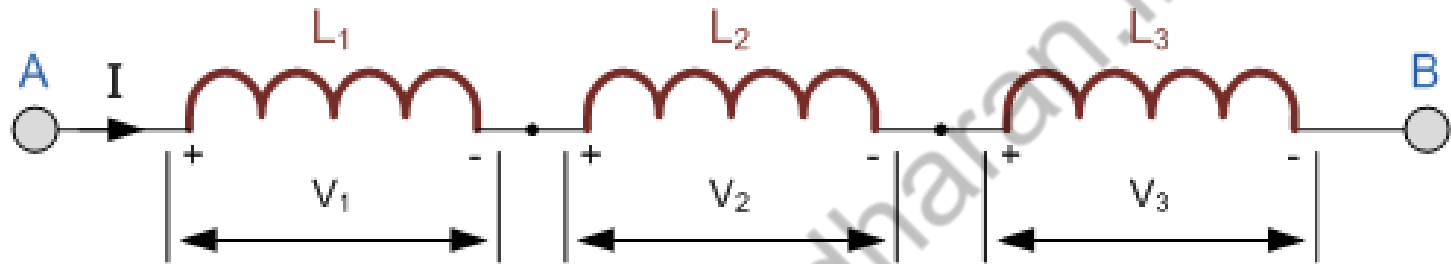


$$I_{L1} = I_{L2} = I_{L3} = I_{AB}$$

$$V_T = V_1 + V_2 + V_3$$

$$L_T \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$

$$L_{\text{total}} = L_1 + L_2 + L_3$$

# Parallel Inductors

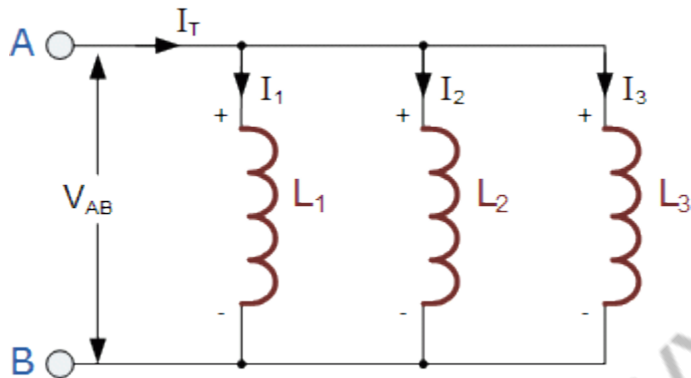


$$V_{L1} = V_{L2} = V_{L3} = V_{AB}$$

$$V_{AB} = L_T \frac{d}{dt} (i_1 + i_2 + i_3) = L_T \left( \frac{di_1}{dt} + \frac{di_2}{dt} + \frac{di_3}{dt} \right)$$

$$V_{AB} = L_T \left( \frac{v}{L_1} + \frac{v}{L_2} + \frac{v}{L_3} \right)$$

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

# Energy Stored in Inductor

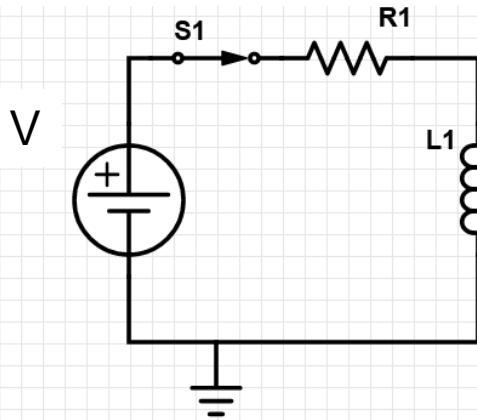

$$\text{Energy stored in Capacitor} = \int_0^V V_C \cdot C dV_C = \frac{1}{2} V^2 * C$$

For Inductors


$$\text{Power} = vi = iL \frac{di}{dt}$$

$$\text{Energy} = \int_0^t P dt = \int_0^I L i di = \frac{1}{2} I^2 * L \text{ where } I = \frac{V}{R}$$

$$\text{Energy consumed from power supply} = V_{DD} \int_0^t i(t) dt = V_{DD} \int_0^t I(1 - e^{-\frac{tR}{L}}) dt = I^2 * L$$

$$\text{Energy dissipated in Resistor} = \frac{1}{2} I^2 * L$$

# Energy Stored in Inductor

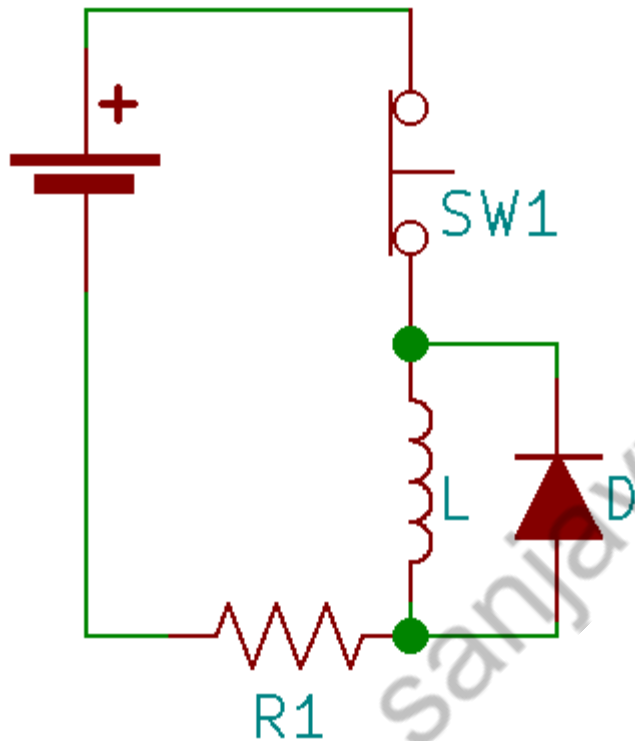


# Applications of Inductors

1. Energy storage
2. Power conditioning
3. RF coupling and decoupling applications
4. LPF, HPF. BPF Filters
5. Oscillators
6. Noise Filters


sanjayvidhyadharan.in

# Energy Stored in Inductors

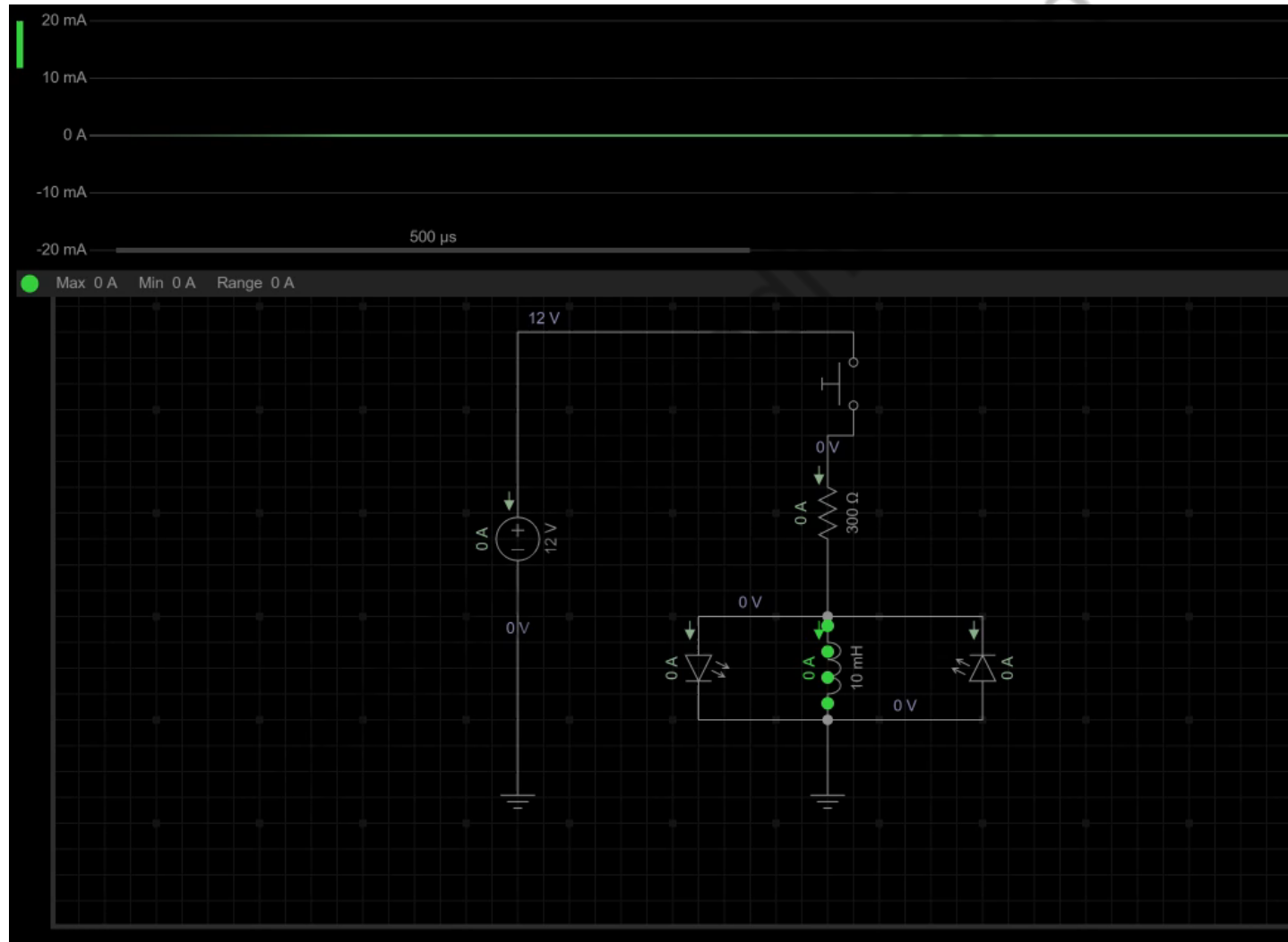



# Energy Stored in Inductors

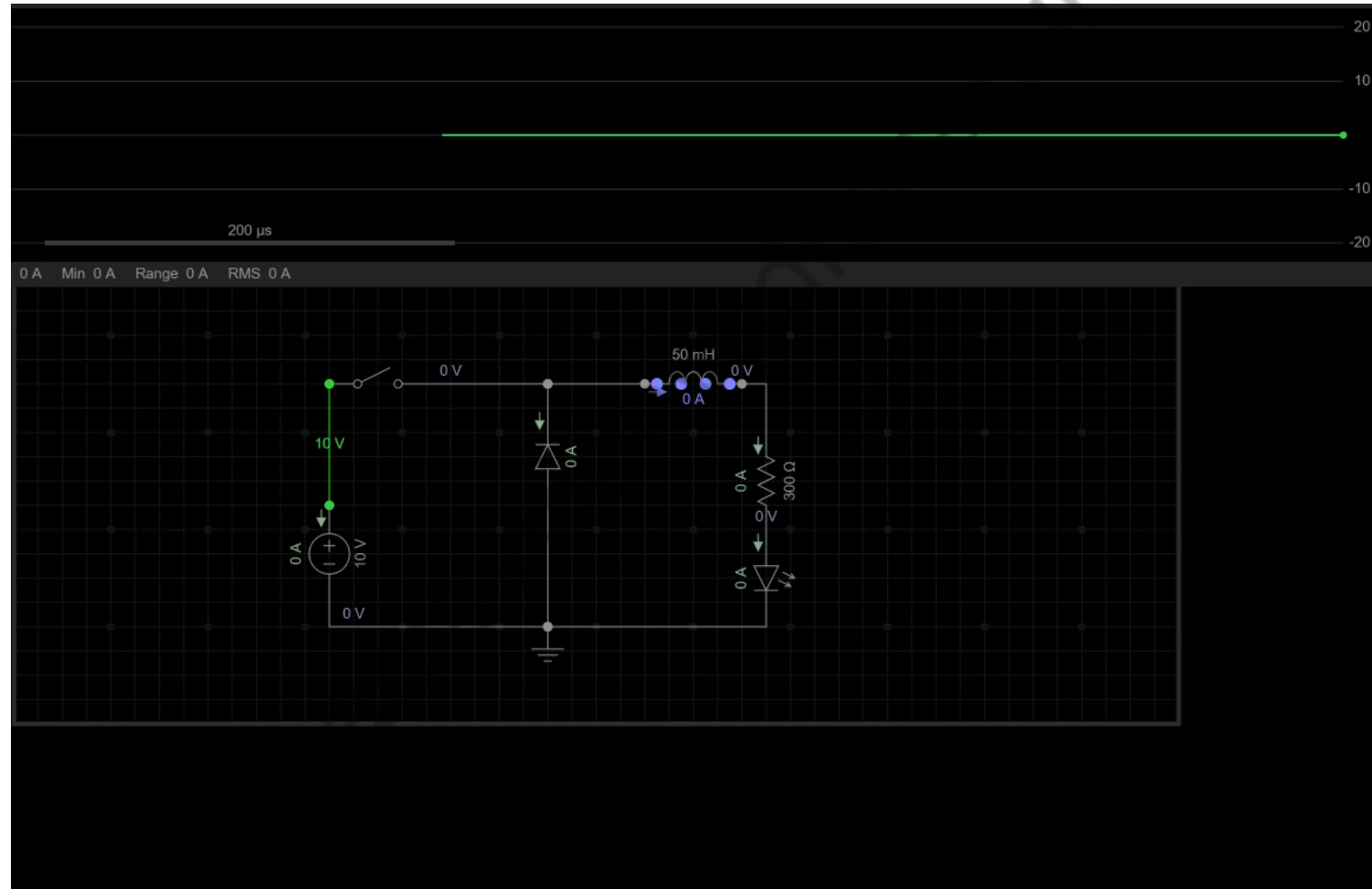

**Thank you**

sanjayvidhyadharan.in