



Electrical Science: 2021-22

Tutorial 1





Power Sources

By Dr. Sanjay Vidhyadharan

sanjayvidhyadharan





Problem 1

Which of the circuits in following figure will give you $V_{ab} = 7\text{ V}$?

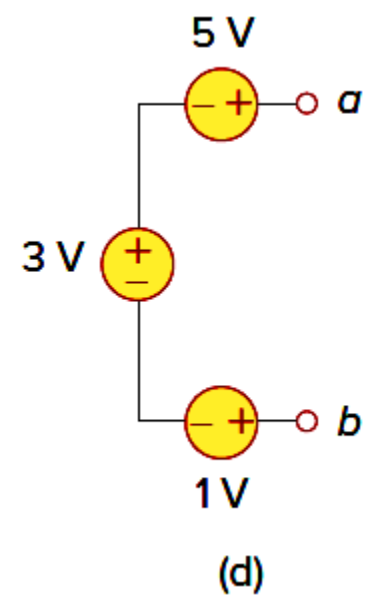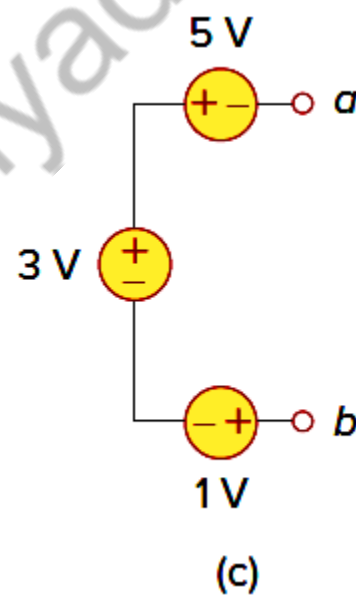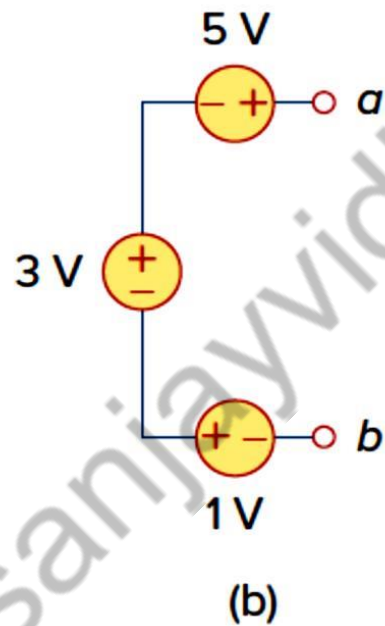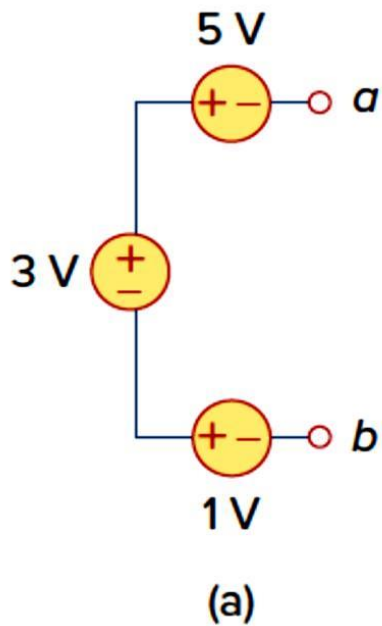

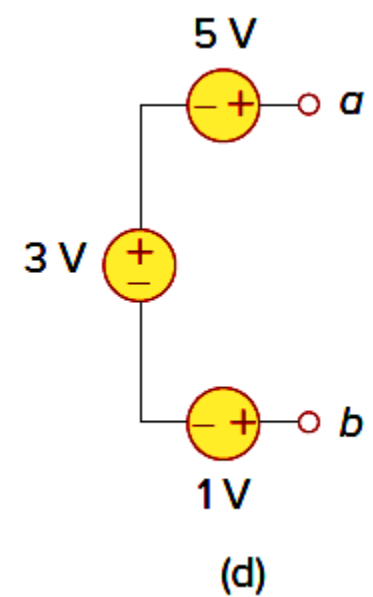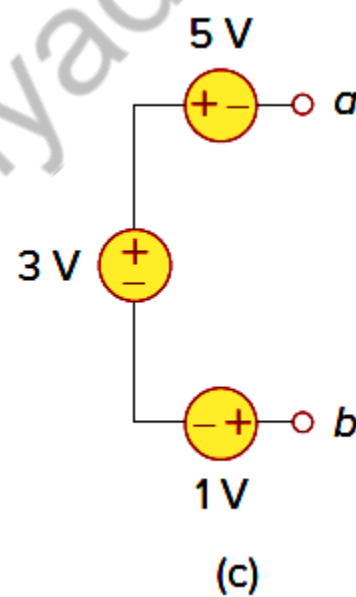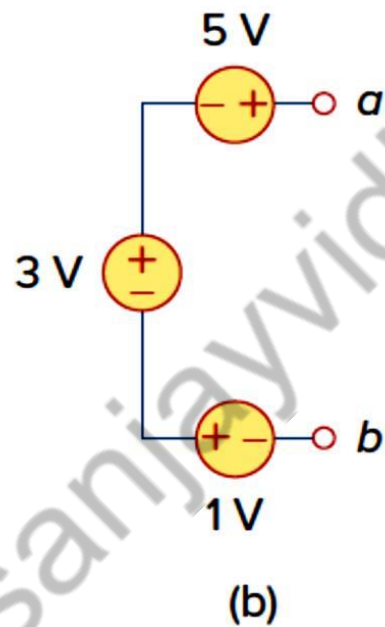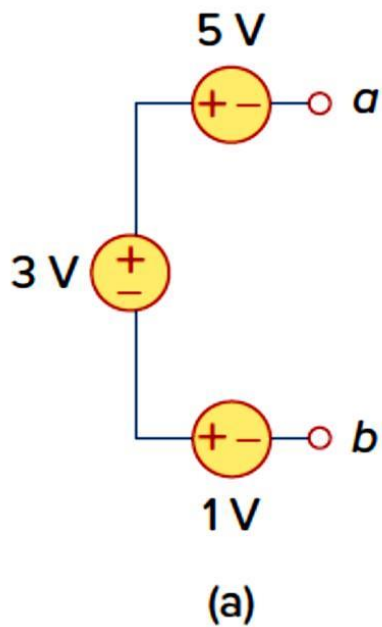Problem 1


Which of the circuits in following figure will give you $V_{ab} = 7\text{ V}$?



Answer: (d)





Problem 2

Use source transformation to find v_o in the circuit of below figure.

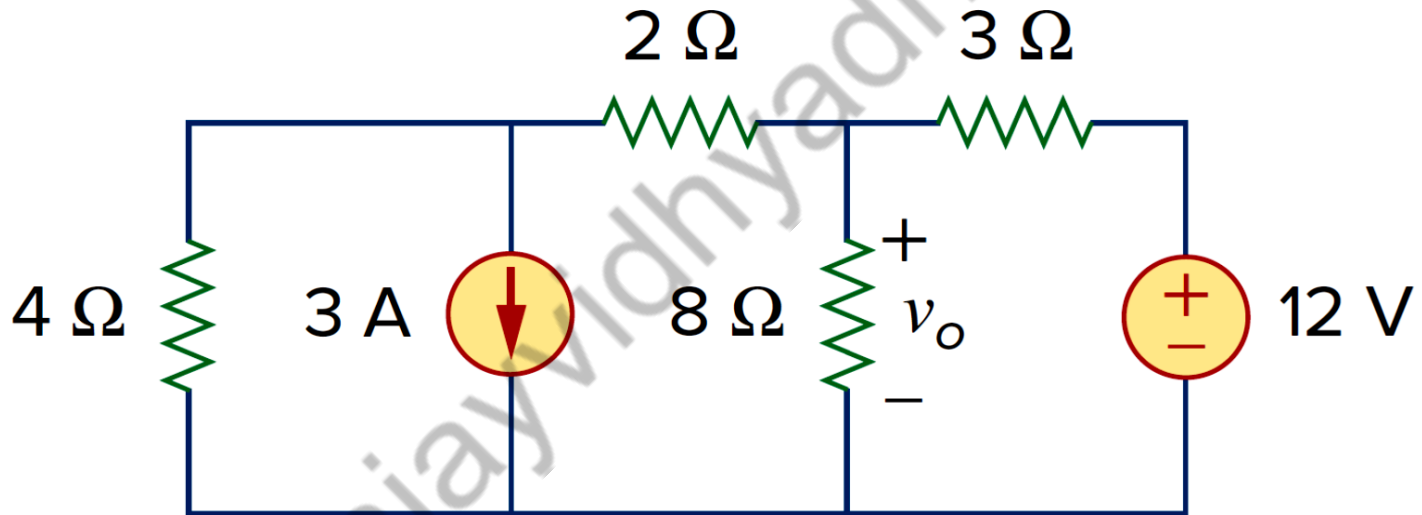

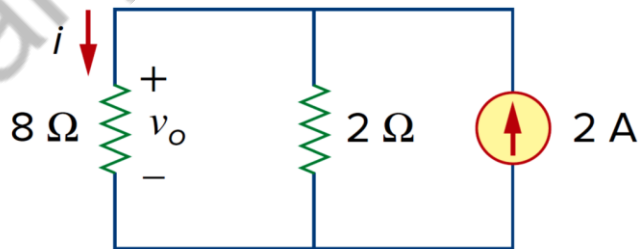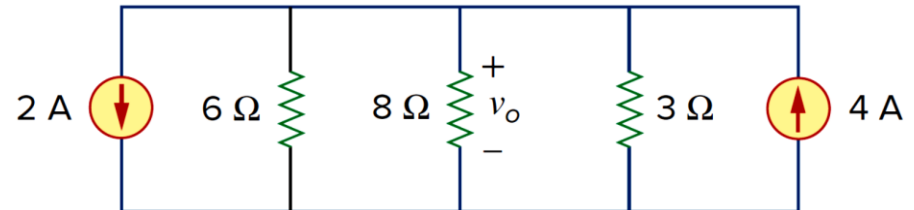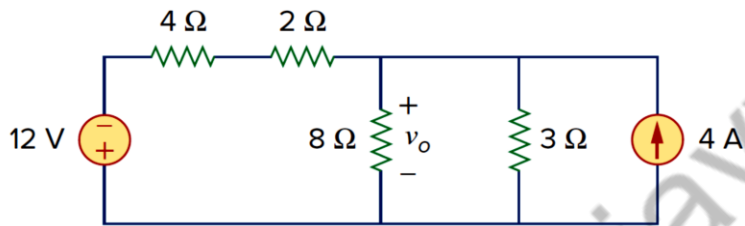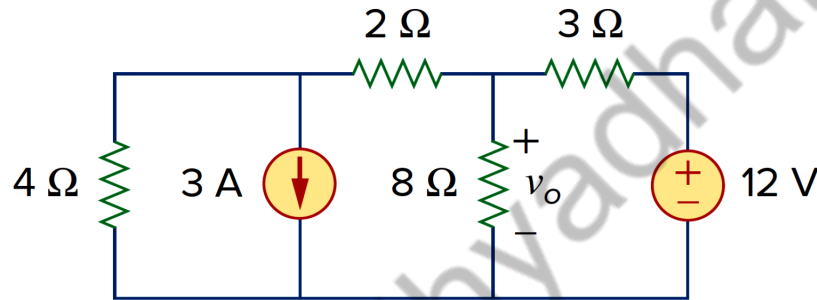Problem 2

Use source transformation to find v_o in the circuit of below figure.




$$i = 2 \times \frac{2}{2+8} = 0.4 \text{ A}$$

$$v_o = 8i = 8(0.4) = 3.2 \text{ V}$$


Problem 3

Find V_{R4}

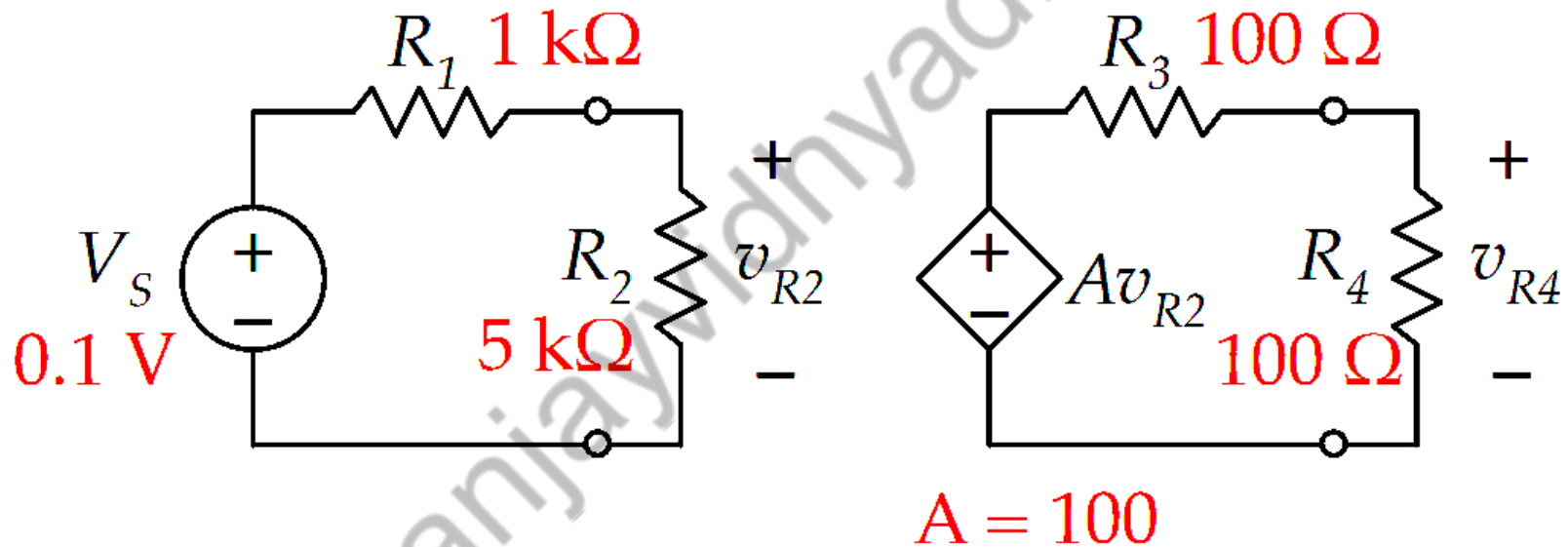

Problem 3

Find V_{R4}

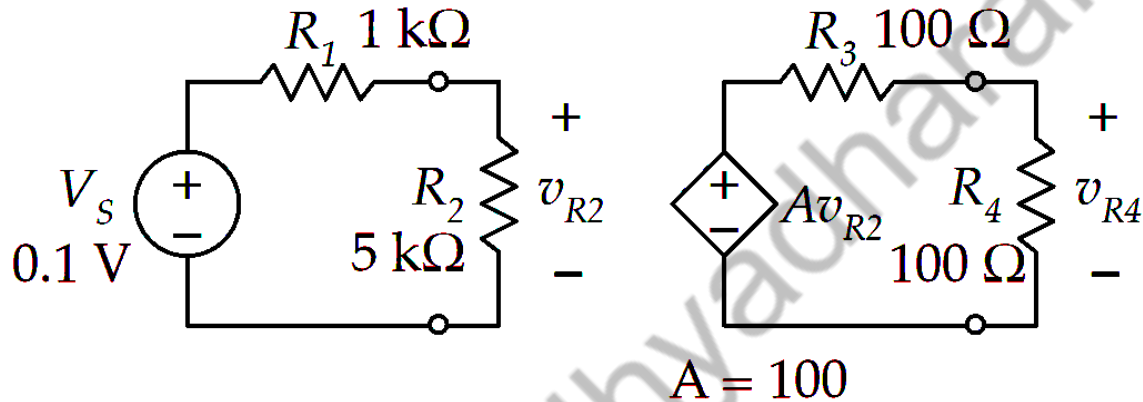


$$v_{R2} = \frac{R_2}{R_1 + R_2} V_s = \frac{5 \text{ k}\Omega}{1 \text{ k}\Omega + 5 \text{ k}\Omega} (0.1 \text{ V}) = 0.0833 \text{ V}$$

$$v_{R4} = \frac{R_4}{R_3 + R_4} (A v_{R2}) = \frac{100 \Omega}{100 \Omega + 100 \Omega} (100) v_{R2} = 50 v_{R2}$$

$$v_{R4} = (50)(0.0833 \text{ V}) = 4.17 \text{ V.}$$



Problem 4

Find V_{RC}

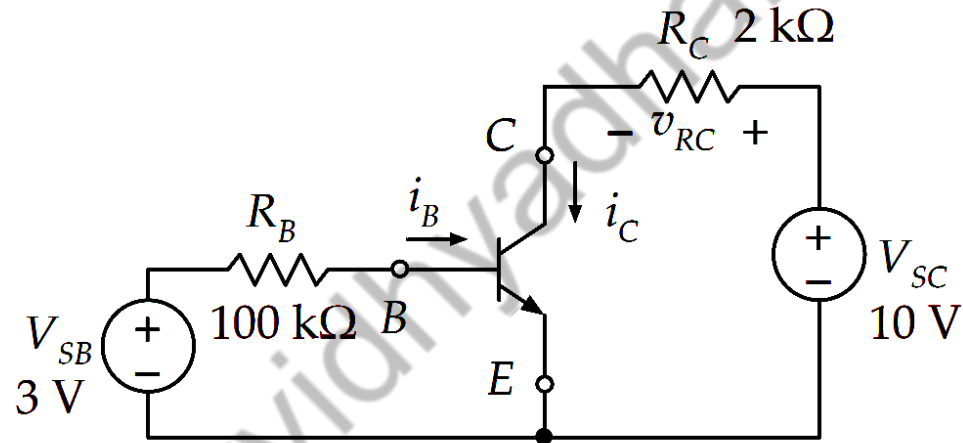


Problem 4

Find V_{RC} Given $\beta = 100$.

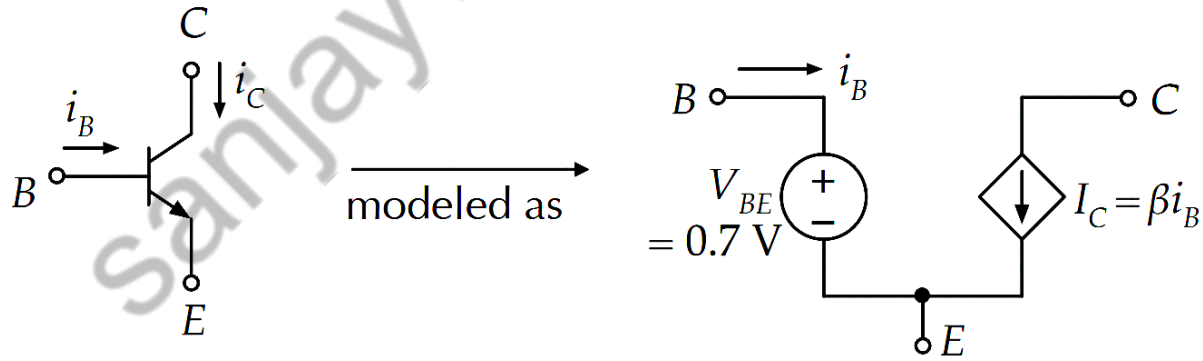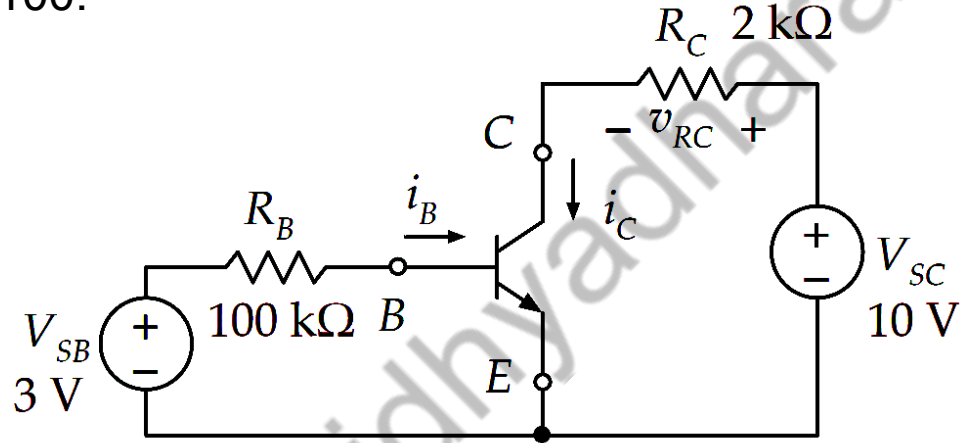

Problem 4

Find V_{RC} Given $\beta = 100$.

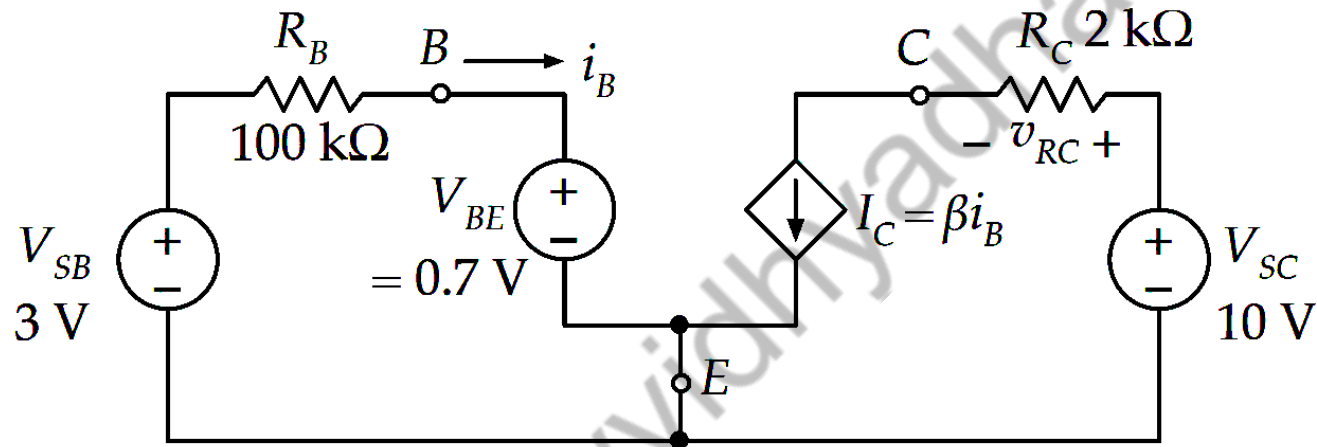

Around the left-hand loop:


$$V_{SB} - i_B R_B - V_{BE} = 0. \quad \frac{V_{SB} - V_{BE}}{R_B} = \frac{3\text{ V} - 0.7\text{ V}}{100\text{ k}\Omega} = 0.023\text{ mA}$$

On the right: $I_C = \beta i_B = (100)(0.023\text{ mA}) = 2.3\text{ mA}$.

Then: $v_{RC} = R_C I_C = (2\text{ k}\Omega)(2.3\text{ mA}) = 4.6\text{ V}$. So easy!


Problem 5

Find the voltage v in the following circuit which contains a CCVS

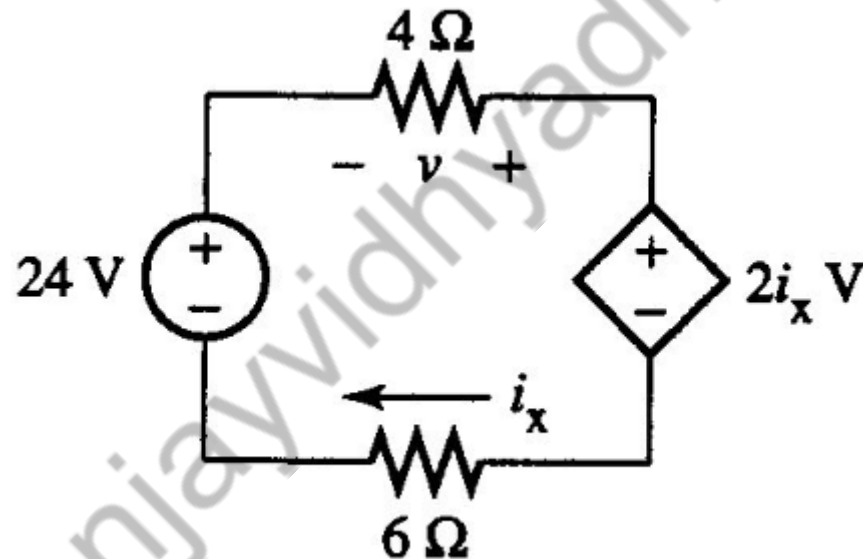

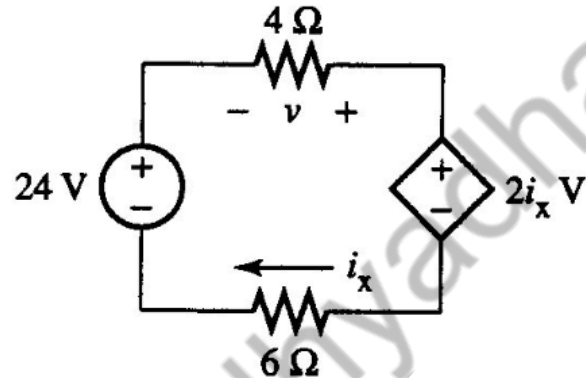Problem 5

Find the voltage v in the following circuit which contains a CCVS



$$v = \frac{4}{4+6}(v_c - 24) = \frac{2}{5}v_c - \frac{48}{5}$$


$$v_c = 2i_x = 2\left(\frac{24 - v_c}{10}\right) = \frac{24}{5} - \frac{v_c}{5}$$

$$6v_c = 24 \quad v_c = 4 \text{ V}$$

$$v = \frac{2}{5} \times 4 - \frac{48}{5} = -8 \text{ V}$$

Problem 6


Find V_o using source Transformation

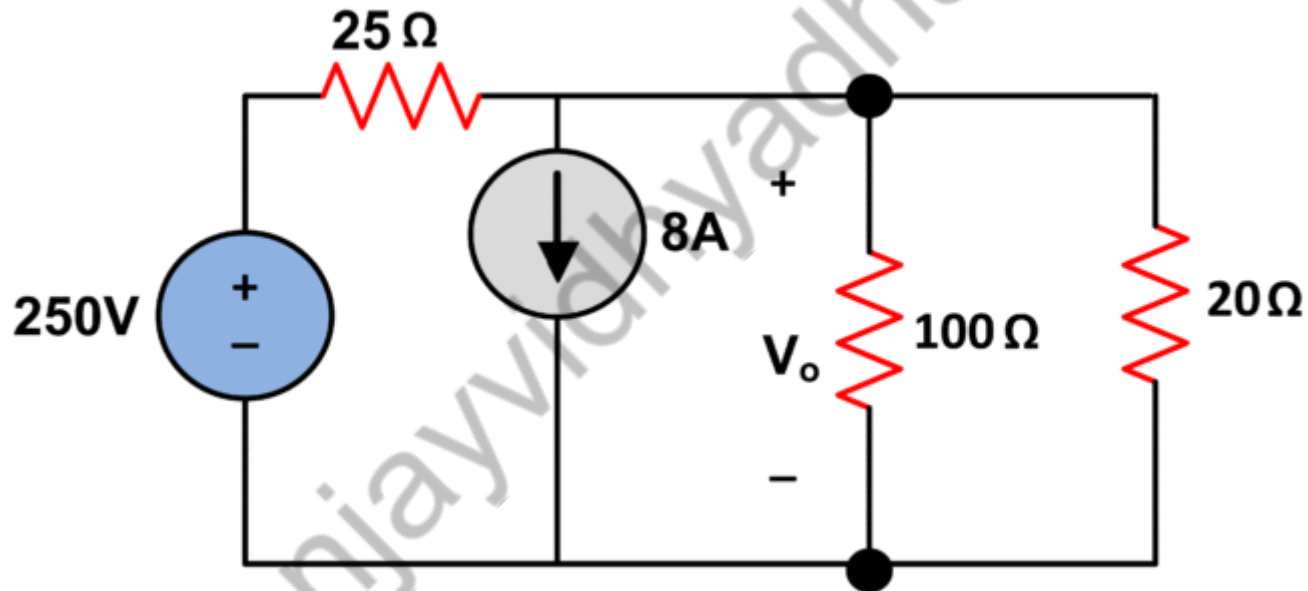

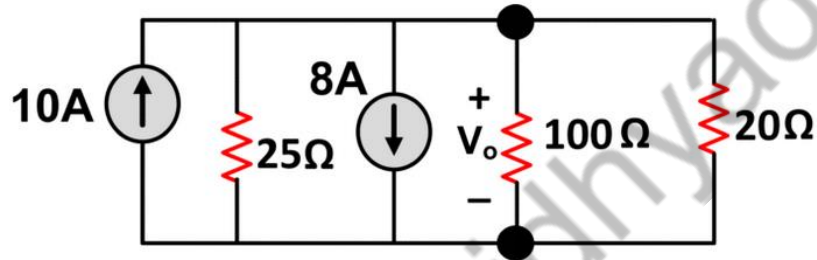
Problem 6

Find V_o using source Transformation

Converting 250V voltage source into current source.




Combining both current sources

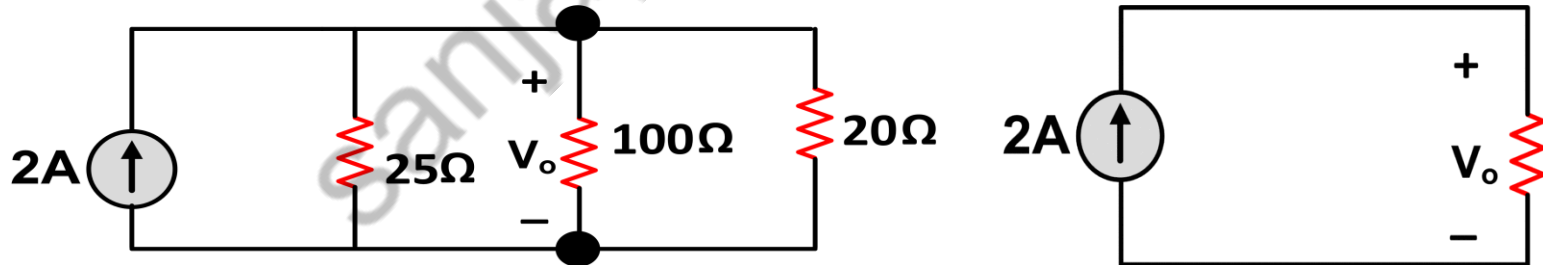


Problem 7

Source Transformation Example with Dependent Source

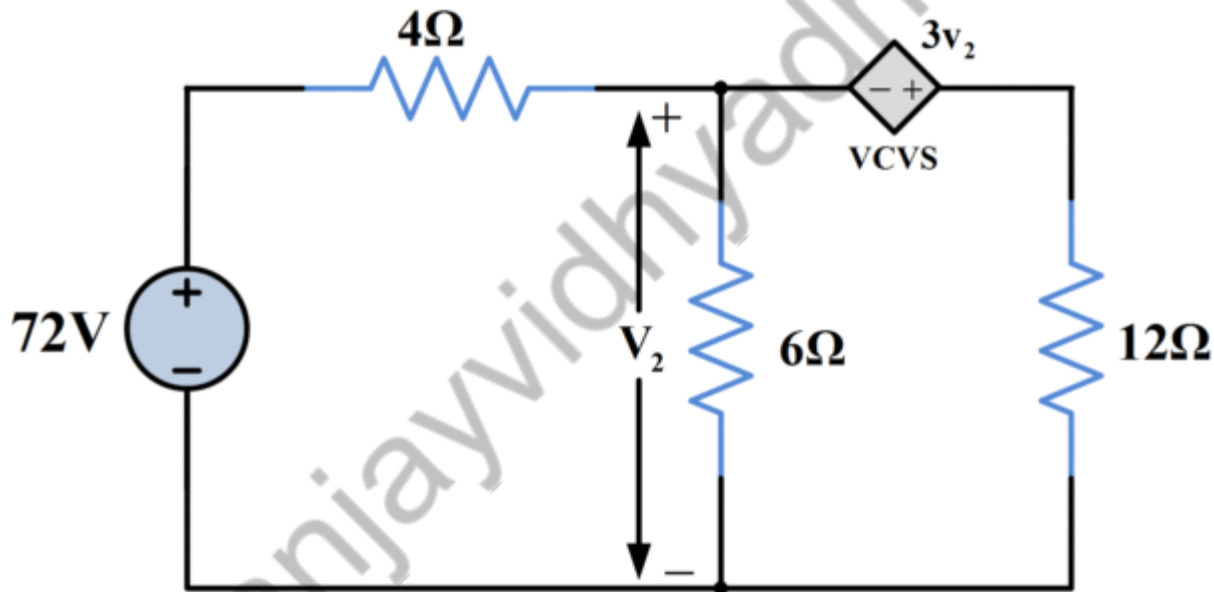

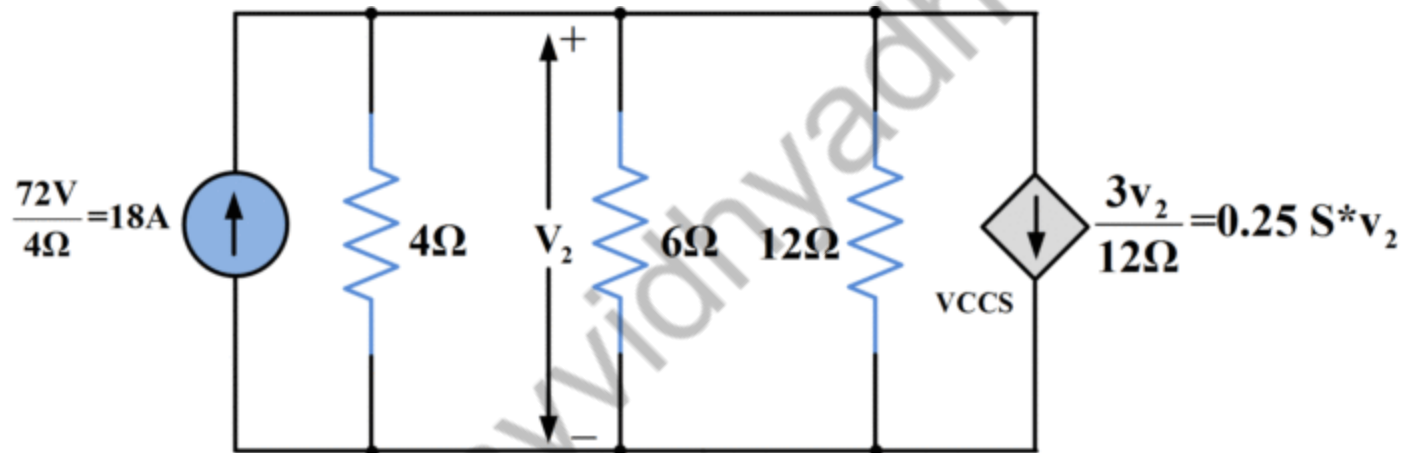Problem 7

Source Transformation Example with Dependent Source



$$4 \parallel 6 \parallel 12 = 2\Omega$$

$$V_2 = 2(18 - 0.25v_2)$$

$$V_2 = 36/1.5 = 24V$$

Thank you

sanjayvidhyadharam