



Electrical Science: 2021-22

Tutorial 2


Mesh and Node Analysis

By Dr. Sanjay Vidhyadharan

sanjayvidhyadharan.in

Problem 1

Find the equivalent resistance


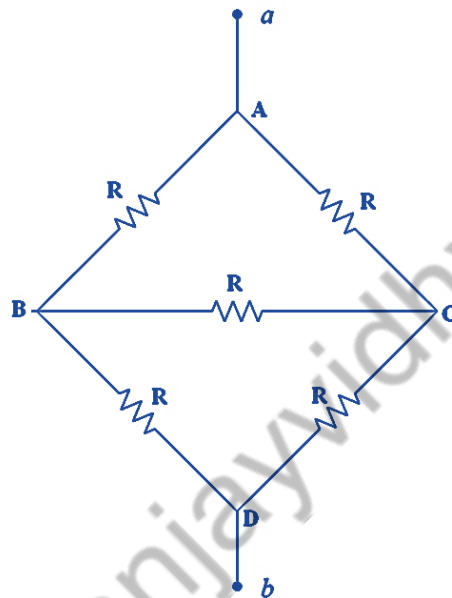


sanjayvidhyadharan.in

Problem 1


Find the equivalent resistance

$$R_Y = \frac{R \times R}{R + R + R} = R/3$$

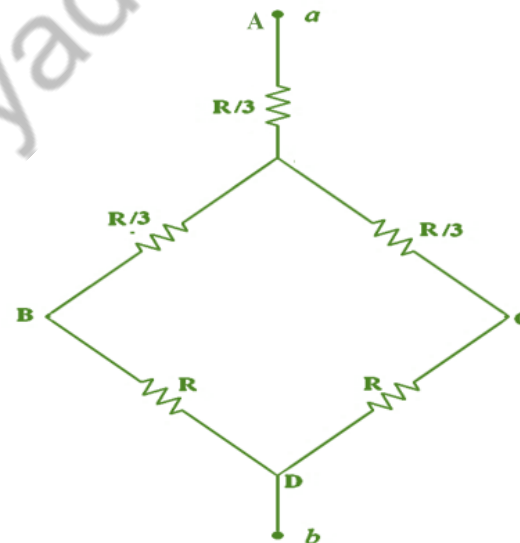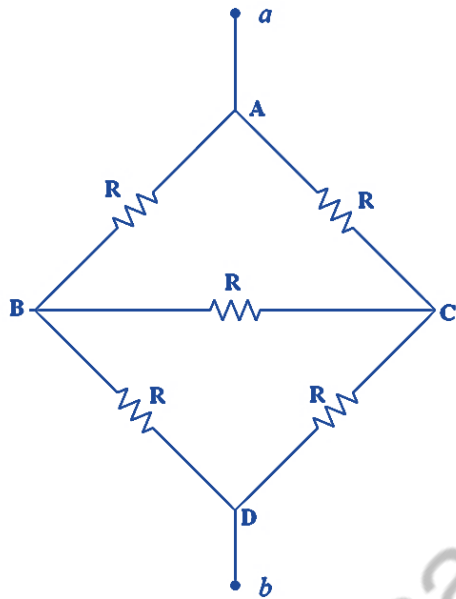




Problem 2

Obtain the equivalent resistance R_{ab} for the circuit and use it to find current i .

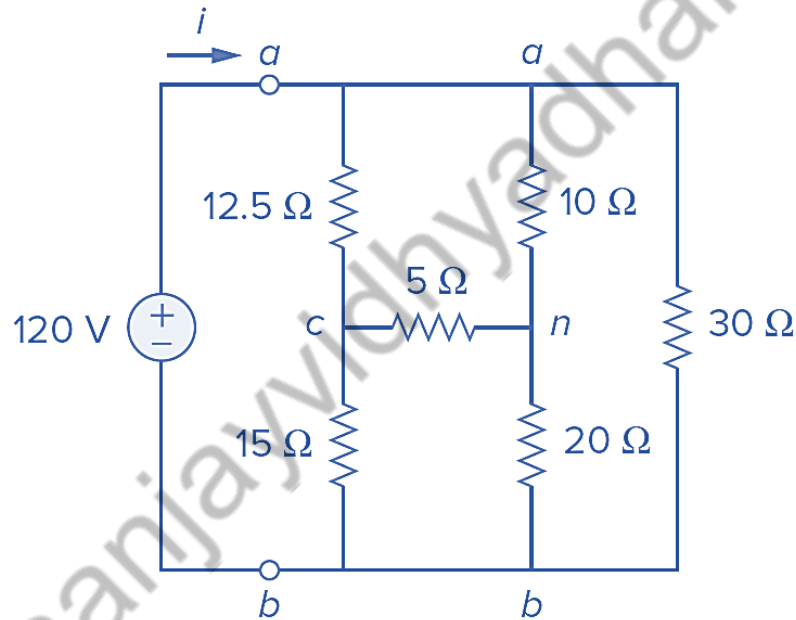

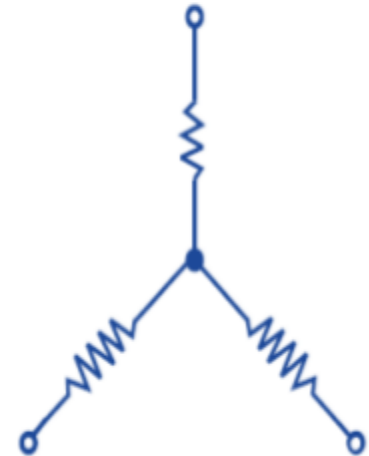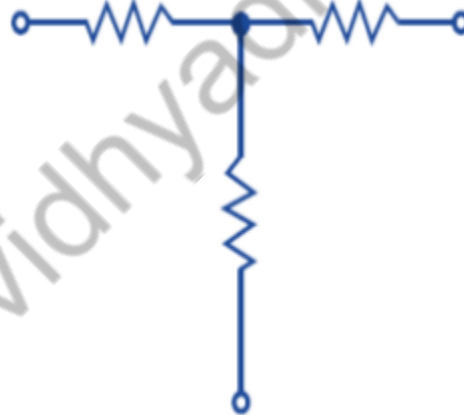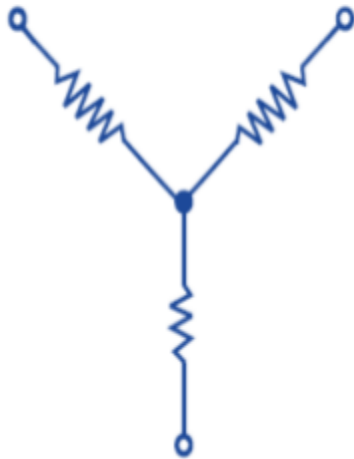Problem 2


Three ways in which star connection may appear in a circuit.



sanjayvidhyadharan.in

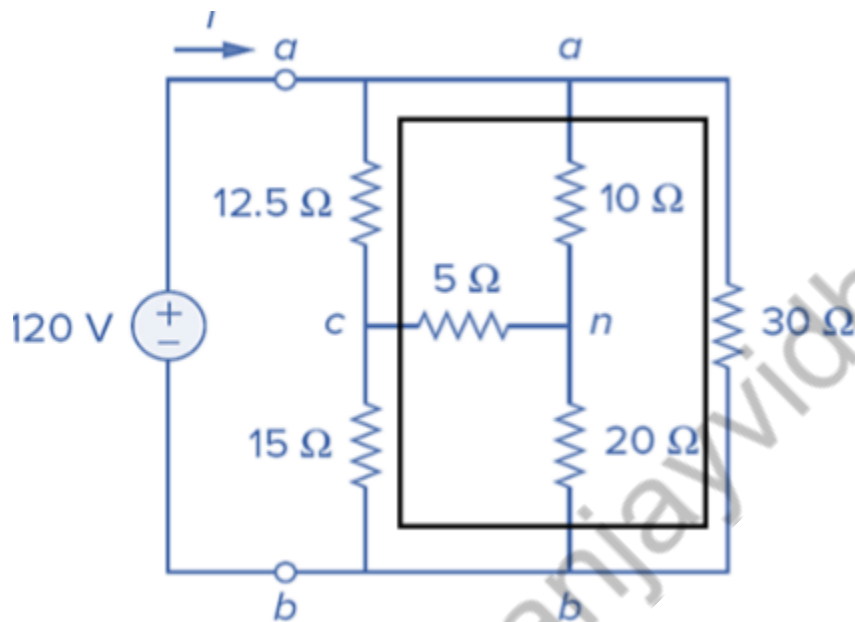Problem 2

Obtain the equivalent resistance R_{ab} for the circuit and use it to find current i .



$$R_1 = 5 + 10 + \frac{5 \times 10}{20} = 17.5 \text{ ohms}$$

(comes in parallel with 12.5 Ω)

$$R_2 = 5 + 20 + \frac{5 \times 20}{10} = 35 \text{ ohms}$$

(comes in parallel with 15 Ω)


$$R_3 = 10 + 20 + \frac{10 \times 20}{5} = 70 \text{ ohms}$$

(comes in parallel with 30 Ω)

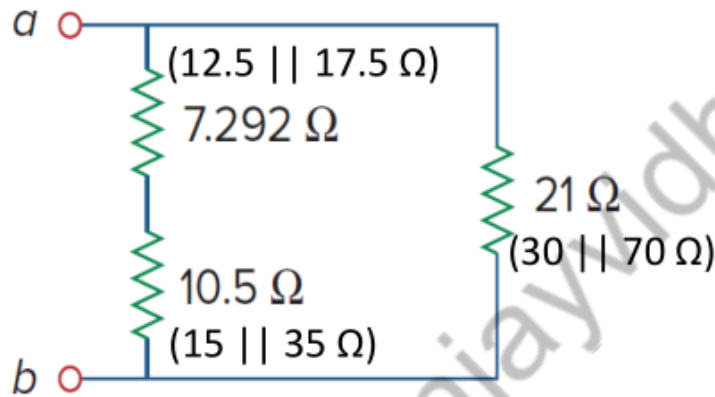Problem 2

Obtain the equivalent resistance R_{ab} for the circuit and use it to find current i .


Combining the three pairs of resistors in parallel, we obtain.




$$R_{ab} = (7.292 + 10.5) \parallel 21 = \frac{17.792 \times 21}{17.792 + 21} = 9.632 \text{ ohms}$$

$$i = \frac{v_s}{R_{ab}} = \frac{120}{9.632} = 12.458 A$$

Problem 3

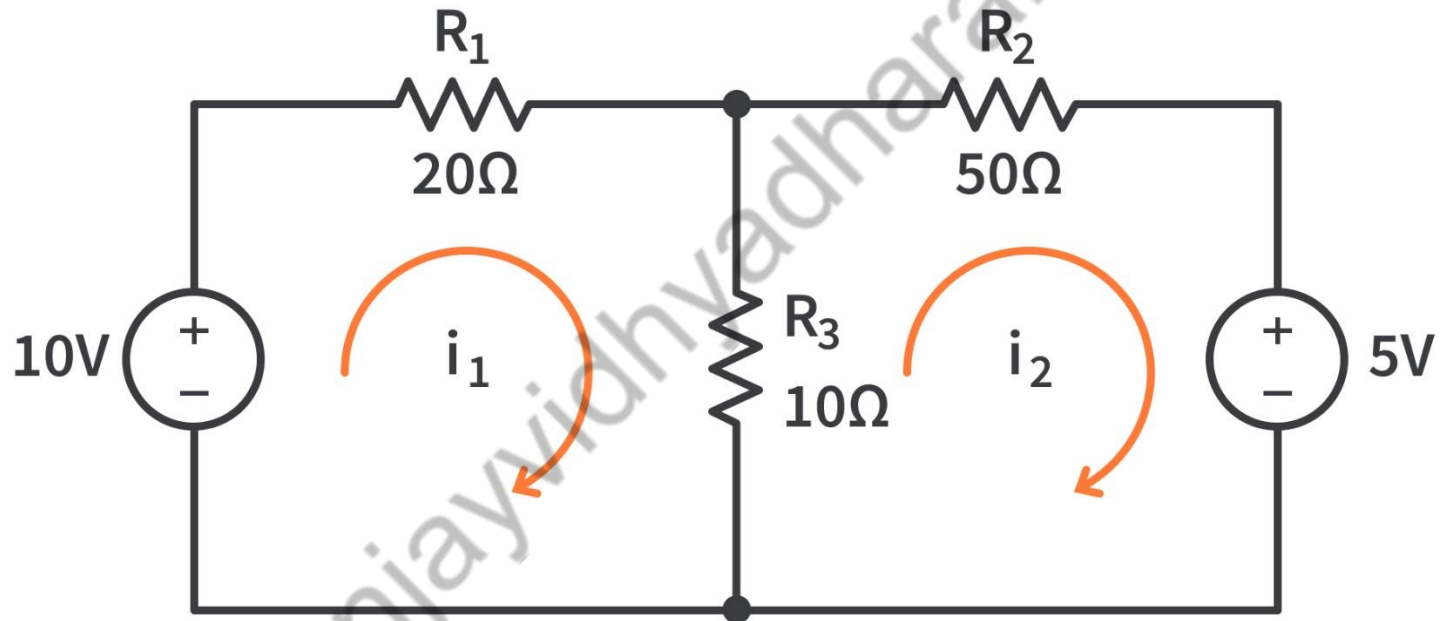

Problem 3

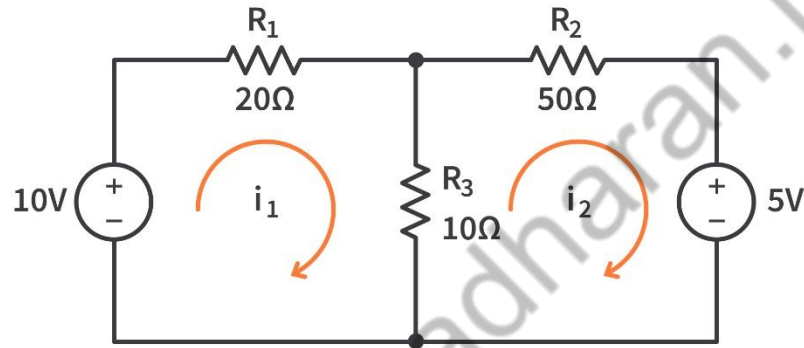

$$10V = i_1(20) + (i_1 - i_2)(10)$$

$$10V + 10i_2 = 30i_1$$

$$i_1 = \frac{1}{3}V + \frac{1}{3}i_2$$

$$-5V = (i_2 - i_1)(10) + i_2(50)$$

$$-60i_2 + 10i_1 = 5$$


$$-60i_2 + 10\left(\frac{1}{3} + \frac{1}{3}i_2\right) = 5$$

$$i_2 = -\frac{5}{170} = -\frac{1}{34} = -0.0294A$$

$$i_1 = \frac{1}{3} + \frac{1}{3}(-0.0294) = 0.324$$


Problem 4

Supermesh

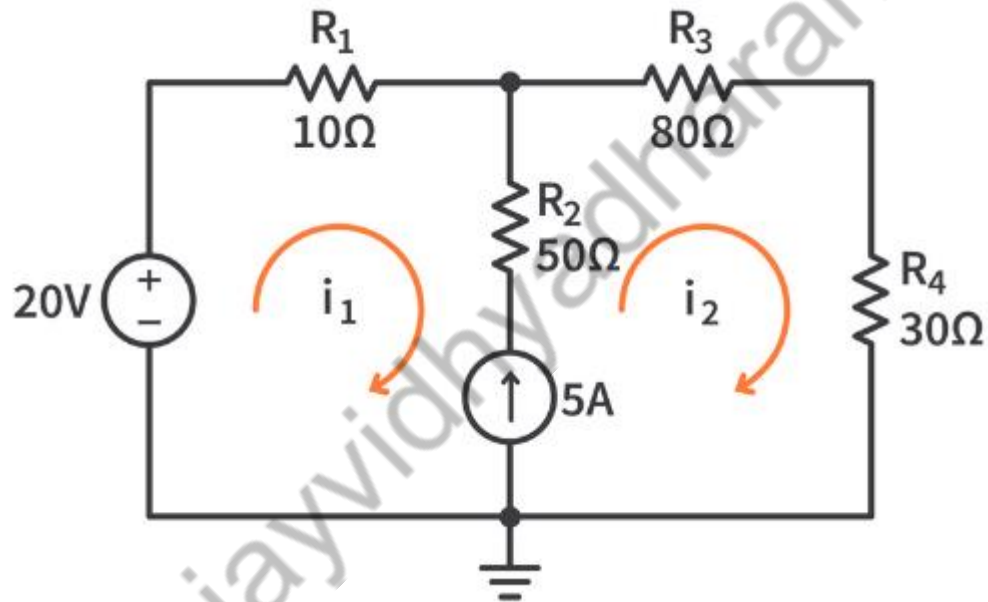

Problem 4

Supermesh

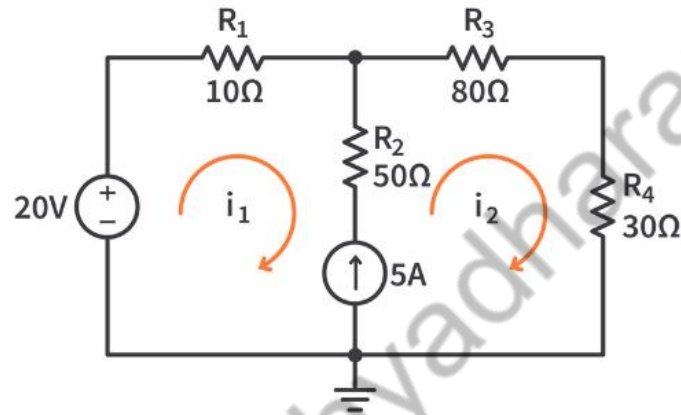

$$+20V - 10i_1 - 80i_2 - 30i_2 = 0$$


$$20 = 10i_1 + 110i_2$$

$$5 + i_1 - i_2 = 0$$

$$i_1 = -\frac{53}{12}A$$

$$i_2 = \frac{7}{12}A$$


Problem 5

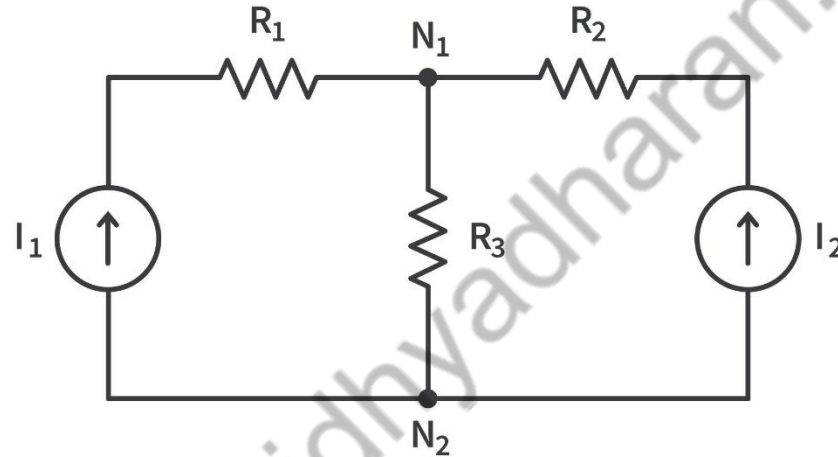

$$R_1 = 10 \quad R_2 = 20 \quad R_3 = 30 \quad I_1 = 1\text{A} \quad I_2 = 2\text{A}$$

sanjayvidhyadharam.in

Problem 5

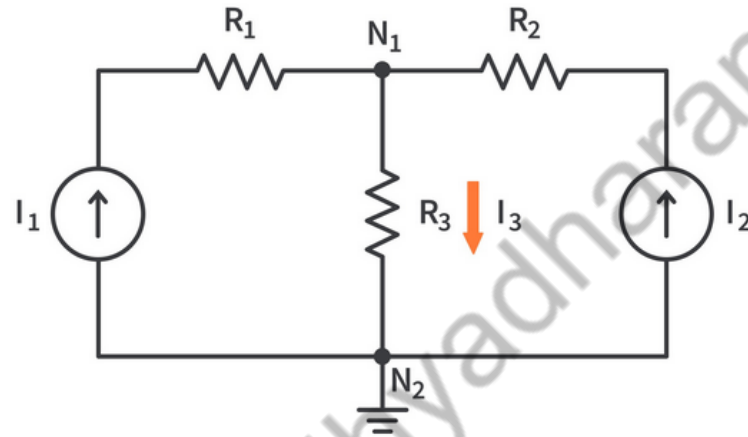


$$R_1 = 10 \quad R_2 = 20 \quad R_3 = 30 \quad I_1 = 1A \quad I_2 = 2A$$

$$I_1 + I_2 = I_3$$


$$V_1 = 90$$

Problem 6

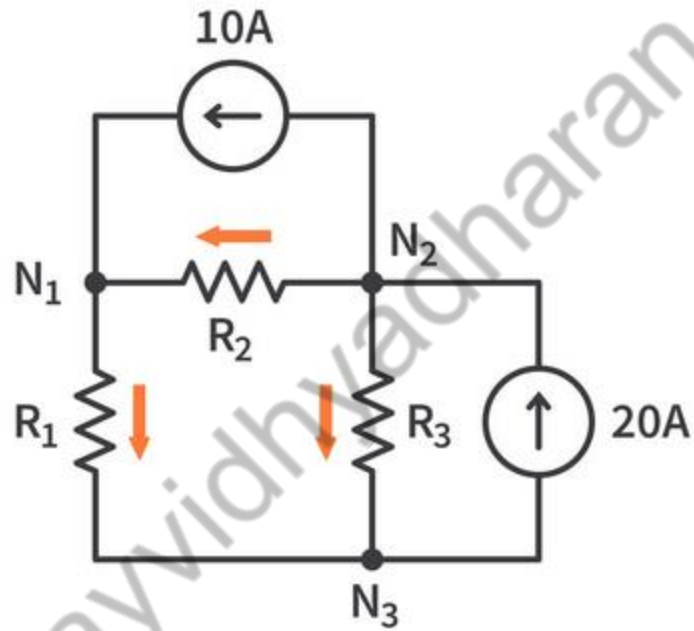

$$R_1 = 10 \quad R_2 = 20 \quad R_3 = 30$$

Problem 6

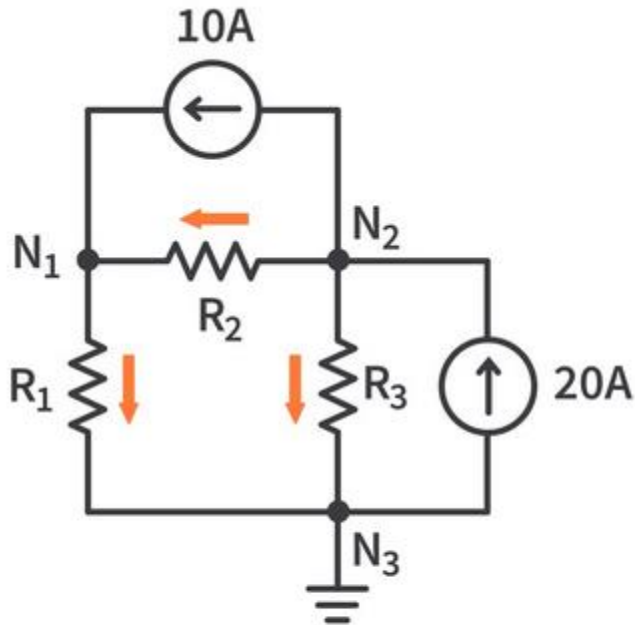

$$R_1 = 10 \quad R_2 = 20 \quad R_3 = 30$$

At Node1:

$$10A + \frac{(V_2 - V_1)}{20} - \frac{V_1}{10} = 0$$


At Node2:

$$20A - 10A - \frac{(V_2 - V_1)}{20} - \frac{V_2}{30} = 0$$


$$V_1 = \frac{400}{3}$$

$$V_2 = 200$$

Problem 7

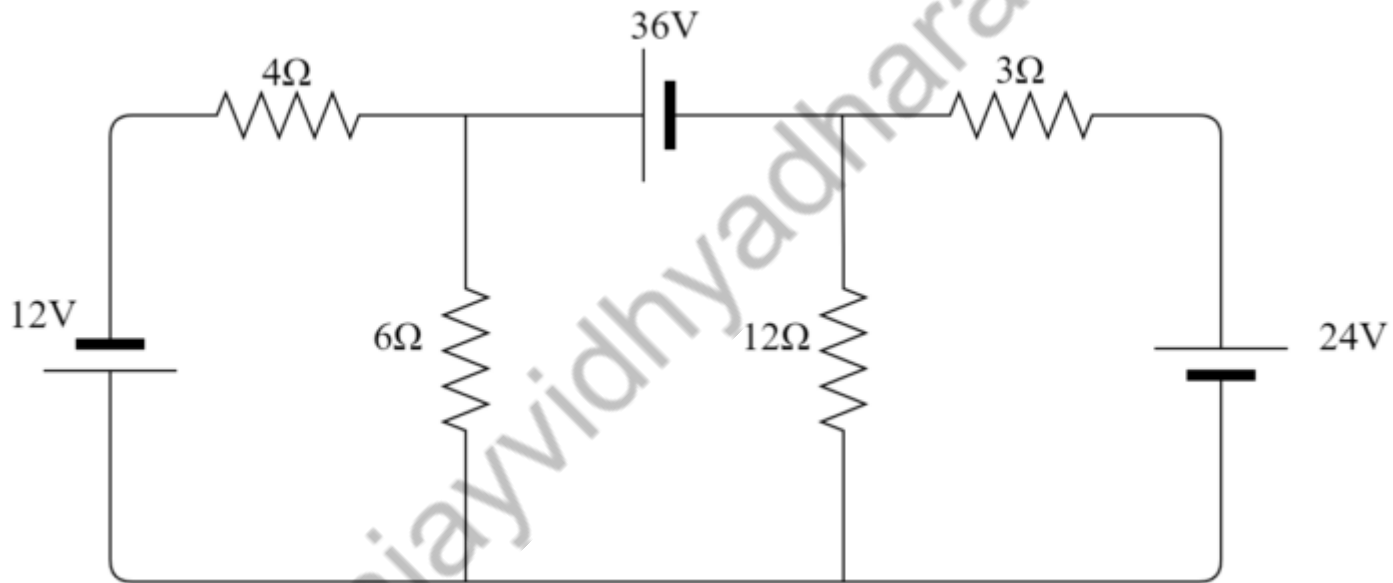

Problem 7

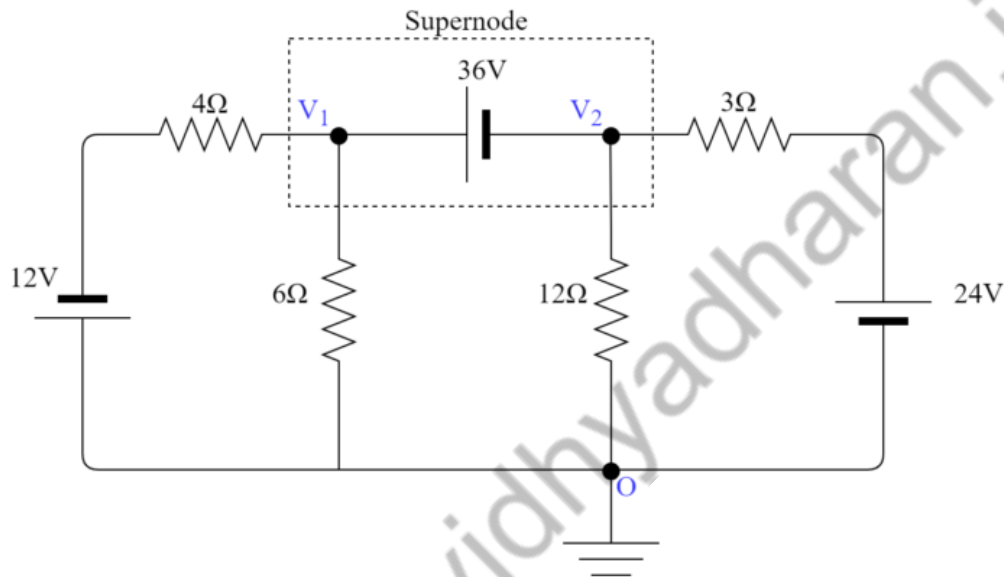

$$V_1 - V_2 = 36 \dots (i)$$

$$I_1 + I_2 + I_3 + I_4 = 0$$

or, $\frac{V_1 + 12}{4} + \frac{V_1}{6} + \frac{V_2}{12} + \frac{V_2 - 24}{3} = 0 \dots (ii)$

$$V_1 = 24 \text{ Volts}$$

$$V_2 = -12 \text{ Volts}$$

Thank you

sanjayvidhyadharan.in