




Electrical Science: 2021-22
Tutorial 3
Thevenin's, Norton's,
Max-Power Transform and
Superposition Theorem

By Dr. Sanjay Vidhyadharan



Problem 1

Find the Thevenin equivalent resistance and Voltage

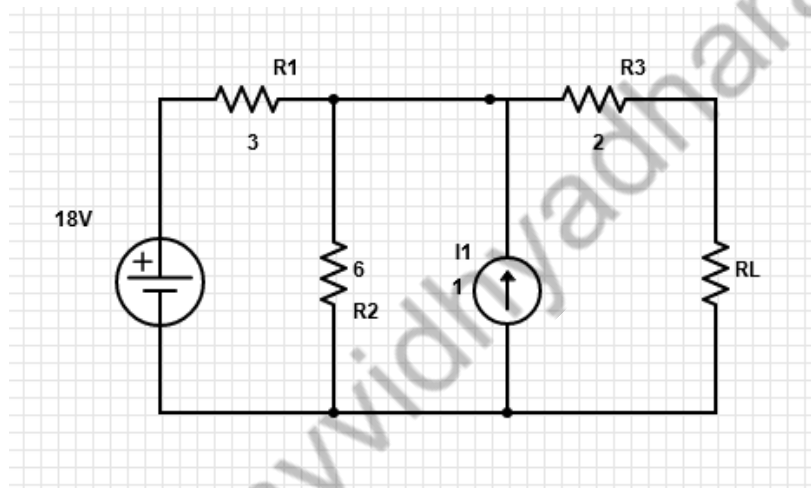

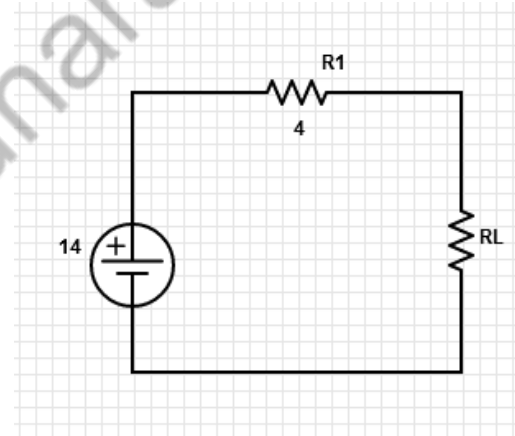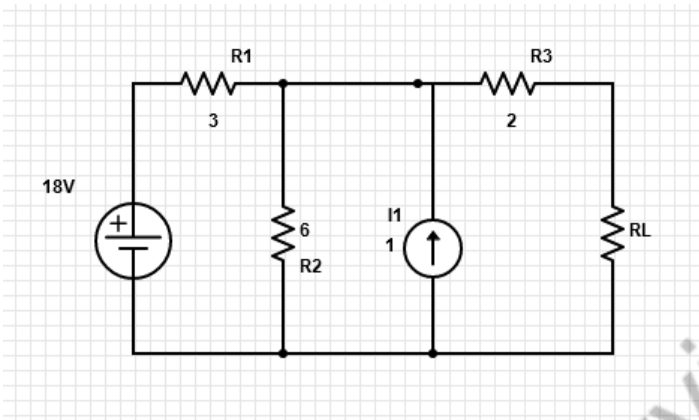Problem 1

Find the Thevenin equivalent resistance and Voltage




$$V_{Th} = \frac{18 * 6}{3 + 6} + \frac{1(6 * 3)}{6 + 3} = 14 V$$

$$R_{Th} = \frac{3 * 6}{3 + 6} + 2 = 4 Ohms$$

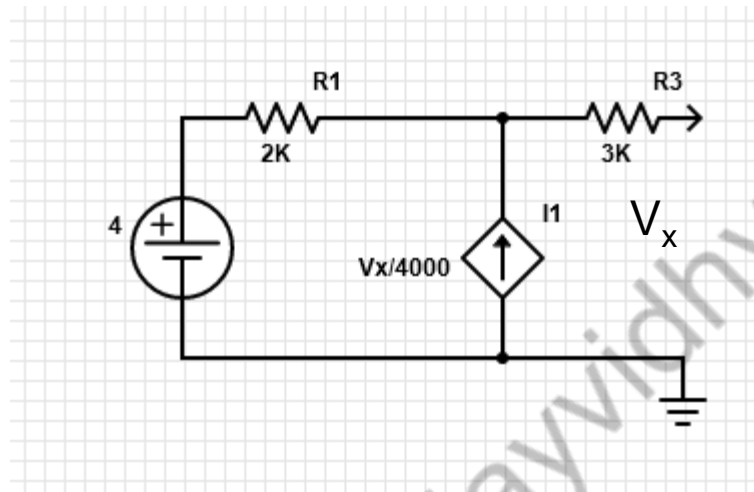Problem 2


Find the Thevenin equivalent resistance and Voltage



sanjayvidhyadharan.in

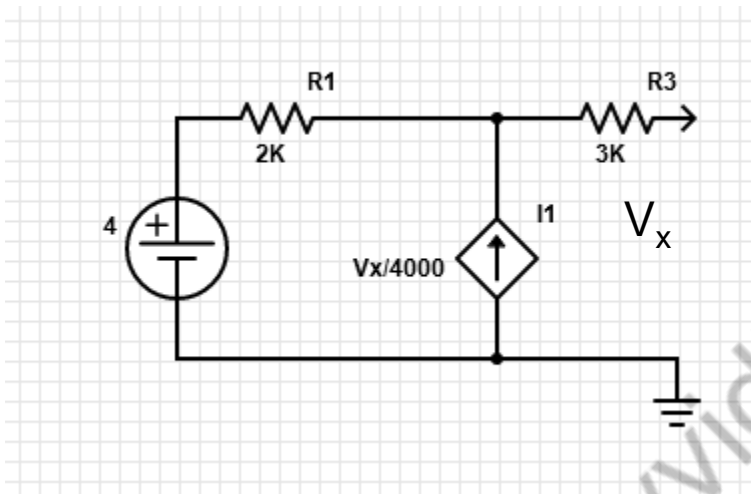Problem 2

Find the Thevenin equivalent resistance and Voltage




$$I_{sc} = \frac{4}{5K} \text{ Amp}$$

$$R_{Th} = \frac{V_{Th}}{I_{sc}} = 10K$$


$$4 = \frac{-2000 \cdot V_x}{4000} + V_x = 0.5 V_x$$

$$V_{Th} = V_x = 8V$$

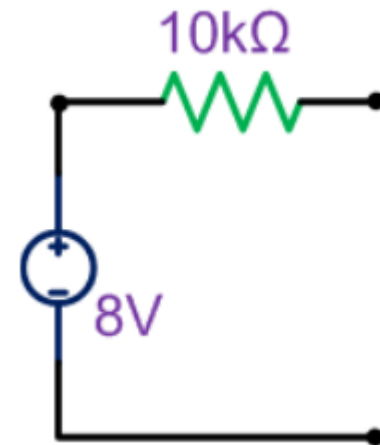


Problem 3

Find the value of R_L for maximum power transfer in the circuit of the shown figure. Find the maximum power.

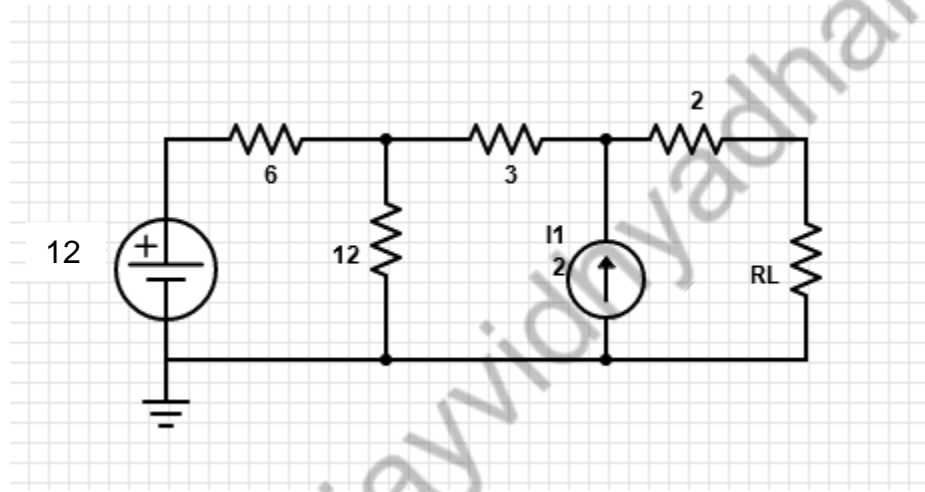

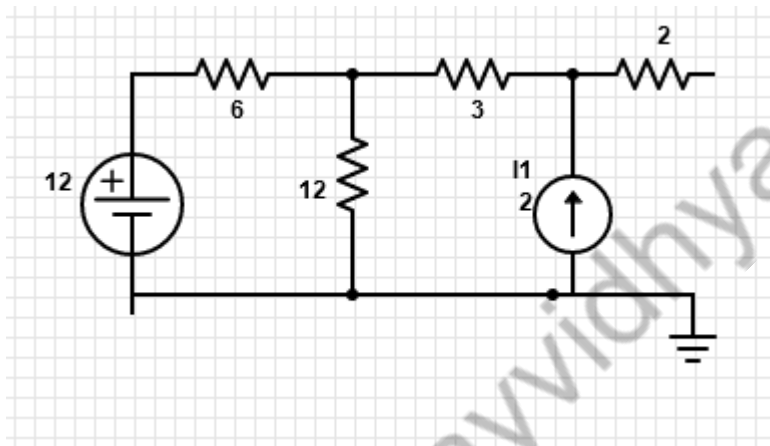Problem 3

Find the value of R_L for maximum power transfer in the circuit of the shown figure. Find the maximum power.




$$R_{Th} = 5 + \frac{6 \cdot 12}{18} = 9 \text{ Ohms}$$

$$V_{Th} = \frac{12 \cdot 12}{18} + 2 \cdot 7 = 22 \text{ V}$$

$$P_{max} = \frac{22^2}{4 \cdot 9} = 13.44 \text{ W}$$


Problem 4

Find the Thevenin equivalent circuit of the circuit in shown figure at terminals a-b

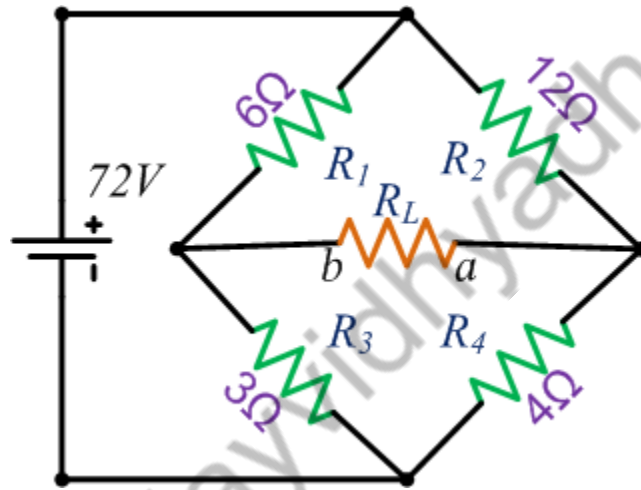

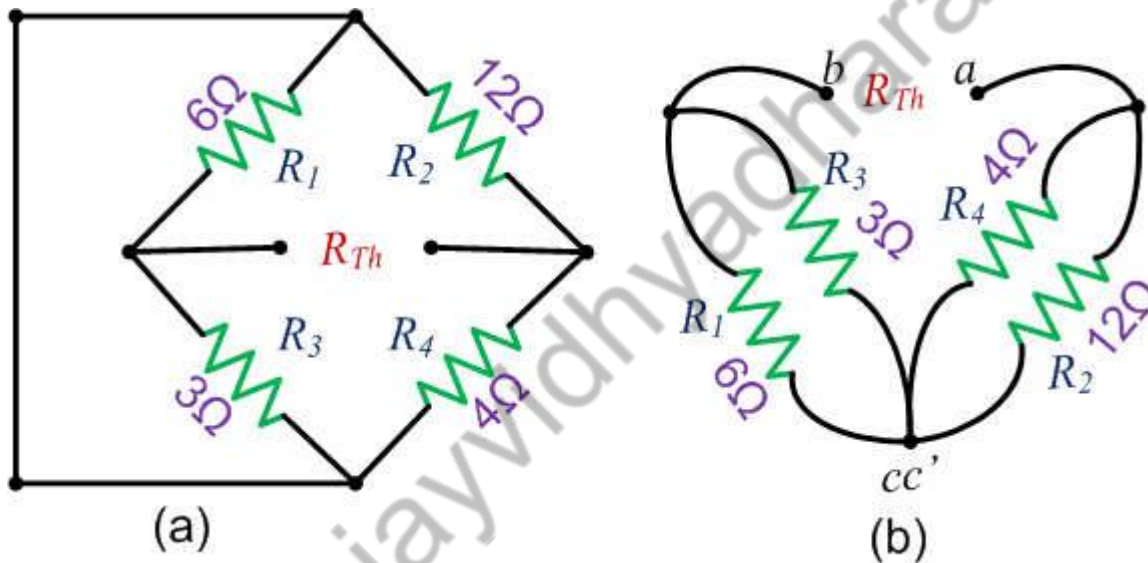Problem 4


Find the Thevenin equivalent circuit of the circuit in shown figure at terminals a-b



$$\begin{aligned} R_{Th} &= R_1 \parallel R_2 + R_3 \parallel R_4 \\ &= 6\Omega \parallel 12\Omega + 3\Omega \parallel 4\Omega \\ &= 2\Omega + 3\Omega = 5\Omega \end{aligned}$$

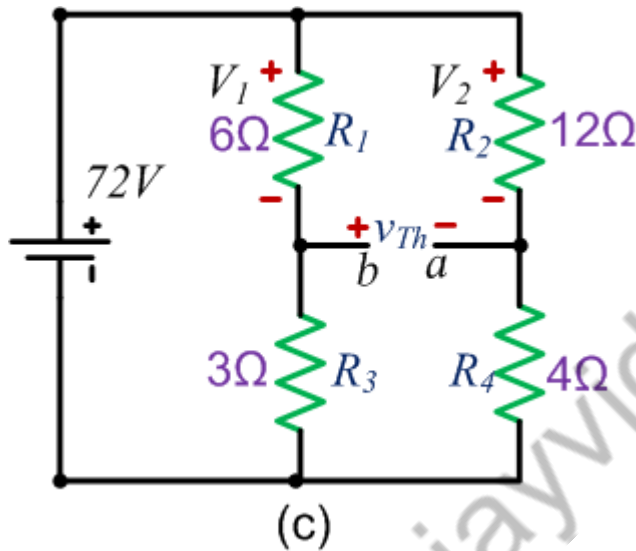Problem 4

Find the Thevenin equivalent circuit of the circuit in shown figure at terminals a-b




$$V_1 = \frac{R_1 E}{R_1 + R_3} = \frac{6 \times 72}{6 + 3} = \frac{432}{9} = 48 \text{ V}$$

$$V_2 = \frac{R_2 E}{R_2 + R_4} = \frac{12 \times 72}{12 + 4} = \frac{864}{16} = 54 \text{ V}$$


applying KVL to the top loop

$$v_{Th} = V_2 - V_1 = 54 - 48 = 6 \text{ V}$$

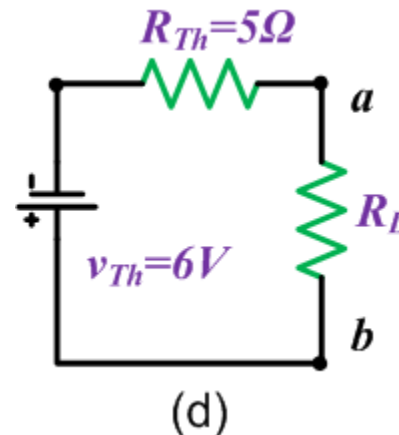


Problem 5

Find the Norton equivalent circuit of the circuit in shown figure at terminals A-B

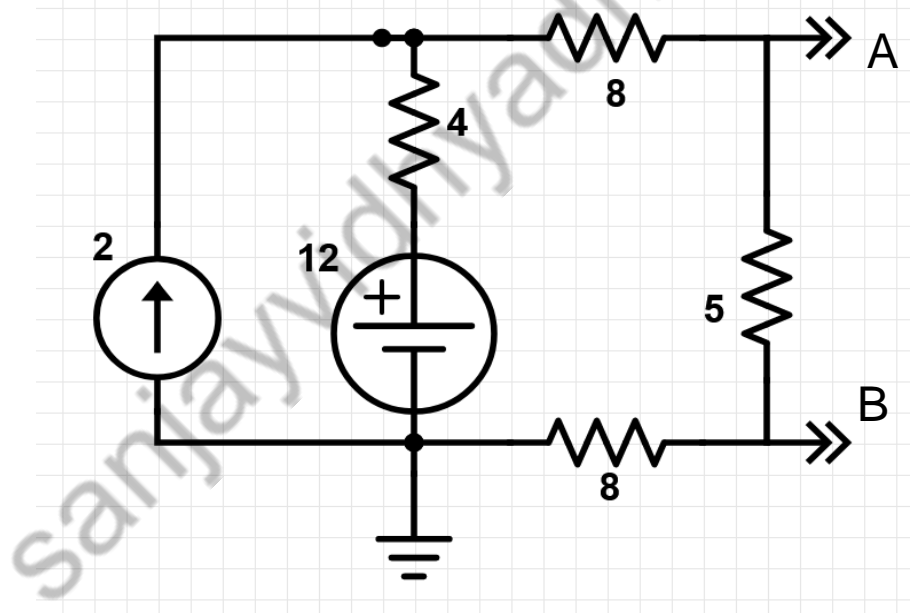


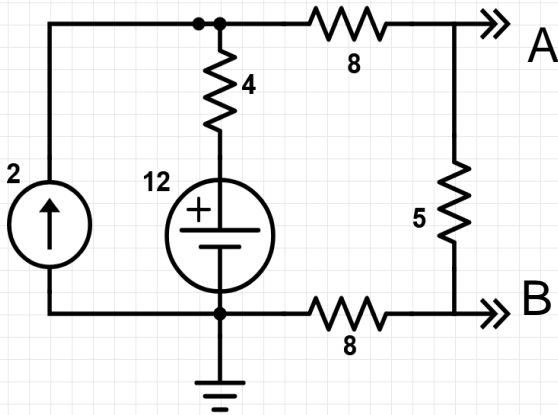Problem 5


Find the Norton equivalent circuit of the circuit in shown figure at terminals A-B


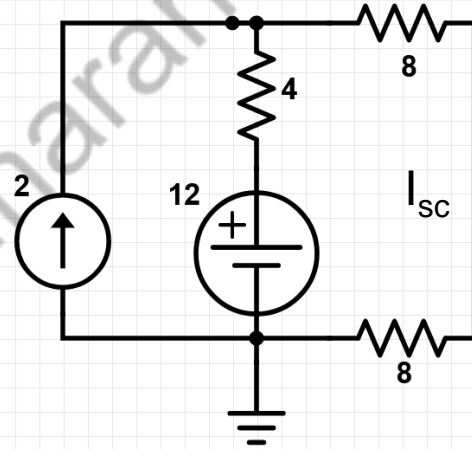
$$R_{Th} = \frac{5 * 20}{5 + 20} = 4 \text{ Ohms}$$




$$I_{sc} = \frac{12}{20} + \frac{2 * 4}{20} = 1 \text{ A}$$

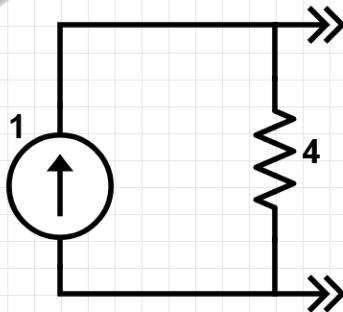


Problem 6

Find V_{CE} and V_{AG}

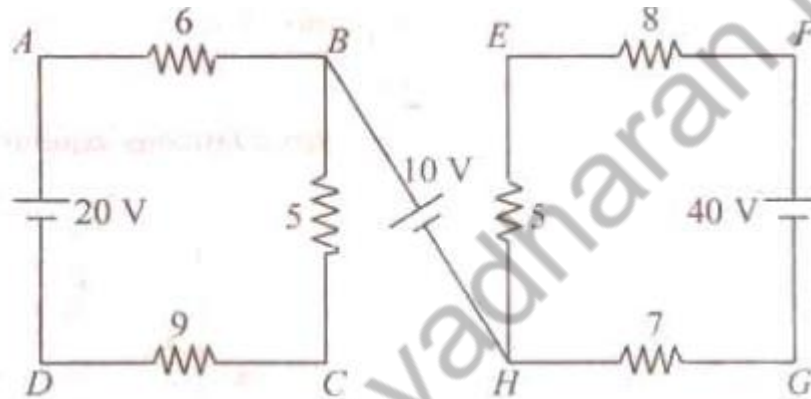

Problem 6

Find V_{CE} and V_{AG}

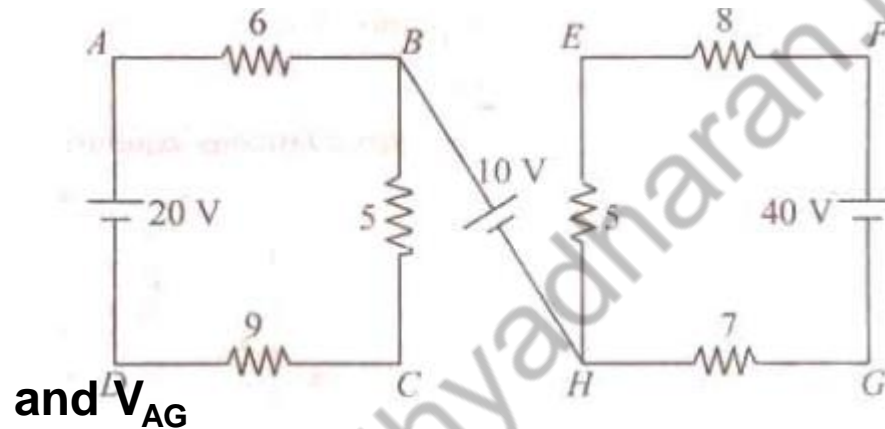


$$I_1 = \frac{20}{6 + 5 + 9} = 1 \quad I_2 = \frac{40}{8 + 5 + 7} = 2$$

$$V_{CE} = -1 * 5 + 10 - 2 * 5 = -5 V$$

$$V_{AG} = 1 * 6 + 10 + 2 * 7 = 30 V$$



Problem 7

Find V

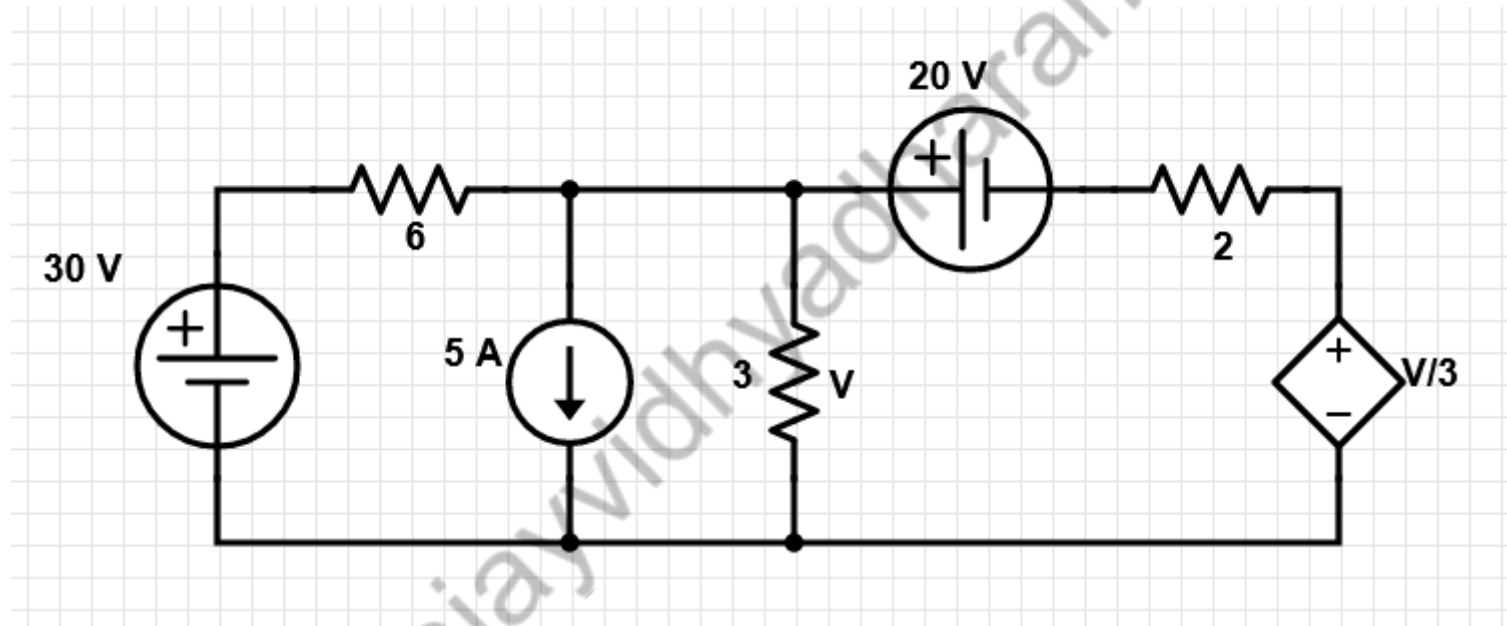


Problem 7

Find V

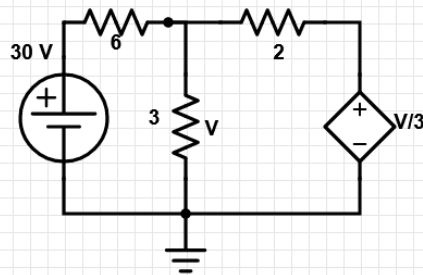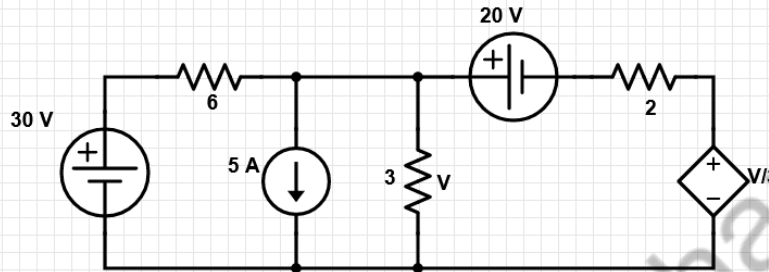


$$\frac{30-v}{6} - \frac{v}{3} + \frac{\left(\frac{v}{3}-v\right)}{2} = 0$$

$$v = 6 \text{ V}$$

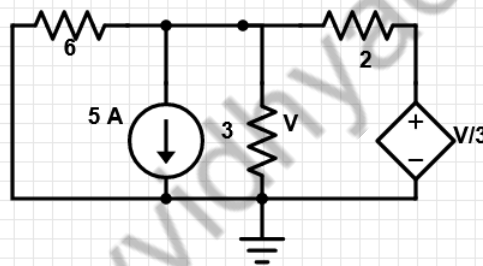

$$\frac{-v}{6} - 5 - \frac{v}{3} + \frac{\left(\frac{v}{3}-v\right)}{2} = 0$$

$$v = -6 \text{ V}$$

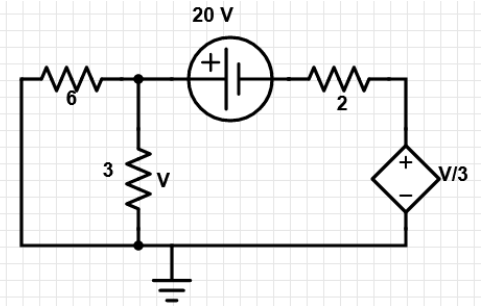

$$20 + \frac{v}{3} = i(2 + 2)$$

$$20 + \frac{i * 2}{3} = i(2 + 2)$$

$$i = 6 \text{ A} \quad v = 12 \text{ V}$$

$$V = 6 - 6 + 12 = 6 \text{ V}$$

Thank you

sanjayvidhyadharan.in