



BITS Pilani

Hyderabad Campus


Department of Electrical Engineering



Digital Design : 2021-22


Lab 1: Implementation of Majority Circuit using TTL Gates in Tinkercad

By Dr. Sanjay Vidhyadharan

 


74XX Series TTL ICs


7400 NAND

 

7400 Quad 2-input NAND Gates

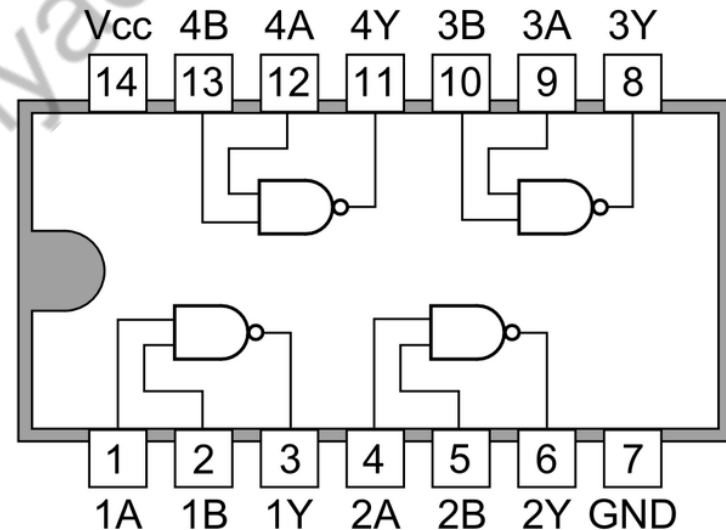

TTL Gate

 

TTL 2 input NAND Gate



74XX Series TTL ICs

7400 NAND DATA SHEET

FAIRCHILD
SEMICONDUCTOR™

September 1986
Revised July 2001

DM7400

Quad 2-Input NAND Gates

General Description

This device contains four independent gates each of which performs the logic NAND function.

Ordering Code:

Order Number	Package Number	Package Description
DM7400M	M14A	14-Lead Small Outline Integrated Circuit (SOIC), JEDEC MS-012, 0.150" Narrow
DM7400N	N14A	14-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300" Wide

Devices also available in Tape and Reel. Specify by appending the suffix letter "X" to the ordering code.

Connection Diagram

Function Table

$Y = \overline{AB}$

Inputs		Output
A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

H = HIGH Logic Level
L = LOW Logic Level

DM7400 Quad 2-Input NAND Gates



74XX Series TTL ICs

7400 NAND DATA SHEET


Recommended Operating Conditions

Symbol	Parameter	Min	Nom	Max	Units
V_{CC}	Supply Voltage	4.75	5	5.25	V
V_{IH}	HIGH Level Input Voltage	2			V
V_{IL}	LOW Level Input Voltage			0.8	V
I_{OH}	HIGH Level Output Current			-0.4	mA
I_{OL}	LOW Level Output Current			16	mA
T_A	Free Air Operating Temperature	0		70	°C

sanjayvidhyadharam

Sample Run


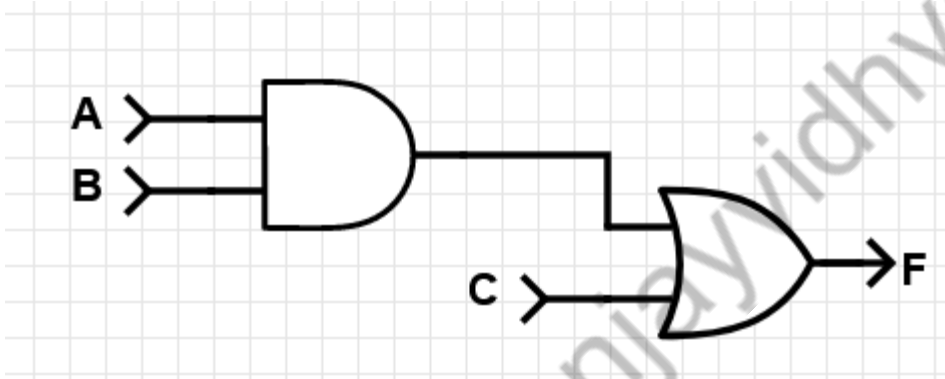
$F = AB + C$ (Implementation with AND & OR Gates)



A	B	C	F
0	0	0	0
0	1	0	0
1	0	0	0
1	1	0	1
0	0	1	1
0	1	1	1
1	0	1	1
1	1	1	1

Sample Run

  $F = AB + C$ Implementation with NAND Gates



Problem Definition for DD: Lab 1

Problem 1: Implement the Majority Circuit

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F = AB + BC + CA + ABC$$

$$F = AB + BC + CA$$

Problem definition for DD: Lab 1


Problem 1: Implement the Majority Circuit

Run1 : Implement F with AND & OR gates

Check output for all combinations of Input

$$F = AB + BC + CA$$

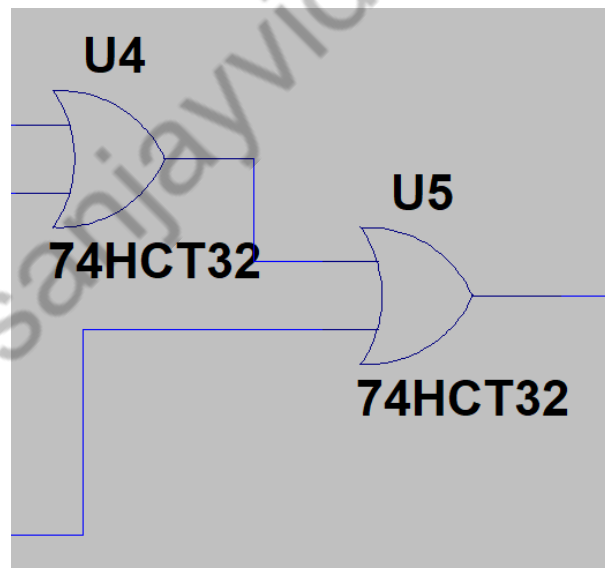Hint: Use Three 2 i/p AND & Two 2 i/p OR GATE



Problem definition for DD: Lab 1

Problem 1: Implement the Majority Circuit

Run1 : Implement F with NAND gates

$$F = AB + BC + CA$$

Check output for all combinations of Input

Hint: Use Three 2 i/p NAND & One 3 i/p NAND GATE

Demonstration