



# **Electrical Science: 2021-22**

## **Lecture 17**

### **Three Phase AC Circuits - Part 1**

**By Dr. Sanjay Vidhyadharan**

# Three Phase Alternating Currents

## Locomotive Engines



## Electric Automobiles




Three phase  
AC motor  
Engine



# Three Phase Alternating Currents

## Pumps


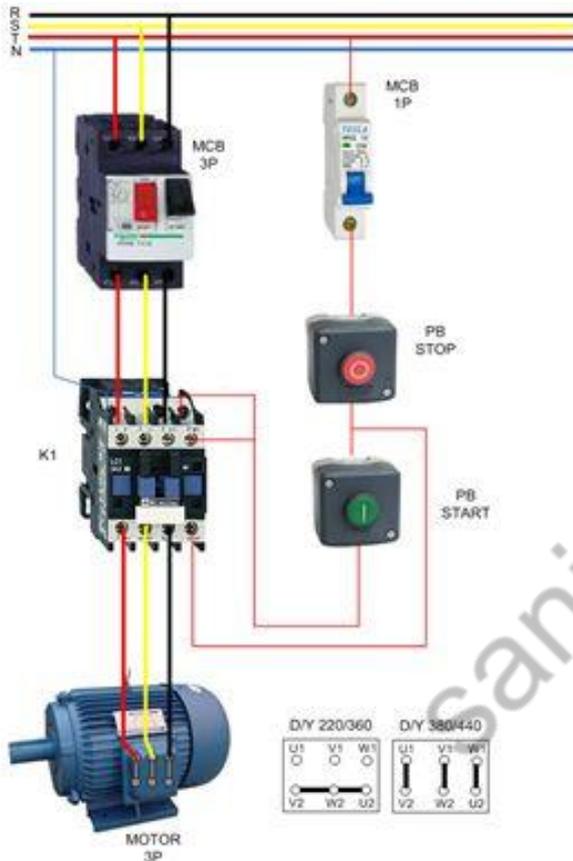


## Welding Machines




# Three Phase Alternating Currents

## Single-Phase System:

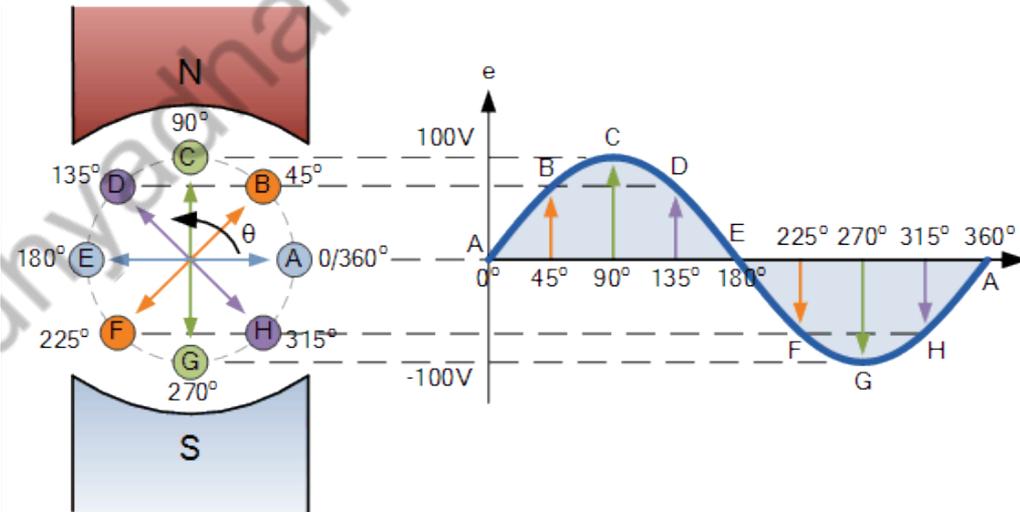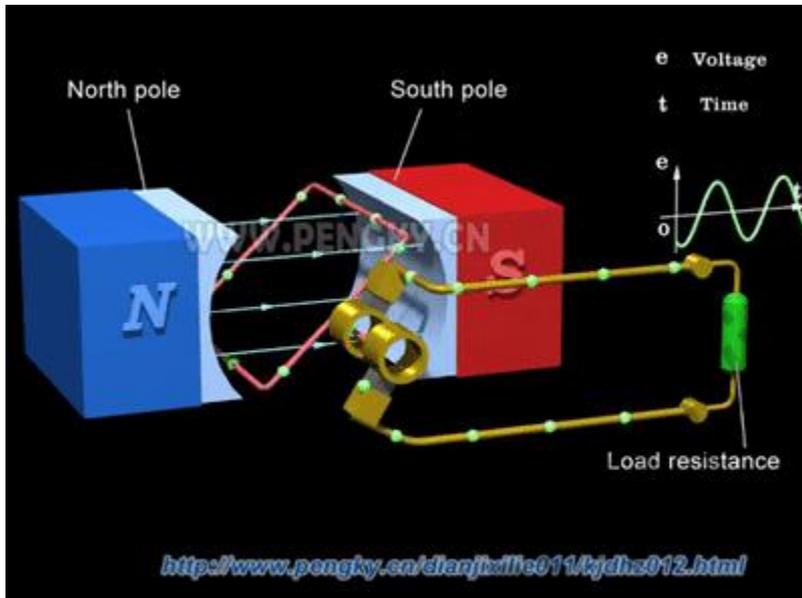

# Three Phase Alternating Currents


Three-Phase System:

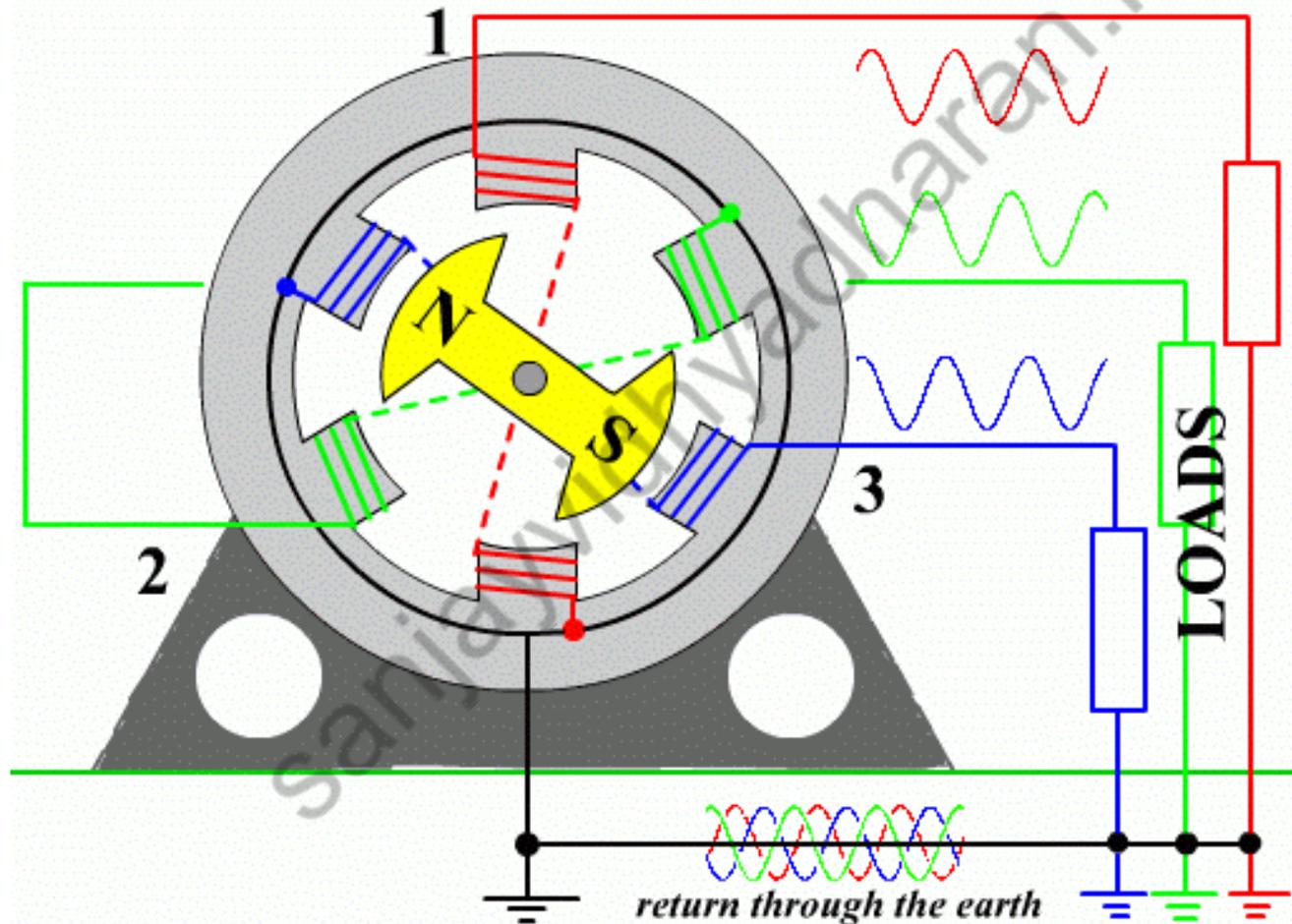
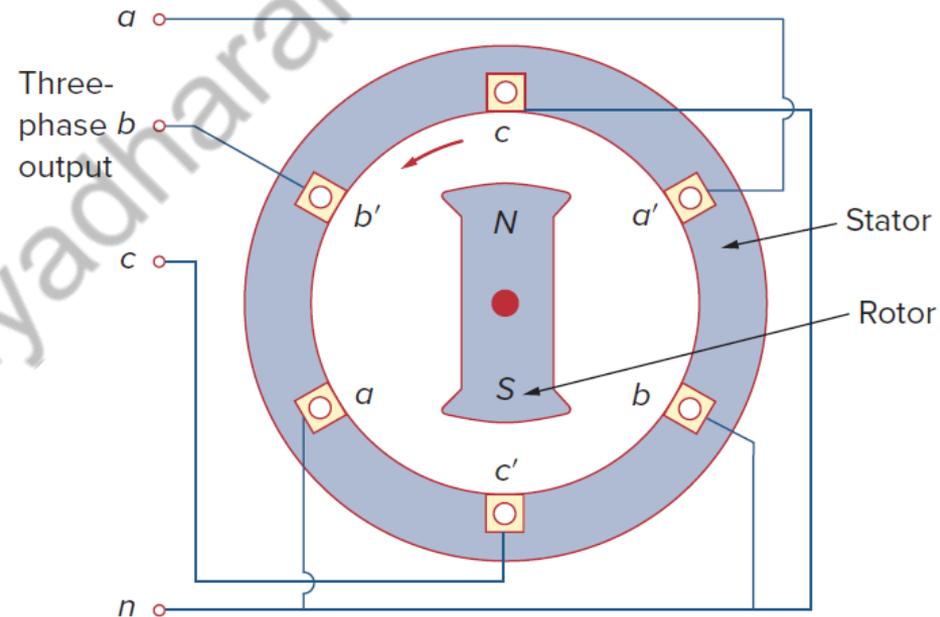
# BALANCED THREE-PHASE VOLTAGES


The generator basically consists of a

- Rotating magnet (called the rotor).
- Stationary winding (called the stator).
- Three separate windings or coils with terminals  $a$ - $a'$ ,  $b$ - $b'$ , and  $c$ - $c'$  are physically placed  $120^\circ$  apart around the stator.



Three-phase generator

# BALANCED THREE-PHASE VOLTAGES

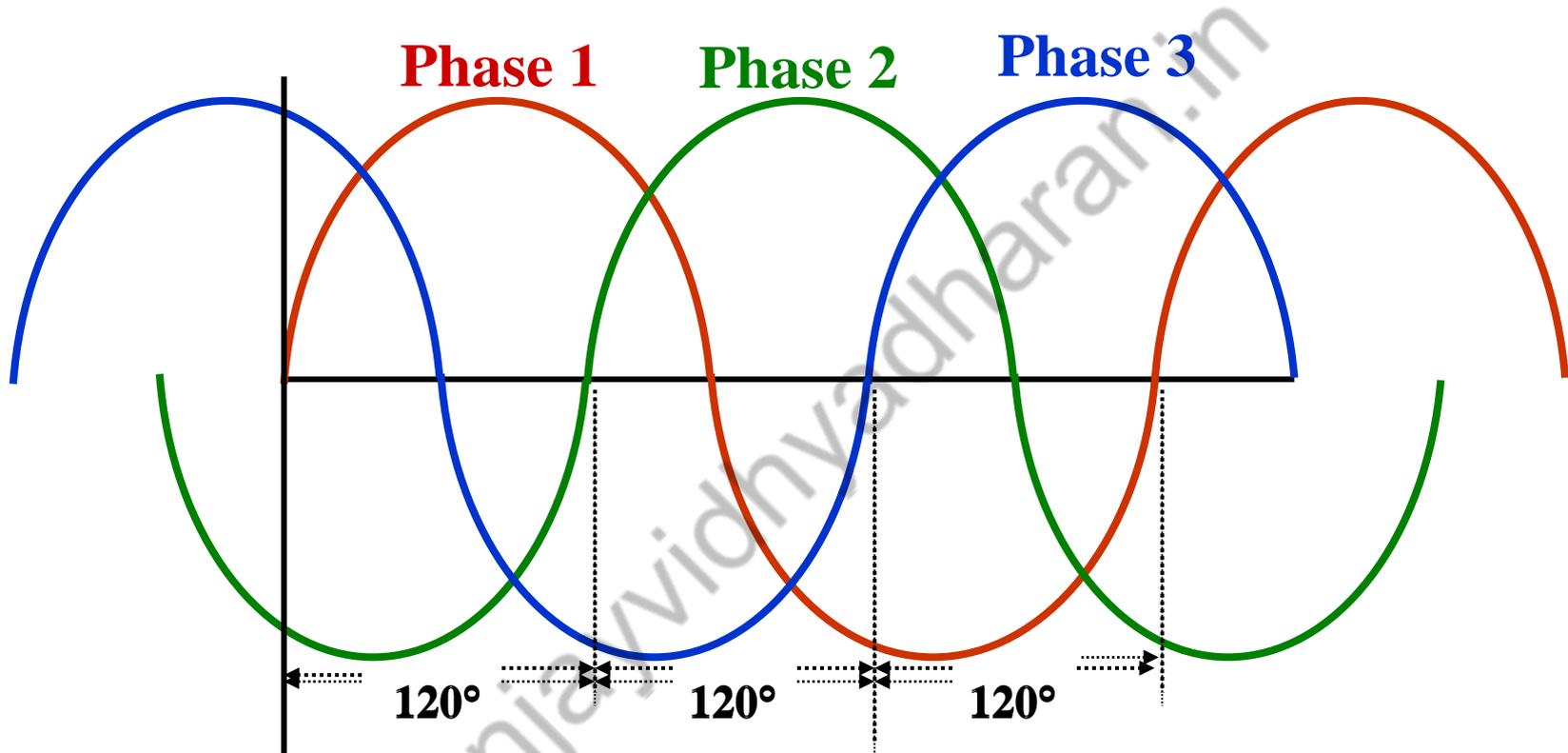


Phase 2 lags phase 1 by  $120^\circ$ .

Phase 2 leads phase 3 by  $120^\circ$ .

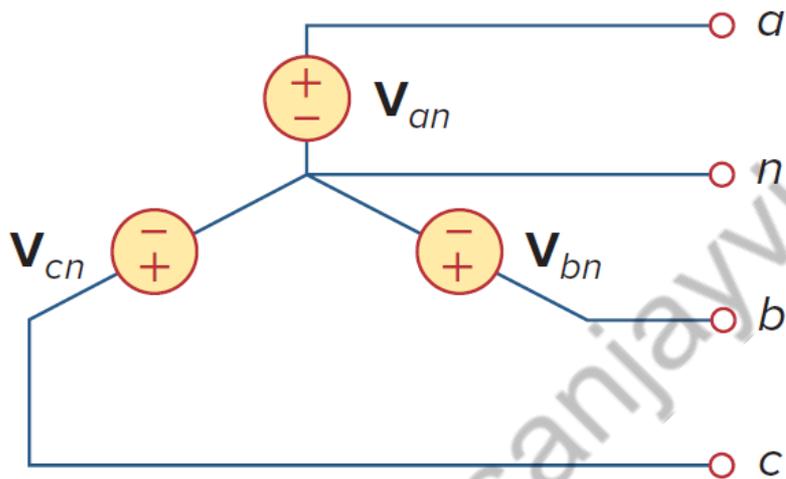
# THREE-PHASE VOLTAGES

A typical three-phase system consists of three voltage sources connected to loads by three or four wires (or transmission lines).

The voltage sources can be either wye connected or delta-connected.



Y-connected source

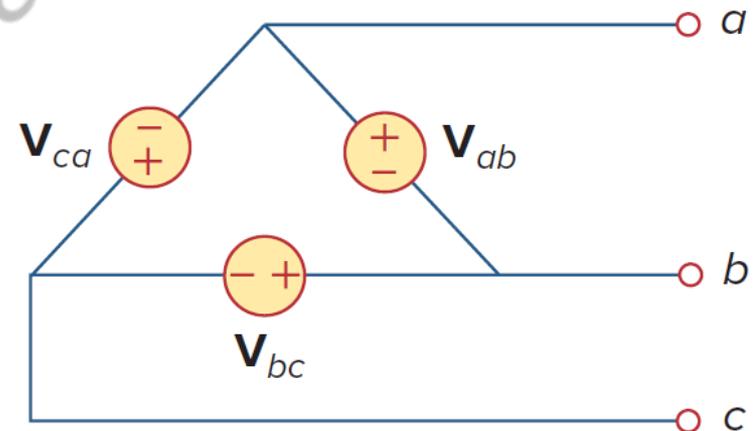


Δ-connected source
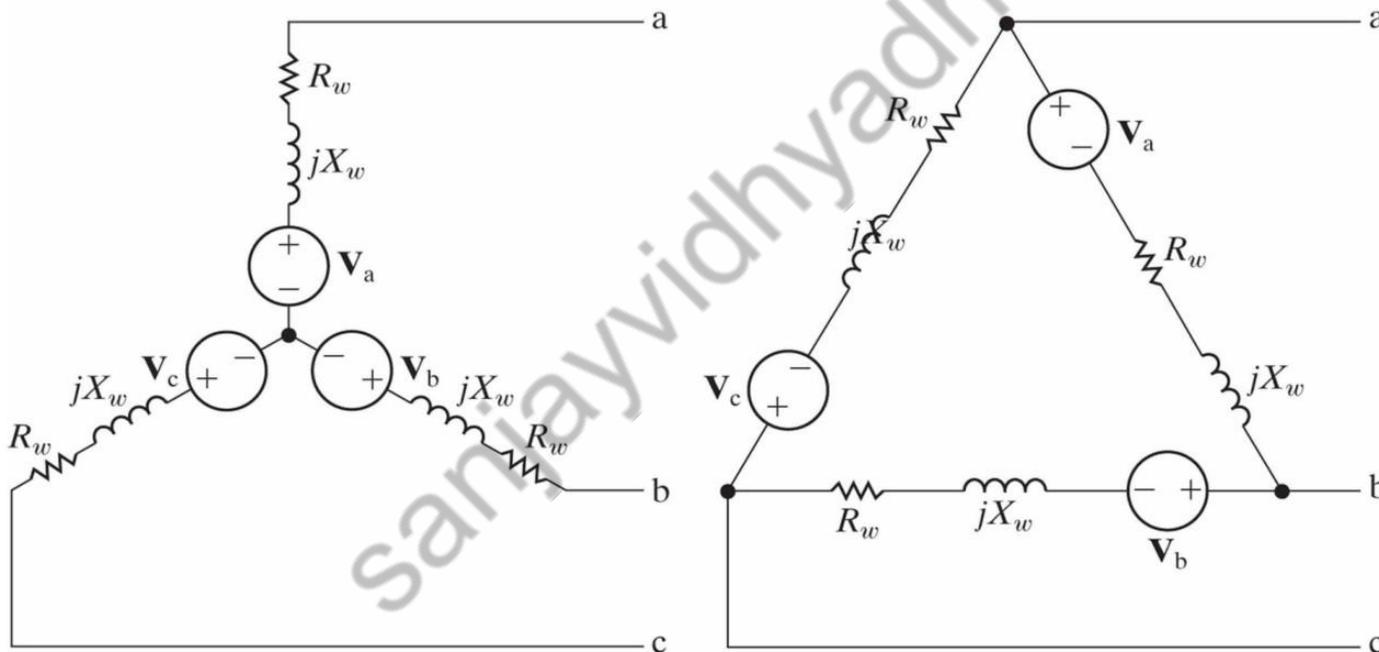
# THREE-PHASE VOLTAGES

A typical three-phase system consists of three voltage sources connected to loads by three or four wires (or transmission lines).

The voltage sources can be either wye connected or delta-connected.





Y-connected source

Δ-connected source

# WYE CONNECTED THREE-PHASE SYSTEM

## Balanced Phase Voltage

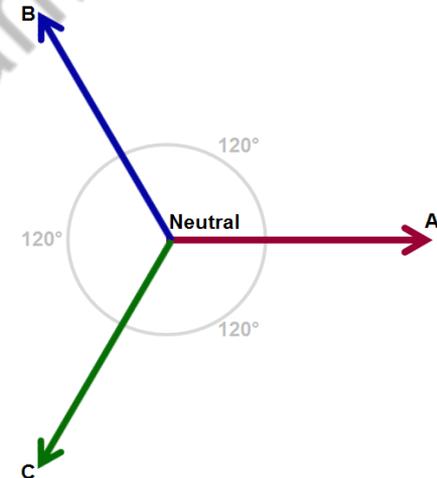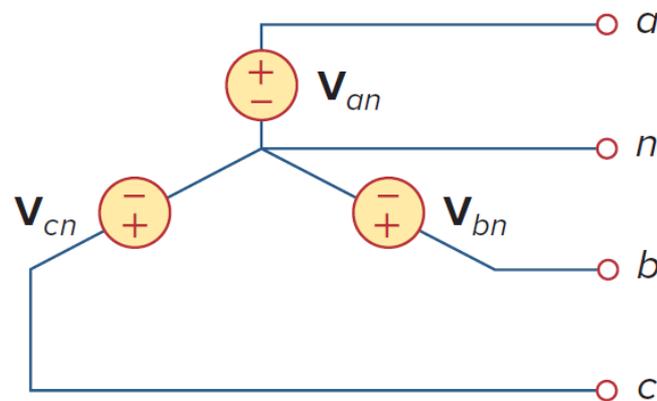

Phase voltages: voltages between lines a, b, and c and the neutral line n ( $V_{an}$ ,  $V_{bn}$ , and  $V_{cn}$ ).

If the voltage sources have the same amplitude and frequency  $\omega$  and are out of phase with each other by  $120^\circ$ , the voltages are said to be balanced.

$$V_{an} + V_{bn} + V_{cn} = 0$$

$$|V_{an}| = |V_{bn}| = |V_{cn}|$$

# WYE CONNECTED THREE-PHASE SYSTEM

## Balanced Phase Voltage


abc Sequence or Positive Sequence

Rotor has to rotate counter-clockwise.

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

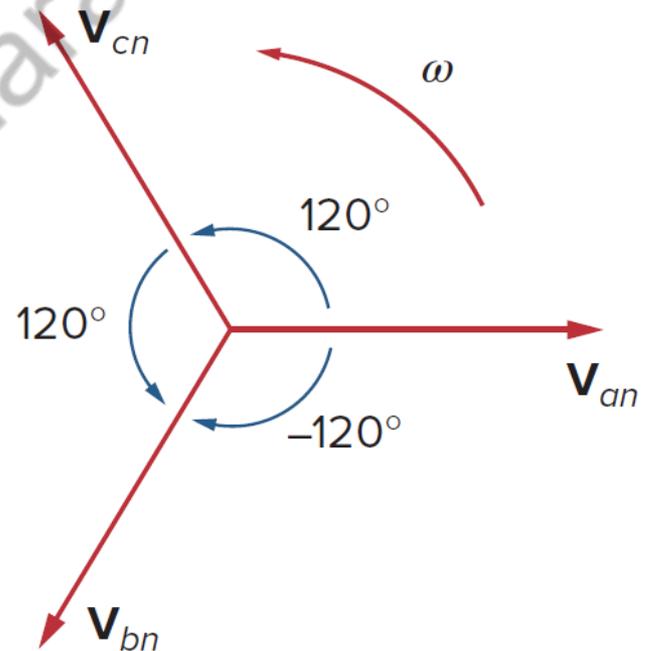
$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$



where  $V_p$  is the effective or **rms value** of the phase voltages.
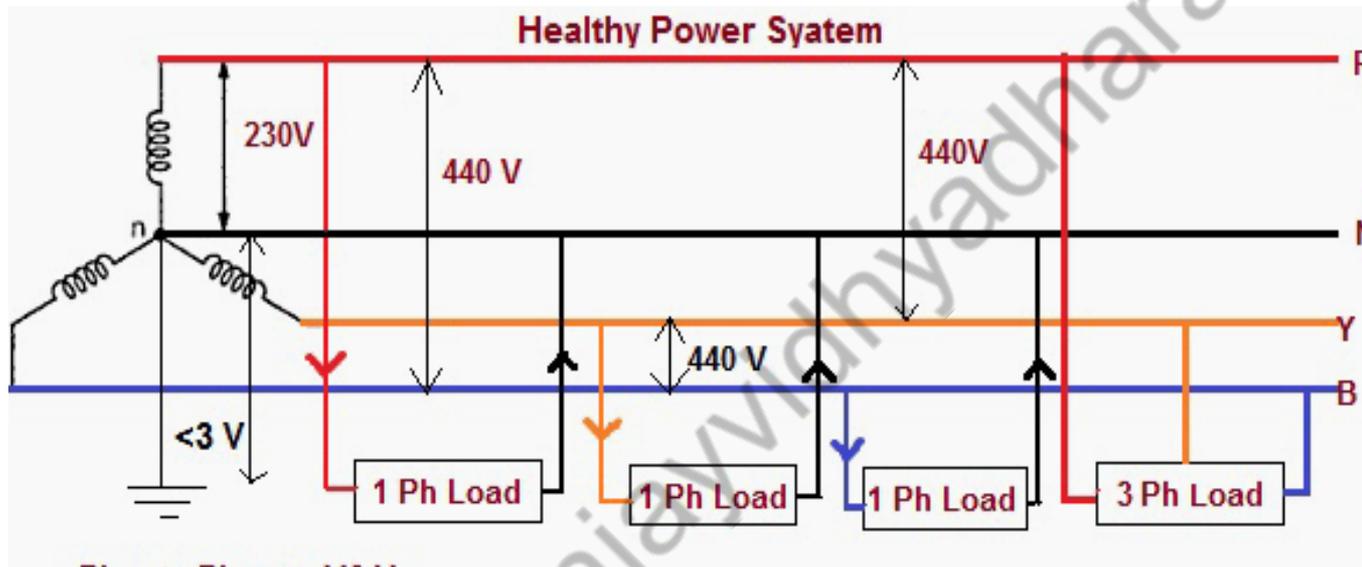
# WYE CONNECTED PHASE VOLTAGE

Phase voltage is measured between the neutral and any line: line to neutral voltage



Phas to Phase = 440 V  
Phas to Neutral = 230 V  
Neutral to Ground < 3 V


$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ$$

$$V_{cn} = V_p \angle -240^\circ = V_p \angle +120^\circ$$
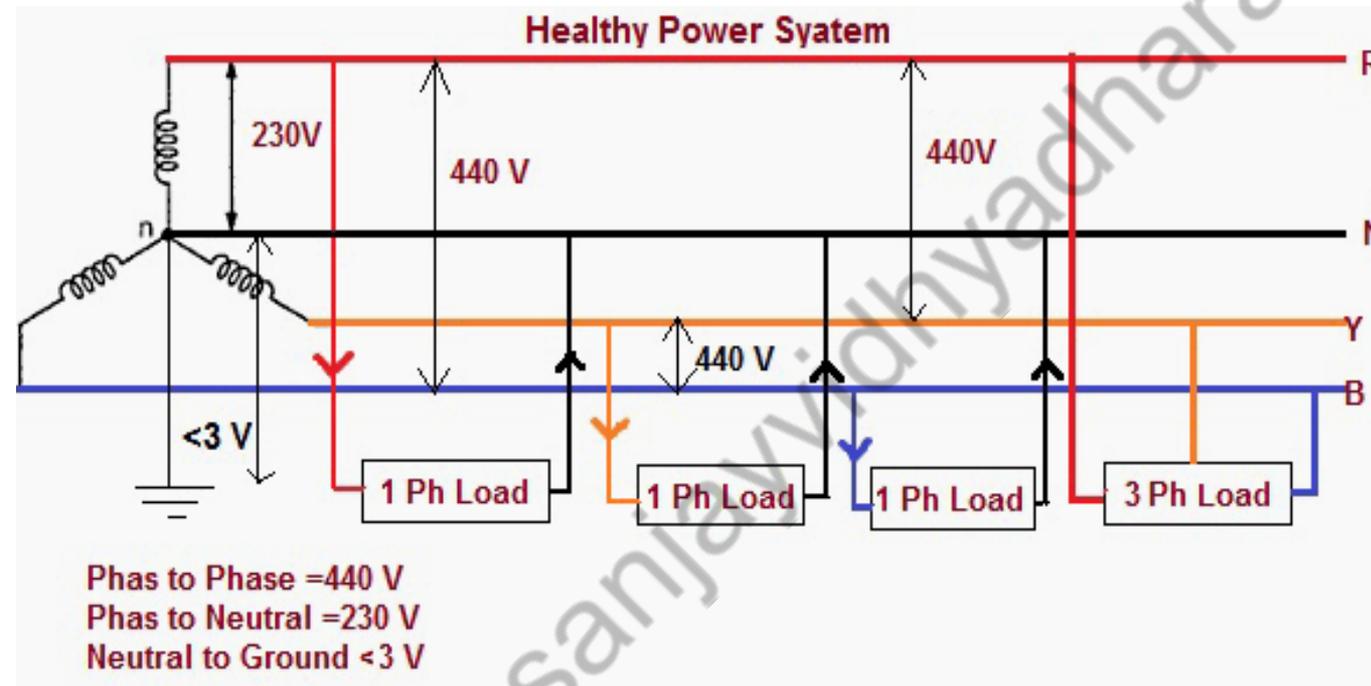
# WYE CONNECTED LINE VOLTAGE

Line voltage is measured between any two of the three lines: line to line voltage.



$$V_L = \sqrt{3}V_P$$

# WYE CONNECTED LINE VOLTAGE

**Line voltage** is measured between any two of the three lines: line to line voltage.


$$V_{an} = V_p \angle 0^\circ, V_{bn} = V_p \angle -120^\circ, V_{cn} = V_p \angle +120^\circ$$

$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} = V_{an} - V_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ \\ &= V_p \left( 1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ \end{aligned}$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_p \angle -90^\circ$$

$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_p \angle -210^\circ$$


$$V_L = \sqrt{3} V_p$$

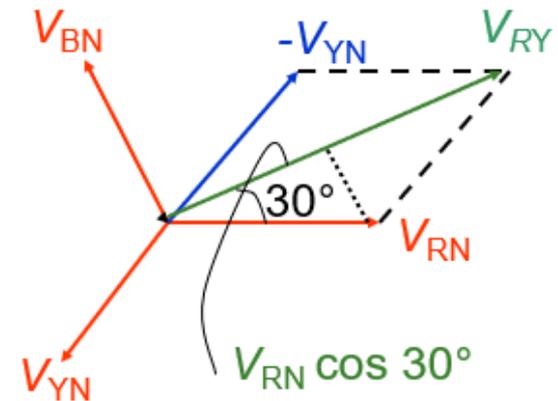

# WYE-WYE CONNECTED THREE-PHASE SYSTEM
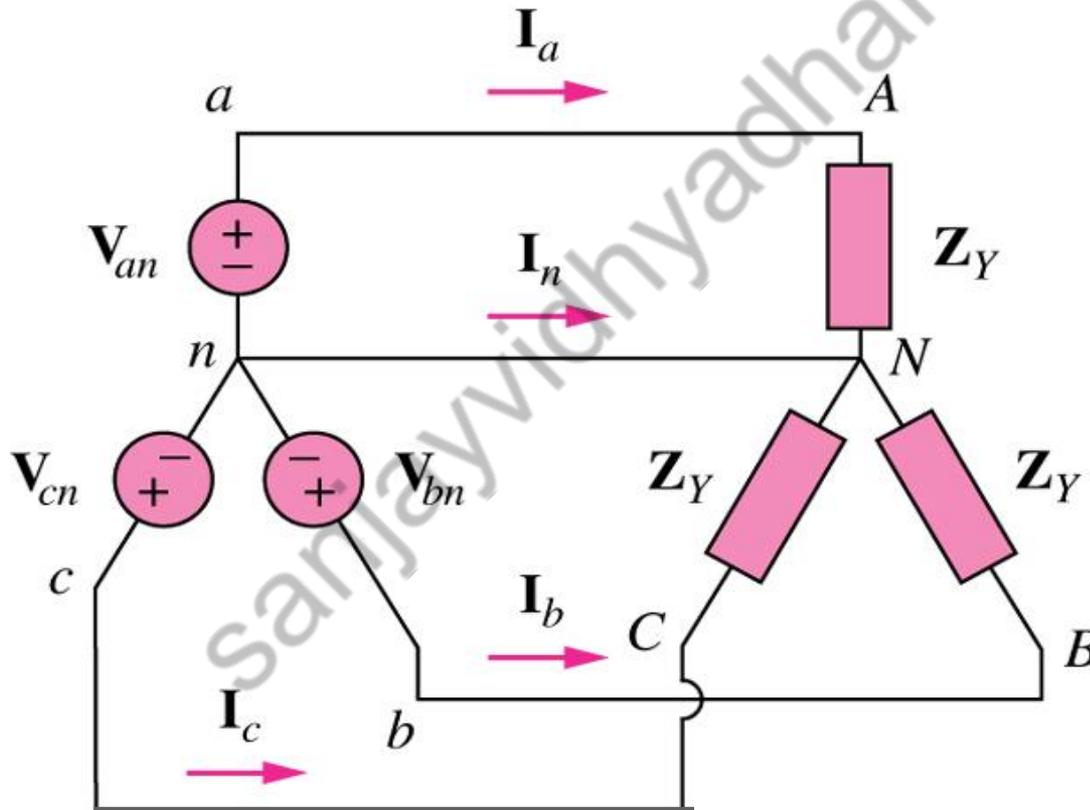
## Balanced Load

The phase impedances are equal in magnitude and in phase.



# WYE-WYE CONNECTED THREE-PHASE SYSTEM


## Balanced Load

The phase impedances are equal in magnitude and in phase.

$$I_a = \frac{V_{an}}{Z_Y}$$

$$I_b = \frac{V_{bn}}{Z_Y} = \frac{V_{an} \angle -120^\circ}{Z_Y} = I_a \angle -120^\circ$$
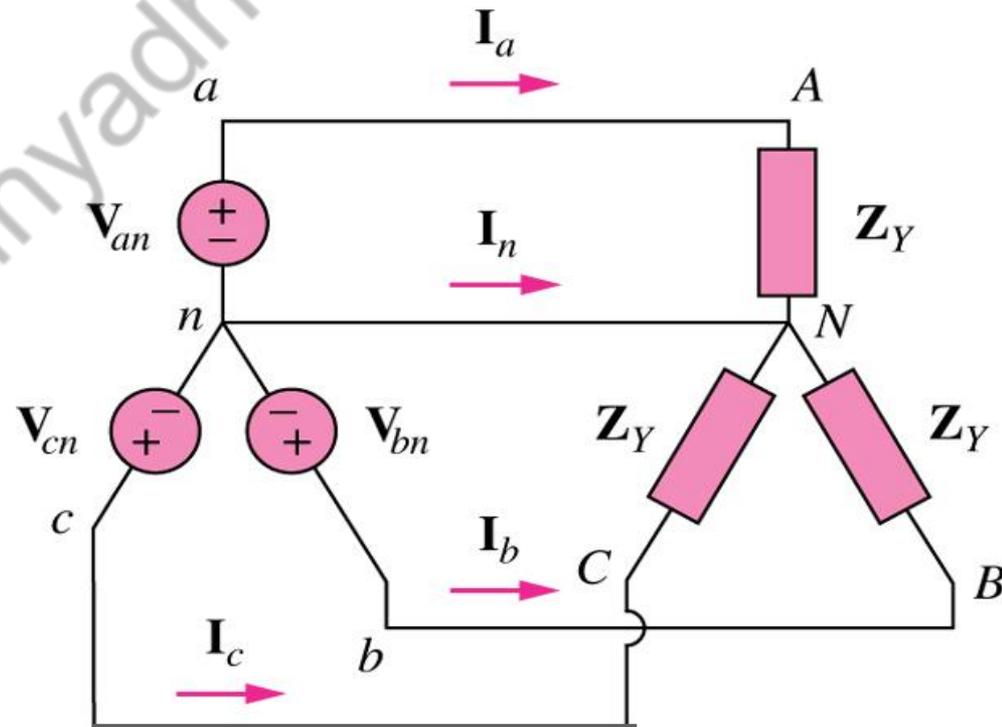
$$I_c = \frac{V_{cn}}{Z_Y} = \frac{V_{an} \angle -240^\circ}{Z_Y} = I_a \angle -240^\circ$$




# WYE CONNECTED THREE-PHASE SYSTEM

## Balanced Load

The phase impedances are equal in magnitude and in phase.

$$I_a + I_b + I_c = 0$$

$$I_n = -(I_a + I_b + I_c) = 0$$

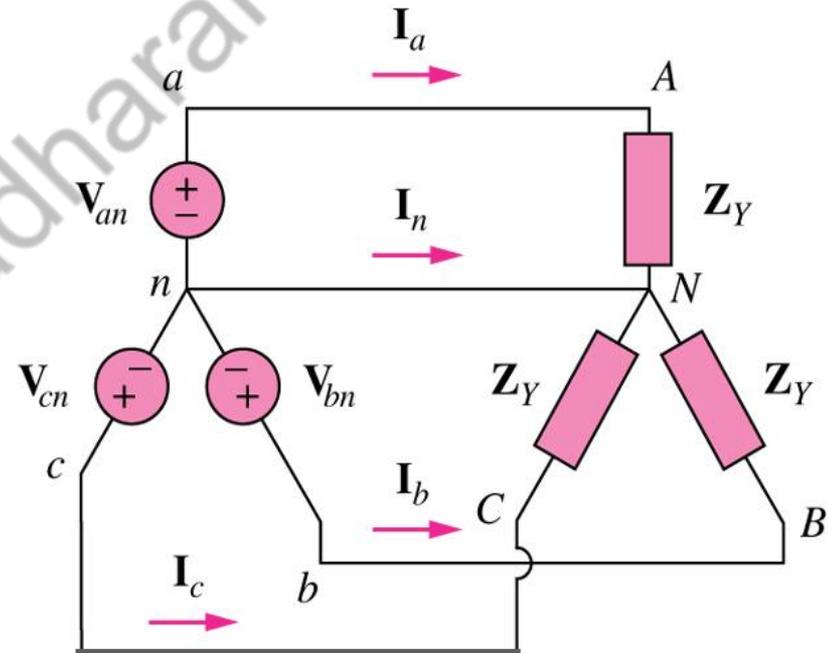


The line current is the current in each line, the phase current is the current in each phase of the source or load.

In the Y-Y system, the line current is the same as the phase current.


# WYE CONNECTED THREE-PHASE SYSTEM

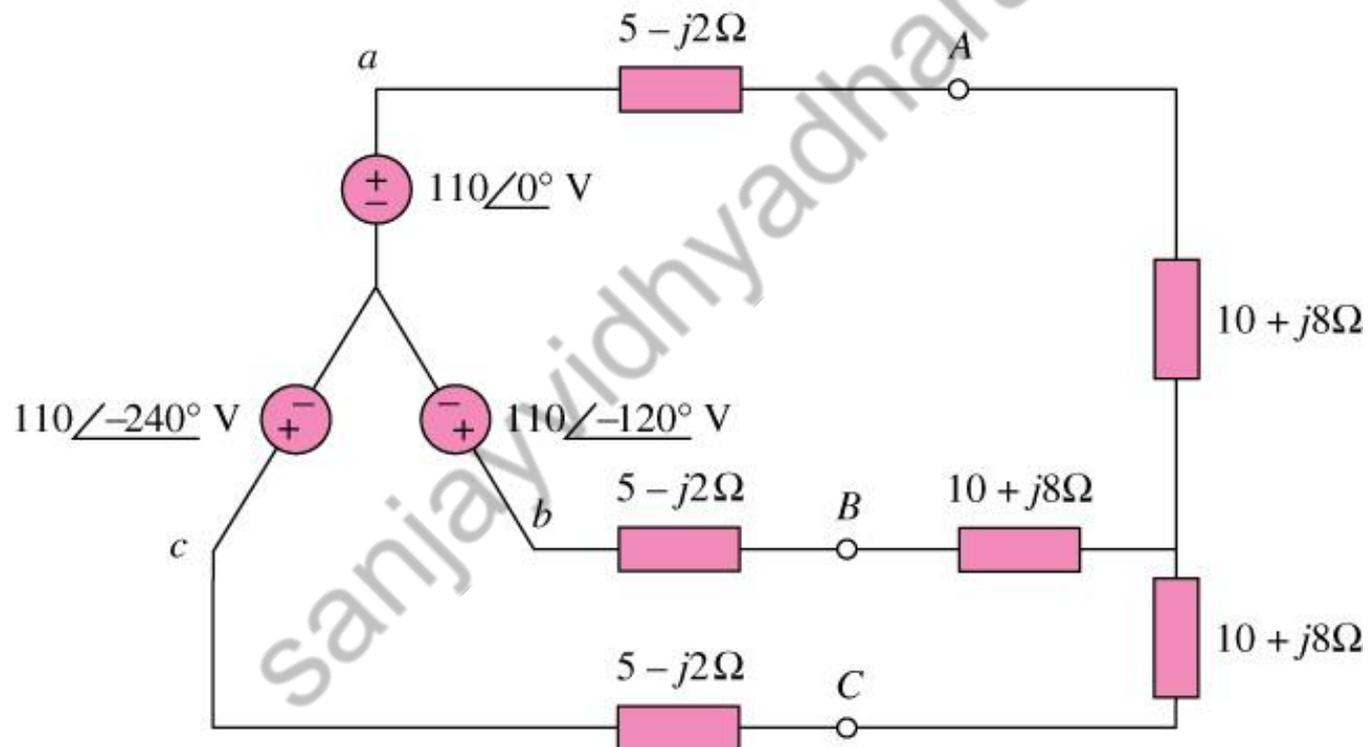**Example 1:** Calculate the line currents in the three-wire Y-Y system



# WYE CONNECTED THREE-PHASE SYSTEM

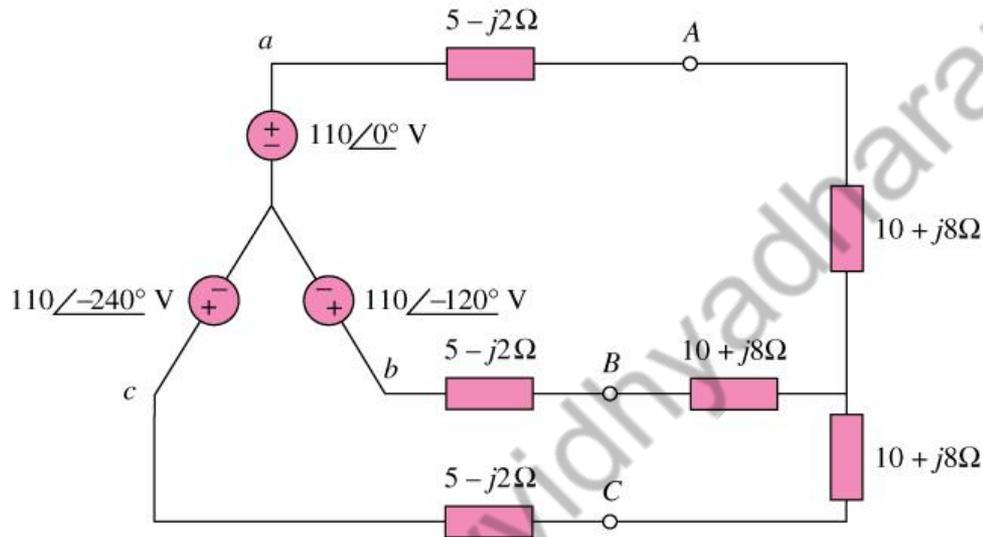**Example 1:** Calculate the line currents in the three-wire Y-Y system



$$Z_Y = (5 - j2) + (10 + j8) = (15 + j6)$$


$$= 16.155 \angle 21.8^\circ$$

$$I_a = \frac{110 \angle 0^\circ}{16.155 \angle 21.8^\circ} = 6.81 \angle -21.8^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 6.81 \angle -141.8^\circ \text{ A}$$

$$I_c = I_a \angle -240^\circ = 6.81 \angle 98.2^\circ \text{ A}$$

# Balanced Wye-Delta Connection

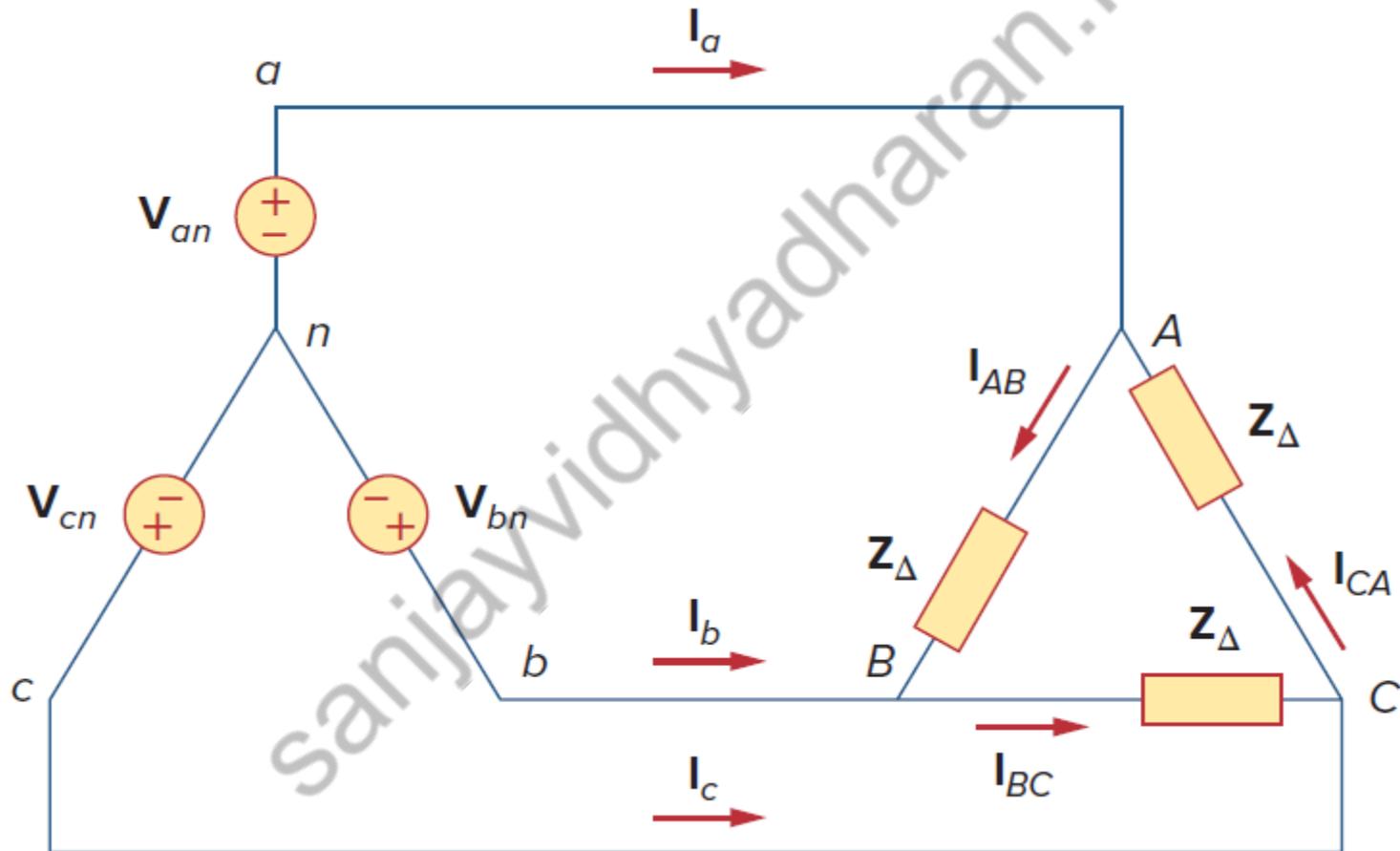

# Balanced Wye-Delta Connection


$$V_{an} = V_p \angle 0^\circ, \quad V_{bn} = V_p \angle -120^\circ, \\ V_{cn} = V_p \angle +120^\circ$$

The line voltages are:

$$V_{ab} = \sqrt{3}V_p \angle 30^\circ = V_{AB}$$

$$V_{bc} = \sqrt{3}V_p \angle -90^\circ = V_{BC}$$

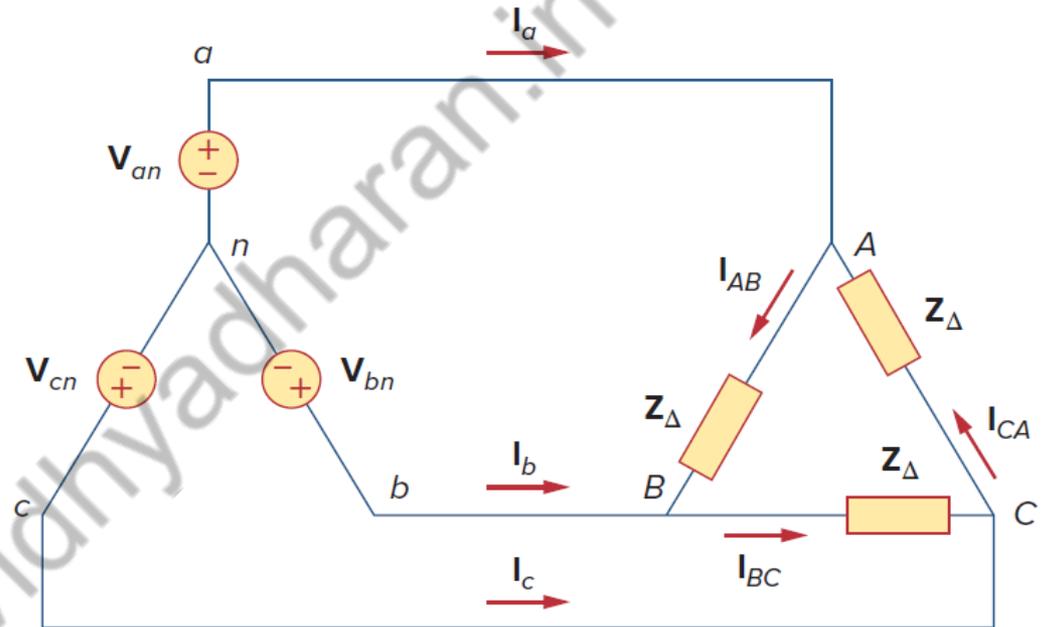
$$V_{ca} = \sqrt{3}V_p \angle 150^\circ = V_{CA}$$


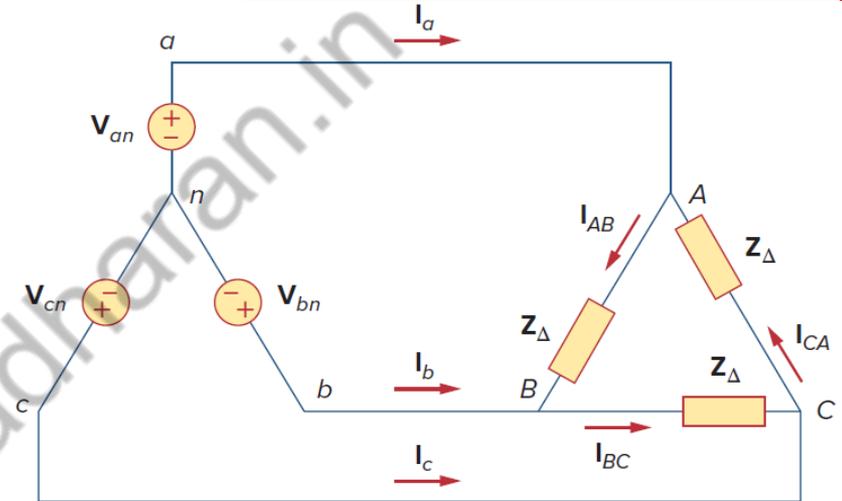
# Balanced Wye-Delta Connection

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}}, I_{BC} = \frac{V_{BC}}{Z_{\Delta}}, I_{CA} = \frac{V_{CA}}{Z_{\Delta}}$$


These currents have the same magnitude but are out of phase with each other by  $120^\circ$ . The line currents are obtained from the phase currents by applying KCL at Nodes A, B, and C. Thus,



$$I_a = I_{AB} - I_{CA}, I_b = I_{BC} - I_{AB}, I_c = I_{CA} - I_{BC}$$

$$\begin{aligned} I_a &= I_{AB} - I_{CA} = I_{AB} (1 - 1 \angle -240^\circ) \\ &= I_{AB} (1 + 0.5 - j0.866) \\ &= I_{AB} \sqrt{3} \angle -30^\circ \end{aligned}$$

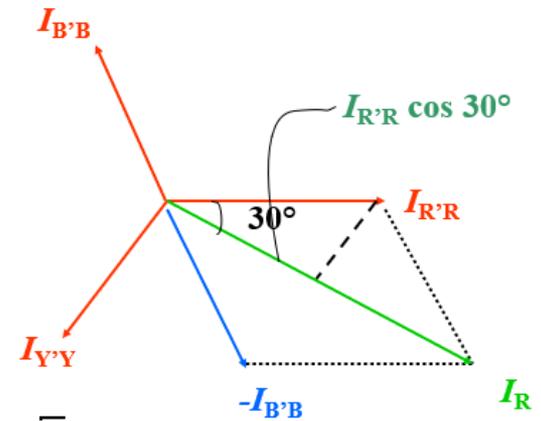Since  $I_{CA} = I_{AB} \angle -240^\circ$ ,



$$I_L = \sqrt{3} I_P$$

# Balanced Wye-Delta Connection

**Example 2:** A balanced abc-sequence Y-connected source which is connected to a  $\Delta$ -connected balanced load  $(8 + j4) \Omega$  per phase. Calculate the phase and line currents.  $V_{an} = 100 \angle 10^\circ \text{ V}$

The load impedance is:

$$Z_{\Delta} = 8 + j4 = 8.944 \angle 26.57^\circ \Omega$$

If the phase voltage  $V_{an} = 100 \angle 10^\circ \text{ V}$ , then the line voltage is

$$V_{ab} = V_{an} \sqrt{3} \angle 30^\circ = 173.2 \angle 40^\circ \text{ V} = V_{AB}$$

# Balanced Wye-Delta Connection

**Example 2:** A balanced abc-sequence Y-connected source with is connected to a  $\Delta$ -connected balanced load  $(8 + j4) \Omega$  per phase. Calculate the phase and line currents.

$$V_{an} = 100 \angle 10^\circ \text{ V}$$

The phase currents are,

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{173.2 \angle 40^\circ}{8.944 \angle 26.57^\circ} = 19.36 \angle 13.43^\circ \text{ A}$$

$$I_{BC} = I_{AB} \angle -120^\circ = 19.36 \angle -106.57^\circ \text{ A}$$

$$I_{CA} = I_{AB} \angle +120^\circ = 19.36 \angle 133.43^\circ \text{ A}$$

The line currents are,


$$I_a = I_{AB} \sqrt{3} \angle -30^\circ = 33.53 \angle -16.57^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 33.53 \angle -136.57^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 33.53 \angle 103.43^\circ \text{ A}$$

# Summary


## WYE-WYE

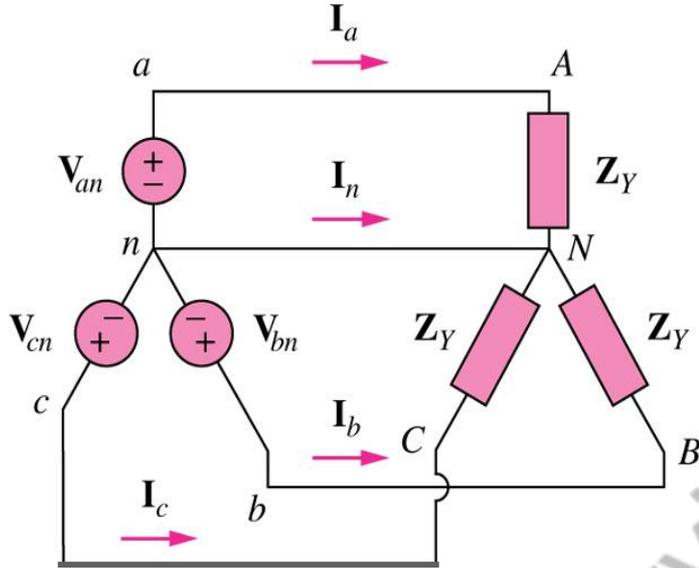

$$V_L = \sqrt{3}V_p$$

$$I_P = I_L$$

## WYE-DELTA

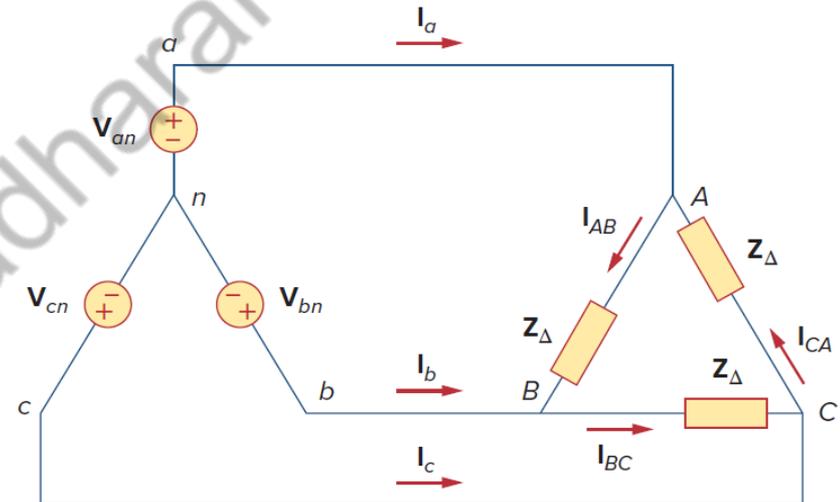

$$V_L = \sqrt{3}V_p$$

$$I_P = \sqrt{3}I_L$$

## Transmission Lines

Loads to be balanced for minimise Transmission loss

## High Torque Motors

**Thank you**

sanjayvidhyadharan.in