




Electrical Science: 2021-22

Lecture 21

Transformer Theory and Operation

By Dr. Sanjay Vidhyadharan

Ideal Transformer

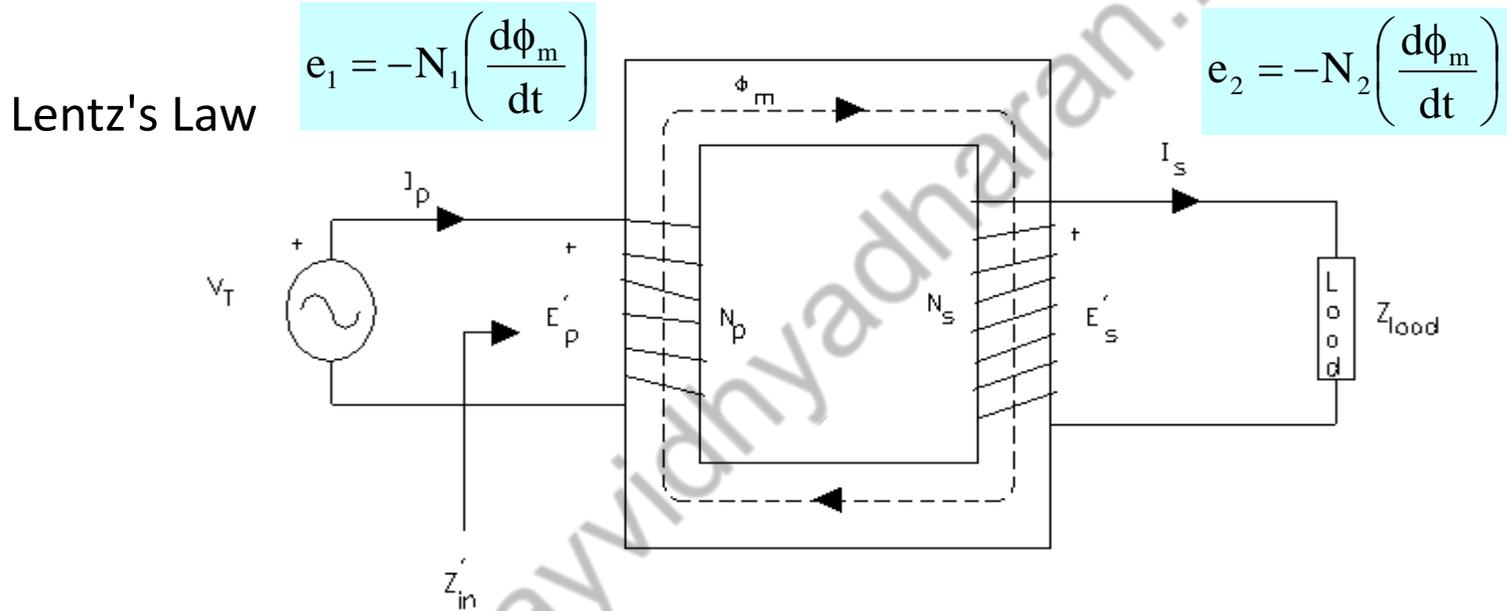


Principle: Stationary coils, time varying flux due to ac current flow. Flux produced by one coil must link to other coil to induce voltage

Ideal Transformer

Lenz's Law

$$e_1 = -N_1 \left(\frac{d\phi_m}{dt} \right)$$
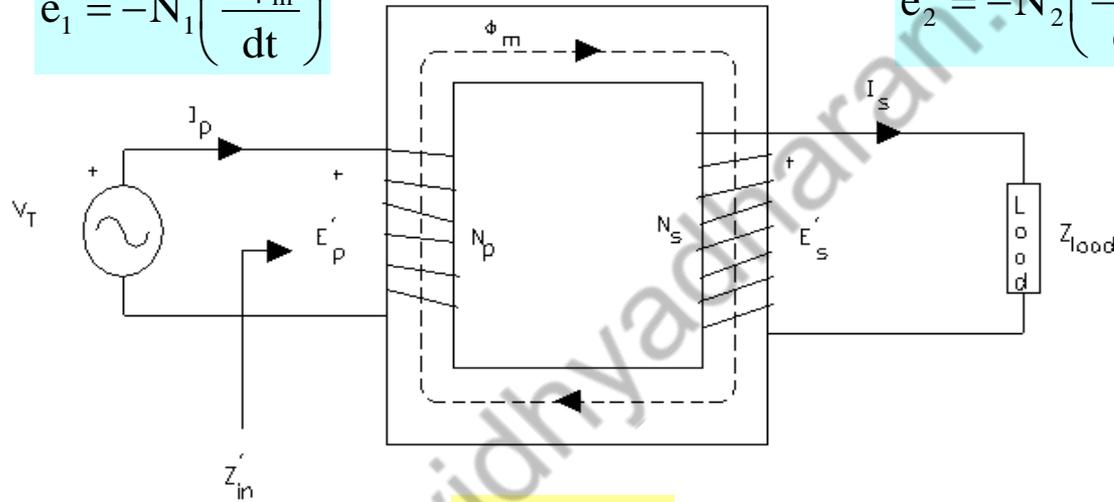
$$e_2 = -N_2 \left(\frac{d\phi_m}{dt} \right)$$



$$\frac{E'_p}{E'_s} = \frac{N_p}{N_s}$$

Where: E'_p = voltage induced in the primary (V)
 E'_s = voltage induced in the secondary (V)
 N_p = turns in the primary coil
 N_s = turns in the secondary coil

Voltage relationship for Ideal transformer

Voltage ratio equals the turns ratio

Ideal Transformer

- 1) All flux produced in the primary coil links to the secondary coil
- 2) no core losses due to hysteresis or eddy currents
- 3) no power losses
- 4) permeability is infinite (no saturation no magnetizing ϕ)
- 5) windings have zero resistance
- 6) no current required to magnetize the iron core

$$\frac{E'_p}{E'_s} = \frac{N_p}{N_s}$$

Voltage relationship
for Ideal transformer

Where: E'_p = voltage induced in the primary (V)
 E'_s = voltage induced in the secondary (V)
 N_p = turns in the primary coil
 N_s = turns in the secondary coil

Voltage ratio equals
the turns ratio


Ideal Transformer Equations

Voltage Ratio

$$a = \frac{E_p}{E_s} = \frac{N_p}{N_s}$$

$$E_p = a \cdot E_s$$

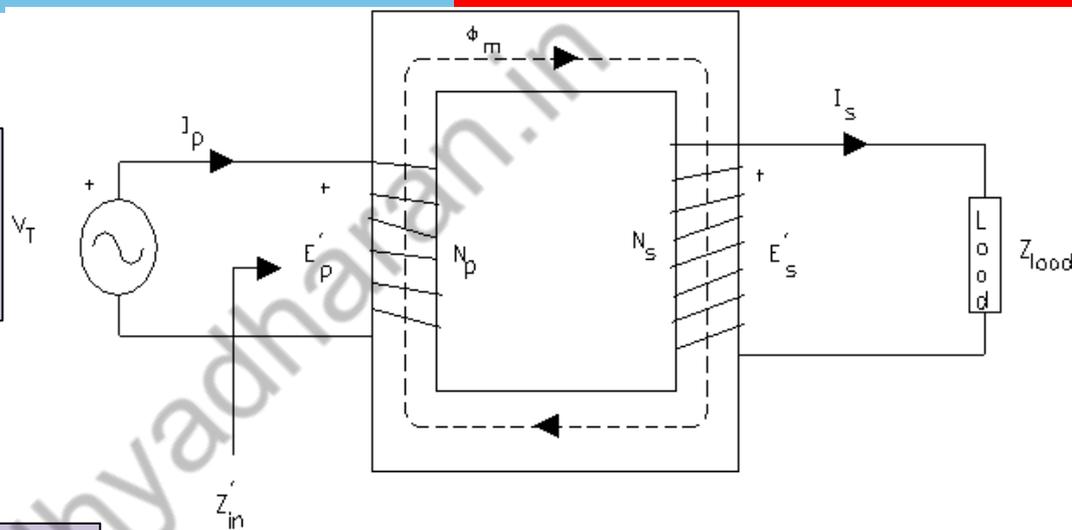The turns ratio is a scalar. Introduces no phase shift



Apparent Power balance

$$E_p \cdot I_p = E_s \cdot I_s$$

$$S_p = S_s$$

No power losses in idea transformer

Current Ratio

$$\frac{I_p}{I_s} = \frac{1}{a}$$


$$I_p = \left(\frac{1}{a} \right) \cdot I_s$$

Current ratio is the inverse of the voltage ratio

Ideal Transformer Equations

Impedances Reflected Through Ideal Transformers

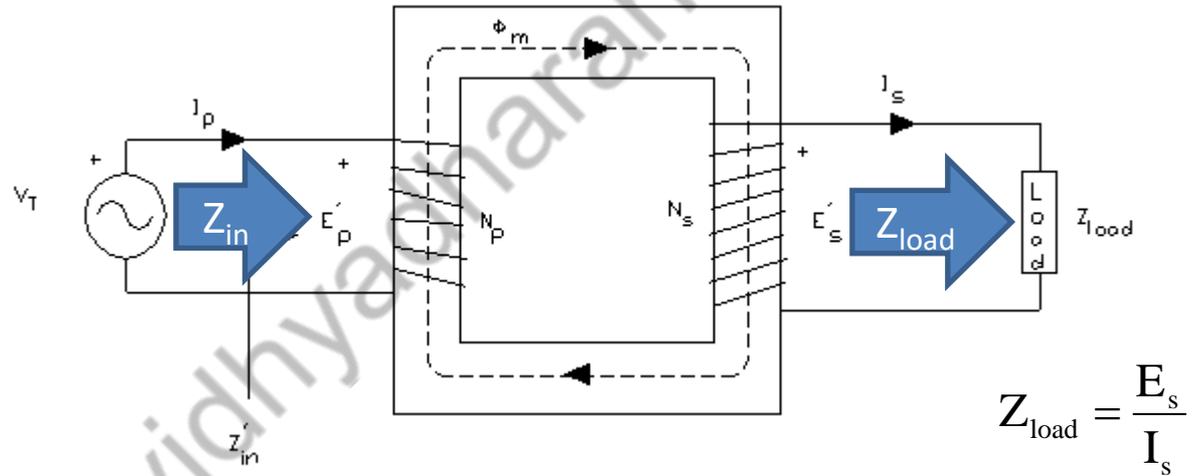Load impedance as seen from primary side of transformer



By Ohm's Law

$$Z_{in} = \frac{E_p}{I_p}$$

$$Z_{load} = \frac{E_s}{I_s}$$

Write E_s and I_s in terms of primary values

$$E_s = \frac{E_p}{a} \quad I_s = a \cdot I_p$$

Load impedance is increased when viewed from primary side

$$\frac{E_s}{I_s} = \frac{\left(\frac{E_p}{a}\right)}{a \cdot I_p} = \left(\frac{E_p}{a}\right) \left(\frac{1}{a \cdot I_p}\right) = \left(\frac{E_p}{I_p}\right) \left(\frac{1}{a^2}\right)$$

$$Z_{load} = Z_{in} \cdot \left(\frac{1}{a^2}\right) \Rightarrow Z_{load} \cdot a^2 = Z_{in}$$

Lesson 8_et332b.pptx

Ideal Transformer Equations

Impedances Reflected Through Ideal Transformers

Load impedance as seen from primary side of transformer


By Ohm's Law

$$Z_{in} = \frac{E_p}{I_p}$$

Write E_s and I_s in terms of primary values

$$\frac{E_s}{I_s} = \frac{\left(\frac{E_p}{a}\right)}{a \cdot I_p} = \left(\frac{E_p}{a}\right) \left(\frac{1}{a \cdot I_p}\right) = \left(\frac{E_p}{I_p}\right) \left(\frac{1}{a^2}\right)$$

Lesson 8_et332b.pptx

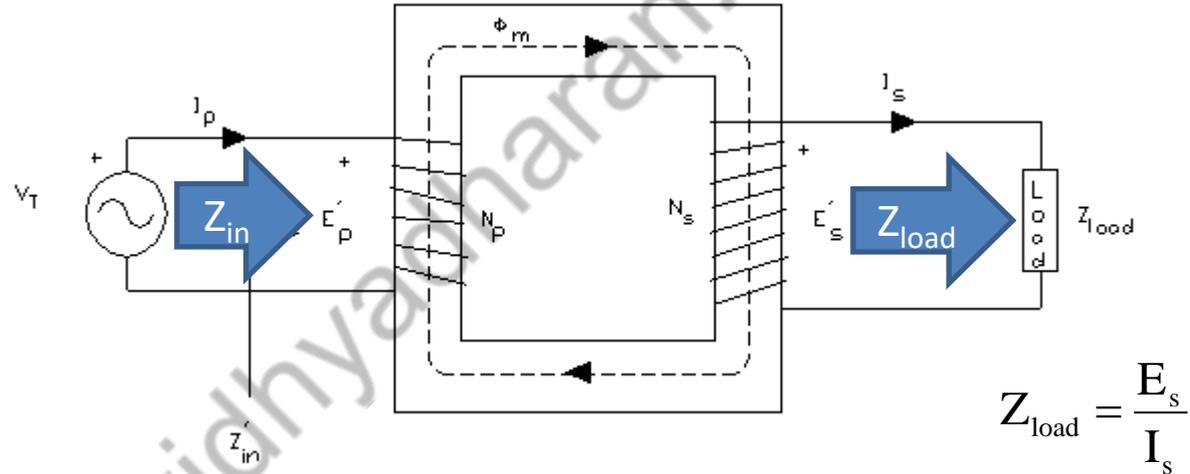

$$E_s = \frac{E_p}{a} \quad I_s = a \cdot I_p$$

$$Z_{load} = \frac{E_s}{I_s}$$

Load impedance is increased when viewed from primary side

$$Z_{load} = Z_{in} \cdot \left(\frac{1}{a^2}\right) \Rightarrow Z_{load} \cdot a^2 = Z_{in}$$

Ideal Transformer Example

Example 300 kVA 2400-120, 60 Hz single phase transformer operates at 2300 volts on the primary side. It supplies 115 kVA to a load that has a power factor of 0.723 lagging. Assume ideal operation and find:

- a.) secondary voltage at operating voltage
- b.) secondary current
- c.) impedance of the load as seen on the secondary side
- d.) impedance of the load as seen on the primary side

Ideal Transformer Example

Example 300 kVA 2400-120, 60 Hz single phase transformer operates at 2300 volts on the primary side. It supplies 115 kVA to a load that has a power factor of 0.723 lagging. Assume ideal operation and find:

- secondary voltage at operating voltage
- secondary current
- impedance of the load as seen on the secondary side
- impedance of the load as seen on the primary side

$$a = \frac{V_{pr}}{V_{sr}} = \frac{2400}{120} = 20$$

$$V_{sr} = \frac{V_{pr}}{a} = \frac{2300}{20} = 115 \text{ V}$$

$$I_s = \frac{115 \text{ KVA}}{115 \text{ V}} = 1000 \text{ A}$$

$$|Z_s| = \frac{115 \text{ V}}{1000 \text{ A}} = 0.115 \Omega$$

$$\phi = \cos^{-1}(0.723) = -43.70$$

$$Z_s = 0.115 \angle -43.70 \Omega$$

$$\begin{aligned} Z_p &= a^2 * 0.115 \angle -43.70 \Omega \\ &= 400 * 0.115 \angle -43.70 \Omega \\ &= 46 \angle -43.70 \Omega \end{aligned}$$

Practical Transformers

Practical transformers draw current with no load connected to secondary winding. Current caused by two non-ideal conditions: power losses and core magnetization

Active power losses


Hysteresis losses - power losses due to repeated change in magnetic polarity. It takes more mmf (NI) to demagnetize core in one direction than the other.

Eddy currents - ac currents induced in iron core due to changing magnetic field

Active power loss Control


Control hysteresis losses - use alloy steels designed for magnetic circuits
Control eddy current losses - laminate core, insulate laminates

Practical Transformers

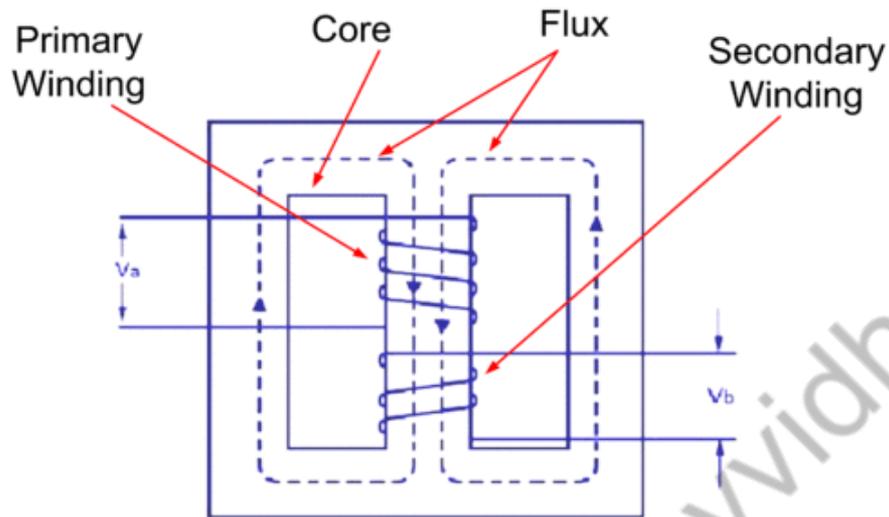


Shell type

Practical Transformers

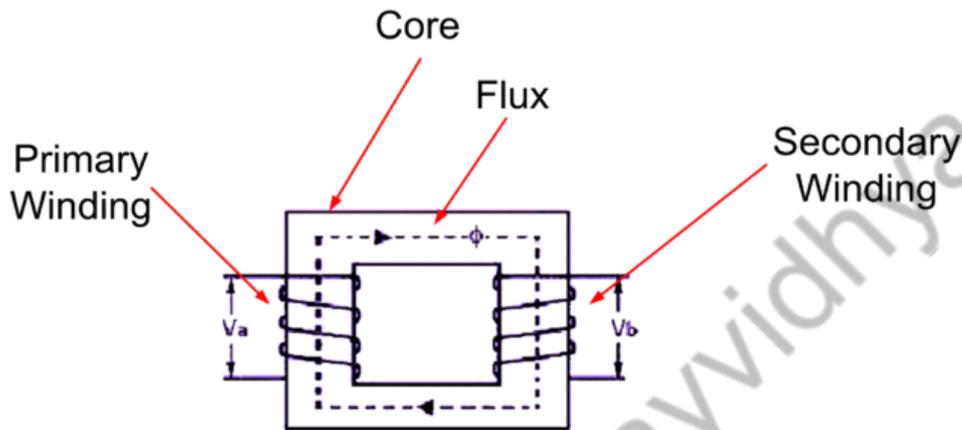


Core type

Practical Transformers

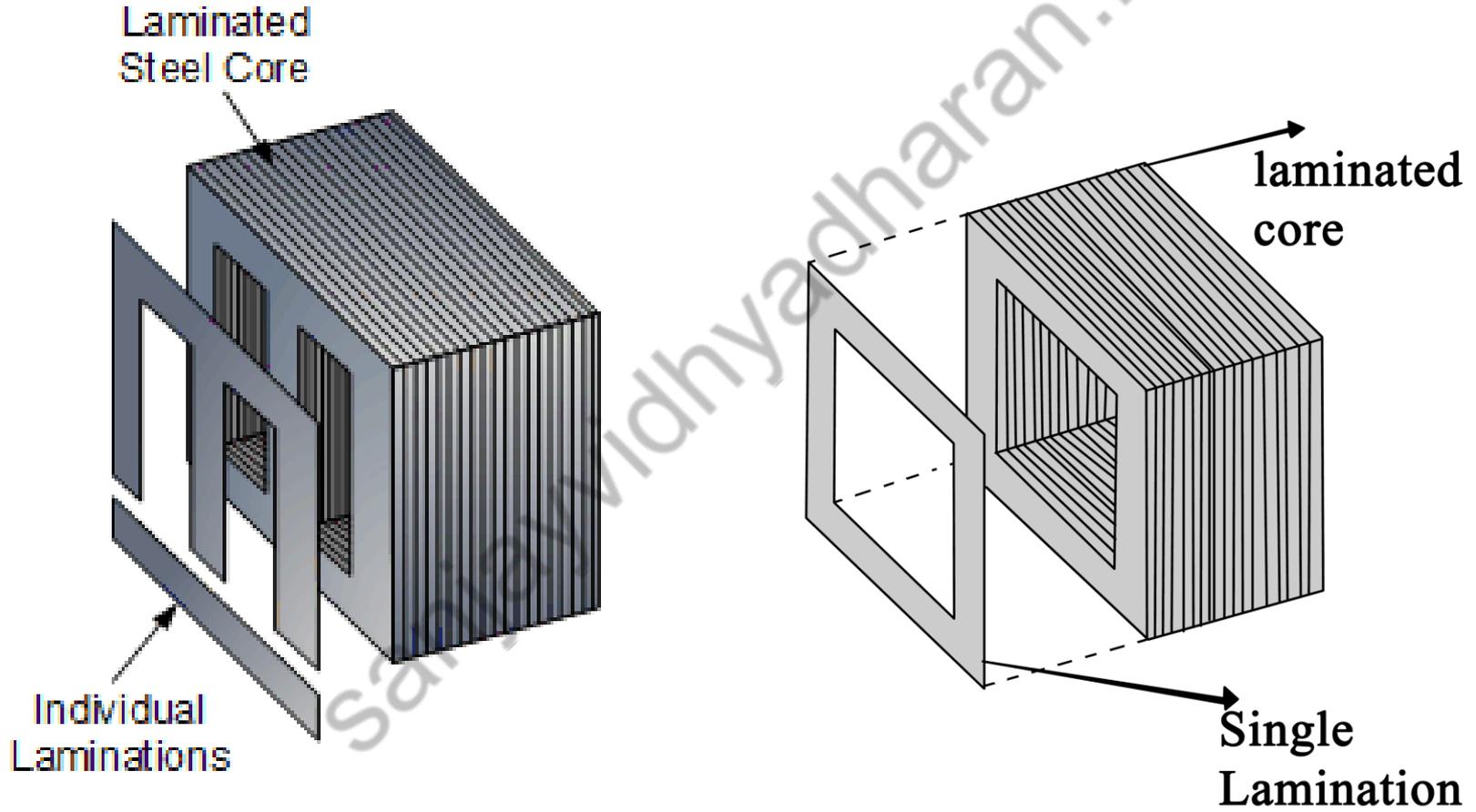

Practical Transformers

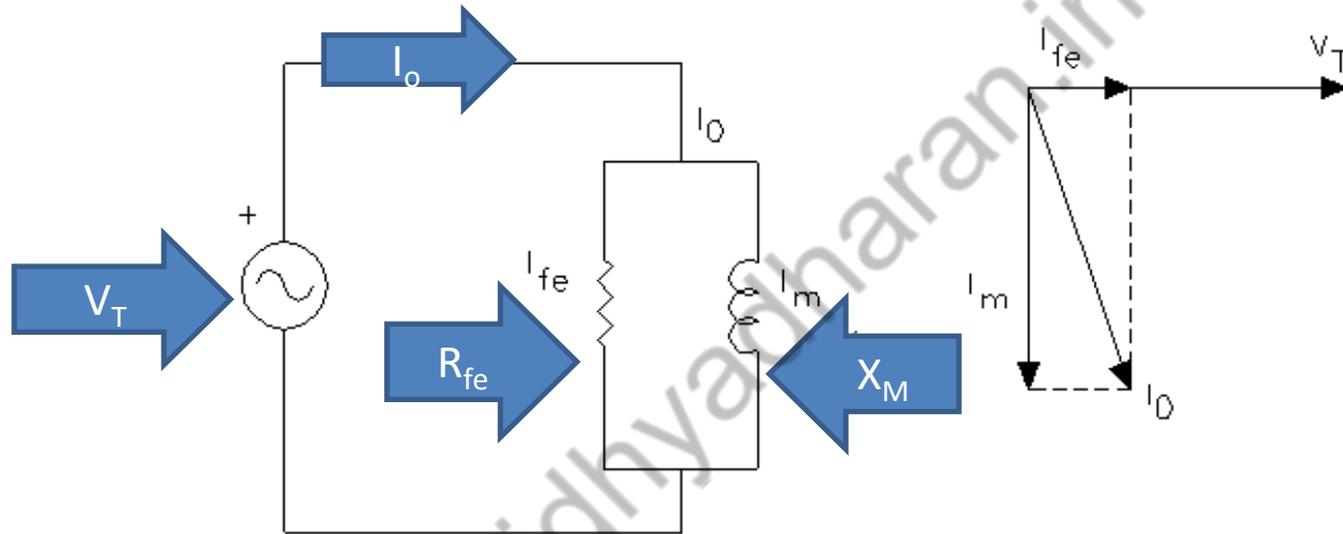

V_T = the primary voltage

I_{fe} = core-loss component

I_0 = exciting current

I_m = magnetizing component

R_{fe} = resistance that represents the core losses

X_m = inductive reactance that represents the core magnetizing L

Practical Transformers

Example. A 50 kVA 7200-240 V, 60 Hz single phase transformer is operating with no load. With the primary connected to a 7200 V system, it draws 248 W and has a power factor of 0.187 lagging. Find:

- a) the exciting current and its components
- b) the magnitudes of magnetizing reactance, X_M and core loss R
- c) Repeat parts a and b if the transformer is energized from the secondary (low voltage) side.

Practical Transformers

Example. A 50 kVA 7200-240 V, 60 Hz single phase transformer is operating with no load. With the primary connected to a 7200 V system, it draws 248 W and has a power factor of 0.187 lagging. Find:

- the exciting current and its components
- the magnitudes of magnetizing reactance, X_M and core loss R

$$\text{Apparent Power} = \frac{248}{0.187} = 1326.2 \text{ VA}$$

$$|I_0| = \frac{1326.2}{7200} = 0.1842 \text{ A}$$

$$\phi = -\cos^{-1}(0.187) = -79.2^\circ$$

$$I_0 = 0.1842 \angle -79.2^\circ \text{ A}$$

$$I_M = 0.1842 \sin 79.2^\circ \text{ A} = 0.1809 \text{ A}$$

$$I_{fe} = 0.1842 \cos 79.2^\circ \text{ A} = 0.0345 \text{ A}$$

$$R_{fe} = \frac{7200}{0.0345} = 209032 \Omega$$

$$X_M = \frac{7200}{0.1809}$$

Practical Transformers

Transformer Voltage Regulation

The output voltage of a transformer varies with the load even if the input voltage remains constant. This is because a real transformer has series impedance within it. Full load Voltage Regulation is a quantity that compares the output voltage at no load with the output voltage at full load, defined by this equation:

$$\text{Regulation up} = \frac{V_{S,nl} - V_{S,fl}}{V_{S,fl}} \times 100\%$$

$$\text{Regulation down} = \frac{V_{S,nl} - V_{S,fl}}{V_{S,nl}} \times 100\%$$

$$\text{At no load } k = \frac{V_s}{V_p}$$

$$\text{Regulation up} = \frac{(V_p / k) - V_{S,fl}}{V_{S,fl}} \times 100\%$$

$$\text{Regulation down} = \frac{(V_p / k) - V_{S,fl}}{V_{S,nl}} \times 100\%$$

Ideal transformer, VR = 0%.

Practical Transformers

Transformer Efficiency

Transformer efficiency is defined as (applies to motors, generators and transformers):

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

Types of losses incurred in a transformer:

Copper I^2R losses

Hysteresis losses

Eddy current losses

Therefore, for a transformer, efficiency may be calculated using the following:

$$\eta = \frac{V_S I_S \cos\theta}{P_{Cu} + P_{core} + V_S I_S \cos\theta} \times 100\%$$

Thank you

sanjayvidhyadharan.in