




Electrical Science: 2021-22

Lecture 22




Diode Rectifiers

By Dr. Sanjay Vidhyadharan


Rectifiers

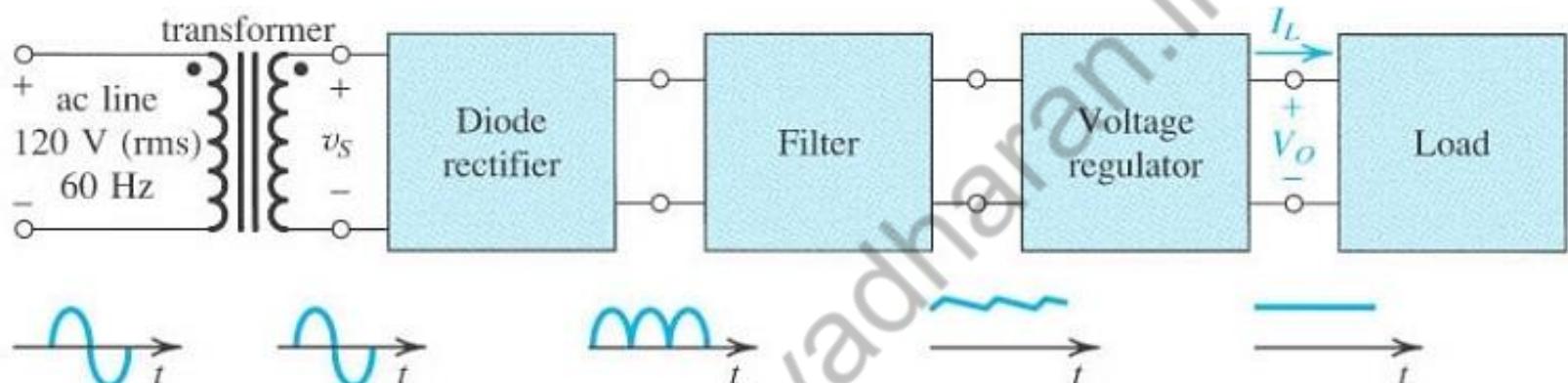


Basics of Semiconductors

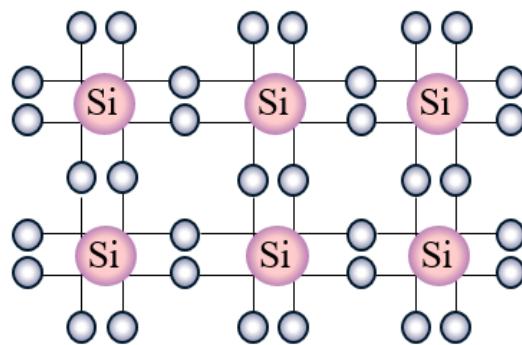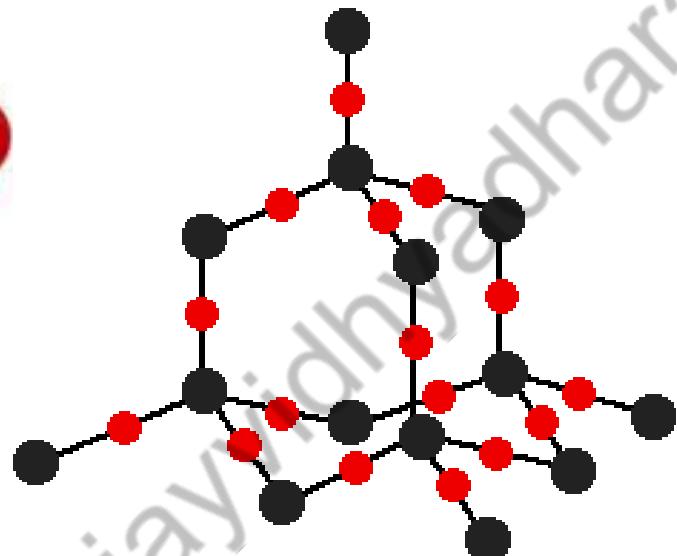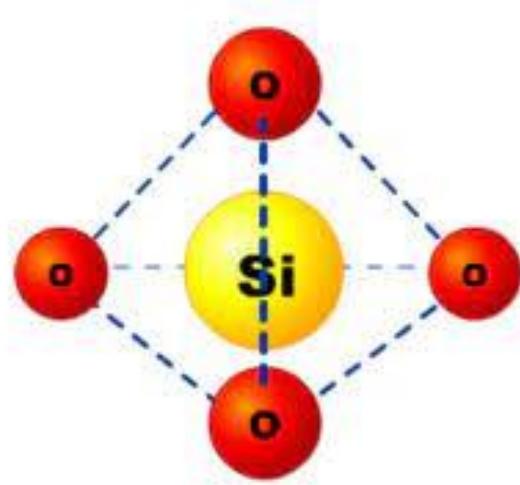

Basics of Semiconductors





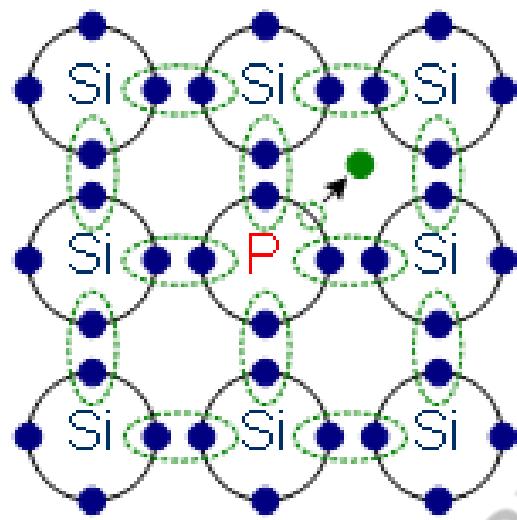


N Dopant- Phosphorus



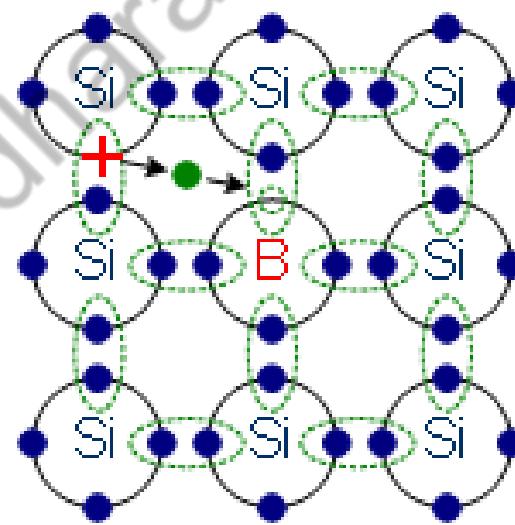


P Dopant- Boron

Diode Characteristics

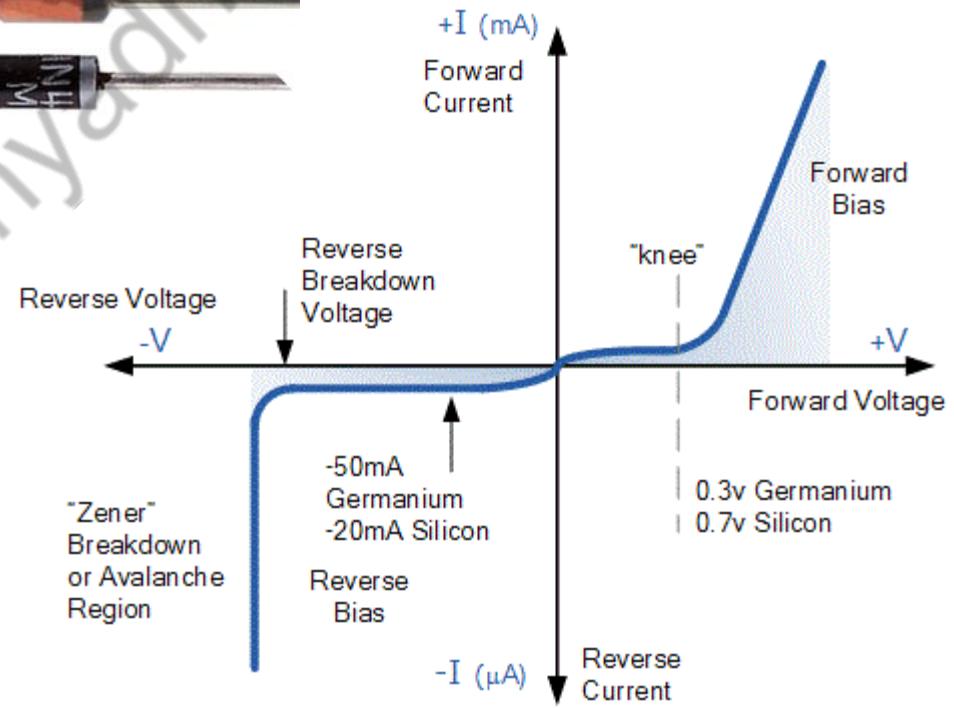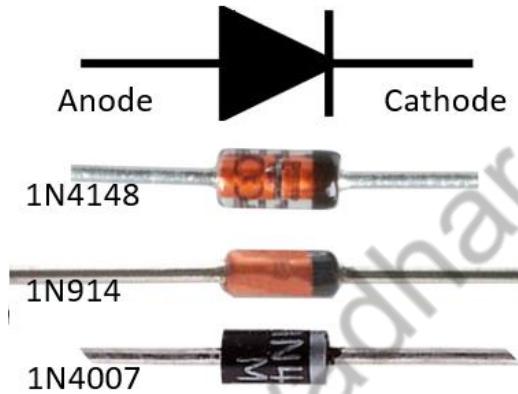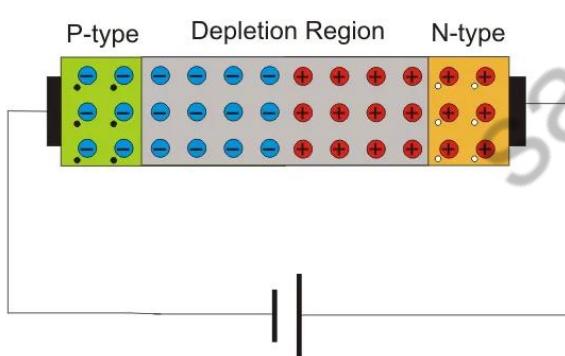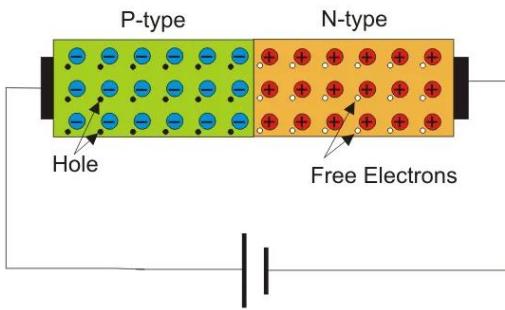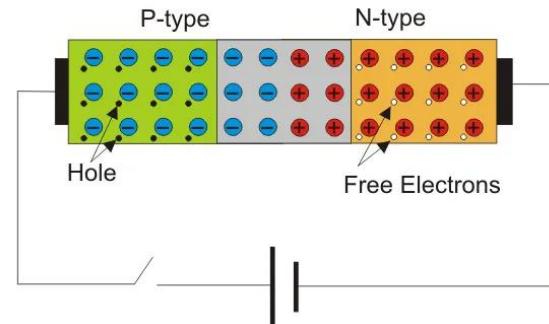

Diode Characteristics

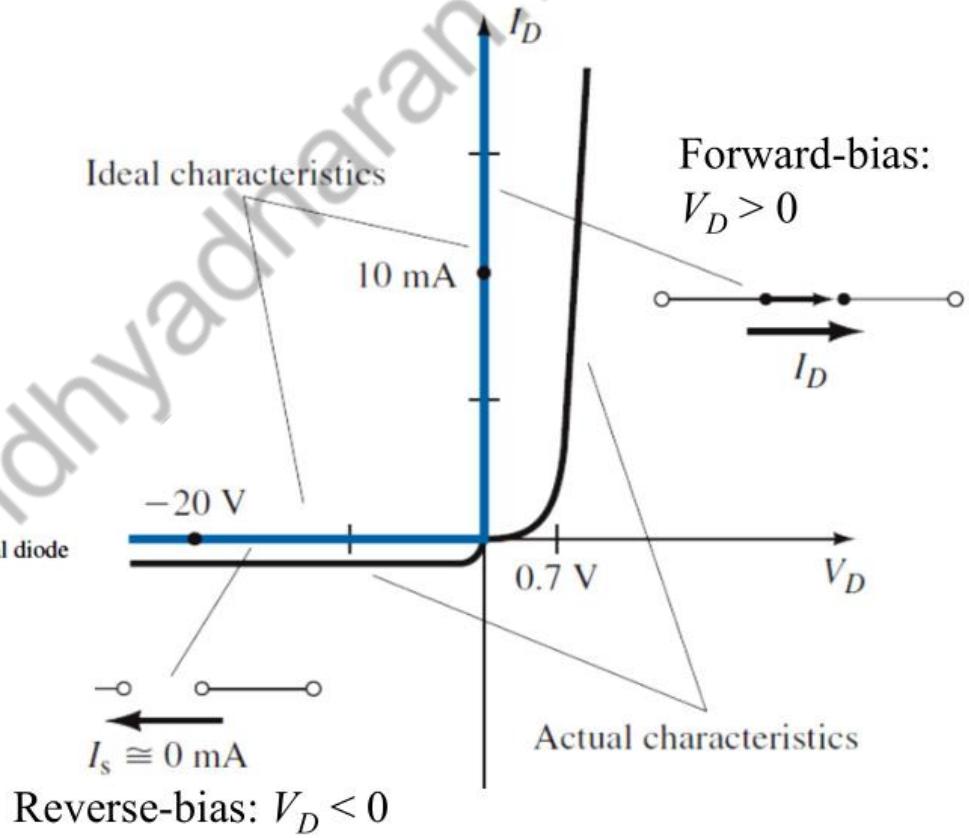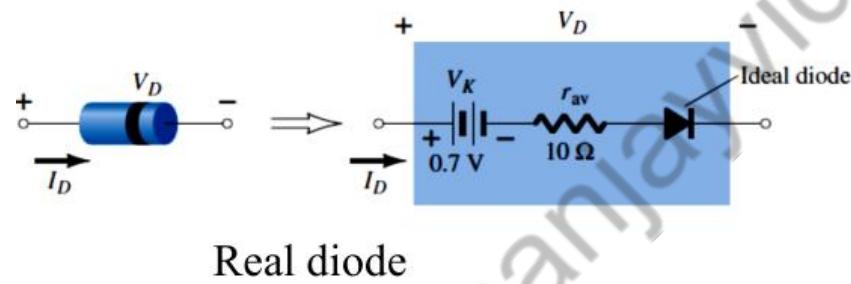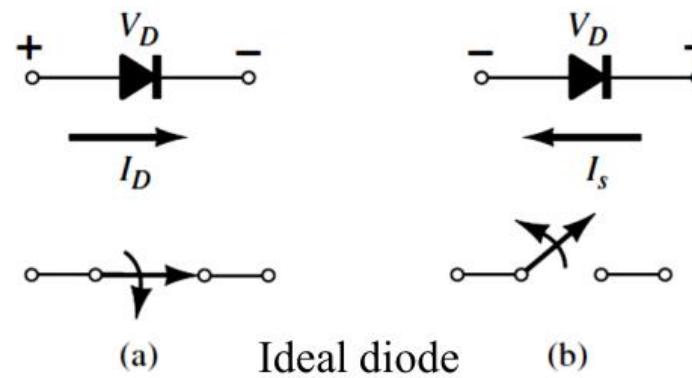

Half-Wave Rectifier

Mean/DC value of the load voltage V_R :

$$V_{dc} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t) = \frac{V_m}{\pi}$$


RMS value of the load voltage V_R :

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 \, d(\omega t)} = \frac{V_m}{2}$$

Rectification efficiency $\eta = (V_{dc}/V_{rms})^2 = 4/\pi^2 \sim 40\%$

$$V_{DC} = V_{avg} = 0.318 V_m$$
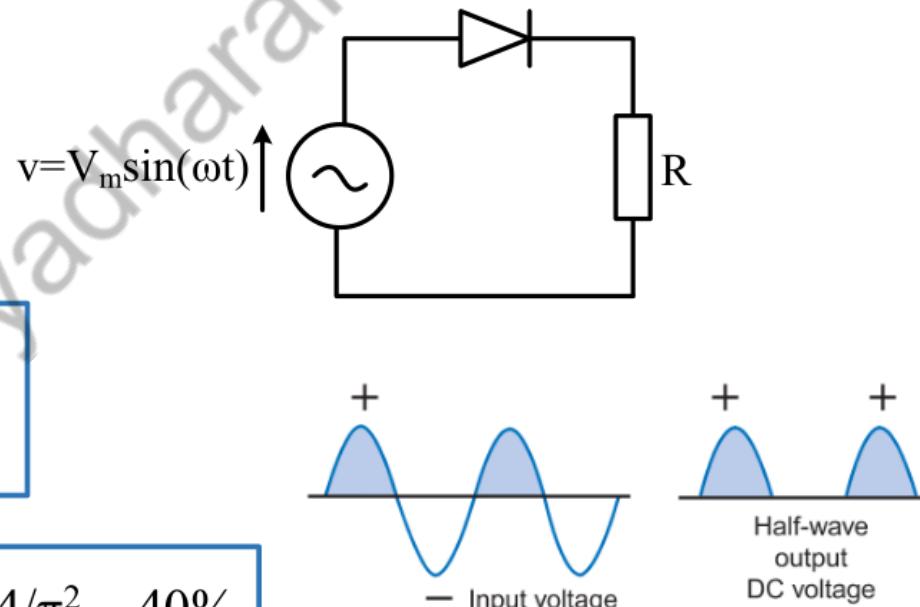
$$I_{DC} = \frac{V_m}{\pi R} \quad I_{rms} = \frac{V_m}{2R} \quad I_{MAX} = \frac{V_m}{R} \quad \text{Peak Inverse Voltage PIV} = V_m$$



Half-Wave Rectifier


$$\text{Form Factor} = \frac{V_{rms}}{V_{av}} \text{ or } \frac{I_{rms}}{I_{av}}$$

$$\text{Form Factor} = \frac{V_{rms}}{V_{av}}$$

$$\text{Form Factor} = \frac{\frac{V_m}{2}}{\frac{V_m}{\pi}}$$

Where V_m is the peak value of AC voltage

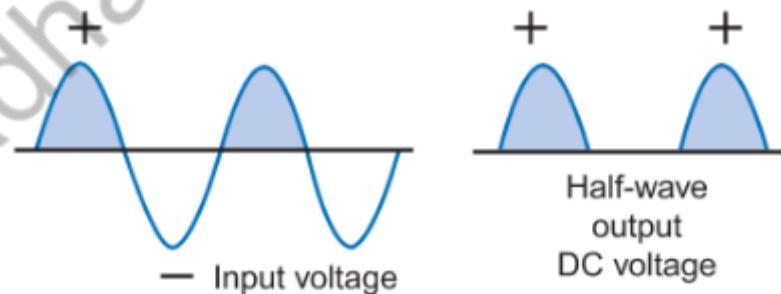
$$\text{Form Factor} = \frac{\pi}{2} = 1.57$$



Half-Wave Rectifier


$$\begin{aligned}\text{Ripple Factor, } \gamma &= \frac{\sqrt{(I_{rms})^2 - (I_{dc})^2}}{I_{dc}} \\ &= \frac{\sqrt{(V_{rms})^2 - (V_{dc})^2}}{V_{dc}}\end{aligned}$$
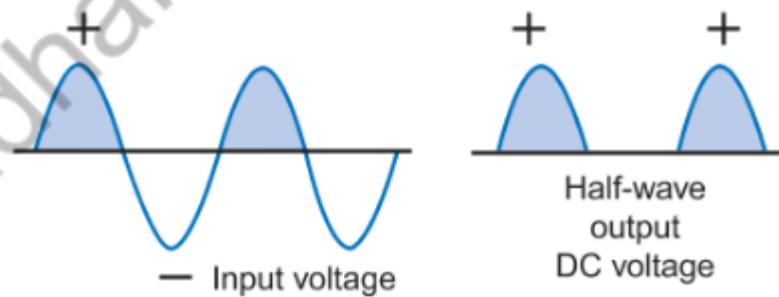
$$\begin{aligned}\text{Ripple Factor} &= \frac{\sqrt{(0.5Im)^2 - (0.318Im)^2}}{0.318Im} \\ &= 1.21\end{aligned}$$




Half-Wave Rectifier

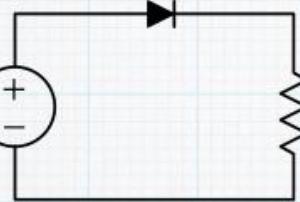
$$V_S(t) = V_p \sin\left(\frac{2\pi}{T}t\right)$$
$$V_p = 3 \text{ V.}$$



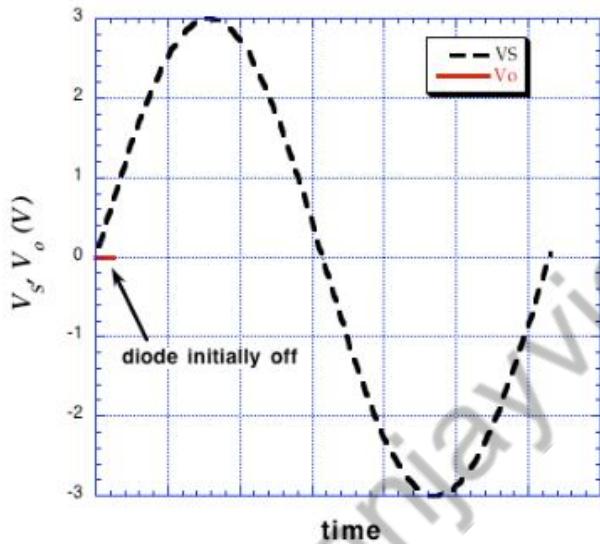+ Resistor represent a load.
- v_R We are trying to deliver
DC power to the load.



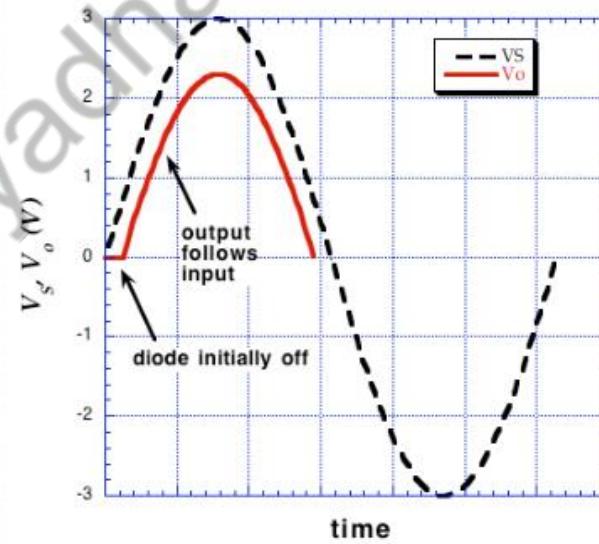Diode is off until $V_S > 0.7 \text{ V}$.



Current flows when diode is in forward conduction. The output tracks the input during positive half cycle.

Half-Wave Rectifier

$$\text{Rectifier efficiency, } \eta = \frac{\text{DC output power}}{\text{Input AC power}}$$

$$\text{DC output power } P_{dc} = I_{dc}^2 * R_L = \left(\frac{I_m}{\pi}\right)^2 * R_L$$


$$\text{AC Input Power } P_{ac} = I_{rms}^2 (r_f + R_L) = \left(\frac{I_m}{2}\right)^2 * (r_f + R_L)$$

$$\eta = \frac{4}{\pi^2 \left(\frac{r_f + R_L}{R_L} \right)} = \frac{0.406}{1 + \frac{r_f}{R_L}} \simeq 0.406$$

Maximum rectifier efficiency = 40.6%.

This means only 40.6% of the input AC power is converted into DC power.


Full-Wave Rectifier

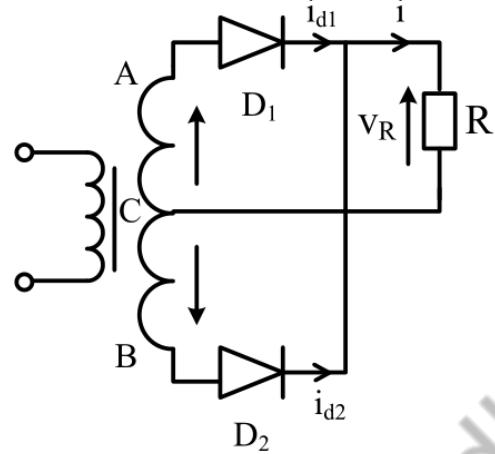

Here C is a centre tap on the secondary of the transformer, thus the e.m.f.s induced in each section of the secondary are equal, and when the potential of A is positive with respect to C, so is that of C positive with respect to B i.e.

$$v_{AC} = v = V_m \sin(\omega t)$$

$$v_{BC} = -v = -V_m \sin(\omega t)$$

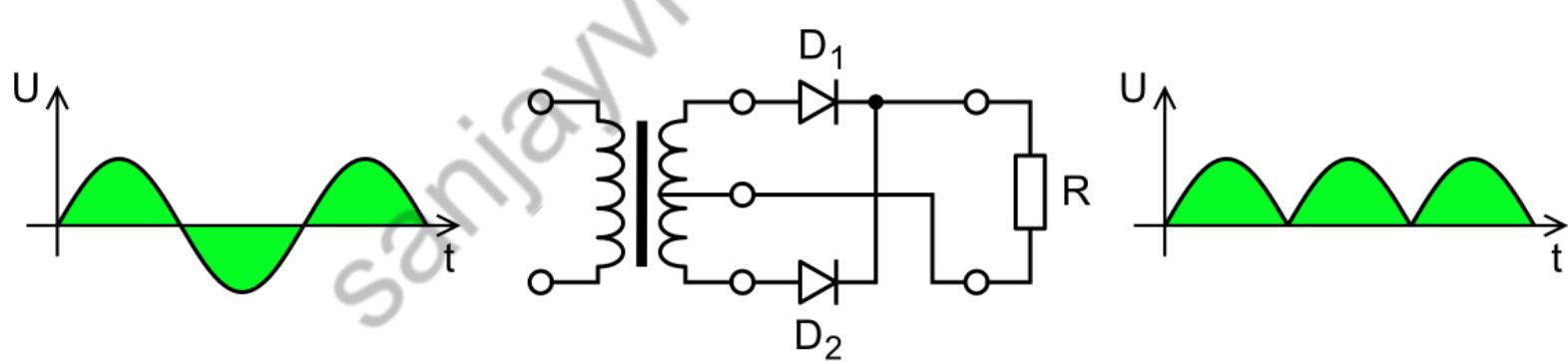

$$\text{Peak Inverse Voltage PIV} = 2 V_m$$

Full-Wave Rectifier

Mean/DC value of the load voltage V_R :

$$V_{dc} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d(\omega t) = \frac{2V_m}{\pi}$$


RMS value of the load voltage V_R :

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 \, d(\omega t)} = \frac{V_m}{\sqrt{2}}$$

Rectification efficiency $\eta = (V_{dc}/V_{rms})^2 = 8/\pi^2 \sim 80\%$


$$V_{DC} = V_{avg} = 0.64 V_m$$
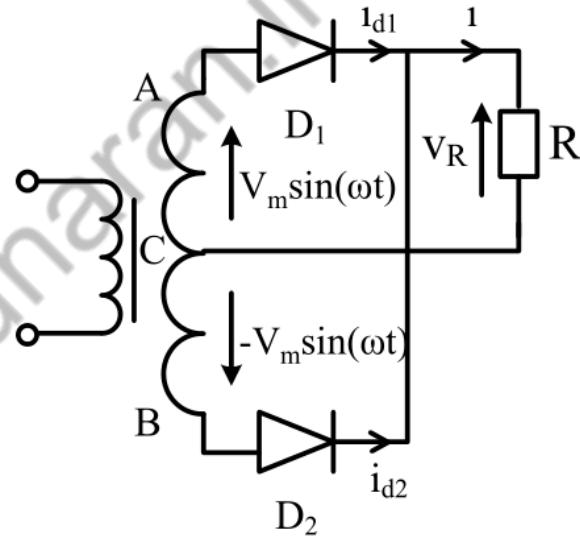
$$I_{DC} = \frac{2V_m}{\pi R} \quad I_{rms} = \frac{V_m}{\sqrt{2}R} \quad I_{MAX} = \frac{V_m}{R}$$



Peak Inverse Voltage PIV = $2V_m$

Full-Wave Rectifier

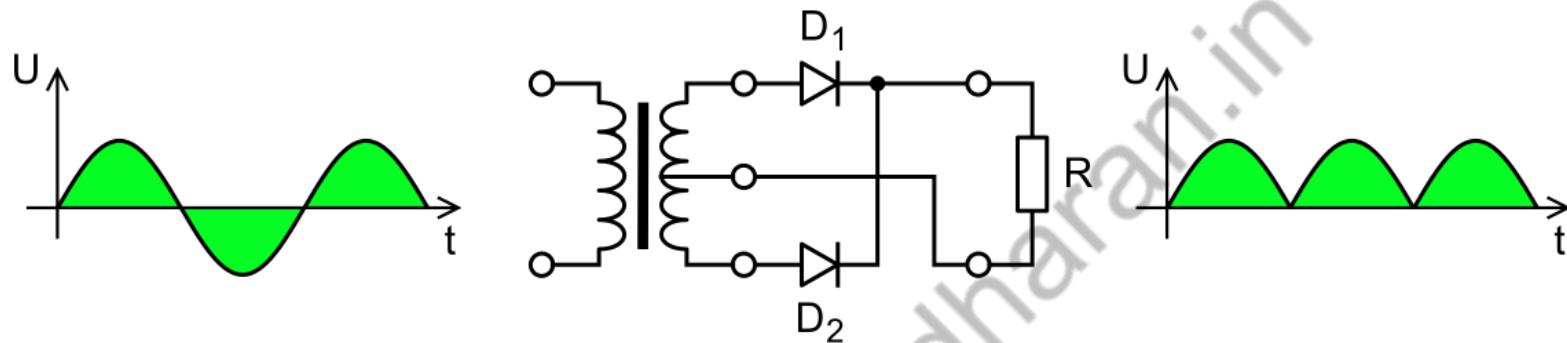


$$\text{Form Factor} = \frac{V_{rms}}{V_{avg}} = \frac{V_m/\sqrt{2}}{2V_m/\pi} = \frac{\pi}{2\sqrt{2}} = 1.11$$

$$\text{Ripple factor} = \sqrt{\left(\frac{I_m/\sqrt{2}}{2I_m/\pi}\right)^2 - 1} = 0.48$$


$$\begin{aligned}\eta &= \frac{Pdc}{Pac} = \frac{4}{\pi*\pi} I^2 max R_L / \frac{1}{2} I^2 max (R_L + R_F) \\ &= \frac{8}{\pi*\pi} \frac{1}{(1+2RF/RL)} = \frac{0.812}{(1+2RF/RL)}\end{aligned}$$

Efficiency of an ideal Full Wave Rectifier Circuit is = 81.2%

Bridge Rectifier

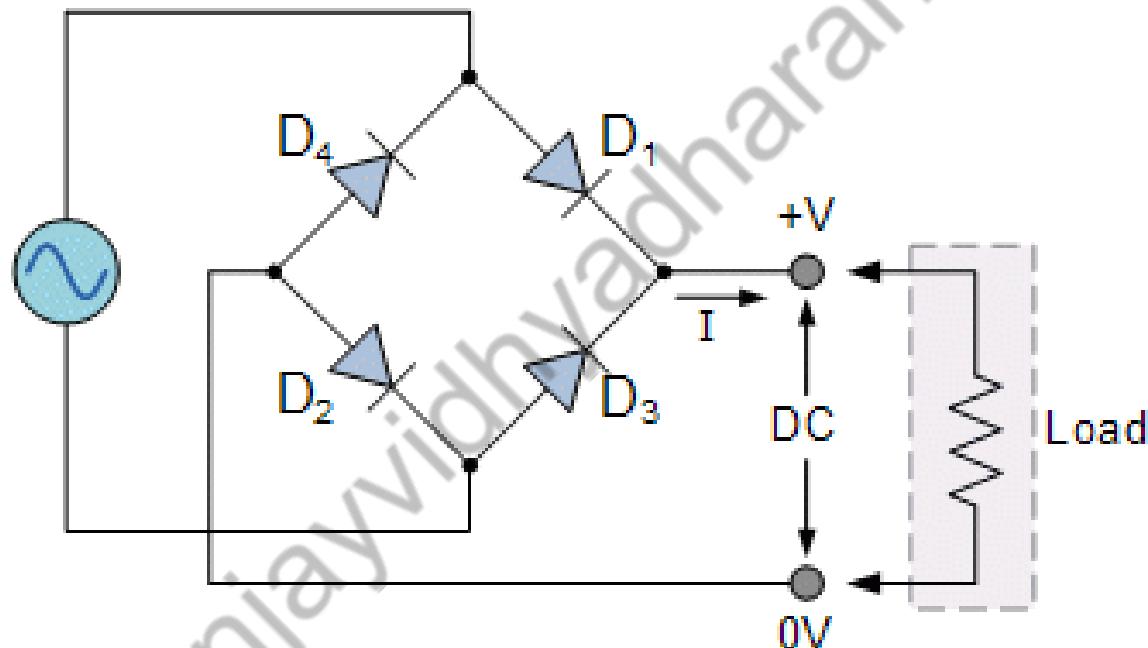

Bridge Rectifier

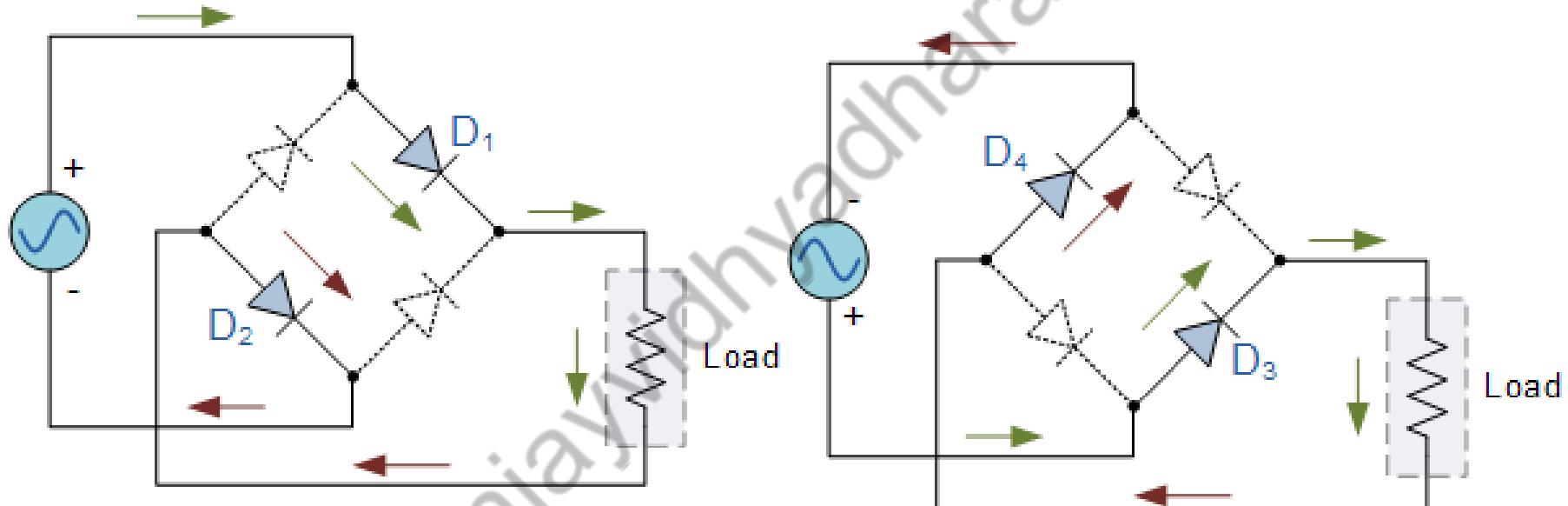

Peak Inverse Voltage PIV = V_m

Bridge Rectifier

Average value of output voltage: $V_{do} = (2\sqrt{2} / \pi)V_s \approx 0.9V_s = (2 / \pi)V_m = 0.637V_m$

where V_s and V_m are the RMS and peak values of input voltage.

Rectification Ratio = $P_{dc}/P_{ac} = 0.81$ or 81%

Form Factor (FF) of DC side voltage (or current) = $V_{rms}/V_{dc} = 1.11$

Ripple Factor = rms value of AC component/DC component = $(FF^2 - 1)^{1/2} = 0.48$



Peak Inverse Voltage PIV = V_m

Comparison Of Rectifiers



Parameters	Half-Wave Rectifiers	Full-Wave Rectifiers
Rectification Efficiency	40.6%	81.2%
Ripple Factor	1.21	0.482
Voltage Regulation	Good	Better
Fundamental frequency of ripple	Equal to Supply Frequency, f	Double of Supply Frequency, $2f$
Form Factor	1.57	1.11
Peak Factor	2	1.414
Number of diodes	Only 1	2 (4 in case of bridge rectifier)
Peak Inverse Voltage	V_s	$2 V_s / (V_s \text{ for Bridge})$
DC Output Voltage	$I_{max}/\pi RL$	$2/\pi RL I_{max}$

Peak Rectifier

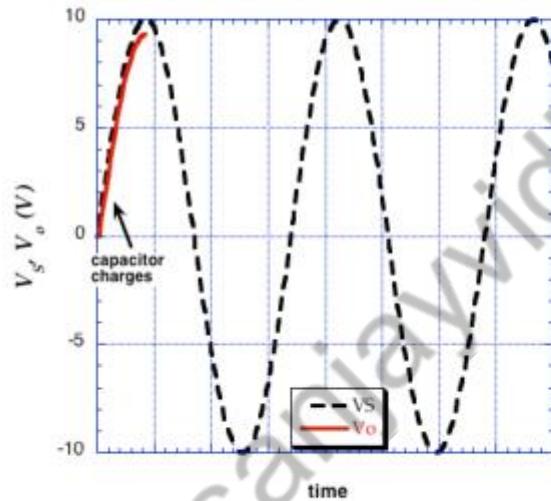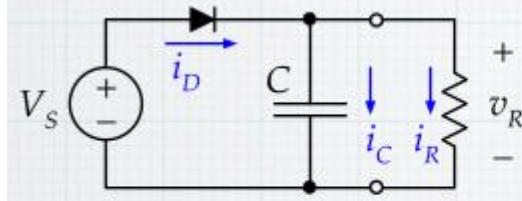Add a largish capacitor after the diode, in parallel with the load.





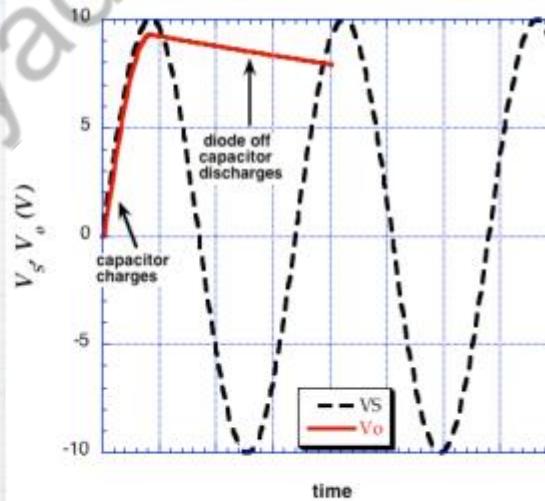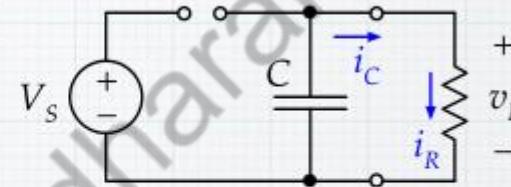Initially, diode is on & cap charges to $V_P - 0.7\text{ V}$.



While $V_S < v_C$, diode is off!
Cap discharges through load.

Peak Rectifier

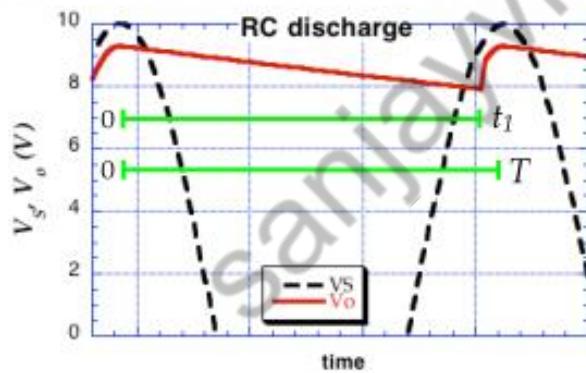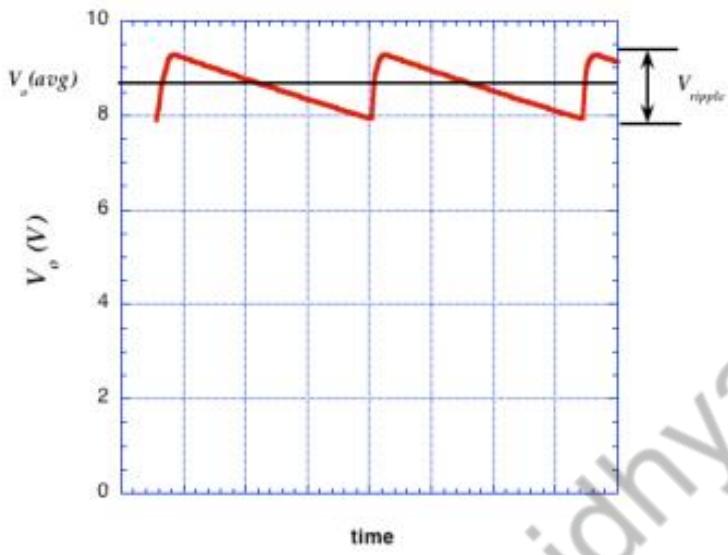

Not a perfect DC voltage at output. There is some variation (ripple) around an average value.

$$V_o(\max) = V_p - 0.7V$$


$$\begin{aligned} V_o(\min) &= [V_p - 0.7V] \exp\left(-\frac{t_1}{RC}\right) \\ &\approx [V_p - 0.7V] \exp\left(-\frac{T}{RC}\right) \end{aligned}$$

$$\begin{aligned} V_{ripple} &= V_o(\max) - V_o(\min) \\ &= [V_p - 0.7V] \left[1 - \exp\left(-\frac{T}{RC}\right)\right] \end{aligned}$$

$$V_o(\text{avg}) \approx V_o(\max) - \frac{V_{ripple}}{2}$$

t_1 = time when diode conducts again.

Peak Rectifier

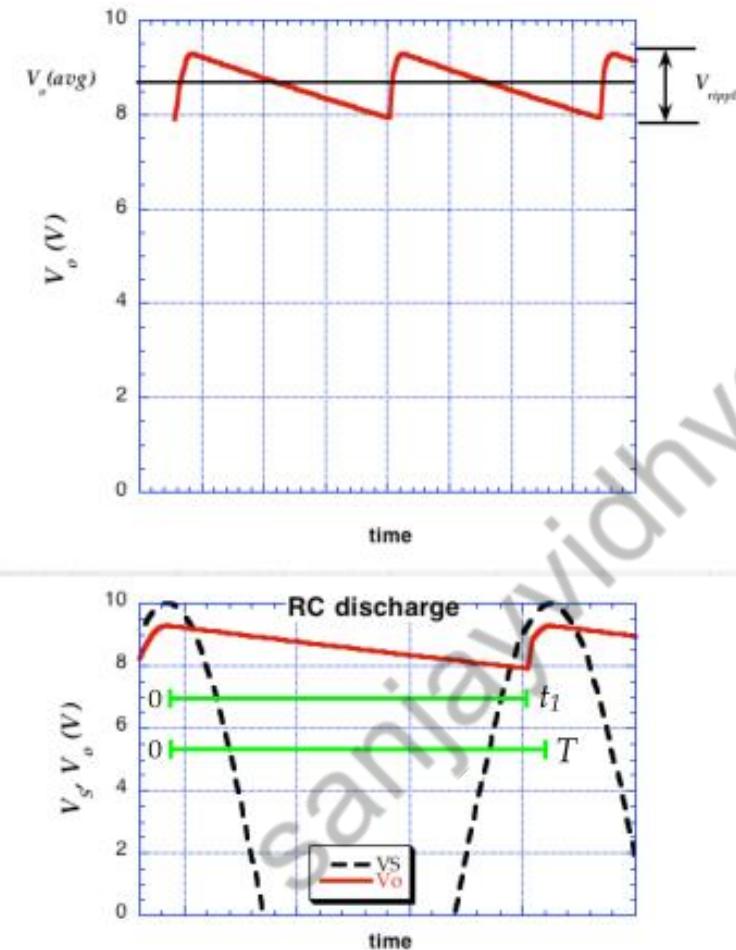

Not a perfect DC voltage at output. There is some variation (ripple) around an average value.

$$V_o(\text{max}) = V_p - 0.7V$$

$$\begin{aligned} V_o(\text{min}) &= [V_p - 0.7V] \exp\left(-\frac{t_1}{RC}\right) \\ &\approx [V_p - 0.7V] \exp\left(-\frac{T}{RC}\right) \end{aligned}$$

$$\begin{aligned} V_{\text{ripple}} &= V_o(\text{max}) - V_o(\text{min}) \\ &= [V_p - 0.7V] \left[1 - \exp\left(-\frac{T}{RC}\right) \right] \end{aligned}$$

$$V_o(\text{avg}) \approx V_o(\text{max}) - \frac{V_{\text{ripple}}}{2}$$

t_1 = time when diode conducts again.



Peak Rectifier

Full-wave peak rectifier

Placing a capacitor in parallel with the load, turns the circuit into a full-wave peak rectifier. It behaves essentially the same as the half-wave peak rectifier except with twice the frequency (half the period).

$$V_S(t) = V_p \sin\left(\frac{2\pi}{T}t\right)$$

$$V_p = 8 \text{ V.}$$

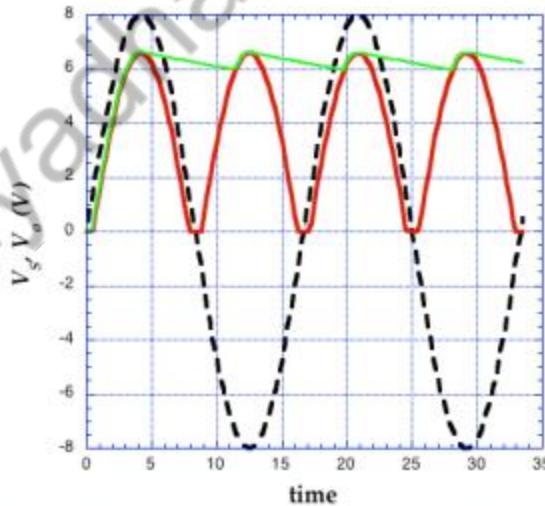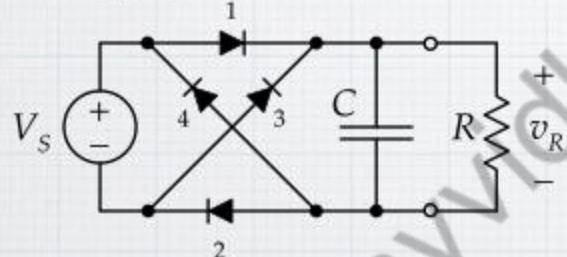

The ripple voltage is calculated in exactly the same way, except that the period is cut in half (frequency doubled).


$$V_{ripple} = [V_p - 1.4V] \left[1 - \exp\left(-\frac{T}{2RC}\right) \right]$$

Same as doubling
capacitance!

Practical Diode Specifications

1N4007 Characteristics:

- Maximum Recurrent Peak Reverse Voltage 1000V
- Maximum RMS Voltage 700V
- Maximum DC Blocking Voltage 1000V
- Average Forward Current: 1.0A
- Peak Forward Surge Current: 30A
- Maximum Instantaneous Forward Voltage: 1.0V
- Maximum DC Reverse Current At Rated DC Blocking Voltage: $5.0\mu A$ @ $25^\circ C$
- Typical Junction Capacitance: 15pF
- Typical Reverse Recovery Time: 2.0us
- Operating Temperature: $-55^\circ C \sim 150^\circ C$

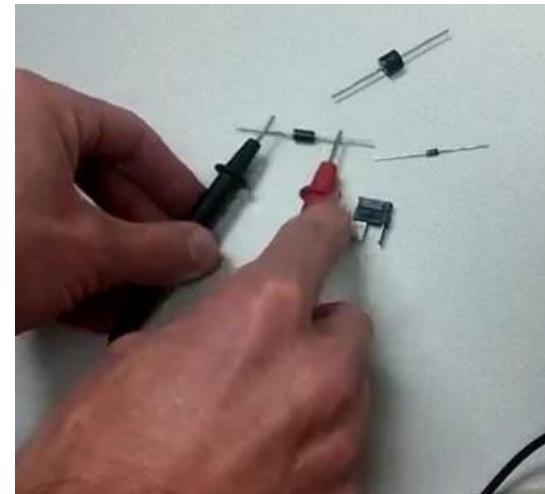

Practical Diode Specifications

VS-95PF80



MAJOR RATINGS AND CHARACTERISTICS

PARAMETER	TEST CONDITIONS	VALUES	UNITS
$I_F(AV)$		95	A
	T_C	140	°C
$I_F(RMS)$		149	A
	50 Hz	2000	A
I_{FSM}	60 Hz	2090	
	50 Hz	20.000	A^2s
I^2t	60 Hz	18 180	
	Range	400 to 1200	V
T_J		- 55 to 180	°C

ELECTRICAL SPECIFICATIONS

VOLTAGE RATINGS				
TYPE NUMBER	VOLTAGE CODE	V_{RRM} , MAXIMUM REPETITIVE PEAK REVERSE VOLTAGE V	V_{RSM} , MAXIMUM NON-REPETITIVE PEAK REVERSE VOLTAGE V	I_{RRM} MAXIMUM AT $T_J = 150$ °C mA
95PF(R)...(W)	40	400	500	9
	80	800	960	
	120	1200	1440	

Thank you