



# **Electrical Science: 2021-22**

## **Lecture 23**

### **Diode Clipper and Clamper Circuits**

**By Dr. Sanjay Vidhyadharan**

# Clippers

- **Clipping circuit:** A wave shaping circuit which controls the shape of the output waveform by removing or clipping a portion of the applied wave.
- Half wave rectifier is the simplest example. (It clips negative half cycle).
- Also referred as voltage limiters/ amplitude selectors/ slicers.
- Applications:
  - In radio receivers for communication circuits.
  - In radars, digital computers and other electronic systems.
  - Generation for different waveforms such as trapezoidal, or square waves.
  - Helps in processing the picture signals in television transmitters.
  - In television receivers for separating the synchronising signals from composite picture signals

# Clippers

## THUMB RULE


Action of biasing on diode

- When diode is forward biased, it acts as a closed switch ( ON state).
- When diode is reverse biased, it acts as an open switch ( OFF state).


sanjayviharacharan.in

# Clippers

Series Positive Clipping:

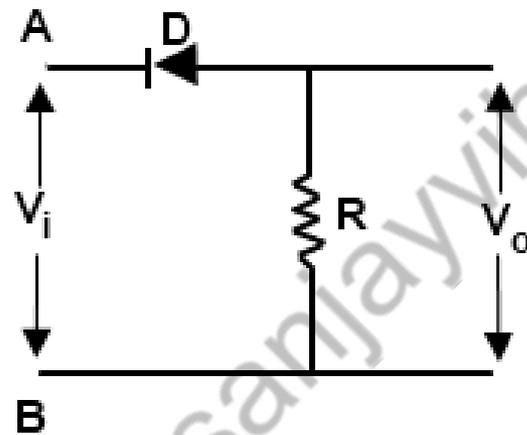


(a) Positive Clipper

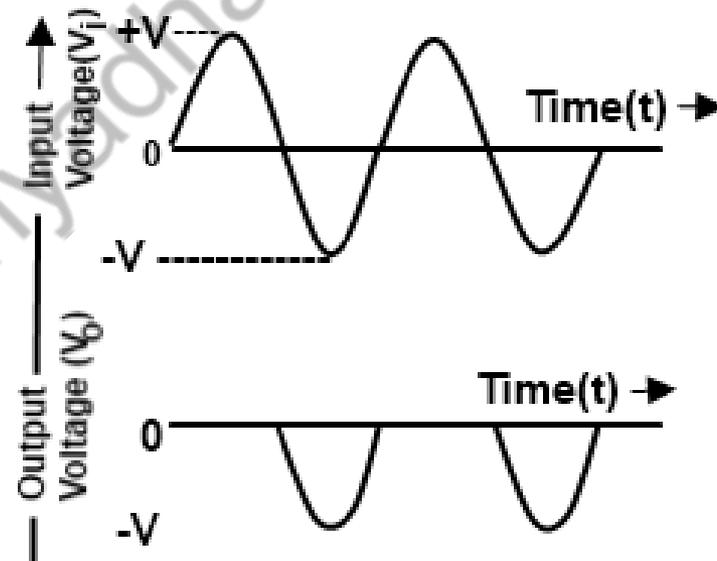

(b) Output Waveform


# Clippers

Series Negative Clipping:

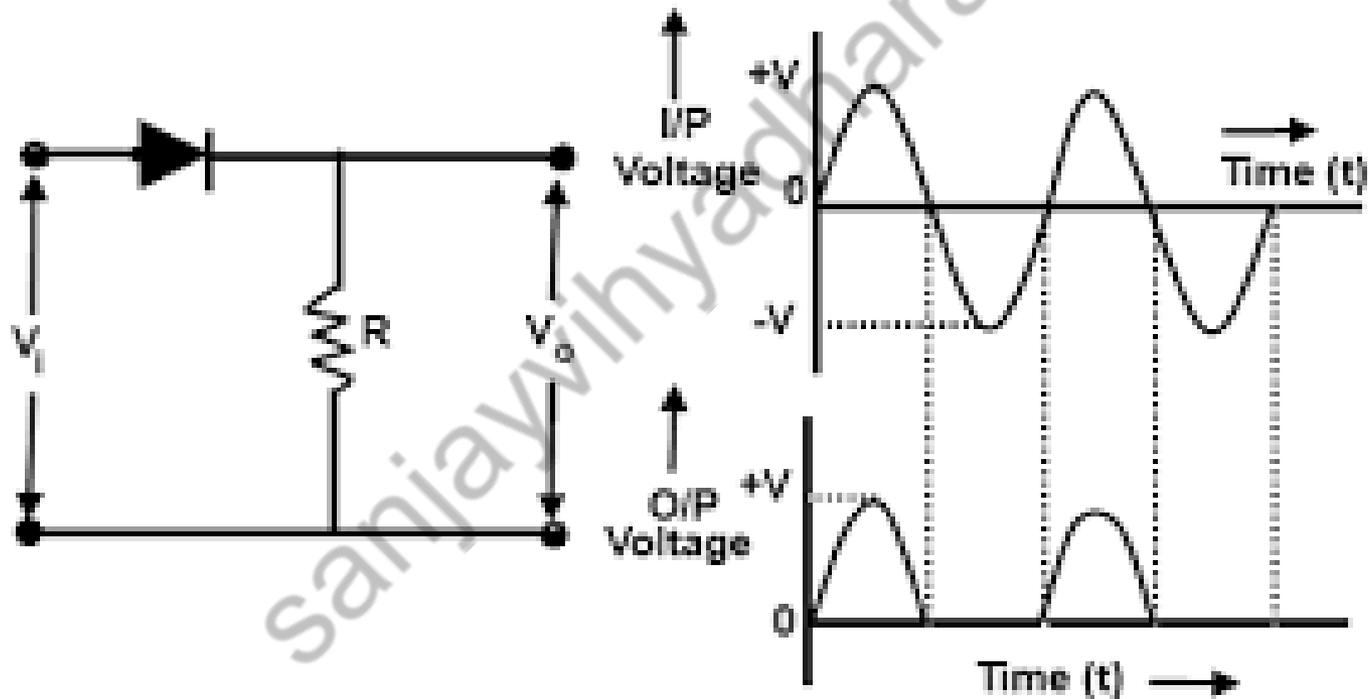


# Clippers

Shunt Positive Clipping:

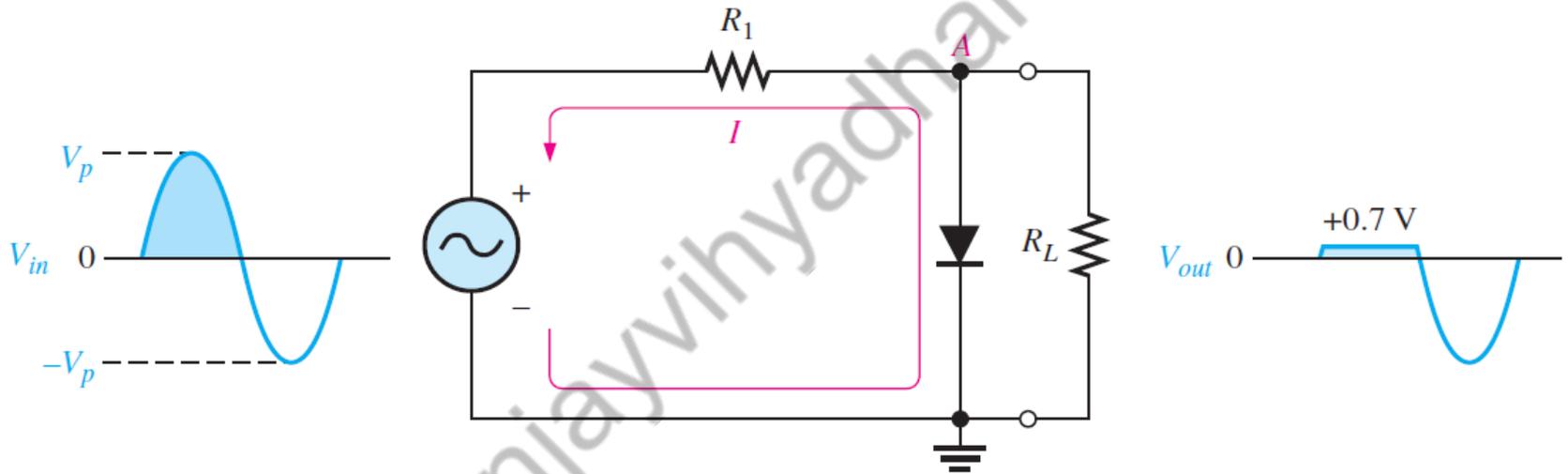

# Clippers


Shunt Negative Clipping:

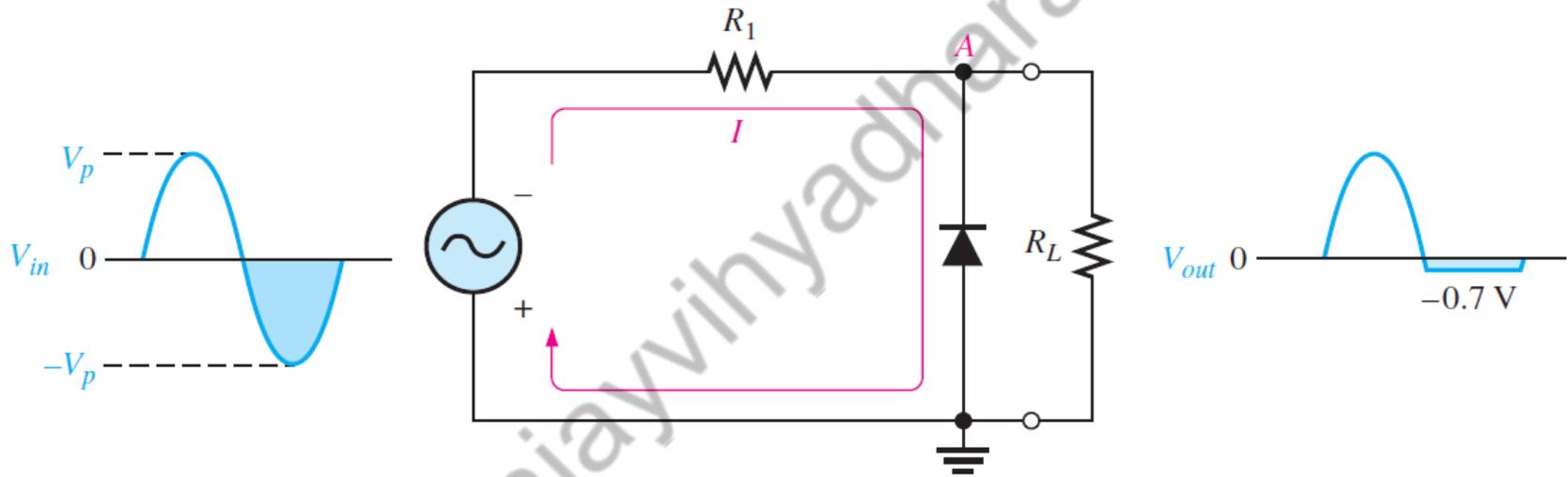
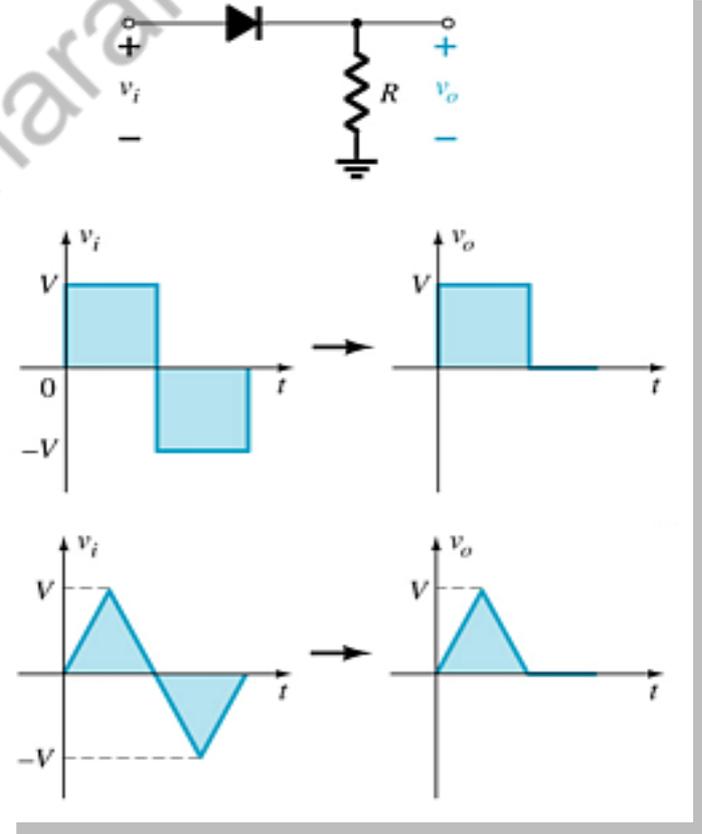
# Clippers



The diode in a **series clipper** “clips” any voltage that does not forward bias it:

- A reverse-biasing polarity
- A forward-biasing polarity less than 0.7 V (for a silicon diode)




# Clippers

## Biased Series Clippers

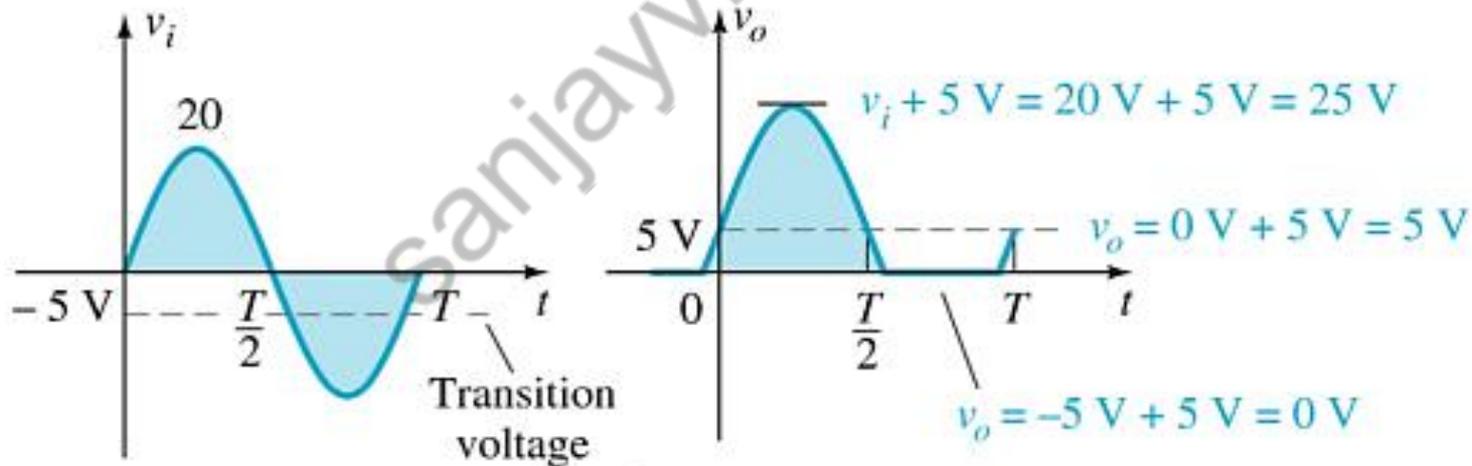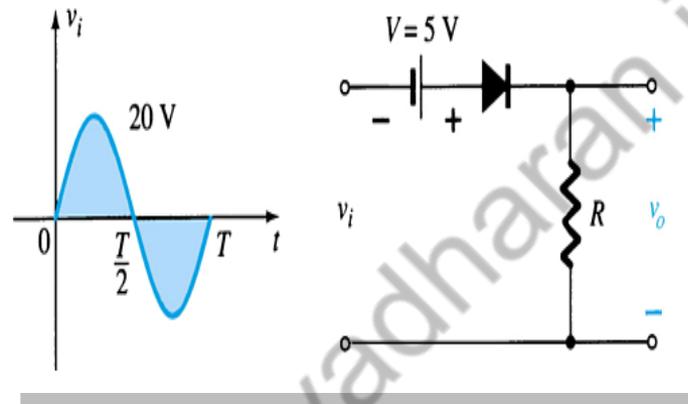


# Clippers

## Biased Clippers

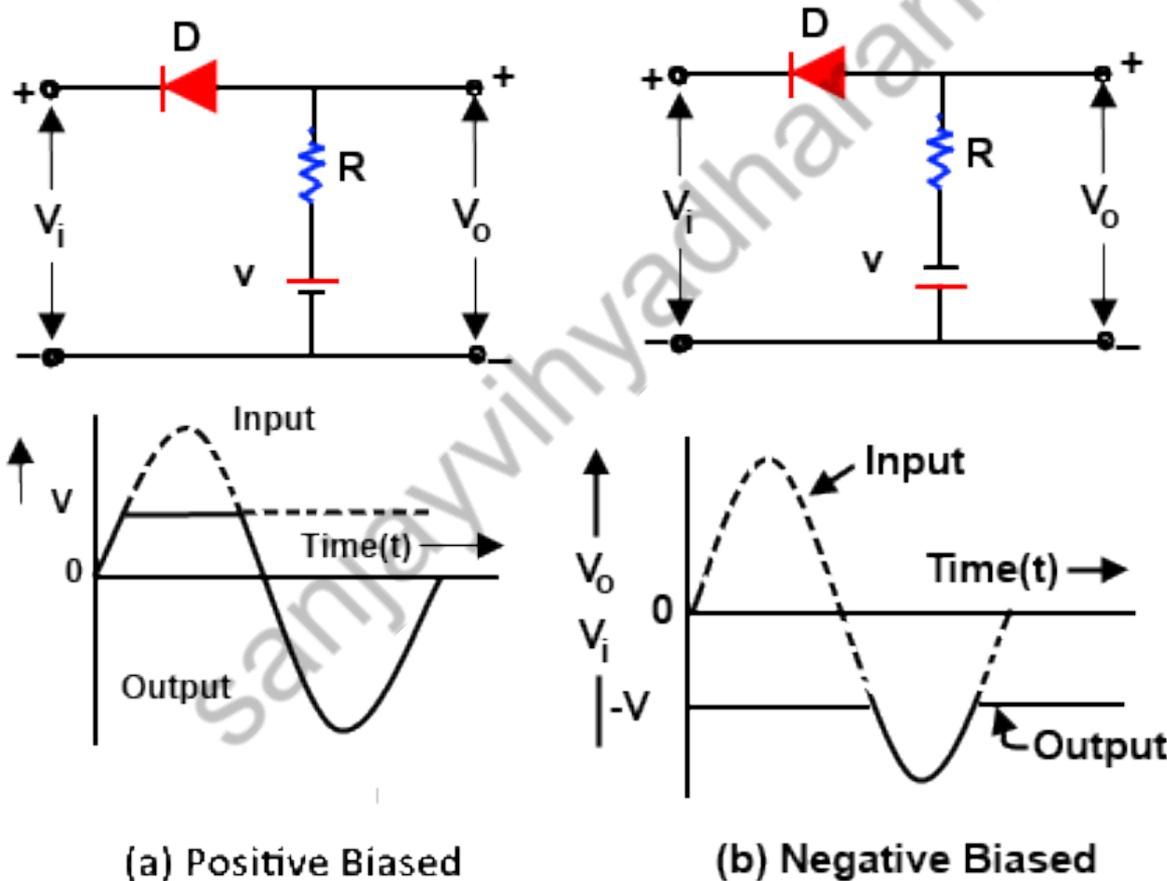


# Clippers

## Biased Clippers

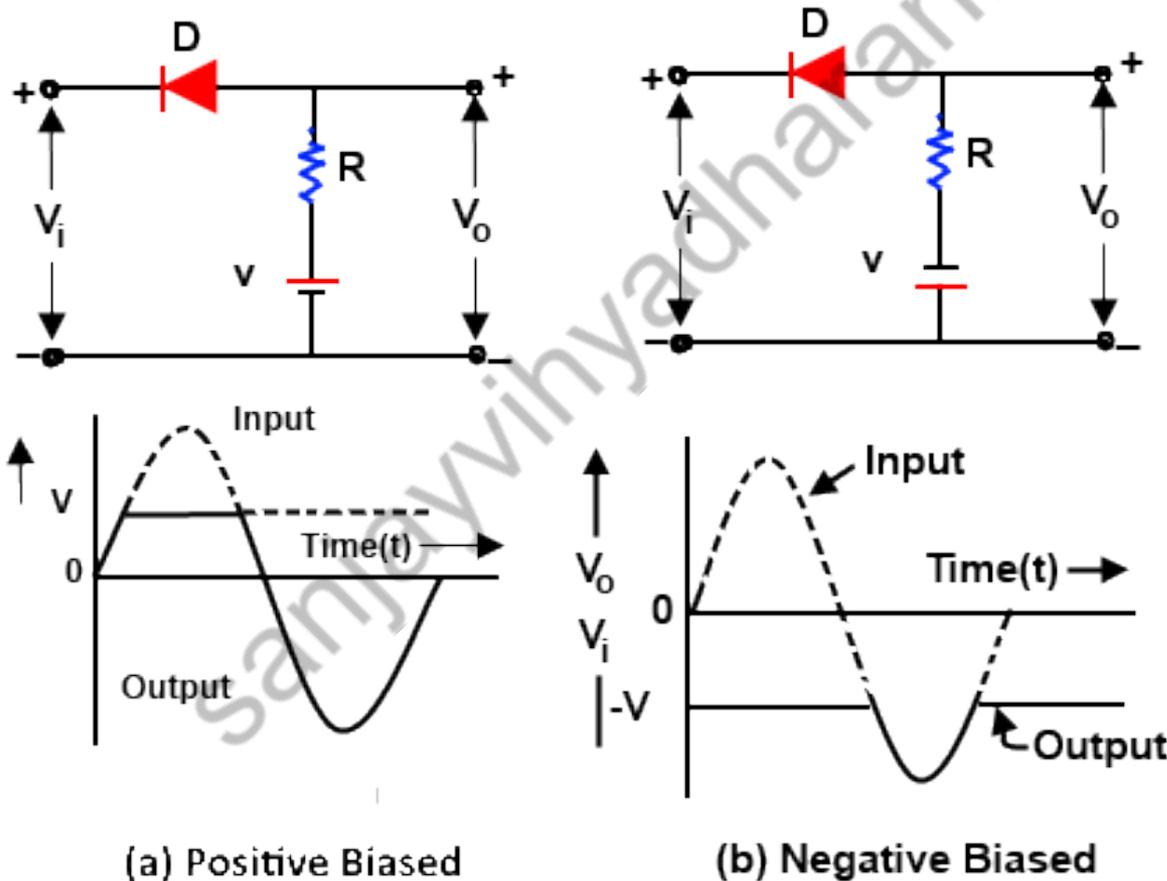


# Clippers


## Combination Clipper

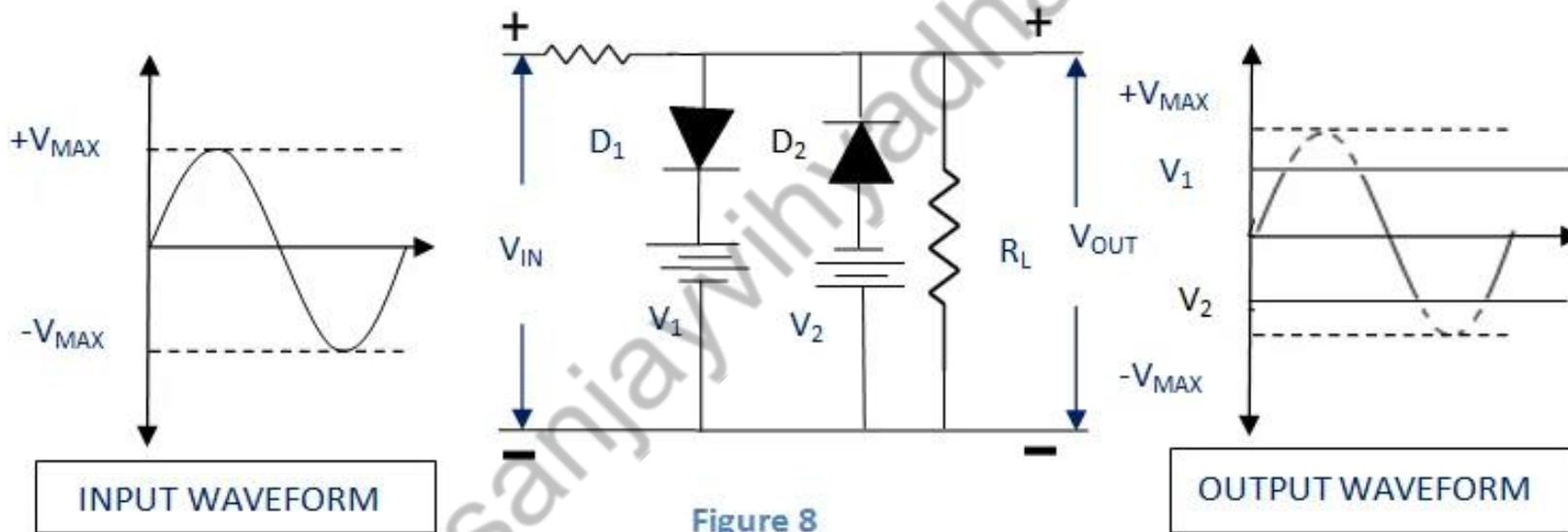



# Zener Diodes

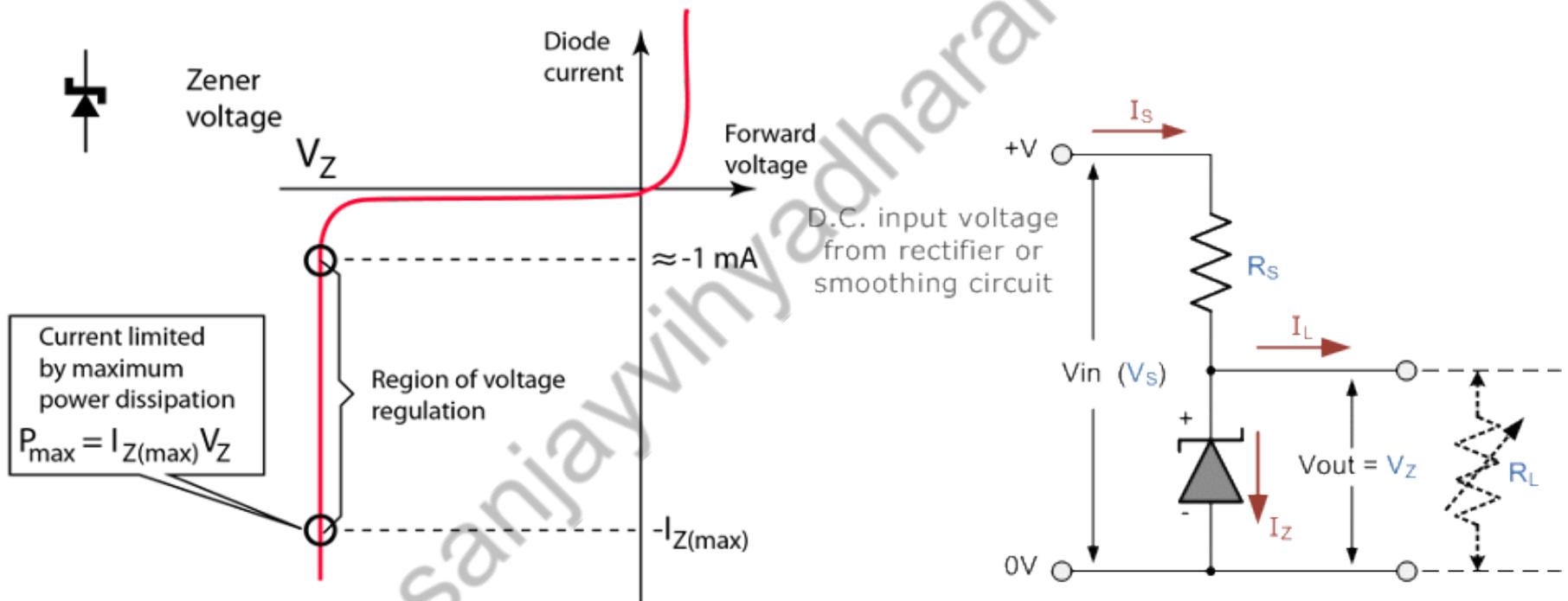



# Zener Diodes

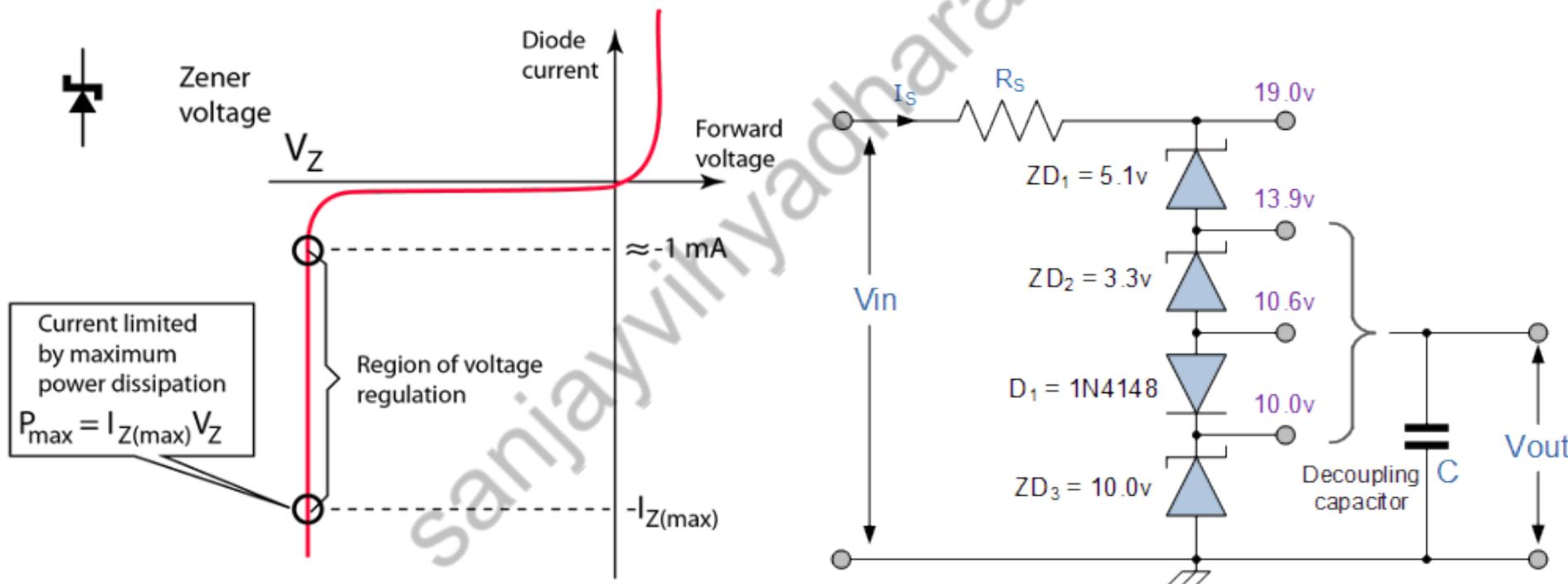


# Zener Clippers

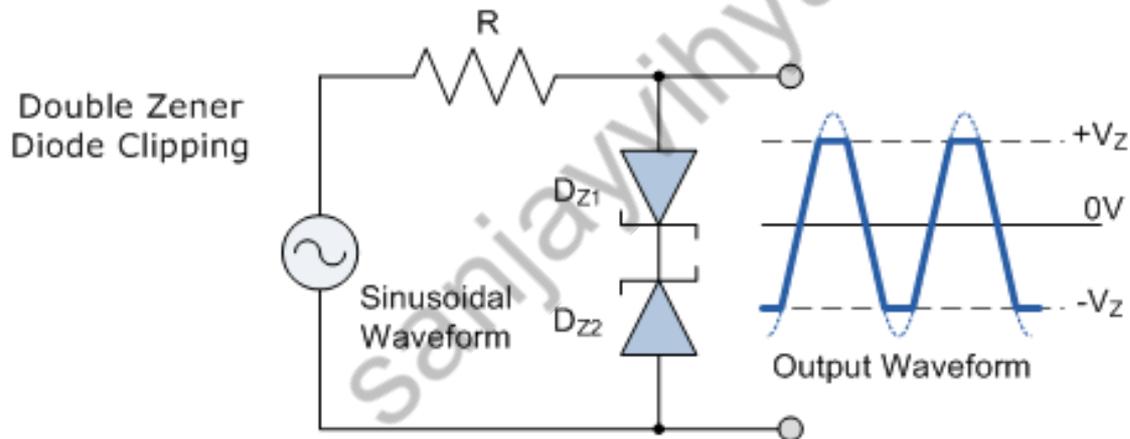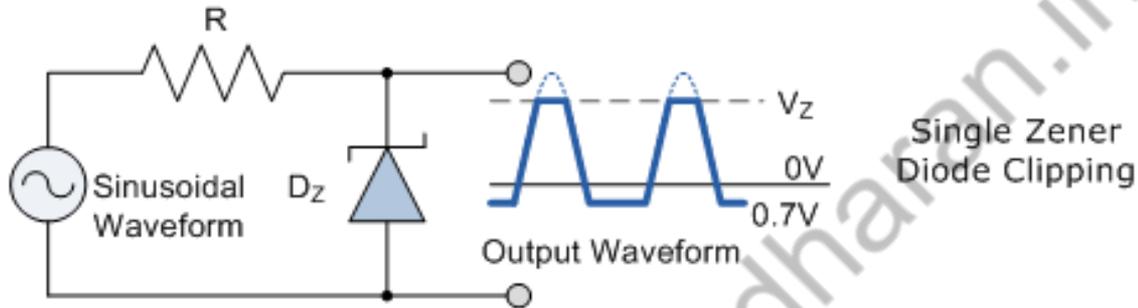


# Clampers

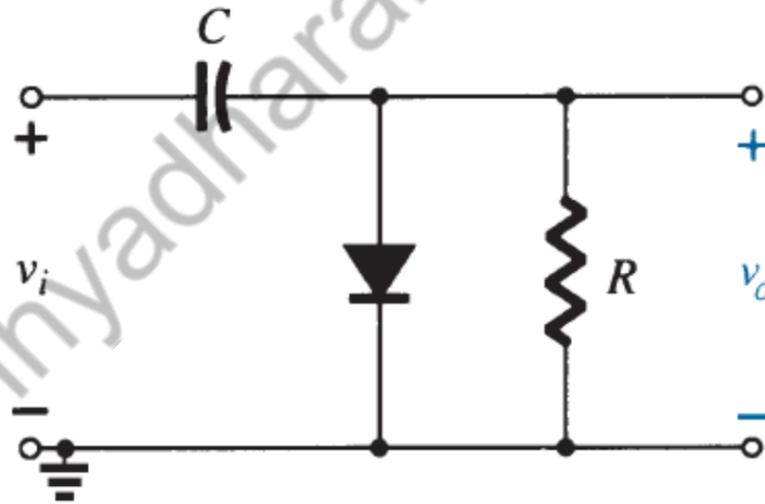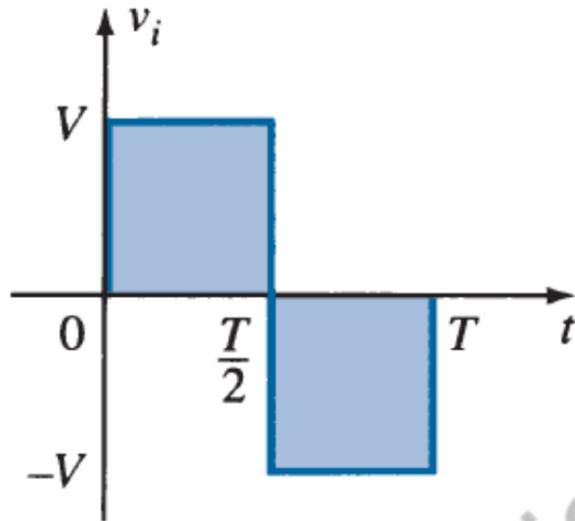


# Clampers

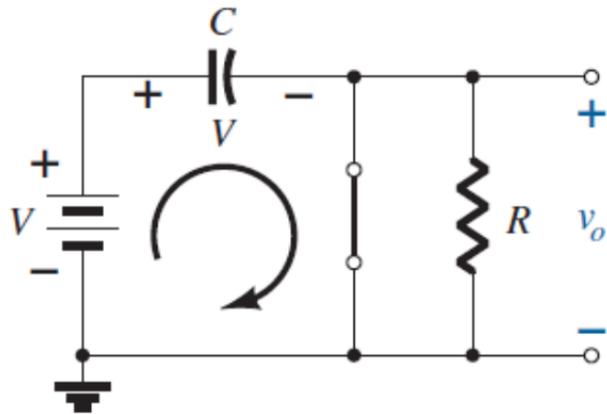

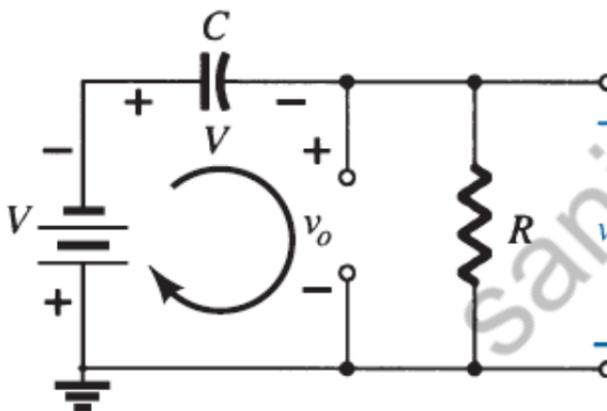Circuit during Diode ON  
(positive half cycle of supply)




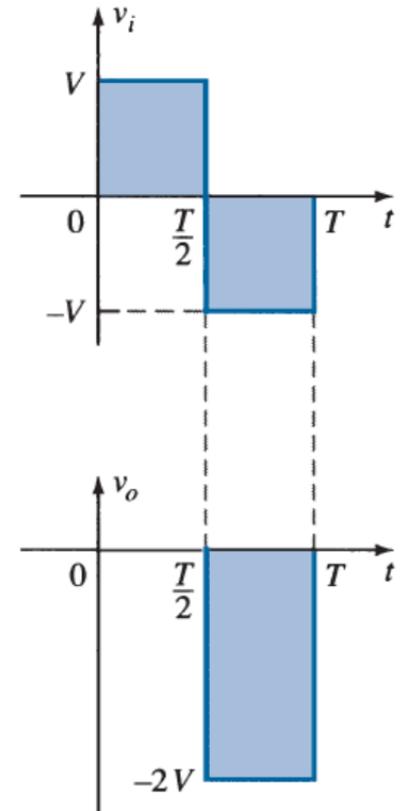Circuit during Diode OFF  
(negative half cycle of supply)




Input and Output voltage waveform




# Clampers

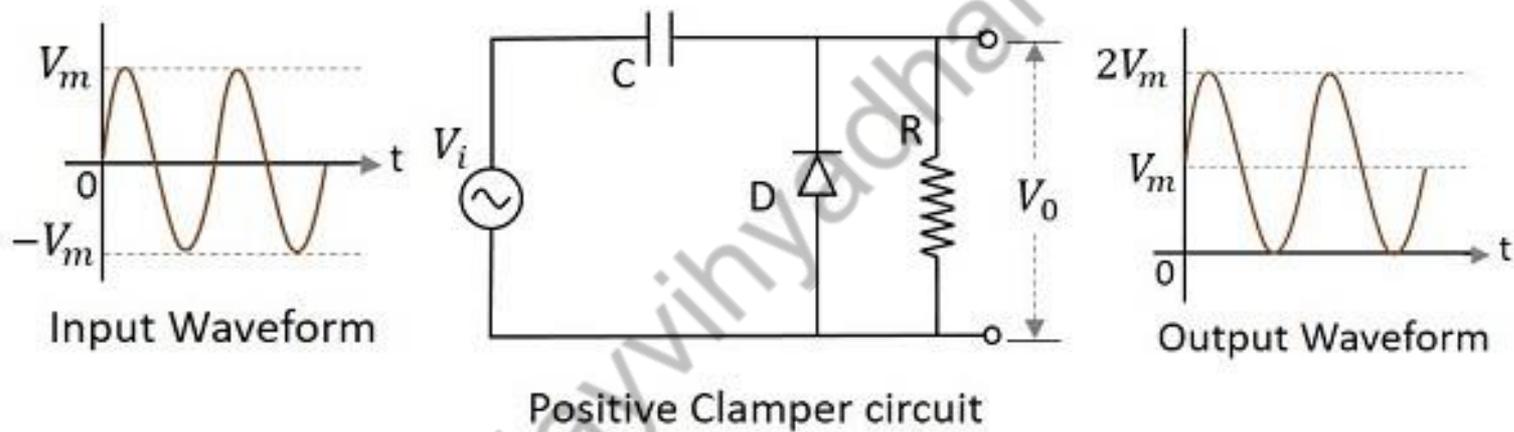

# Clampers

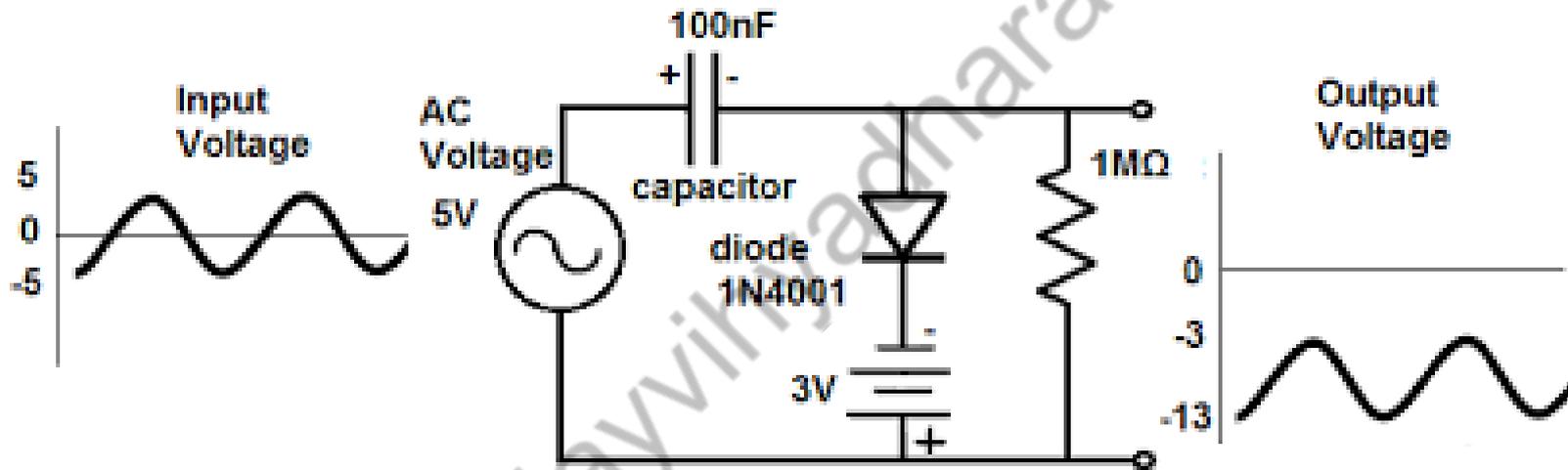

# Clampers

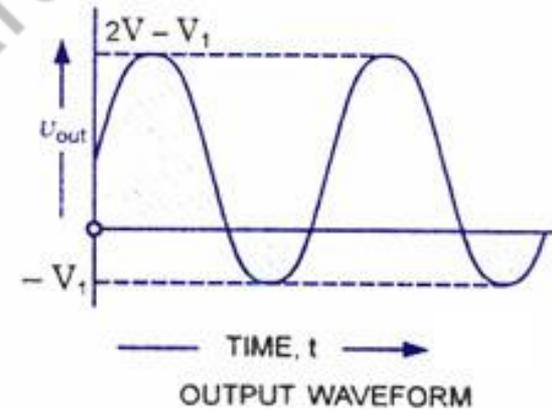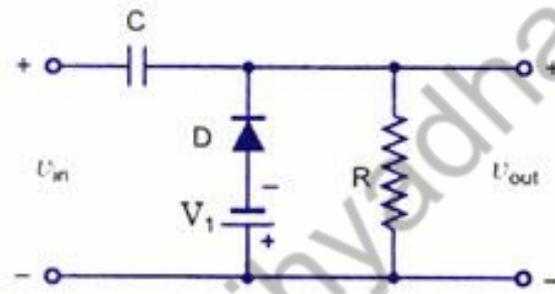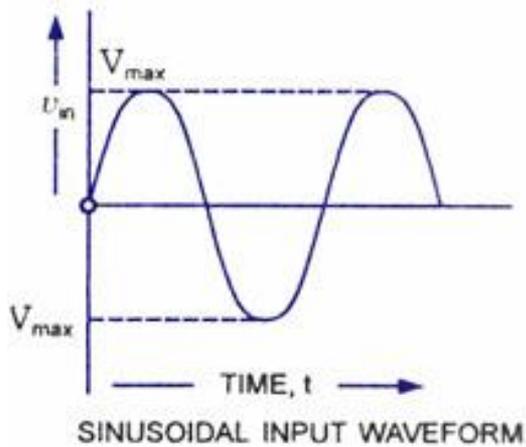

*Different Clamping Circuits*

**Thank you**

sanjayviharadharan.in