

VLSI Design Using LT SPICE

Wing Commander (Retd.) Dr. Sanjay Vidhyadharan
Dept. of EEE (WILP)
BITS Pilani



Aim of the Workshop

➤ Session 1

- Introduction to CMOS Design
- Importing TSMC 180 nm Technology File in LT SPICE
- NMOS and PMOS Characterization

➤ Session 2

- Inverter Design and Characterization
 - Home Assignment : VCO

➤ Session 3

- Static CMOS Design: Full Adder Design
 - Home Assignment : SR Latch

➤ Session 4

- Dynamic CMOS Design: Dynamic Full Adder Design
 - Home Assignment : D-Flip Flop

Aim of the Workshop

➤ Session 5

- **Pass Transistor Logic: PTL Full Adder Design**
 - **Home Assignment : Multiplexer Design**

➤ Session 6

- **Memory Design : 6T SRAM**
 - **Home Assignment : 4T / 7T SRAM , DRAM**

sanjayvidhyajadharam.in

History of CMOS

- **Original idea of a FET introduced by Julius Lilienfeld in the year of 1925**
- **A structure closely reassembling the MOSFET was proposed in 1935 by Oskar Heil**
- **In 1960s MOSFETs began to enter production**
- **In 1963 Fairchild company produces gates using both nMOS and pMOS transistor → earning the name **CMOS****
- **CMOS circuits consumed only nanowatts of power → six order of magnitude less than their bipolar counterparts.**

Pentium



1993 : Technology : 0.8 μm (16.7 mm by 17.6 mm)

Latest CPUs and GPUs

Latest Trends :- Intel : 14 nm AMD : 7nm





- Billions of Transistors/ Chip
- Frequency of Operation in GHz
- Complex Computational Capability



Limitations of CMOS Technology


ITRS Prediction of Power Consumption

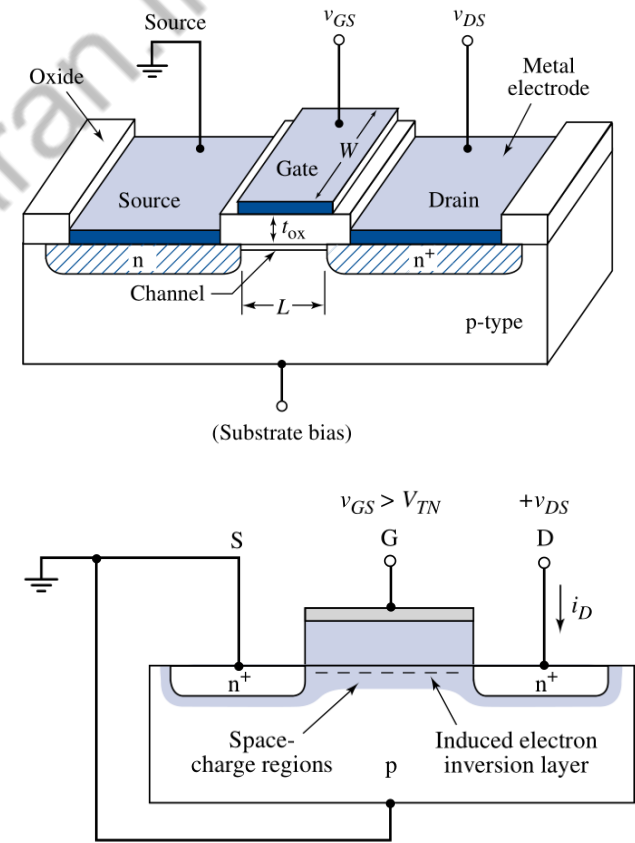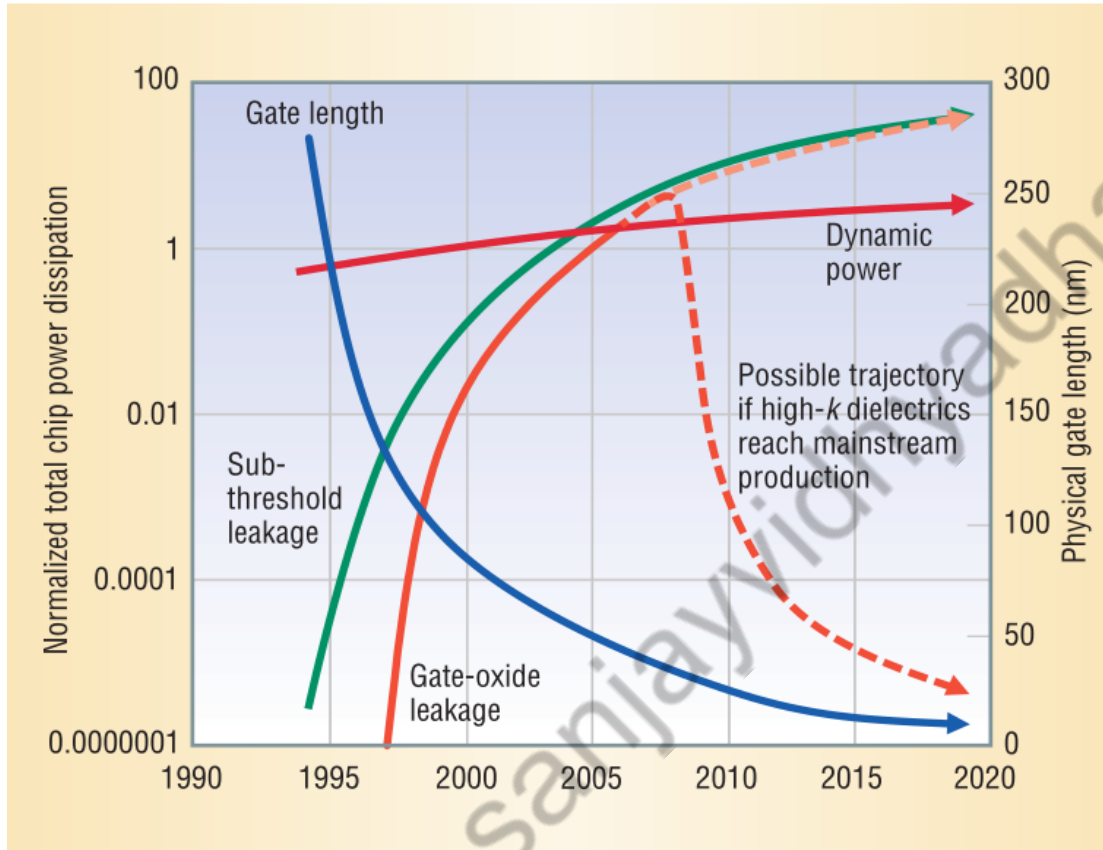

[1] Semiconductor Industry Assoc., International Technology Roadmap for Semiconductors, 2002 Update; <http://public.itrs.net>.

Limitations of CMOS Technology

Intel's Prediction of Power Consumption

 




[2] Online Available: <http://computerscience.chemeketa.edu/cs160Reader/Parallel Processing/MooresLaw.html>

MOSFET OPERATION AS SWITCH

Switch OFF

NMOSFET

Switch ON

   

I_{OFF}
Ideal = 0 Practically in pico amperes



R_{OFF}
Ideal = ∞ Practically in Mega/Giga Ohms

I_{ON}
Ideal = ∞ Practically in micro amperes

R_{ON}
Ideal = 0 Practically in few Ohms

MOSFET REGION OF OPERATION



NMOSFET

  

Cut Off	$V_{GS} \leq V_T$	$I_{DS} = 0$
Linear	$V_{GS} > V_T, V_{DS} \leq V_{GS} - V_T$	$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$
Saturation	$V_{GS} > V_T, V_{DS} > V_{GS} - V_T$	$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$

MOSFET OPERATION AS SWITCH



NMOSFET AS SWITCH

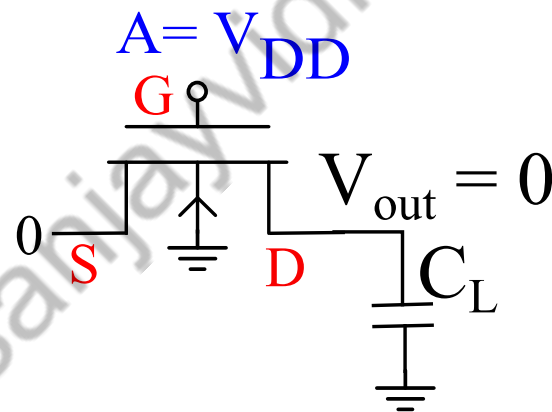 

➤ NMOS can pass perfect 0 but not 1

MOSFET OPERATION AS SWITCH

PMOSFET

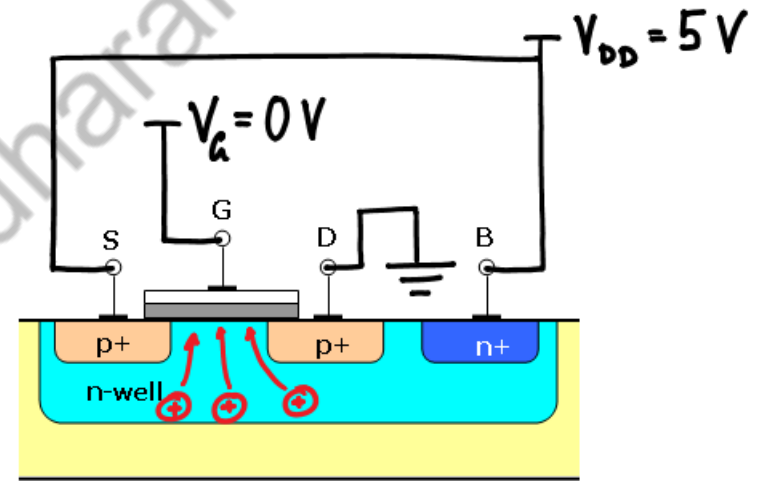 


I_{OFF}
Ideal = 0 Practically in pico amperes

R_{OFF}
Ideal = ∞ Practically in Mega Ohms

I_{ON}
Ideal = ∞ Practically in micro amperes



R_{ON}
Ideal = 0 Practically in few Ohm

MOSFET OPERATION AS SWITCH

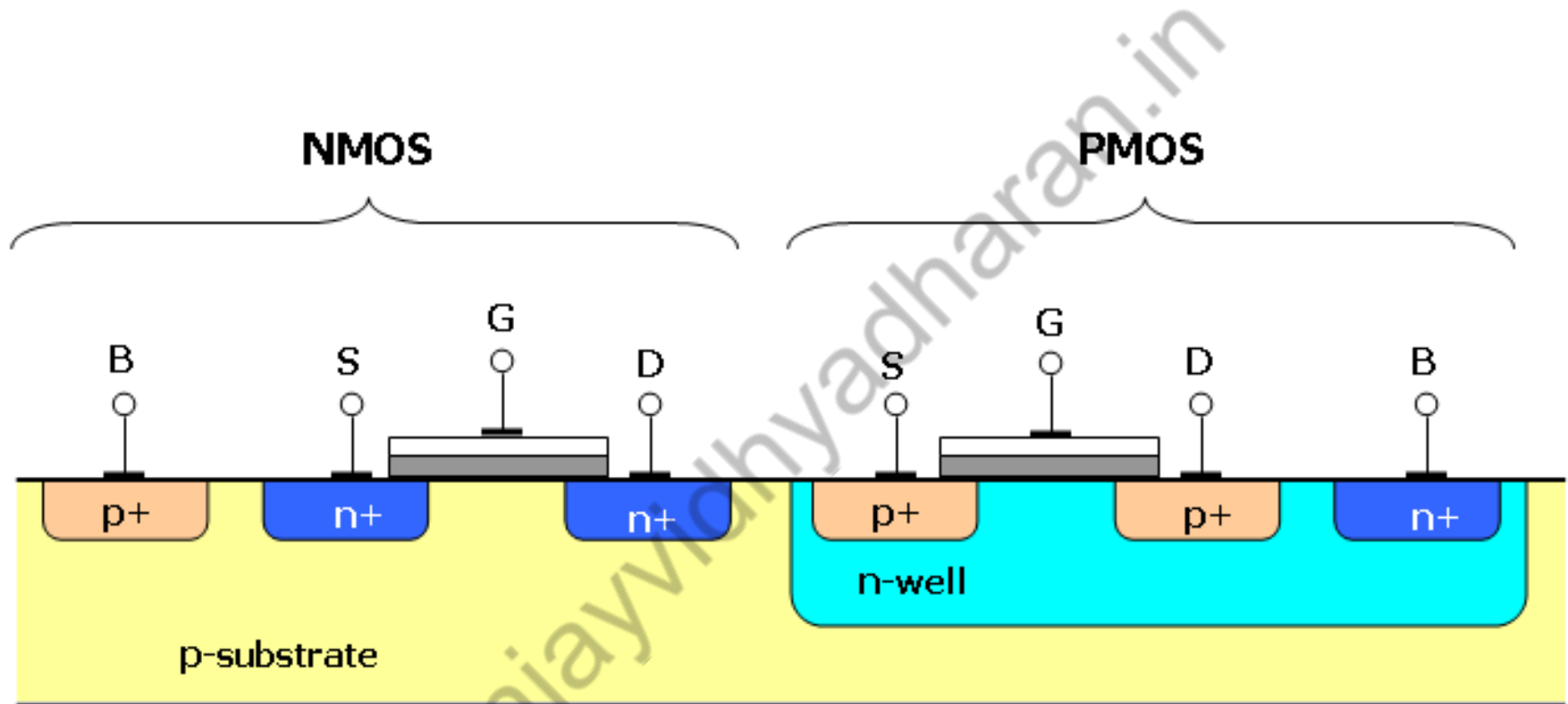



MOSFET OPERATION AS SWITCH

PMOSFET AS SWITCH

  



➤ PMOS pass perfect 1 but not 0

MOSFET BODY CONNECTION

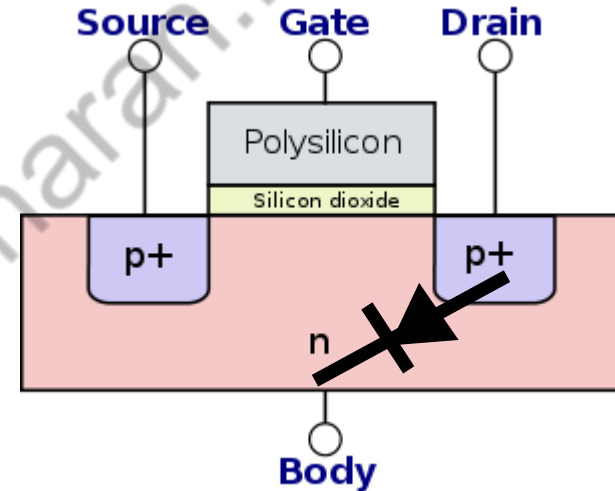
 


- NMOS Body to Lowest Possible Potential (Gnd)
- PMOS Body to Highest Possible Potential (V_{DD})


MOSFET BODY CONNECTION

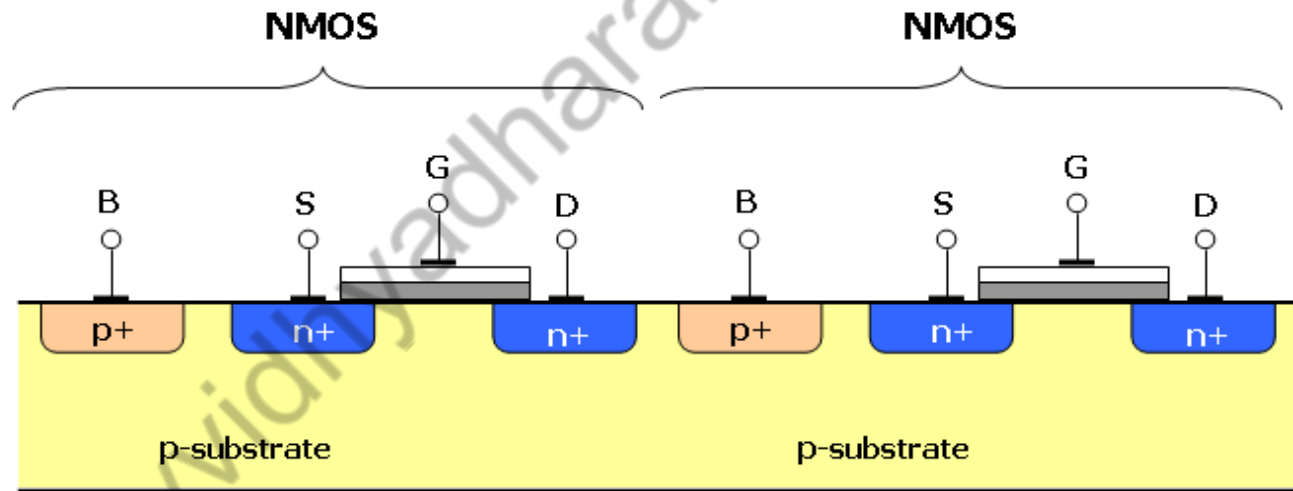 

MOSFET BODY CONNECTION

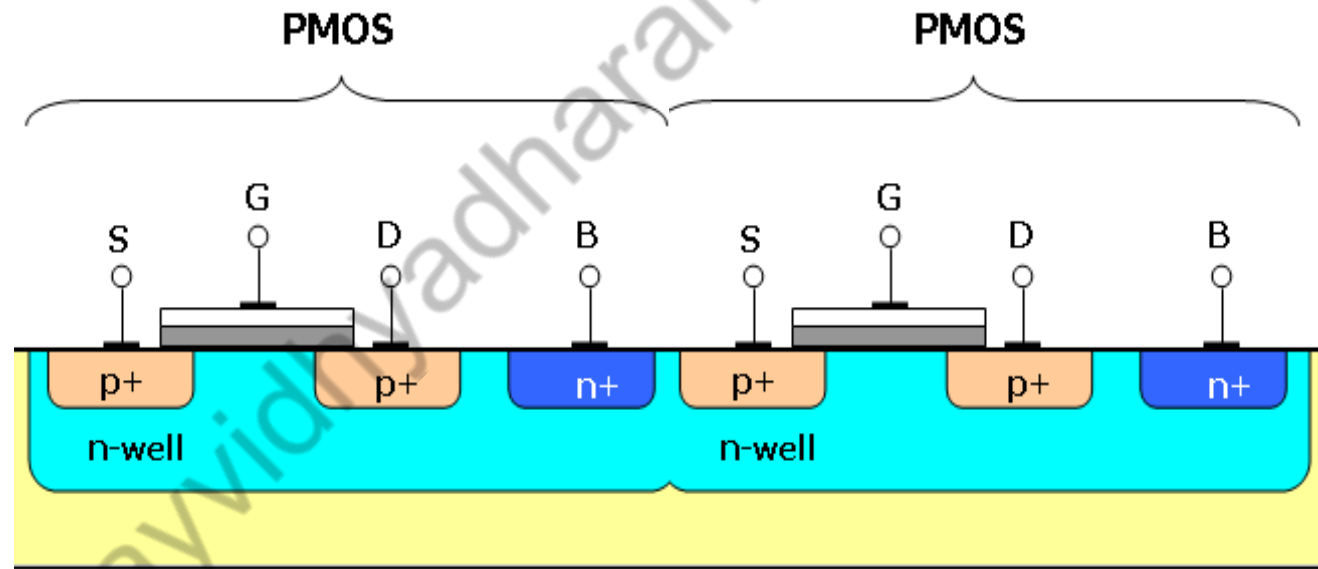 


MOSFET BODY CONNECTION

 


- MOS Double well : Body not same as Substrate

Power Dissipation in CMOS Circuits

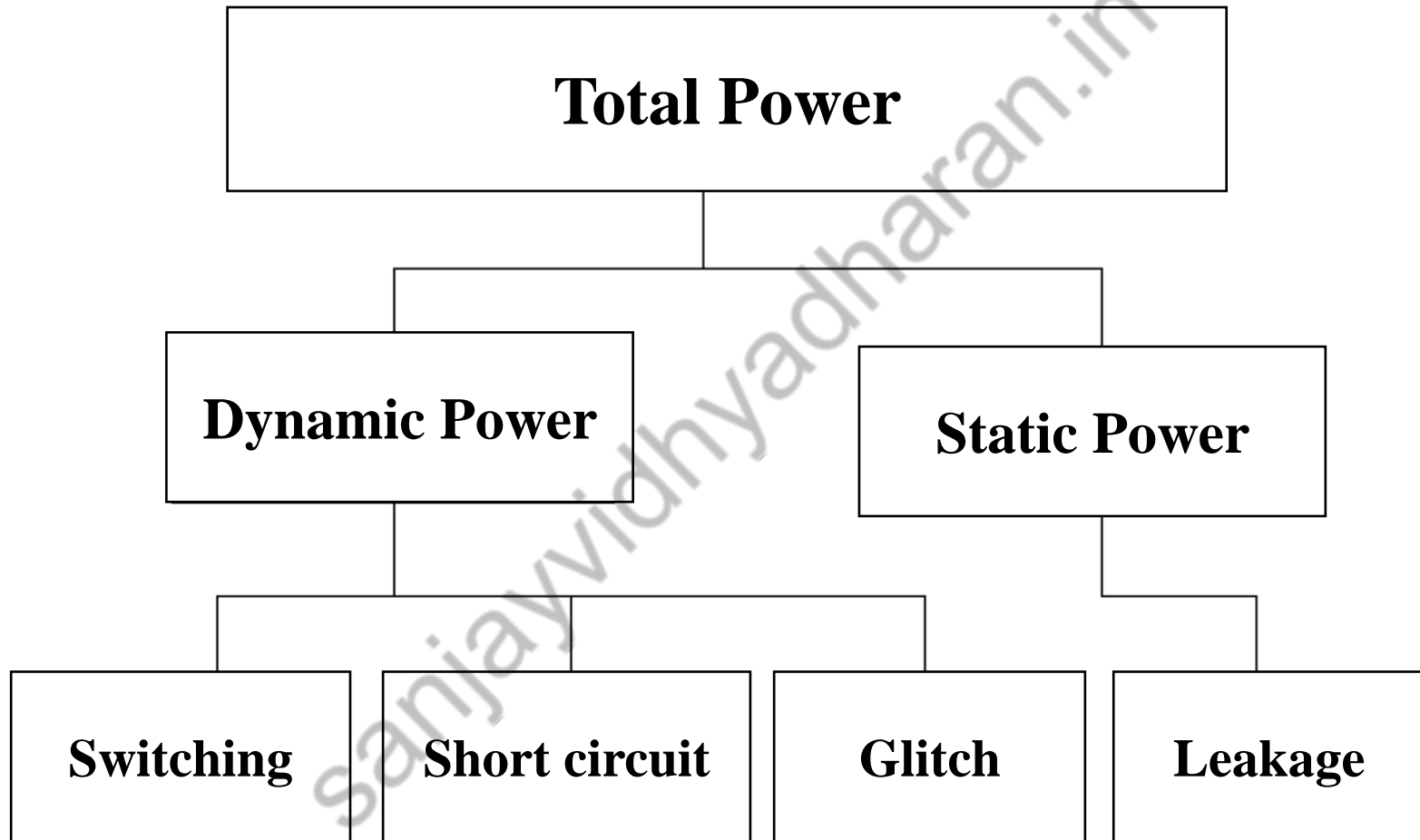

Static Loss

 

Static Power Dissipation in CMOS

Static Loss


➤ Causes for High Static Power Consumption

Effect of Decreasing V_{DD} on Delay



$$\text{Propagation Delay } (t_{pd}) = \frac{K_1 C_L}{I_D} = \frac{K_2 C_L}{(V_{DD} - V_{th})^2}$$

Effect of Decreasing V_{th} on Power


 
- Intel estimated leakage power consumption at more than 50W for a 100nm technology node.
- Leakage depends strongly on a Threshold voltage (V_{th}) of the transistor



Static Loss

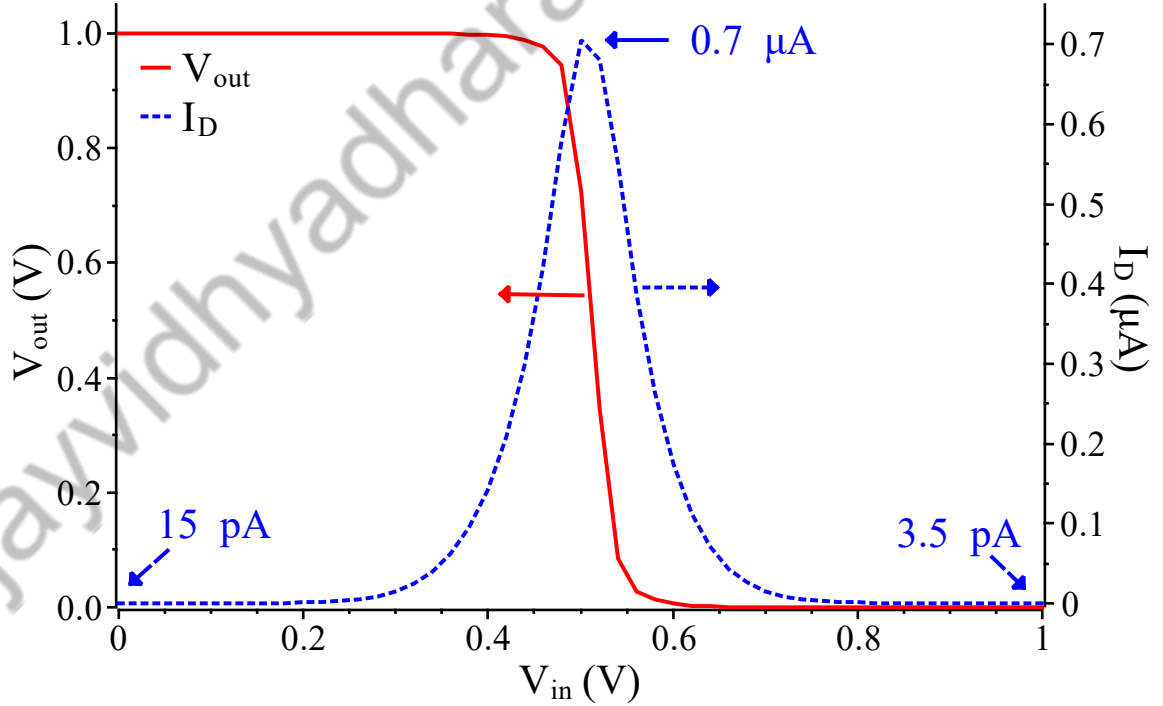 


Short Circuit Loss

  

- Use devices with V_{th} close to $\frac{V_{DD}}{2}$ & steep switching characteristics
- Short Circuit loss reduces with C_{load}

Switching Loss

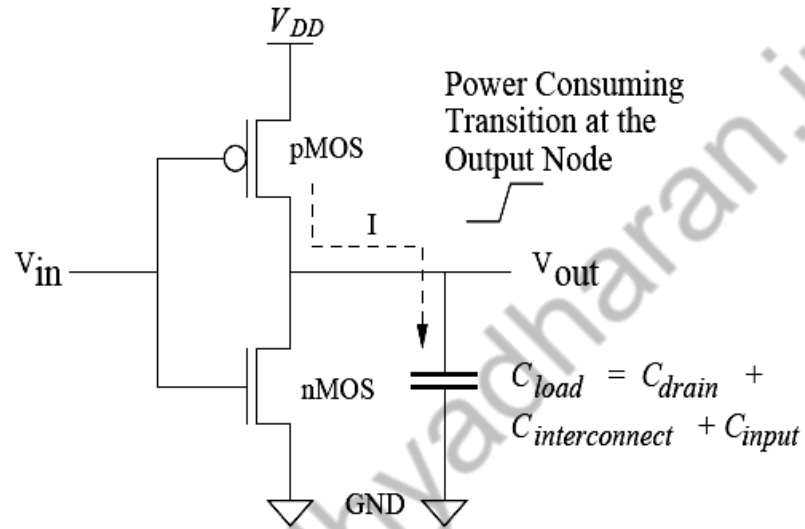

$$\text{Energy stored in } C_{Load} (C_L) = \int_0^{V_{DD}} V_C \cdot C_L dV_C = \frac{1}{2} \cdot V_{DD}^2 \cdot C_L$$

$$\text{Energy consumed from power supply} = V_{DD} \int_0^T i(t) dt = V_{DD} \cdot Q_{CL} = V_{DD}^2 \cdot C_L$$

$$\text{Energy dissipated in pMOSFET during charging} = \frac{1}{2} \cdot V_{DD}^2 \cdot C_L$$

$$\text{Energy dissipated in nMOSFET during discharging} = \frac{1}{2} \cdot V_{DD}^2 \cdot C_L$$

$$\text{Power Consumption} = \text{Frquency} \cdot V_{DD}^2 \cdot C_L$$

High Dynamic Power Consumption

$$P_{\text{Dynamic}} = \text{Freq} * V_{\text{DD}}^2 * C_{\text{L}}$$

- V_{DD} & C_{L} : Reduced by 30 % each generation
- Frequency : 43 % Increase
 - Architectural optimizations
 - Consumer requirements
- Transistors per chip : Increased exponentially
 - Advancement in lithography
 - Multilayer metallization
 - Efficient partitioning and routing techniques

Figure of Merits of a Digital Circuit

1. Noise Margin

 


Figure of Merits of a Digital Circuit

2. Propagation Delay (Eg. Inverter)

 


Figure of Merits of a Digital Circuit

3. Rise Time and Fall Time

 


Figure of Merits of a Digital Circuit

4. Fan-in and Fan-Out

 


Figure of Merits of a Digital Circuit

5. Power and Energy Consumption


- **Power consumption of design determine**
 - How much energy is consumed per operation
 - How much heat the circuit dissipates
- **Determine critical design decision**
 - Power supply capacity, battery lifetime,
 - Supply line sizing, packaging and cooling
- **Peak power is important for supply line sizing**
- **Average power dissipation is important for cooling or battery requirements**

Figure of Merits of a Digital Circuit

 6. Power Delay Product

$$P_{\text{Dynamic}} = \text{Freq} * V_{\text{DD}}^2 * C_L$$

$$\text{Propagation Delay (tpd)} = \frac{K_1 C_L}{I_D} = \frac{K_2 C_L}{(V_{\text{DD}} - V_{\text{th}})^2}$$



Thankyou

sanjayvidhyasadhan.in