





# **Advanced VLSI Design: 2021-22**

## **Lecture 2**

### **Sequential Circuits: Latch and Flip-flops**


**By Dr. Sanjay Vidhyadharan**

# Combinational vs. Sequential Circuits

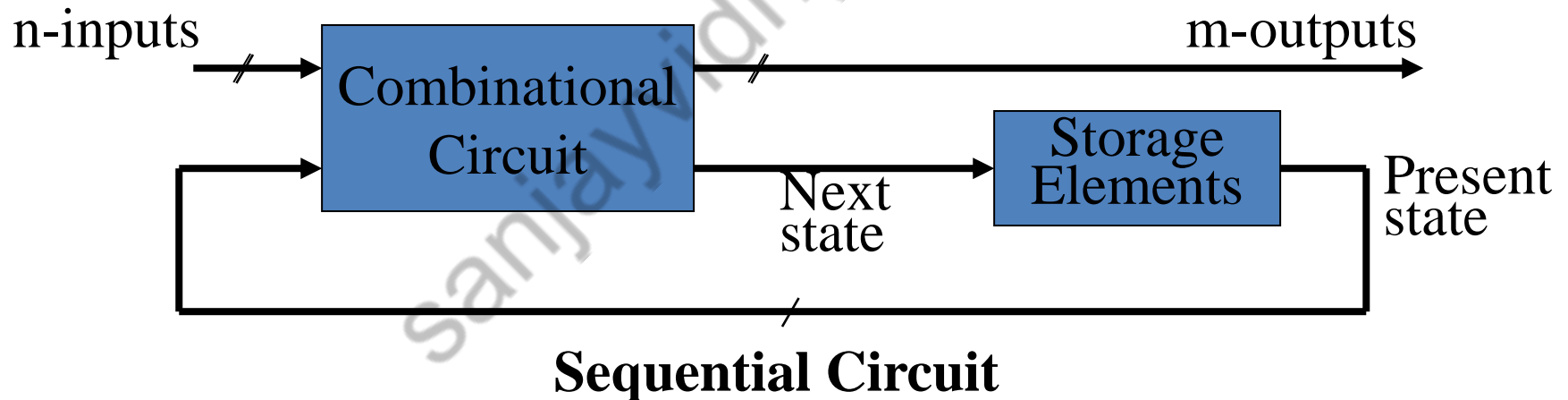 

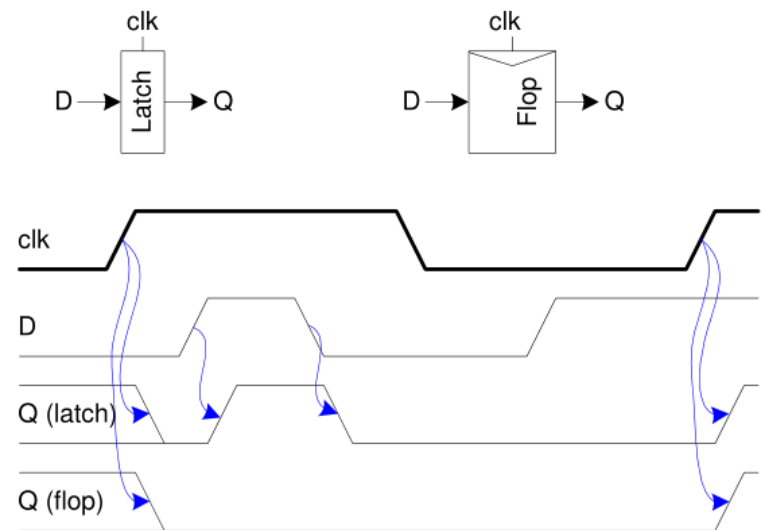
# Latch vs. Flip-flop

- **Latch:** Level sensitive
  - a.k.a. transparent latch, D latch
- **Flip-flop:** edge triggered
  - A.k.a. master-slave flip-flop, D flip-flop, D register
- **Timing Diagrams**
  - Transparent
  - Opaque
  - Edge-trigger



# Latch


Storing 1

 

Stores 1 as Long as Power Supply is Provided

# Latch

Storing 0

 

Stores 0 as Long as Power Supply is Provided

# Latch




How to Write Data into a Latch?



We are going to use this property of NOR and NAND to write data into the latch




# SR Latch

$S$	$R$	$Q$	$\bar{Q}$
0	0	$Q$	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	0	0

   

# SR Latch




S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	0	0

   



# SR Latch

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	0	0

   

# SR Latch

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	0	0

No change


Reset  $Q = 0$

Set  $Q = 1$


Forbidden

# SR Latch

## SR Latch with NOR Gates

 

(a) Schematic diagram

 

(b) Logic symbol


$S$	$R$	$Q$	$\bar{Q}$
0	0	$Q$	$\bar{Q}$
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State

(c) Characteristic table

# SR Latch

## SR Latch with NAND Gates

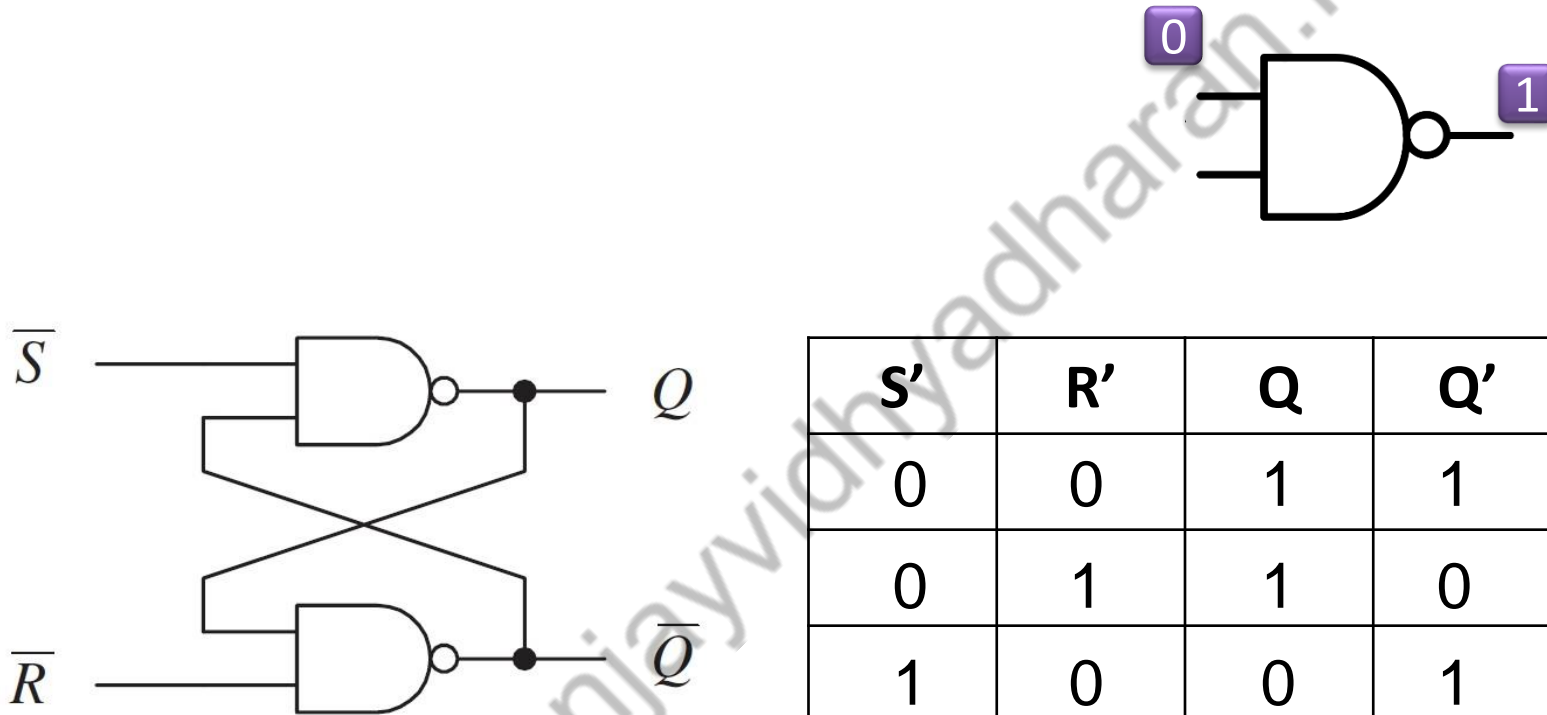

$S'$	$R'$	$Q$	$Q'$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	$Q$	$Q'$

Forbidden


Set

Reset


No change

# SR Latch

## Clocked SR Latch

 



**NAND Implementation**

 


**AND-NOR Implementation**

# SR Latch

## Clocked SR Latch

  


# D Latch

 

Static D latch


# D Latch

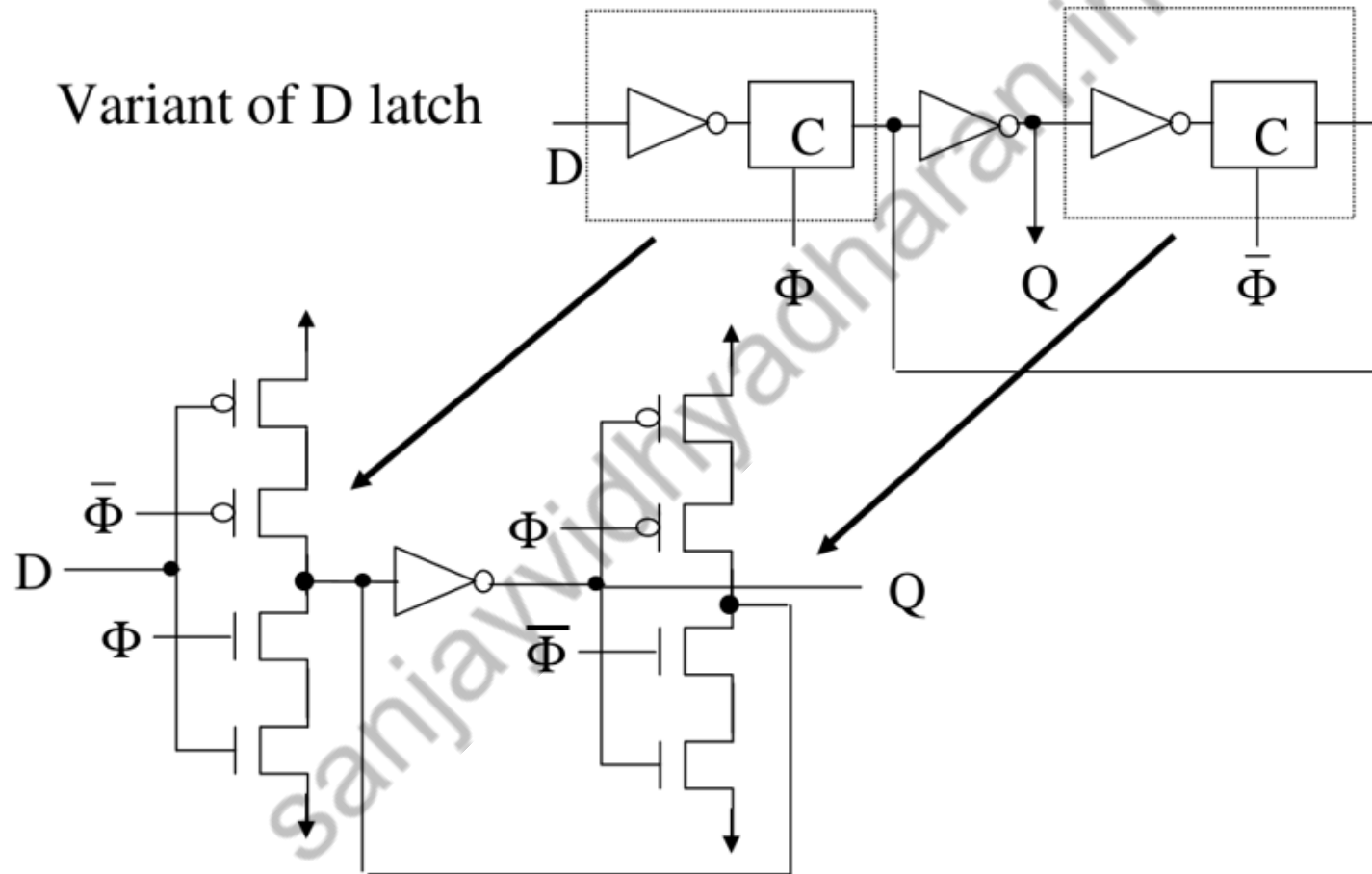



# D Latch


## Mux Based Latch

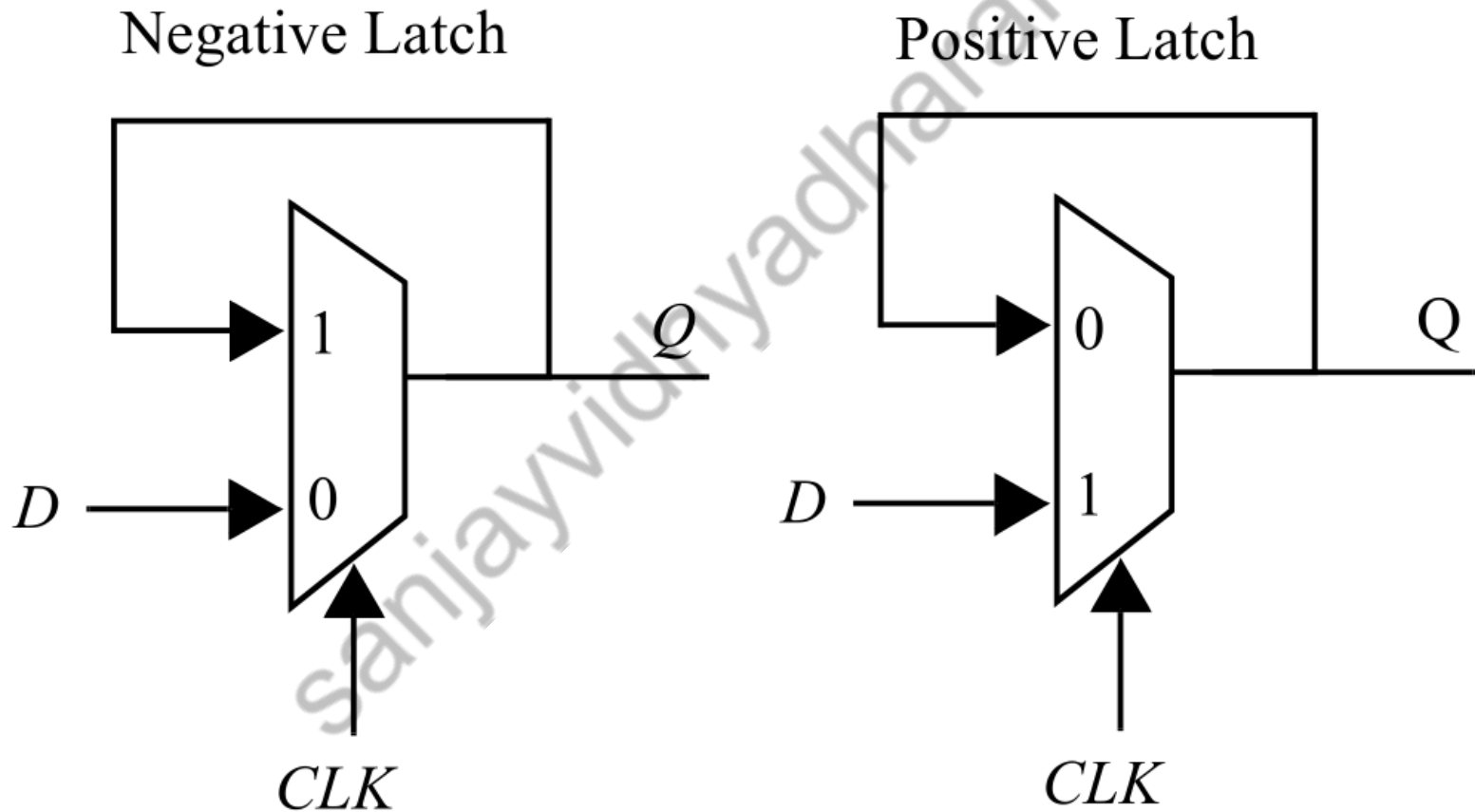



 
# D Latch

Multiplexer-based NMOS latch using NMOS-only pass transistors.




(a) Schematic diagram

 


(b) Non-overlapping clocks

# Race around in Latches

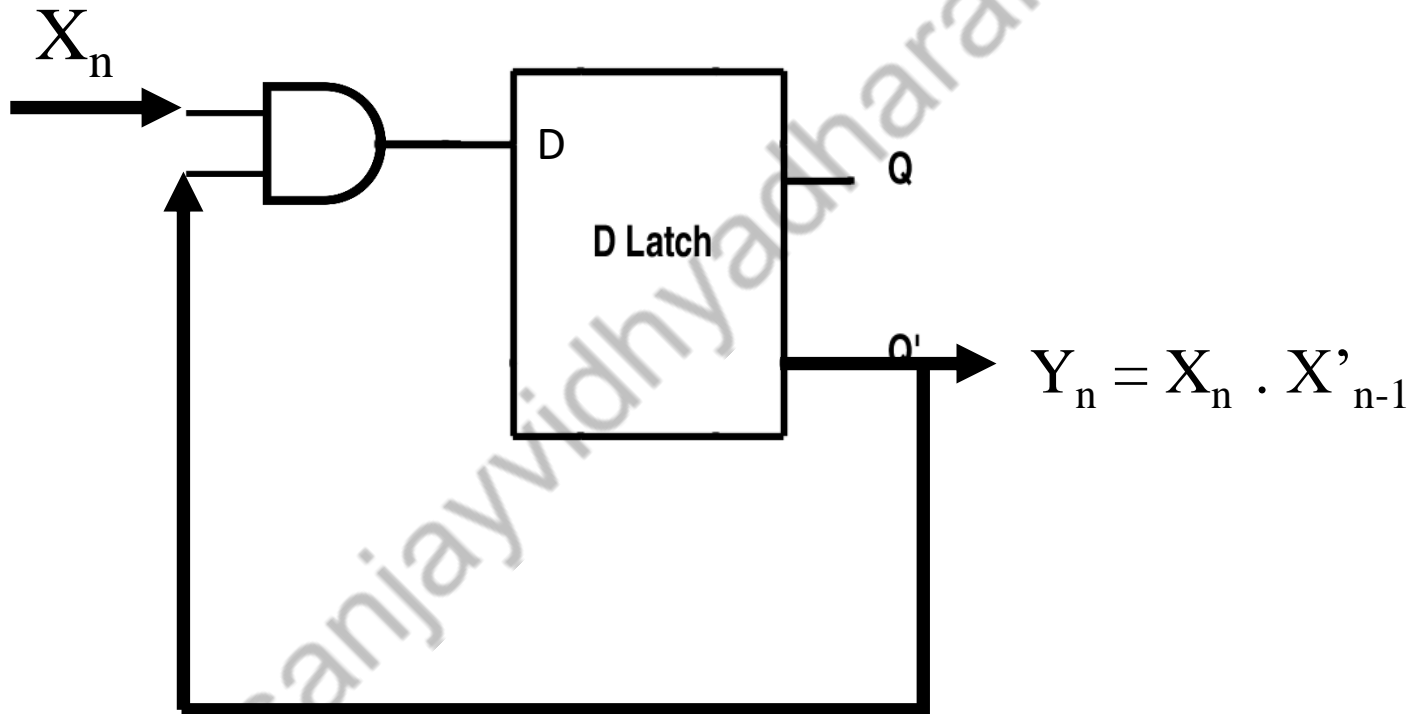

 
# Latch vs. Flip-flop

Latch – Responds to change in level of clock pulse




 The key to the proper operation of a flip-flop is to trigger it only during signal transition.




# Timing Constraints of a Flip-flop

- Setup Time
- Hold Time

 
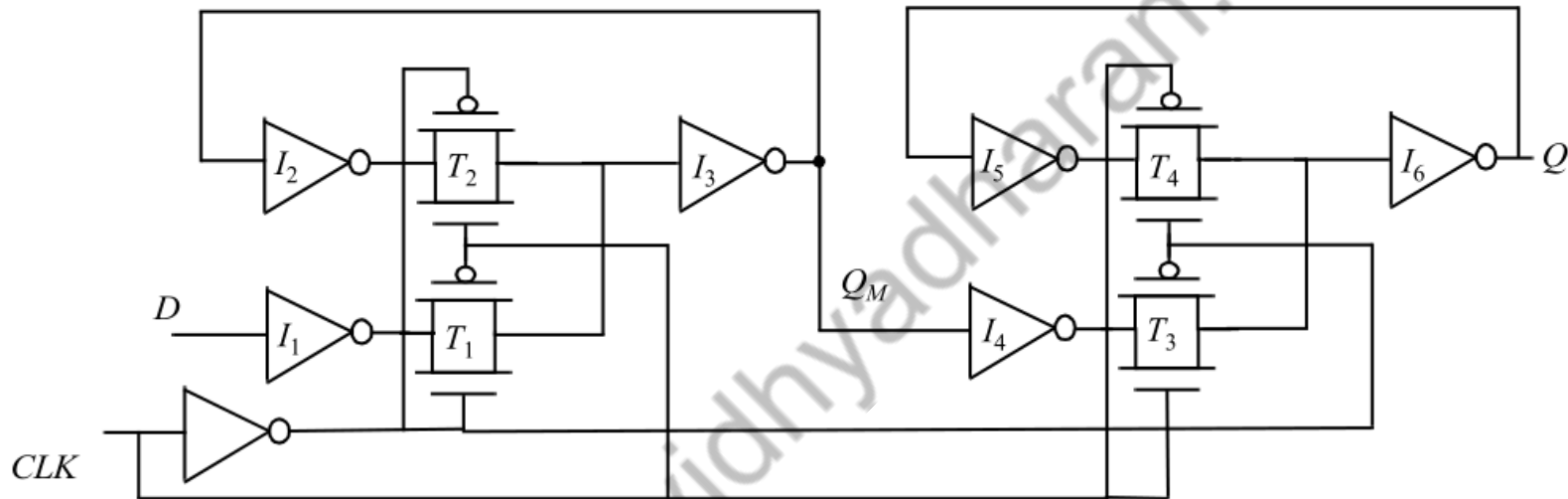
# Flip-Flop

Master-slave positive edge-triggered register using multiplexers.




The set-up time is equal to  $3 \cdot t_{pd\_inv} + t_{pd\_tx}$

Hold time is Nil


Propagation delay =  $t_{pd\_tx} + t_{pd\_inv}$

# Flip-Flop

## Set-up time simulation

 

(a)  $T_{setup} = 0.21$  nsec

 


(b)  $T_{setup} = 0.20$  nsec




# Flip-Flop

Simulation of propagation delay

 
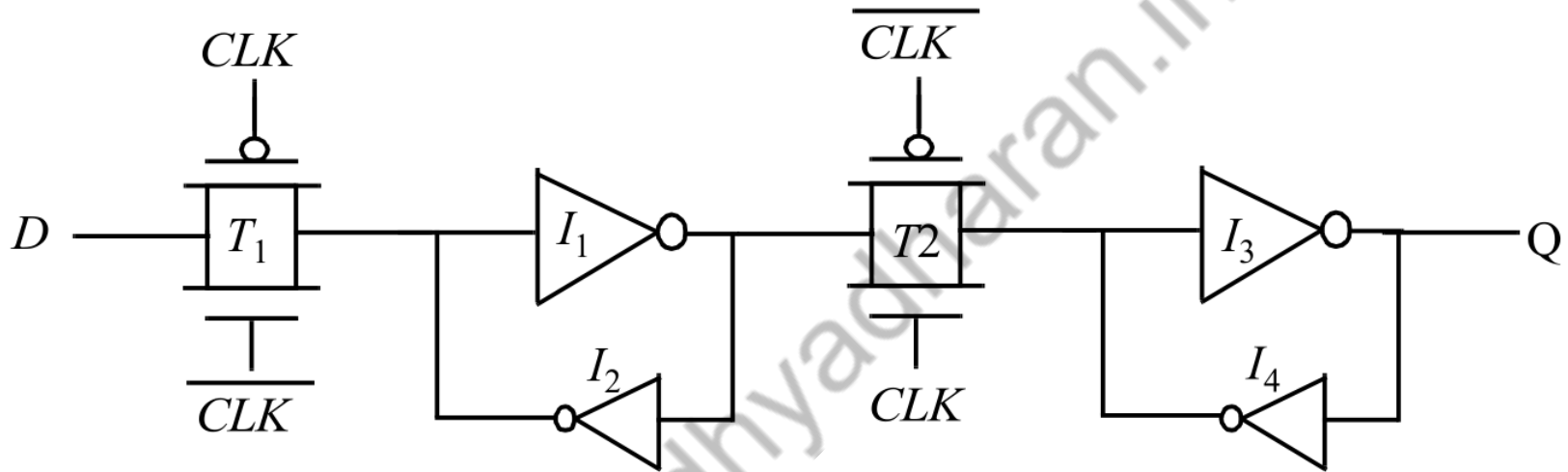
# Flip-Flop

Reduced load clock load static master-slave register.




The penalty for the reduced clock load is increased design complexity. The transmission gate ( $T_1$ ) and its source driver must overpower the feedback inverter ( $I_2$ ) to switch the state of the cross-coupled inverter.


The transistors of inverter  $I_2$  should be made weaker. This can be accomplished by making their channel-lengths larger than minimum.

# Flip-Flop

## Clock Jitter

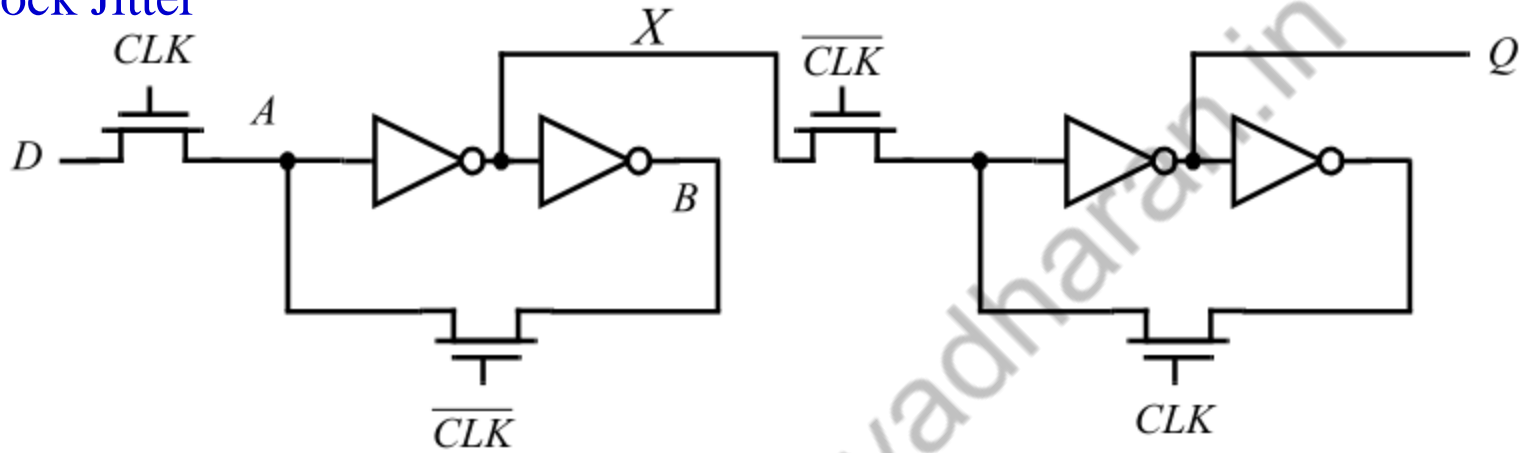



(a) Schematic diagram

 


When the clock goes high, the slave stage should stop sampling the master stage output and go into a hold mode. However, since  $CLK$  and  $\overline{CLK}$  are both high for a short period of time (the overlap period), both sampling pass transistors conduct and there is a direct path from the  $D$  input to the  $Q$  output. As a result, data at the output can change on the rising edge of the clock, which is undesired for a negative edge-triggered register.

# Flip-Flop


## Two-phase non-overlapping clocks

 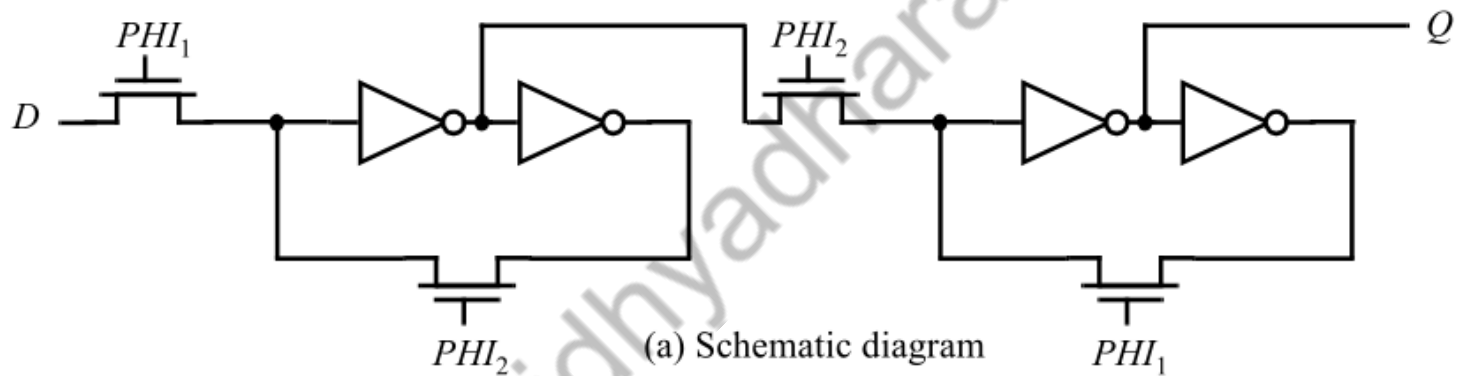

(b) Two-phase non-overlapping clocks

 



# Single Phase Global Clock Generation

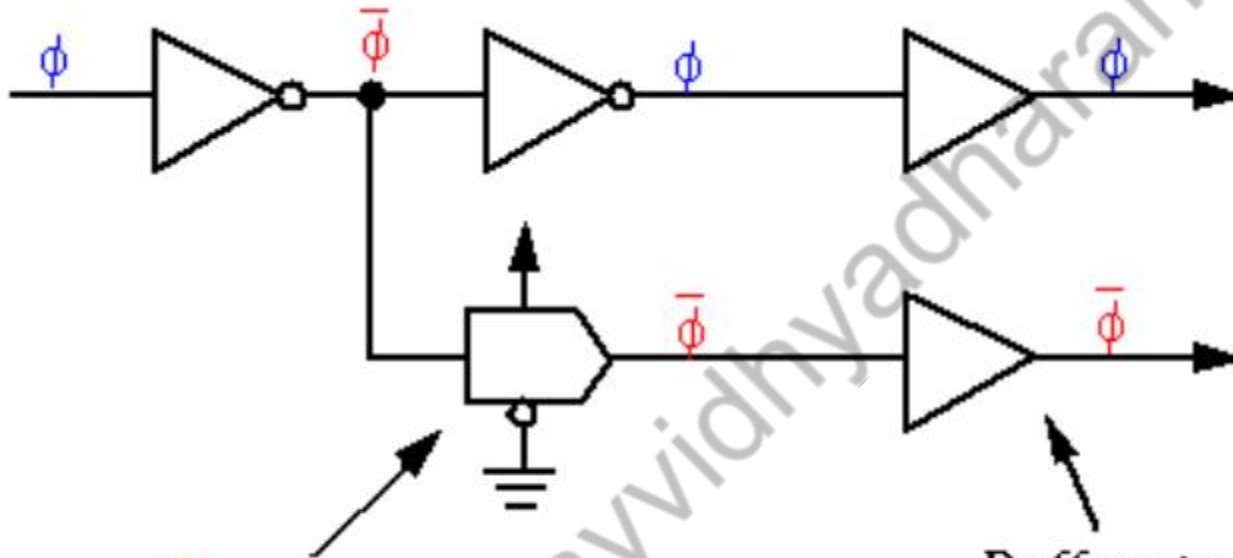

Pass  $\bar{\phi}$  through a transmission gate as a means of calibrating for  $\phi$ 's inverter delay.


Buffers to drive large loads.

# Non-overlapping Clock Generation

  
 
# Flip-Flop

Solving the leakage problem using multiple-threshold CMOS.



- During normal mode of operation, the sleep devices are tuned on.
- The shaded inverters and transmission gates are implemented in low-threshold devices.



**Thank you**

*sanjayvidhyadharan.in*