



Digital Design : 2021-22

Lecture 15 : Decoders and Encoders

By Dr. Sanjay Vidhyadharan

Decoder

A Decoder is a combinational circuit that converts binary information from 'n' input lines to 2^n output lines


An Example: 2 to 4 Line Decoder

X	Y
0	0
0	1
1	0
1	1

D₀	D₁	D₂	D₃
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1

Decoder

An Example: 2 to 4 Line Decoder

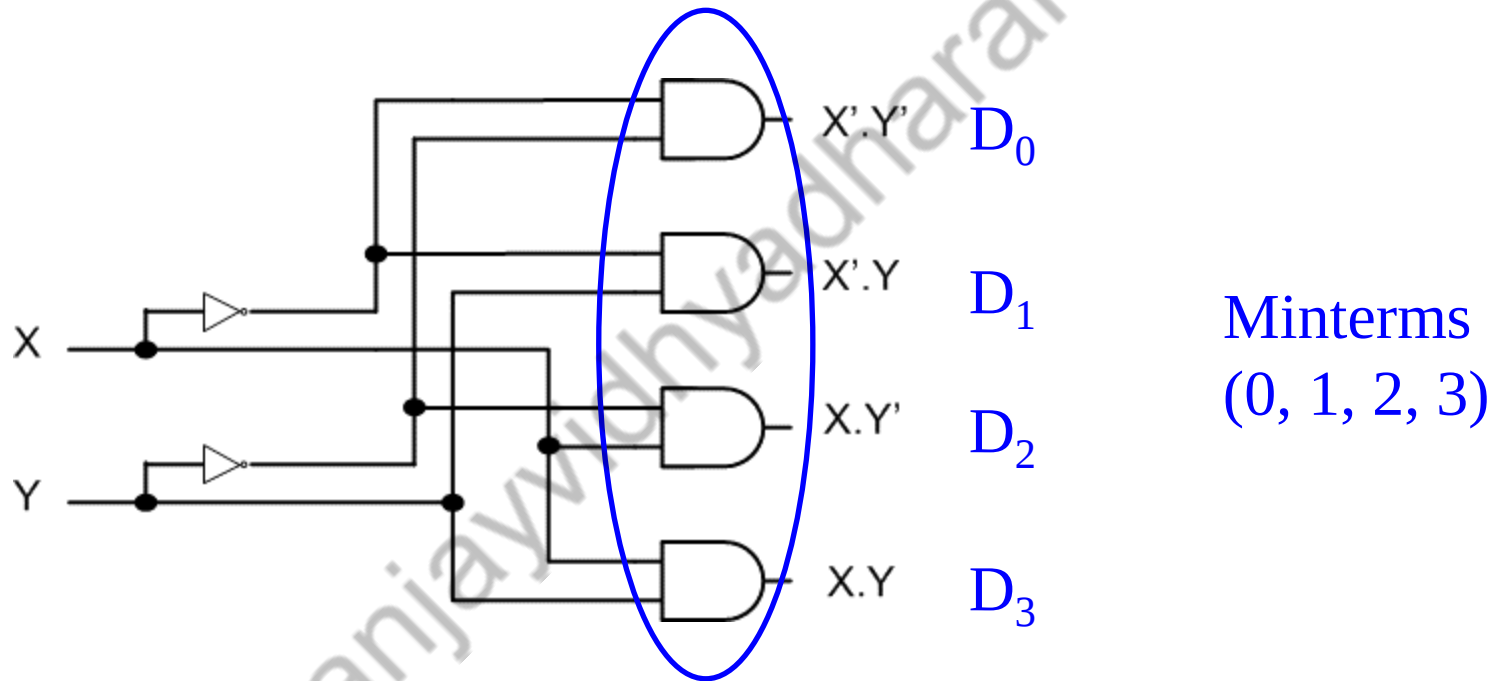

Minterm Generating circuit

Decoder

An Example: 2 to 4 Line Decoder with Enable

E	X	Y
1	0	0
1	0	1
1	1	0
1	1	1
0	X	X


D₀	D₁	D₂	D₃
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1
0	0	0	0

Decoder with enable pin is also called as **Demultiplexer**

X and Y – Select Lines E- Input line

Decoder

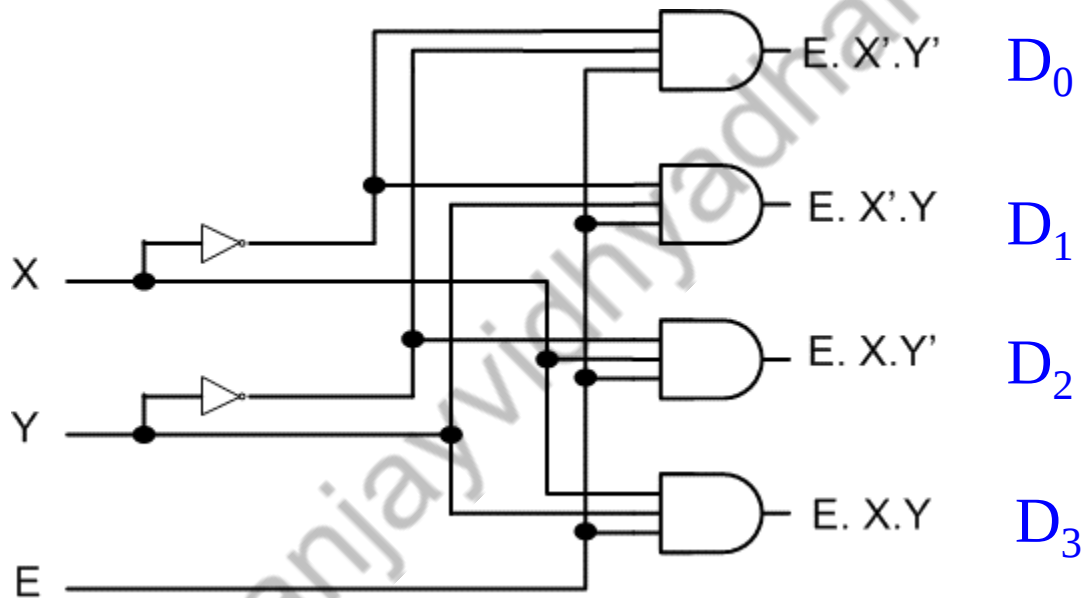An Example: 2 to 4 Line Decoder with Enable



Decoder

An Example: 3 to 8 Line Decoder

X	Y	Z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


Direct Implementation – Home Assignment

Decoder

Implementing a 3 to 8 decoder using two 2 to 4 decoders with enable pin


X	Y	Z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
1	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	0	0	1	0	0	0
0	0	0	0	0	1	0	0
0	0	0	0	0	0	1	0
0	0	0	0	0	0	0	1

 


Decoder

 Implementing a 3 to 8 decoder using two 2 to 4 decoders with enable pin



Decoder


3 to 8 decoder

 

Decoder

4 to 16 decoder


INPUTS				OUTPUTS															
A ₃	A ₂	A ₁	A ₀	Y ₁₅	Y ₁₄	Y ₁₃	Y ₁₂	Y ₁₁	Y ₁₀	Y ₉	Y ₈	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

 

Decoder

4 to 16 decoder


INPUTS				OUTPUTS															
A ₃	A ₂	A ₁	A ₀	Y ₁₅	Y ₁₄	Y ₁₃	Y ₁₂	Y ₁₁	Y ₁₀	Y ₉	Y ₈	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

 

Decoder

Implementing function using Decoders
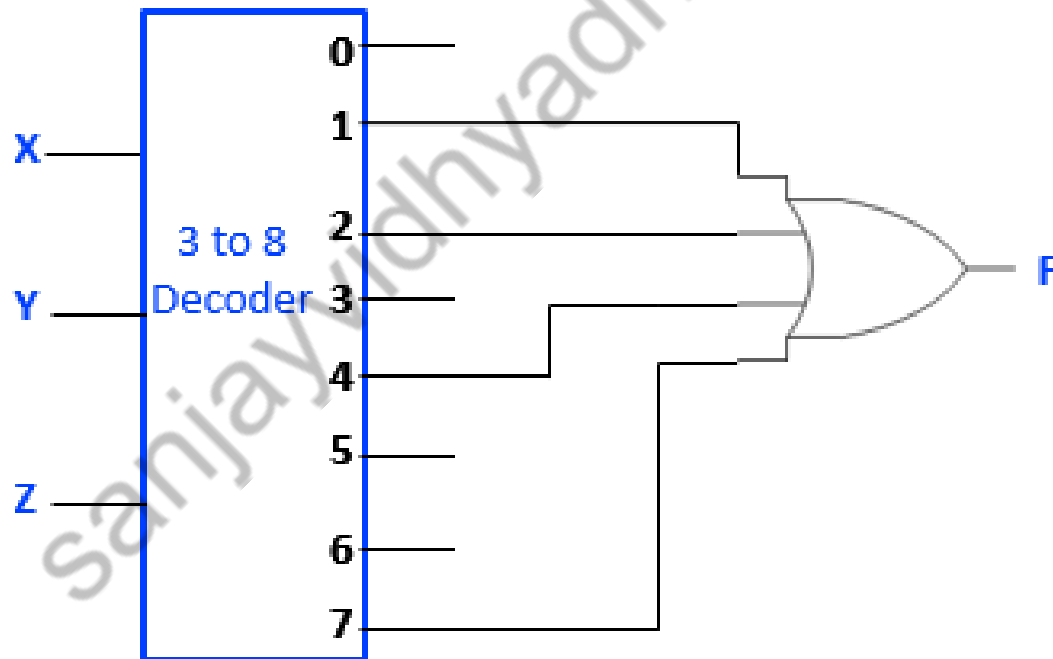
$$F = \sum (1, 2, 4, 7) = X'Y'Z + X'YZ' + XY'Z' + XYZ$$



Encoder

Encoder - combinational circuit that performs inverse operation of decoder

Has 2^n or fewer input lines and n output lines

An Example:

$$X = D_2 + D_3$$

$$Y = D_1 + D_3$$

D_0	D_1	D_2	D_3
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1

X	Y
0	0
0	1
1	0
1	1

Encoder

$$X = D_2 + D_3$$

$$Y = D_1 + D_3$$

D_0	D_1	D_2	D_3	X	Y
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

Limitations:

If two ones appear i.e. if D_1 and D_2 are '1' then both X and Y will be '1' resulting in output 11

If all the inputs are zeros then output is 00 – which indicates that D_0 is 1

Priority Encoder

Encoder circuits must establish input priority

If high priority is given to inputs with higher subscripts

If both D_1 and D_2 are '1' then resulting o/p should be 10

If all the inputs are zeros then output is 00 – which indicates that D_0 is 1

This ambiguity can be resolved by providing one more output.

Extra Output indicates whether at least one input is equal to 1

Priority Encoder

D_0	D_1	D_2	D_3
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1

X	Y
0	0
0	1
1	0
1	1

Encoder

$$X = D_2 + D_3$$

$$Y = D_1 + D_3$$

D_0	D_1	D_2	D_3
1	0	0	0
X	1	0	0
X	X	1	0
X	X	X	1
0	0	0	0

X	Y	V
0	0	1
0	1	1
1	0	1
1	1	1
X	X	0

Priority Encoder

$$X = D_2 + D_3$$

$$Y = D_1 D_2' + D_3$$

$$V = D_0 + D_1 + D_2 + D_3$$

Priority Encoder


Priority Encoder

$$X = D_2 + D_3$$


$$Y = D_1 D_2' + D_3$$

$$V = D_0 + D_1 + D_2 + D_3$$

D_0	D_1	D_2	D_3	X	Y	V
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1
0	0	0	0	X	X	0

 


Binary to Gray Using Encoder-Decoder

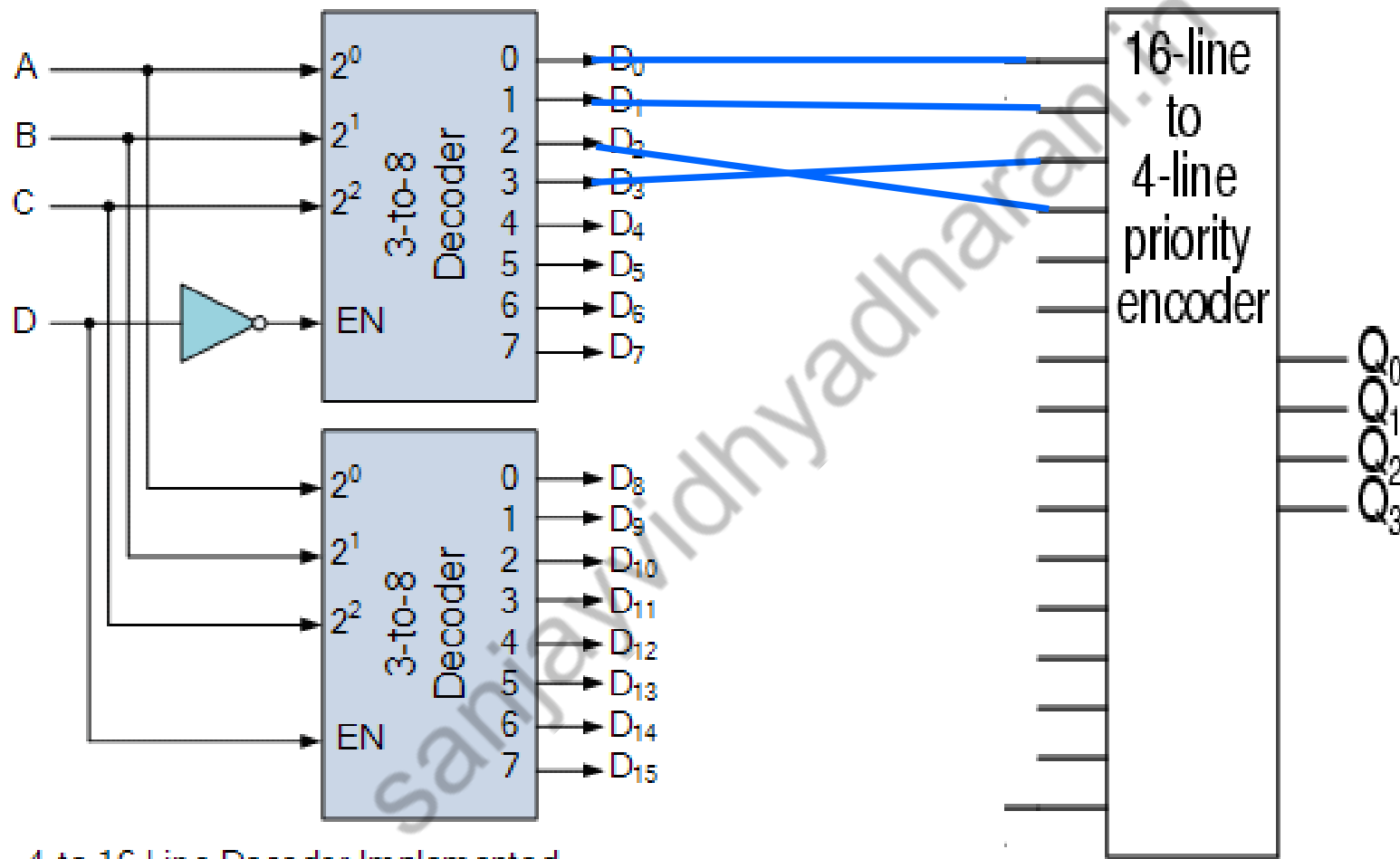


4-to-16 Line Decoder Implemented with two 3-to-8 Decoders


Encoder Applications

 


Encoder Applications

 


Encoder Applications

 

Decoder Applications

 

TTL Encoder and Decoder

 

Thank you