



Digital Design : 2021-22

Lecture 16 : Multiplexers and De-multiplexers

By Dr. Sanjay Vidhyadharan

Multiplexers

Multiplexer - combinational circuit that selects binary information from one of many input lines and directs it to single output line

The selection is controlled by Select lines

Normally 2^n input lines, n selection lines and 1 output line

Also called Data Selector

Multiplexers


2:1 Multiplexer – 2:1 MUX

I_0 and I_1 are input lines and S is select line

If $s=0$ then o/p = I_0

$s=1$ then o/p = I_1

 
$$\text{o/p} = I_0 \cdot S' + I_1 \cdot S$$



Multiplexers

4:1 Multiplexer – 4:1 MUX

S_1	S_0	O/P
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 


$$O/P = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$$

Direct Implementation

Multiplexers

4:1 MUX Using 2:1 MUX


S_1	S_0	O/P
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

Multiplexers

4:1 MUX Using 2:1 MUX


S_1	S_0	O/P
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

Multiplexers

4:1 MUX Using 2:1 MUX


S_1	S_0	O/P
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

Multiplexers


4:1 MUX Using 2:1 MUX

S_1	S_0	O/P
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

Multiplexers

Multiple Bit Selection Logic

 


E	S	Output Y
1	0	
1	1	
0	0	
0	1	



Analyze and Complete the table

Multiplexers

Tri State Buffer

 


2:1 MUX using Tri-state buffer

  

Switch implementation of tri-state gate.


Multiplexers

 4:1 MUX using Tri-state buffers and 2 to 4 Decoder



74HCT125 Quad Tri-State Buffer

LOGIC SYMBOL

 


Multiplexers

Boolean Function implementation

$$F(X, Y, Z) = \sum (1, 2, 6, 7)$$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


Multiplexers

Boolean Function implementation

$$F(X, Y, Z) = \sum (1, 2, 6, 7)$$


X	Y	Z	F	
0	0	0	0	F = Z
0	0	1	1	
0	1	0	1	F = Z'
0	1	1	0	
1	0	0	0	F = 0
1	0	1	0	
1	1	0	1	F = 1
1	1	1	1	

4:1
Multiplexer

 


Multiplexers



Boolean Function implementation

 

Multiplexers

 


Multiplexers and De-multiplexers

  


74XX series ICs


74HCT125 Quad Tri-State Buffer

 


Tristate Buffer

 

Decoder

 

Mux

 

Encoder

Thank you