



Digital Design : 2021-22


Lecture 18 : Sequential Logic – Flipflops

By Dr. Sanjay Vidhyadharan


sanjayvidhyadharan.in

Latch vs. Flip-flop

 
Latch – Responds to change in level of clock pulse



 The key to the proper operation of a flip-flop is to trigger it only during signal transition.



Race around in Latches

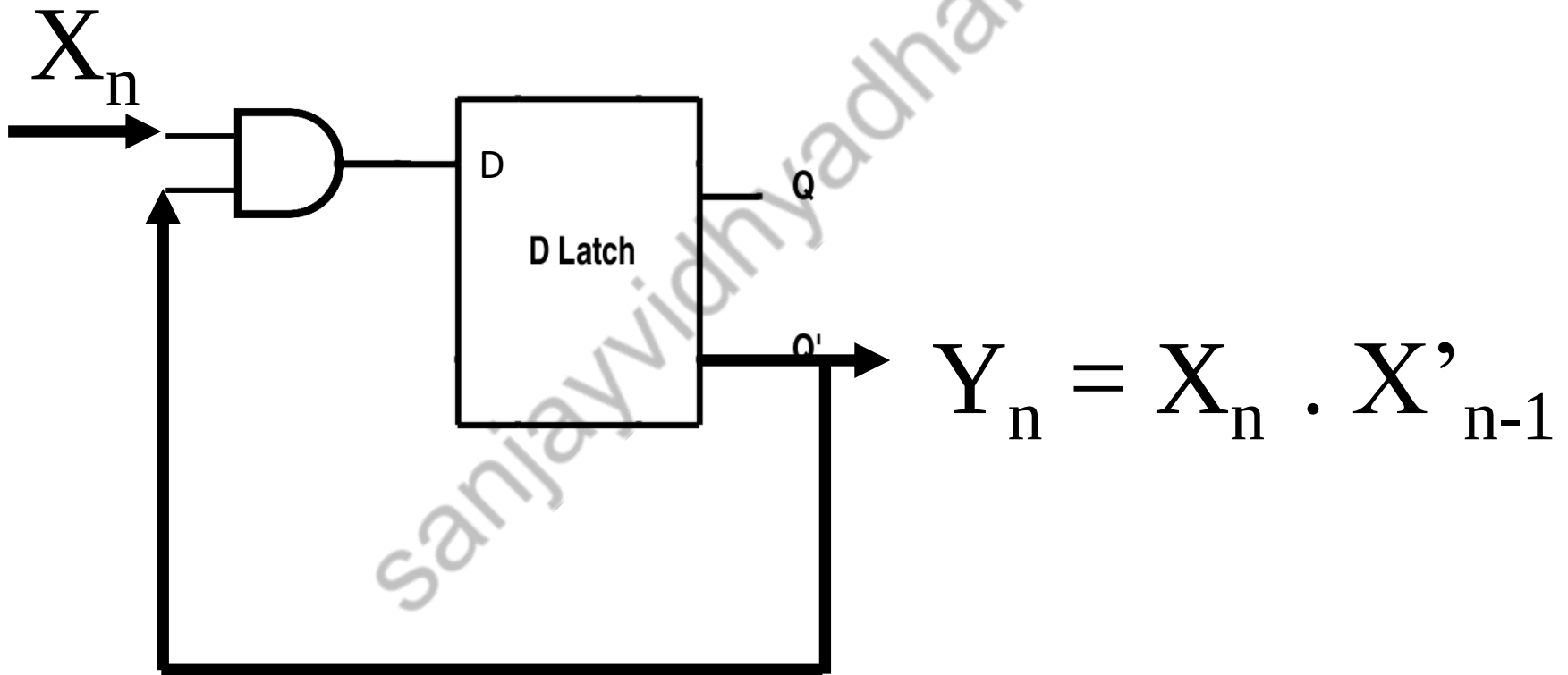

Flip-flops


Two ways to build a flip flop

Special configuration of two latches to isolate the output of flip-flop

Gate based design which triggers only during signal transition of clock and is disabled during rest of clock pulse


Flip-flops

Master-Slave Flip-flop

 


Flip-flops

Master-Slave Flip-flop

 


Flip-flops

Master-Slave Flip-flop

 



MASTER-SLAVE D FLIP FLOP

 - i) Positive edge triggered
- ii) Note that Slave is controlled by Clk and Master by Clk'
- iii) In Negative Edge Triggered, Master is run with Clk



Edge Triggered D Flip-Flops

D-type positive edge triggered

  

Case I:

$$\text{CLK} = 0$$

$$\text{CLK} = 0 \Rightarrow S' = 1, R' = 1$$


$$D = 0 \rightarrow 1 \rightarrow 0$$

$$S' = 1, R' = 1 \text{ for } S'R' \text{ latch}$$

Hence Previous state of Q and Q' is maintained

Edge Triggered D Flip-Flops

D-type positive edge triggered

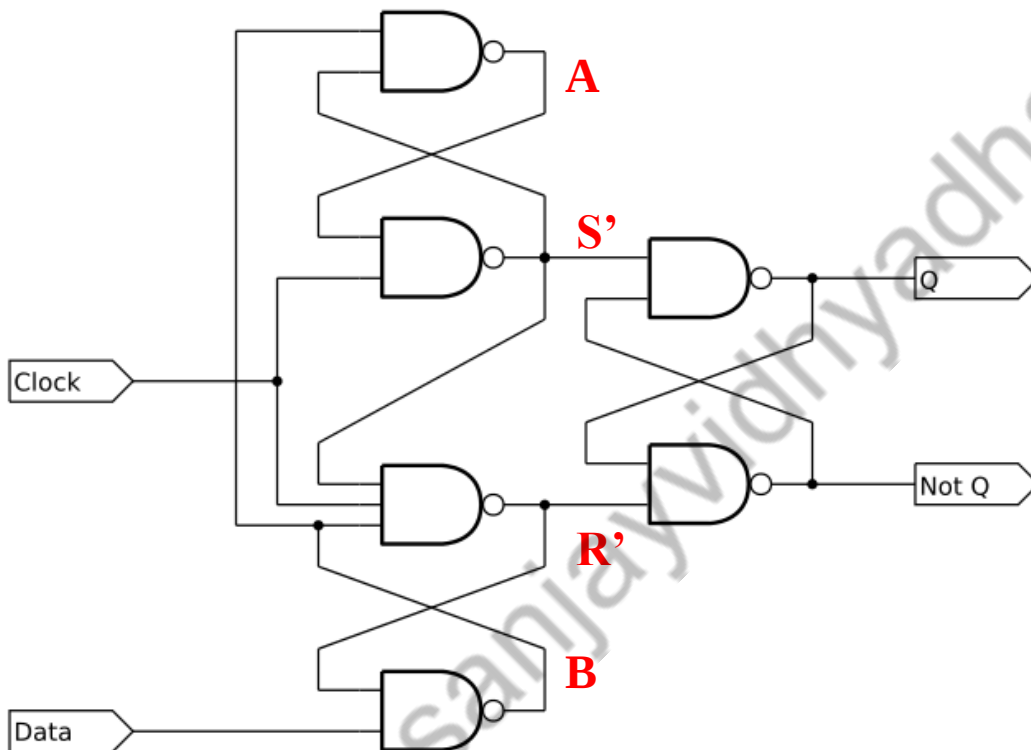

Case 2:

$CLK = 1$, $D=0$, $S'=1$, $R'=0$

$B=1$, $A=0$

$D \rightarrow 0 \rightarrow 1 \rightarrow 0$

$B = 1$ Since $R'=0$

Case 3:

$CLK = 1$, $D=1$, $S'=0$, $R'=1$

$B=0$, $A=1$

$D \rightarrow 1 \rightarrow 0 \rightarrow 0$

$B \rightarrow 0 \rightarrow 1 \rightarrow 0$


$R'=1$ Since $S'=0$

$A=1$ Since $S'=0$

Hence Initial state of Q and Q' is maintained 9

Edge Triggered D Flip-Flops

D-type positive edge triggered

 

Case 4:

$\text{CLK} = 0$, $D=0$, $S'=1$, $R'=0$

$B=1$, $A=1$, $Q=0$

$D \rightarrow 1$

$B=0$

$\text{CLK} \rightarrow 1$

$R'=1$



$A=1$

$S'=0$

$Q=1$



Edge Triggered D Flip-Flops

D-type positive edge triggered

  


Edge Triggered D Flip-Flops

D-type positive edge triggered

  

JK Flip-Flop

 

Characteristic Table


J	K	Q(t+1)	
0	0	Q(t)	No Change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Toggle/Complement

Characteristic Equation??



$$Q(t+1) = JQ' + K'Q$$

JK Flip-Flop

Positive Edge triggered

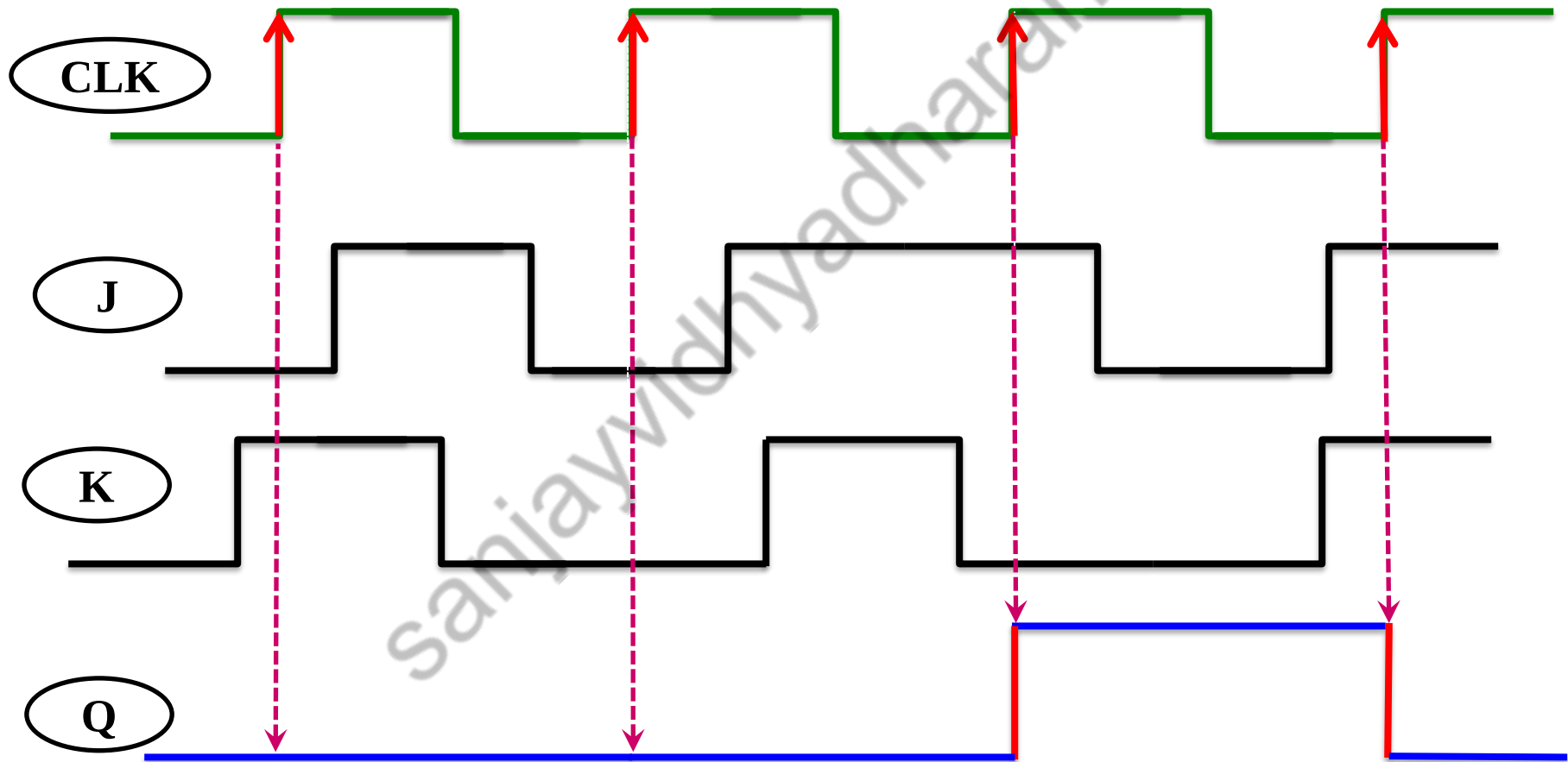

JK Flip-Flop

  


Design J-K Flip-flop using D flip-flop

$$Q(t+1) = D$$

$$Q(t+1) = JQ' + K'Q$$

T Flip-Flop

 

Characteristic Table


T	Q(t+1)	
0	Q(t)	No Change
1	Q'(t)	Toggle

Characteristic Equation??




$$Q(t+1) = T \oplus Q$$

T Flip-Flop

Positive Edge triggered

 

T Flip-Flop

 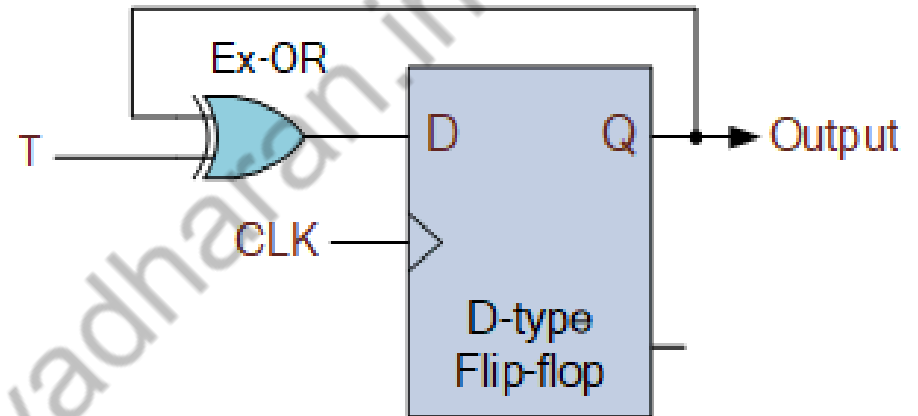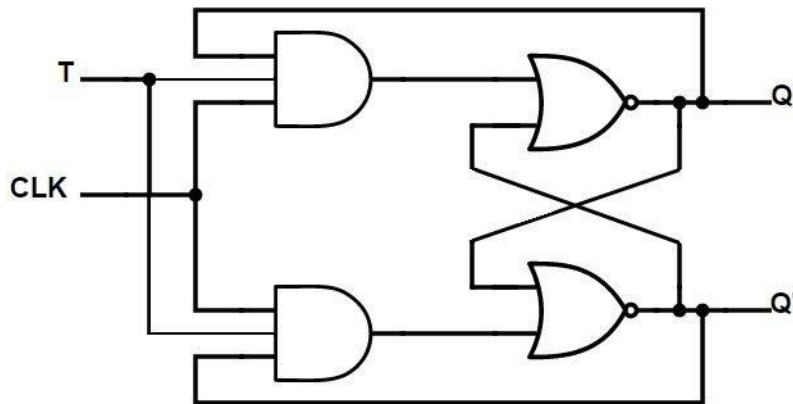

Thank you