



VLSI Design : 2021-22

Lecture 9

CMOS Static Logic

By Dr. Sanjay Vidhyadharan

Static CMOS


Pull UP Network

- Build using p-MOS
- Turns ON when Function is TRUE

• Pull DOWN Network

- Build using n-MOS
- Turns ON when Function is FALSE

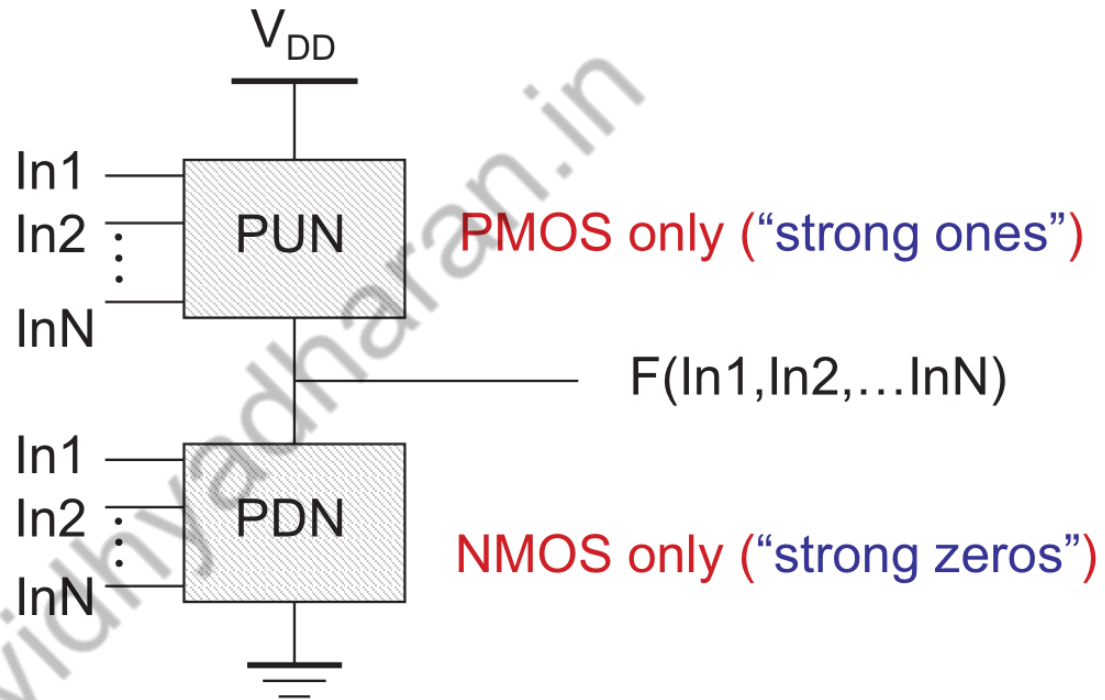- Operationally Complement
- Topologically Dual (n)




Pull-up Network (PUN) and Pull-down Network (PDN) connected in a Mutually exclusive fashion

STATIC CMOS

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

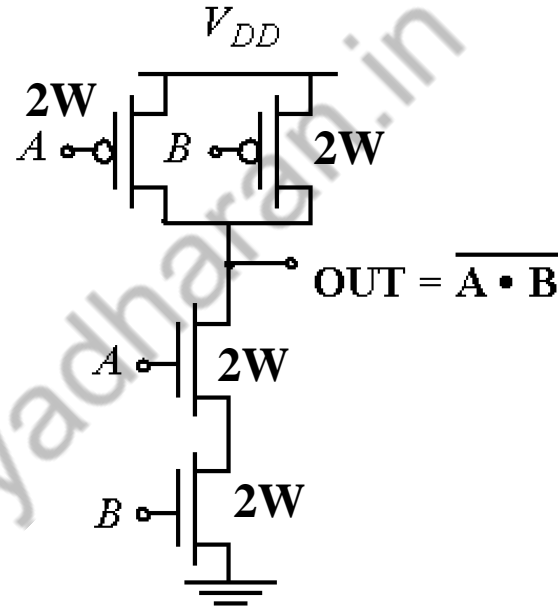

PDN By Taking complementary of the Required Function = $A \cdot B$



PUP By Taking the Function Directly = $A' + B'$

(Inversion of Function Taken care of by PMOS)

AND Implemented by Series Connection

OR Implemented by Parallel Connection

STATIC CMOS

 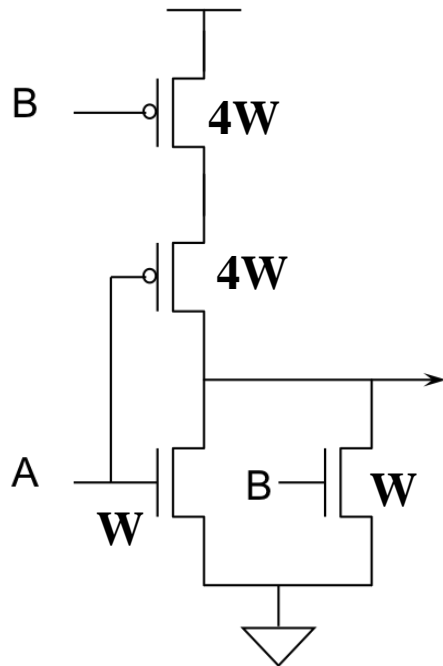

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

PDN By Taking complementary of the Required Function = $A+B$

PUP By Taking the Function Directly = $A' \cdot B'$

(Inversion of Function Taken care of by PMOS)


AND Implemented by Series Connection

OR Implemented by Parallel Connection


2/19/2022

Body-Effect

$$V_{T'n} = V_{FB} + 2|\phi_F| + \frac{1}{C_{ox}} \sqrt{2q\epsilon_{Si}N_a(2|\phi_F| + V_{SBn})} \pm \frac{qD_I}{C_{ox}}$$


 


DIBL

 


The physical origin of DIBL is the increase of the depletion layer due to a high value of V_{ds} that reduces the equivalent channel length and consequently decreases the threshold voltage

Static Two-Input NAND Gate

  


Noise margins are input/pattern dependent!!

Static Two-Input NAND Gate

 

Static Two-Input NAND Gate

 


Input Data Pattern	Delay (psec)
$A = B = 0 \rightarrow 1$	69
$A = 1, B = 0 \rightarrow 1$	62
$A = 0 \rightarrow 1, B = 1$	50
$A = B = 1 \rightarrow 0$	35
$A = 1, B = 1 \rightarrow 0$	76
$A = 1 \rightarrow 0, B = 1$	57

Delays are input/pattern dependent!!

Transistor Sizing for a Complex Gate

Shortest Path First Sizing

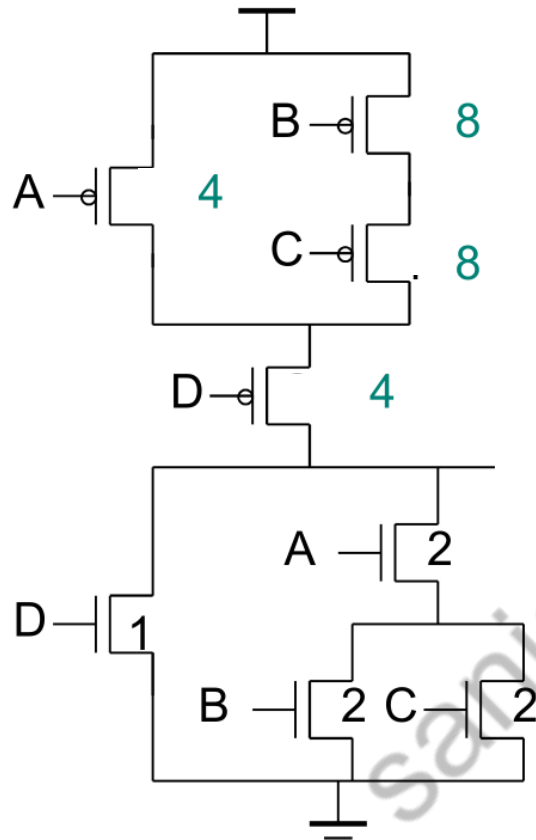

$$\text{OUT} = !(D + A \cdot (B + C))$$

- Total $W_p = 24$
- Shortest path resistance:

- $$R_{p_{\text{eff}}} = \beta(1/4 + 1/4)$$

$$= 2 \times (1/2) = 1$$

(same as for an inverter)

- Worst case path resistance:

- $$R_{p_{\text{eff}}} = \beta(1/8 + 1/8 + 1/4)$$

$$= 2 \times (1/2) = 1$$

- Best case pull up resistance:

- $$R_{p_{\text{eff}}} = \beta [((1/8 + 1/8) \parallel (1/4)) + 1/4]$$

$$= \beta [1/8 + 1/4] = (3/8)\beta = 0.75$$


$$R_N = \frac{12.5}{(W/L)_n} \text{ k}\Omega$$

$$R_P = \frac{30}{(W/L)_p} \text{ k}\Omega$$

Transistor Sizing for a Complex Gate

Worst Path First Sizing
 
$$\frac{1}{X} + \frac{1}{6} = \frac{1}{2}$$




$$OUT = \neg(D + A \cdot (B + C))$$

- Total $W_p=21$ (less area, intrinsic cap)
- Worst case path resistance:
 - $R_{p_{eff}} = \beta(1/6 + 1/6 + 1/6)$
 $= 2 \times (1/2) = 1$
 (same as for an inverter)
- Shortest path resistance:
 - $R_{p_{eff}} = \beta(1/3 + 1/6)$
 $= 2 \times (1/2) = 1$
- Best case pull up resistance:
 - $R_{p_{eff}} = \beta [((1/6 + 1/6) \parallel (1/3)) + 1/6]$
 $= \beta [1/6 + 1/6] = (1/3)\beta = 0.66$
 (even better than shortest path first sizing!)
 Creates larger disparity in delays as a function of inputs

Transistor Sizing for a Complex Gate

Chain Network Elmore Delay

 


Elmore delay equation $\tau_{DN} = \sum c_i r_{ii} = \sum_{i=1}^N c_i \sum_{j=1}^i r_j$

If all resistors are equal size,

$$\tau_{Di} = C_1 r_{eq} + 2C_2 r_{eq} + 3C_3 r_{eq} + \dots + iC_i r_{eq}$$

Transistor Sizing for a Complex Gate

Fanin considerations

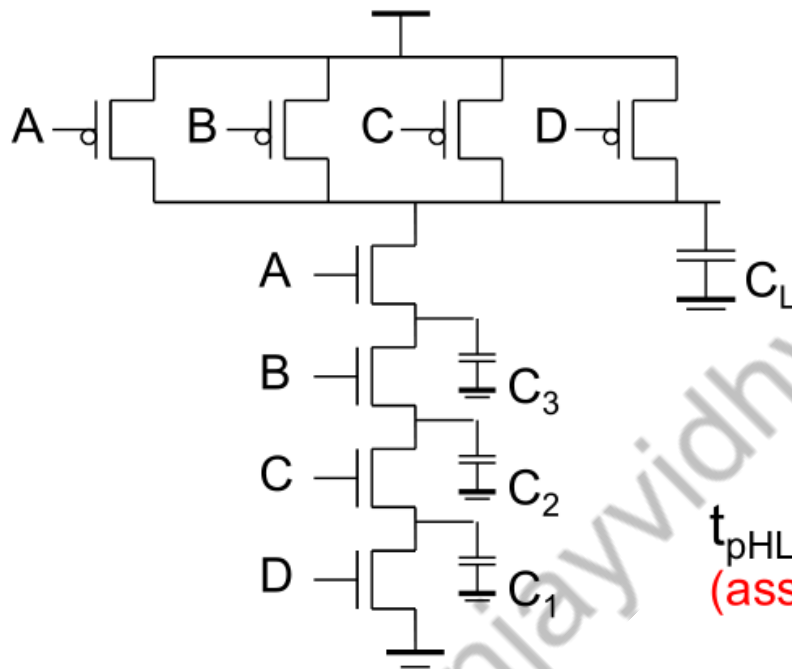

Distributed RC model
(Elmore delay)


$$t_{pHL} = 0.69 R_{eqn} (C_1 + 2C_2 + 3C_3 + 4C_L)$$

(assuming all NMOS equally sized)

Propagation delay deteriorates rapidly as a function of fanin:
quadratically in the worst case.

Transistor Sizing for a Complex Gate


Propagation Delay as a function of fanin

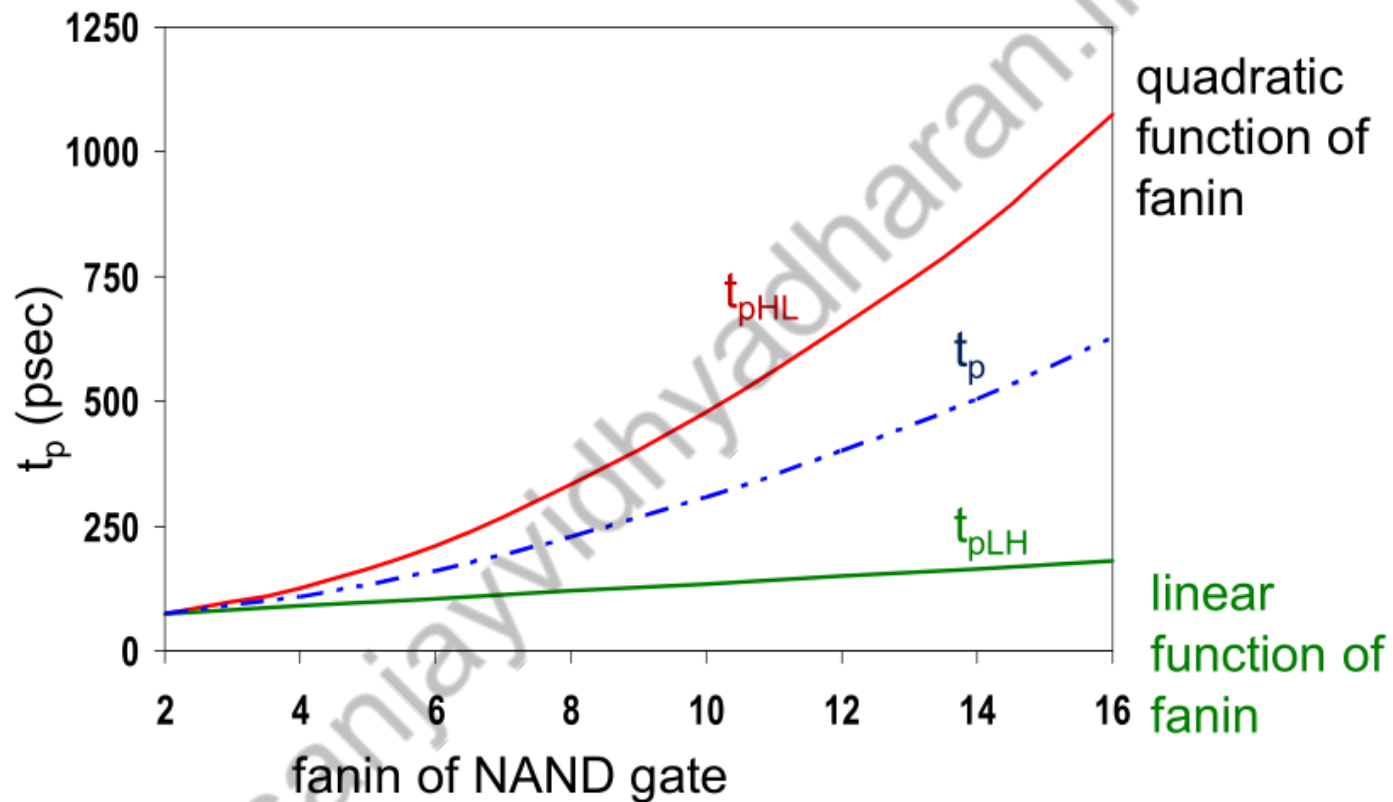

Gates with a fan-in greater than 4 should be avoided.

Transistor Sizing for a Complex Gate

Design Technique 1 : Progressive sizing

 



As long as fan-out capacitance dominates $M1(R1)$ appears N times in the delay equation, the resistance of $M2(R2)$ appears $N-1$ times, etc.

The FET closest to the output should be the smallest
Can reduce delay by more than 20%;
decreasing gains as technology shrinks

While progressive resizing of transistors is relatively easy in a schematic diagram, it is not as simple in a real layout.

Transistor Sizing for a Complex Gate

Design Technique 2 : Input re-ordering

  


- An input signal to a gate is called critical if it is the last signal of all inputs to assume a stable value.
- The path through the logic which determines the ultimate speed of the structure is called the critical path.
- Putting the critical-path transistors closer to the output of the gate can result in a speed-up.

Transistor Sizing for a Complex Gate

Design Technique 3 : Logic Restructuring

$$F = ABCDEFGH$$

 

Manipulating the logic equations can reduce the fan-in requirements and hence reduce the gate delay

Transistor Sizing for a Complex Gate

Design Technique 4 : Isolating fan-in from fan-out using buffer insertion





Thank you

sanjayvidhyadharan.in