



Digital Design : 2021-22

Lecture 23 : Synchronous Counters

By Dr. Sanjay Vidhyadharan

sanjayvidhyadharan.in

Binary Synchronous Counter

3 bit binary counter

0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
0	0	0	0


- Idea:
 - to use same clock for all flip-flops

sanjayvidhyadheran.in

Synchronous Counters

- There is a common clock
 - that triggers all flip-flops simultaneously
 - If $T = 0$ or $J = K = 0$ the flip-flop does not change state.
 - If $T = 1$ or $J = K = 1$ the flip-flop does change state.
- Design procedure is so simple
 - no need for going through sequential logic design process
 - A_0 is always complemented
 - A_1 is complemented when $A_0 = 1$
 - A_2 is complemented when $A_0 = 1$ and $A_1 = 1$
 - so on

4-bit Binary Synchronous Counter

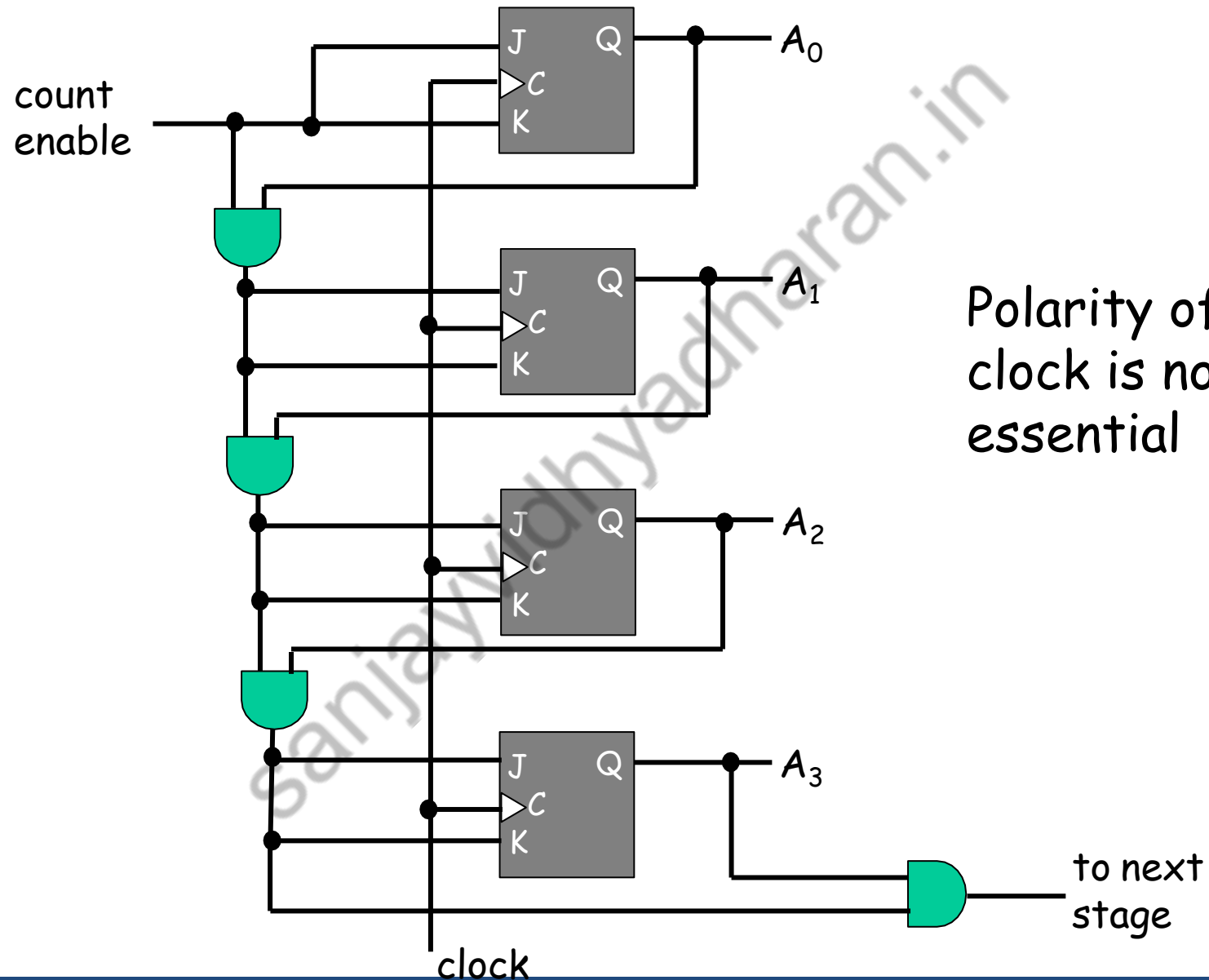


Up-Down Binary Counter

- When counting downward
 - the least significant bit is always complemented (with each clock pulse)
 - A bit in any other position is complemented if all lower significant bits are equal to 0.
 - For example: 0100
 - Next state: 0011
 - For example: 1100
 - Next state: 1011

STATE TABLE

COUNT	Q1	Q0
3	1	1
2	1	0
1	0	1
0	0	0

Up-Down Binary Counter

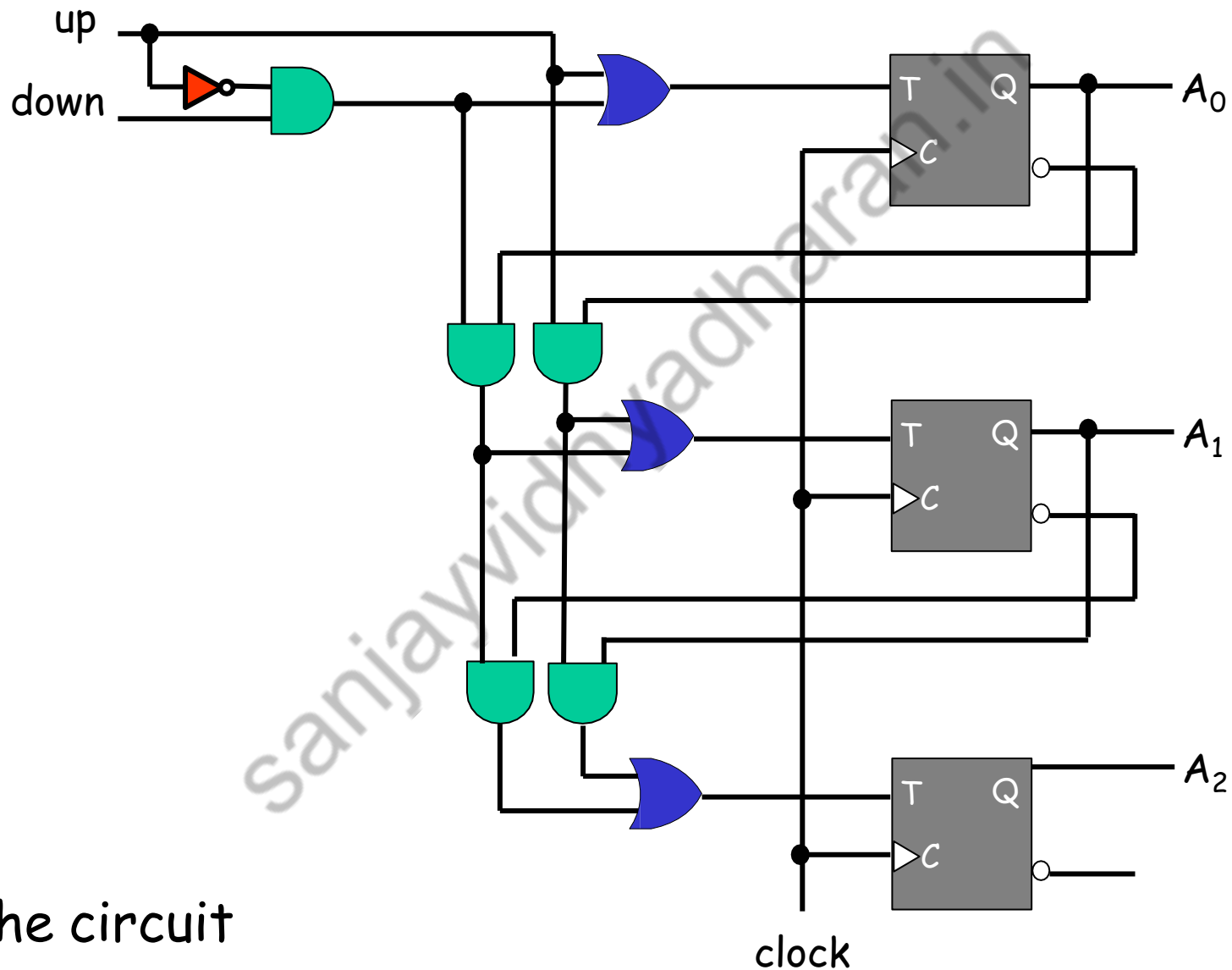

- The circuit

Synchronous BCD Counter


- Better to apply the sequential circuit design procedure

Present state				Next state				output	Flip-Flop inputs			
A_8	A_4	A_2	A_1	A_8	A_4	A_2	A_1	Y	T_8	T_4	T_2	T_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

Synchronous BCD Counter

- The flip-flop input equations
 - $T_1 = 1$
 - $T_2 = A_8' A_1$
 - $T_4 = A_2 A_1$
 - $T_8 = A_8 A_1 + A_4 A_2 A_1$
- Output equation
 - $y = A_8 A_1$
- Cost
 - Four T flip-flops
 - four 2-input AND gates
 - one OR gate
 - one inverter

Binary Counter with Parallel Load

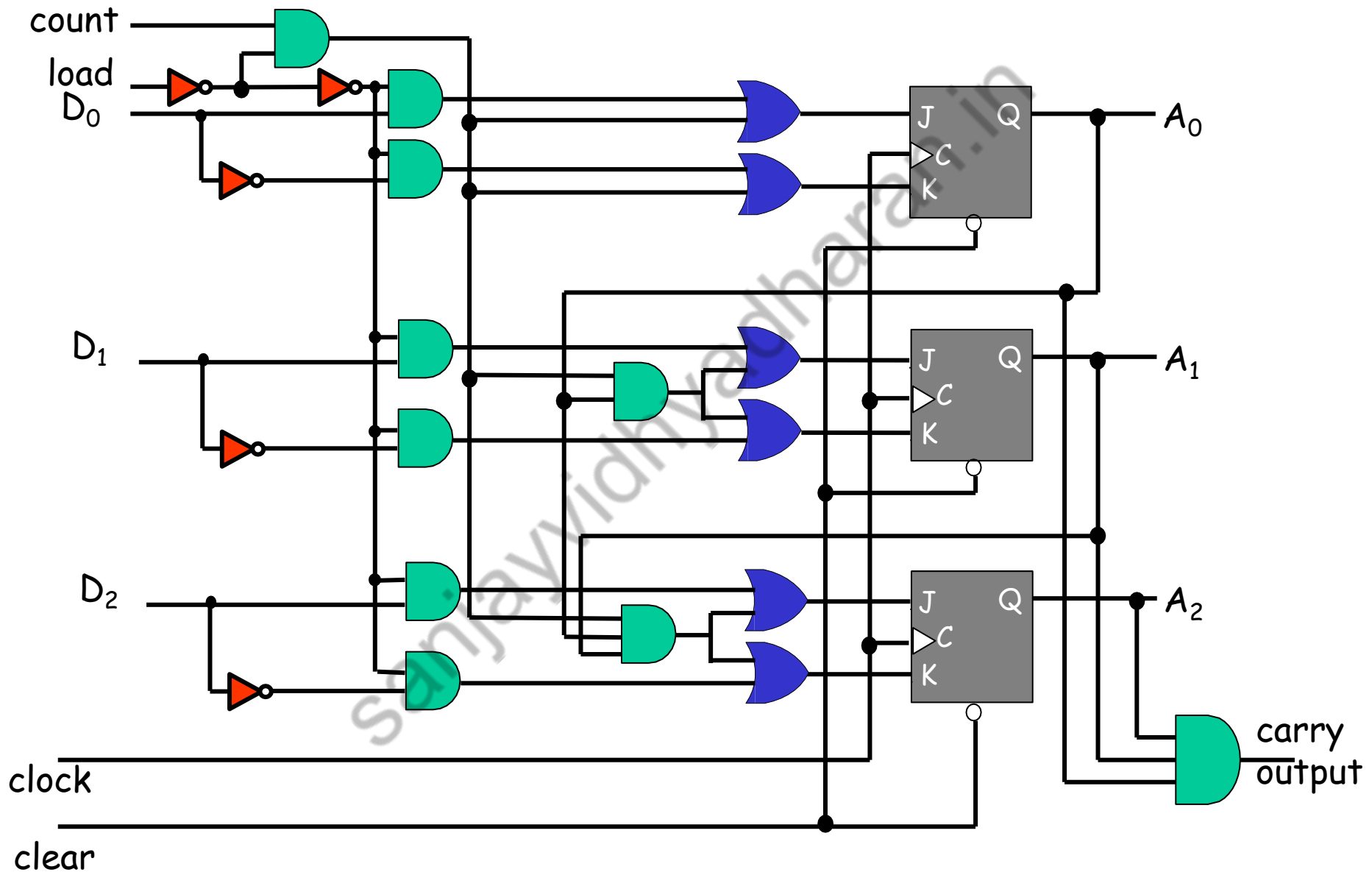

Binary Counter with Parallel Load


Function Table

clear	clock	load	Count	Function
0	X	X	X	clear to 0
1	↑	1	X	load inputs
1	↑	0	1	count up
1	↑	0	0	no change

Other Counters


- Ring Counter

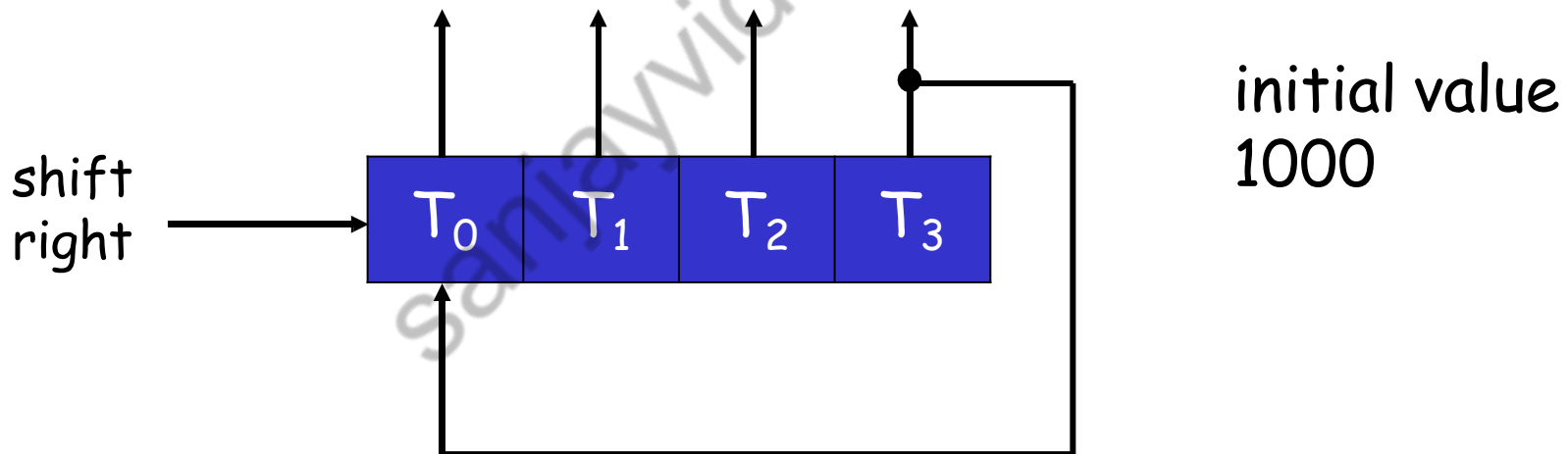- Timing signals control the sequence of operations in a digital system
- A ring counter is a circular shift register with only one flip-flop being set at any particular time, all others are cleared.




Ring Counter

- Sequence of timing signals

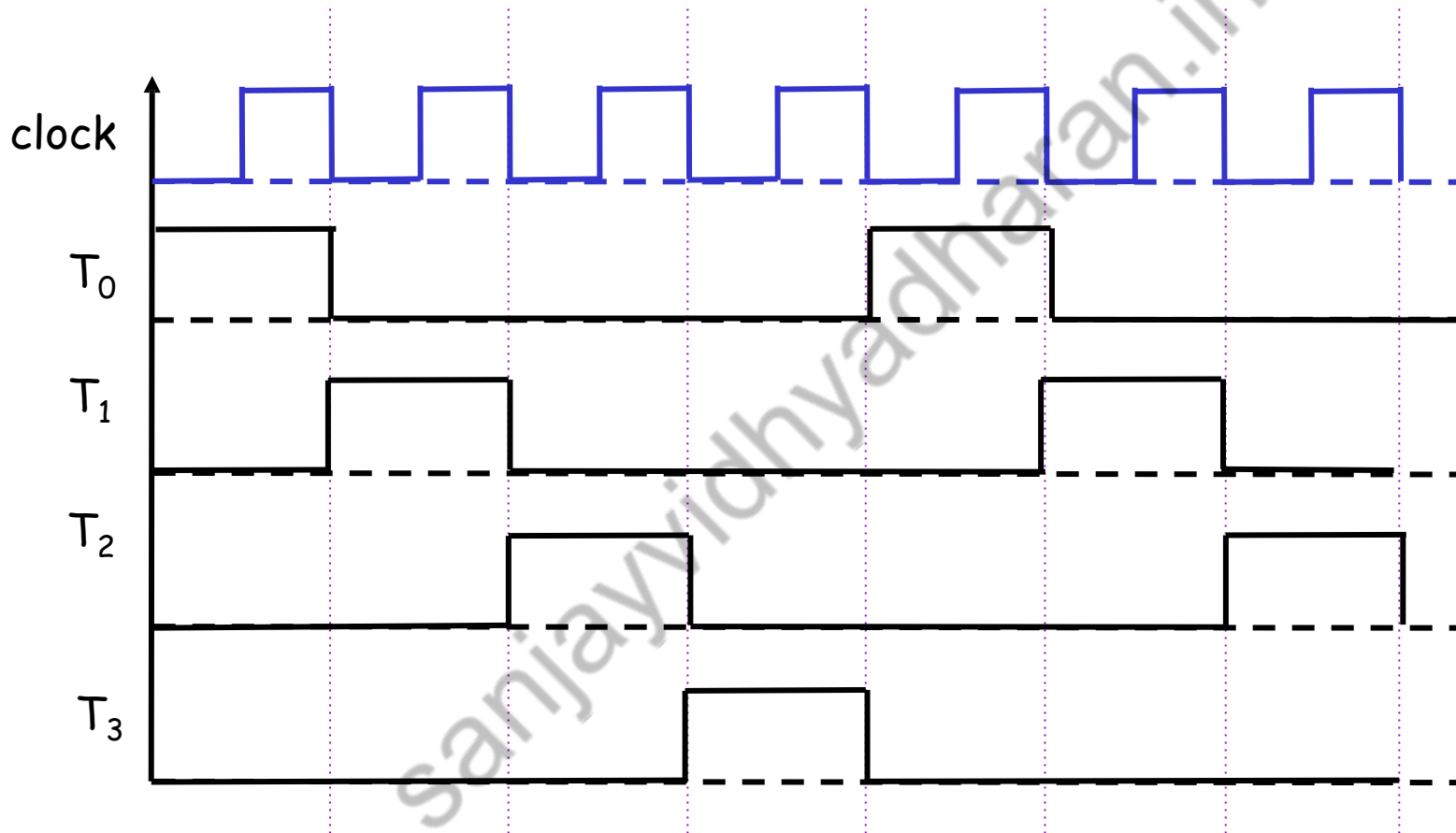

Ring Counter

 - To generate 2^n timing signals,
 - we need a shift register with 2^n flip-flops
- or, we can construct the ring counter with a binary counter and a decoder



Cost:


- 2 flip-flop
- 2-to-4 line decoder

Cost in general case:

- n flip-flops
- n -to- 2^n line decoder

Johnson Counter

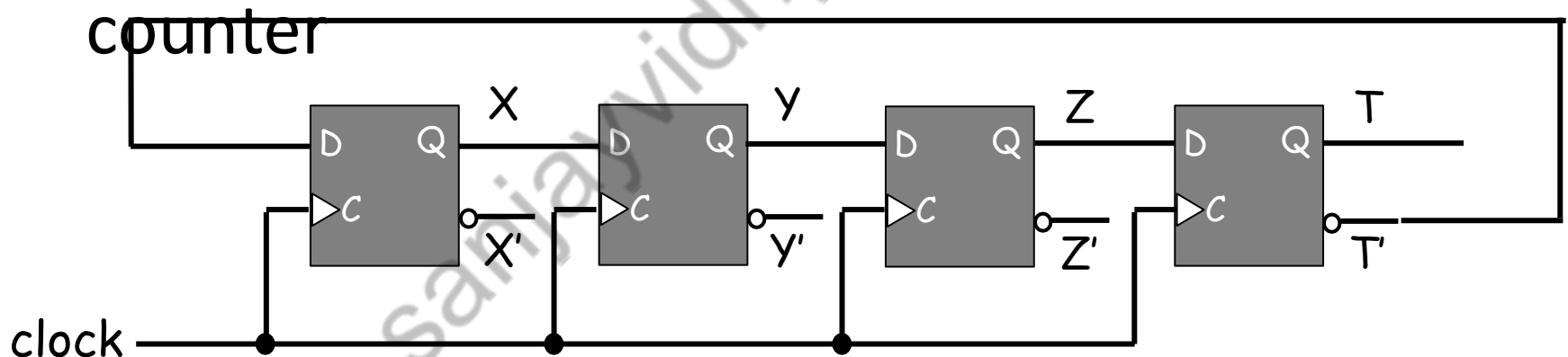- A k-bit ring counter can generate k distinguishable states
- The number of states can be doubled if the shift register is connected as a switch-tail ring counter




Johnson Counter

- Count sequence and required decoding

sequence number	Flip-flop outputs				Output
	X	Y	Z	T	
1	0	0	0	0	$X'T'$
2	1	0	0	0	XY'
3	1	1	0	0	YZ'
4	1	1	1	0	ZT'
5	1	1	1	1	XT
6	0	1	1	1	$X'Y$
7	0	0	1	1	$Y'Z$
8	0	0	0	1	$Z'T$


Johnson Counter

- Decoding circuit

 

Unused States in Counters

- 4-bit Johnson counter

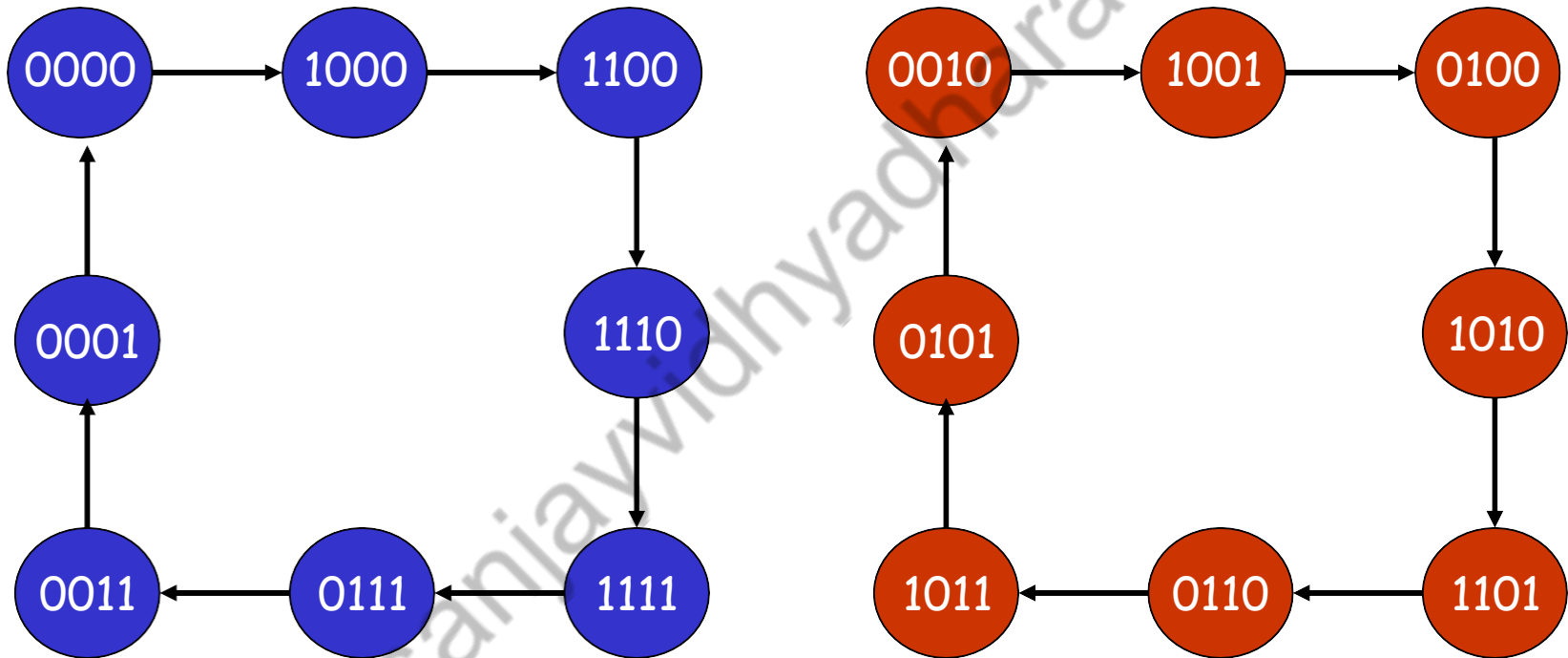

Johnson Counter

Inputs				Outputs			
X	Y	Z	T	X	Y	Z	T
0	0	0	0	1	0	0	0
1	0	0	0	1	1	0	0
1	1	0	0	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	1	1	1
0	1	1	1	0	0	1	1
0	0	1	1	0	0	0	1
0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	1
1	1	0	1	0	1	1	0
0	1	1	0	1	0	1	1
1	0	1	1	0	1	0	1
0	1	0	1	0	0	0	0
0	0	1	0	1	0	0	1
1	0	0	1	0	1	0	0
0	1	0	0	1	0	0	0

K-Maps

		ZT			
		00	01	11	10
XY	00	1			1
	01	1			1
	11	1			1
	10	1			1

$$X = T'$$

		ZT			
		00	01	11	10
XY	00				
	01				
	11	1	1	1	1
	10	1	1	1	1

$$Y = X$$

		ZT			
		00	01	11	10
XY	00				
	01			1	1
	11	1	1	1	1
	10				


$$Z = XY + YZ$$

		ZT			
		00	01	11	10
XY	00			1	1
	01			1	1
	11			1	1
	10			1	1

$$T = Z$$


Unused States in Counters

- Remedy

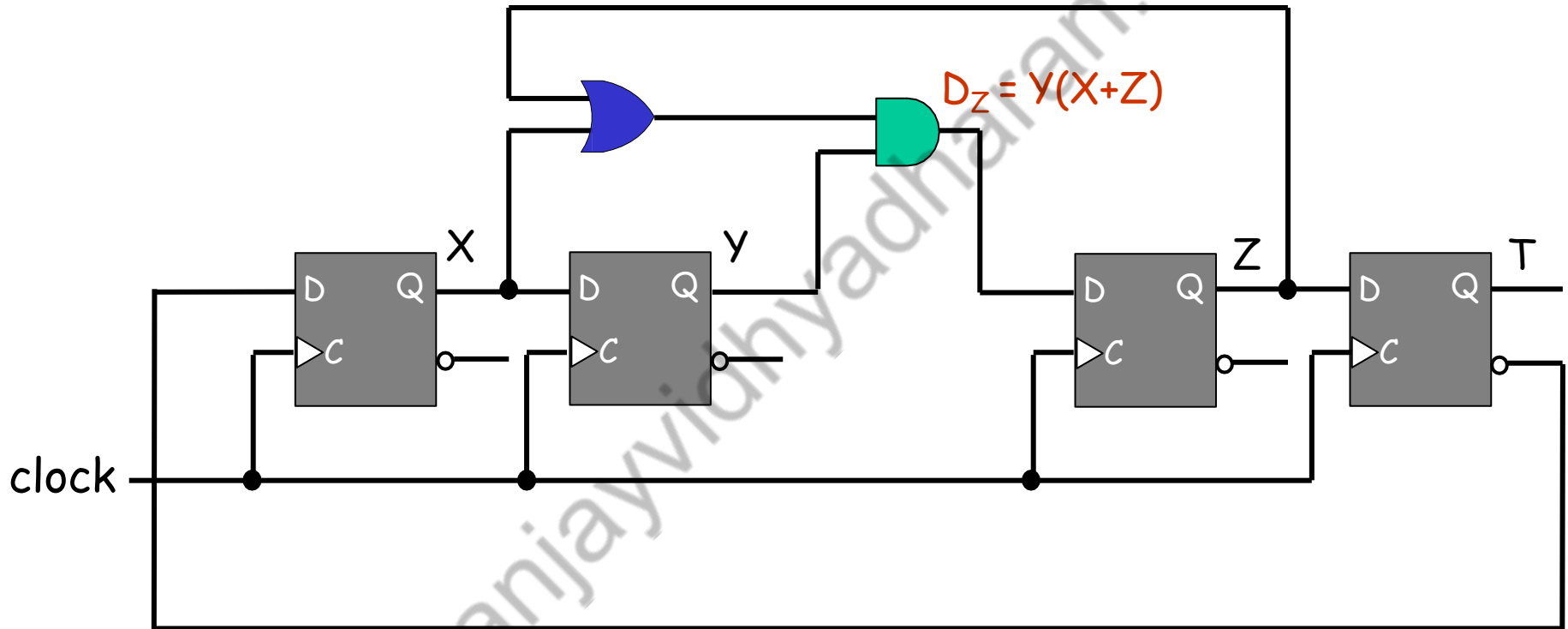

Unused States in Counters

- State diagram

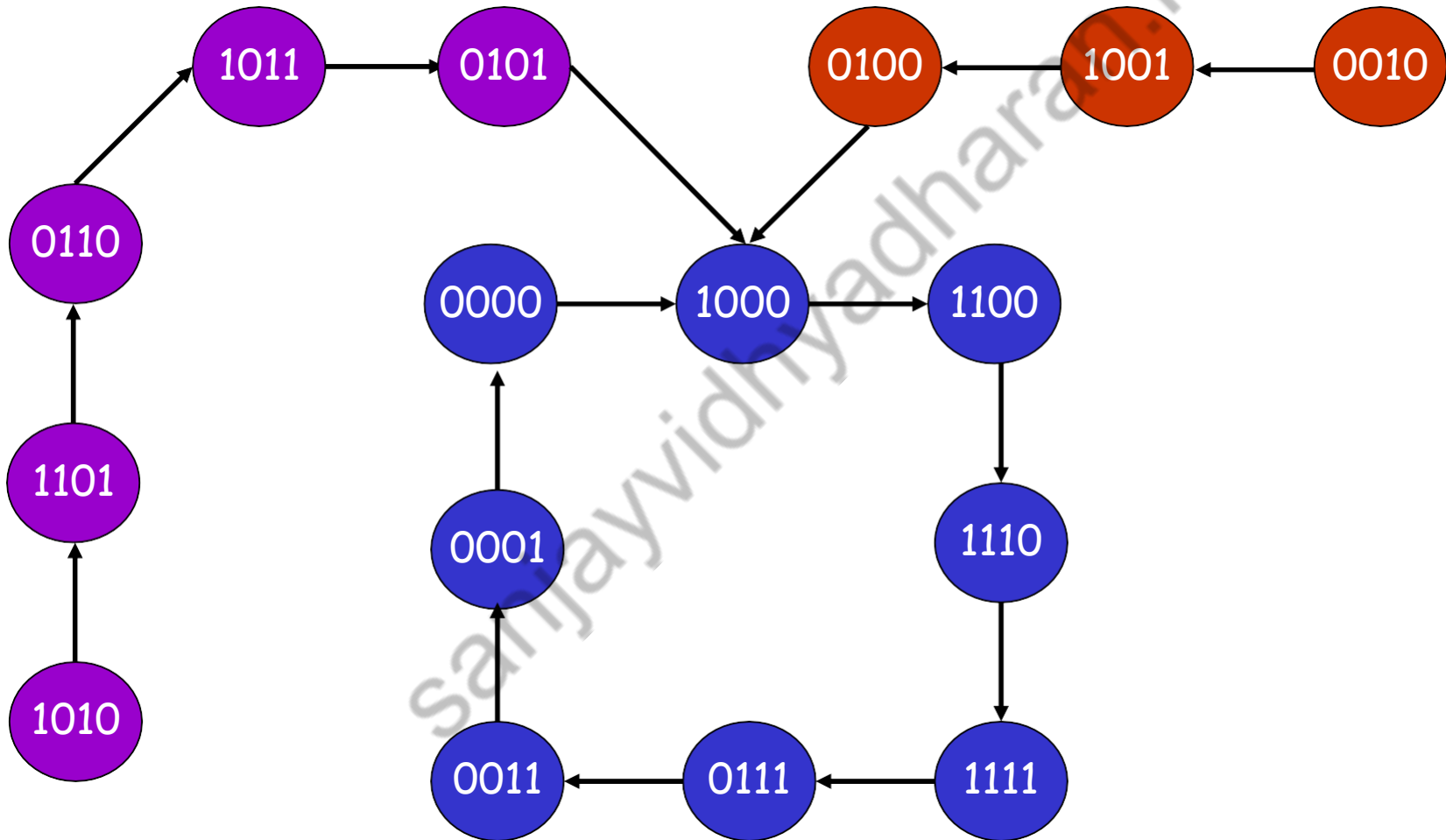

Thank you

sanjayvidhyadharan.in