



VLSI SYSTEMS AND ARCHITECTURE

2021-22

Lab-5 : Decoder Design in Xilinx

By Dr. Sanjay Vidhyadharan

The Decoder

module

Decoder(a,b,c,d0,d1,d2,d3,d4,d5,d6,d7);

input a,b,c;

output d0,d1,d2,d3,d4,d5,d6,d7;

assign d0=(~a&~b&~c),

d1=(~a&~b&c),

d2=(~a&b&~c),

d3=(~a&b&c),


d4=(a&~b&~c),

d5=(a&~b&c),

d6=(a&b&~c),

d7=(a&b&c);

endmodule

 

3/19/2022

The Conditional Statement

If statement in Verilog

```
if (sel == 1) f = a;  
else f = b;
```

Example : X is output of a Decoder, Y is output Function

```
begin  
    if (x[3] == 1'b1) y = 2'b11;  
    else if (x[2] == 1'b1) y = 2'b10;  
    else if (x[1] == 1'b1) y = 2'b01;  
    else y = 2'b00;  
end
```

The Decoder

```
module decoder (in,out);  
input [2:0] in;  
output [7:0] out;  
assign out =  
(in == 3'b000 ) ? 8'b0000_0001 :  
(in == 3'b001 ) ? 8'b0000_0010 :  
(in == 3'b010 ) ? 8'b0000_0100 :  
(in == 3'b011 ) ? 8'b0000_1000 :  
(in == 3'b100 ) ? 8'b0001_0000 :  
(in == 3'b101 ) ? 8'b0010_0000 :  
(in == 3'b110 ) ? 8'b0100_0000 :  
(in == 3'b111 ) ? 8'b1000_0000 :  
8'h00;  
endmodule
```

Full Adder

```
module Full_Adder (  
  
input [2:0] in,  
output Sum, Carry);  
  
wire[7:0]W;  
  
decoder G (in,W);  
assign Sum=(W[1]|W[2]|W[4]|W[7]);  
assign Carry=(W[3]|W[5]|W[6]|W[7]);  
endmodule
```

Thank you