



VLSI SYSTEMS AND ARCHITECTURE

2021-22


Lab-6 : Multiplexer Design in Xilinx

By Dr. Sanjay Vidhyadharan

sanjayvidhyadharan.in


The Multiplexer
 
```
module m41 (out, a, b, c, d, s0, s1);  
output out;  
input a, b, c, d, s0, s1;  
wire sobar, s1bar, T1, T2, T3, T4;  
not (s0bar, s0), (s1bar, s1);  
and (T1, a, s0bar, s1bar),  
    (T2, b, s0bar, s1),  
    (T3, c, s0, s1bar),  
    (T4, d, s0, s1);  
or(out, T1, T2, T3, T4);  
endmodule
```



The Multiplexer
 
```
module Mux(  
    input [7:0] I,  
    input [2:0] S,  
    output Y  
);  
    assign Y = I[S];  
endmodule
```



S2	S1	S0	Y
0	0	0	I0
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Full Adder

```
module FullAdder(  
    input A,  
    input B,  
    input Cin,  
    output Sum, Carry  
);  
wire [7:0] s;  
wire [7:0] c;  
assign s = 8'b10010110;  
Mux m1 (s,{A,B,Cin},Sum);  
assign c = 8'b11101000;  
Mux m2 (c,{A,B,Cin},Carry);  
endmodule
```

```
module Mux(  
    input [7:0] I,  
    input [2:0] S,  
    output Y  
);  
assign Y = I[S];  
endmodule
```

Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Thank you