



VLSI SYSTEMS AND ARCHITECTURE

2021-22

Lecture 3


Computer Arithmetic Algorithms and Implementations

By Dr. Sanjay Vidhyadharan

Half Adder


Inputs		Output	
A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

K-map for Sum

 


$$S = xy' + x'y$$

K-map for Carry

 

$$C = xy$$

 

$$\text{Sum} = X \cdot Y' + X' \cdot Y = X \oplus Y$$

$$\text{Carry} = X \cdot Y$$

Time Delay for the Half Adder?

1 gate delay

A gate delay of an xor for the half sum

A gate delay of an AND gate for the carry out

Full Adder

Full-adder can also implemented with two half adders and one OR gate.

$$S = A \oplus B \oplus C_{in}$$


$$C_{out} = AB + BC_{in} + AC_{in}$$

$$= AB + C_{in}(A+B)$$

$$= AB + C_{in}(A \oplus B + AB)$$


$$= AB + C_{in}(A \oplus B) + C_{in}AB = AB(1 + C_{in}) + C_{in}(A \oplus B)$$

$$= AB + C_{in}(A \oplus B)$$

 

Ripple Carry Adder

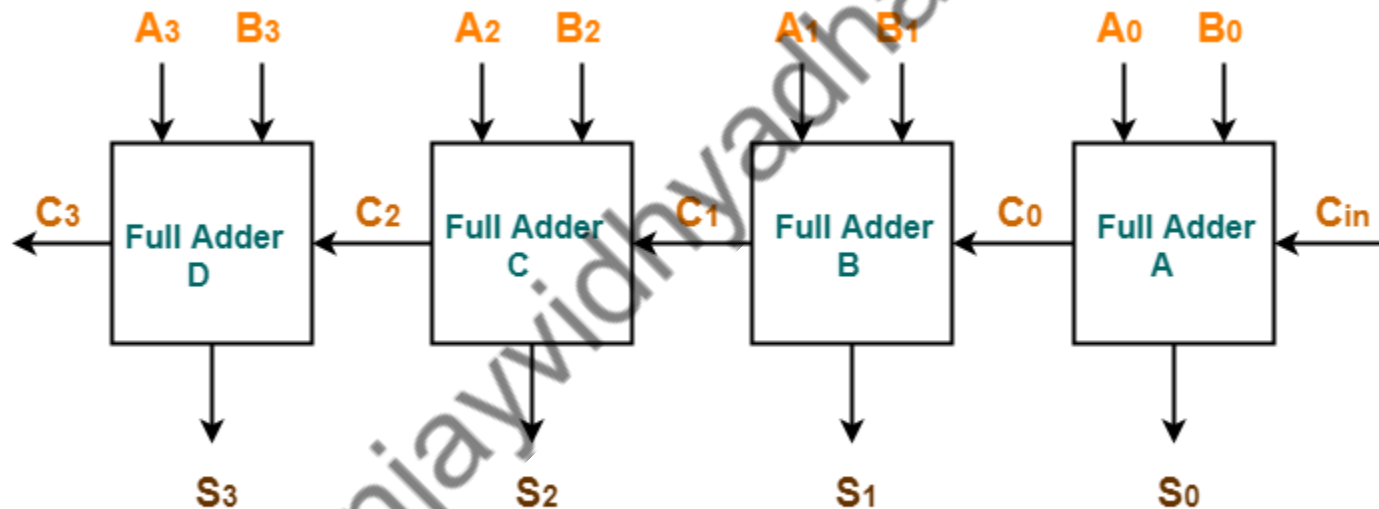This is called Ripple Carry Adder, because of the construction with full adders are connected in cascade.




4-bit Ripple Carry Adder

Delay = 4 X Full Adder Delay = 12 Gate Delays


Carry Look-Ahead Adder

1-bit CLA

 


Carry Look-Ahead Adder

CLA

 


CLLB

 


$$C_1 = G_0 + P_0 C_0$$

Carry Look-Ahead Adder

 


$$C_2 = G_1 + P_1 C_1$$
 
$$\begin{aligned} C_2 &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$



Carry Look-Ahead Adder

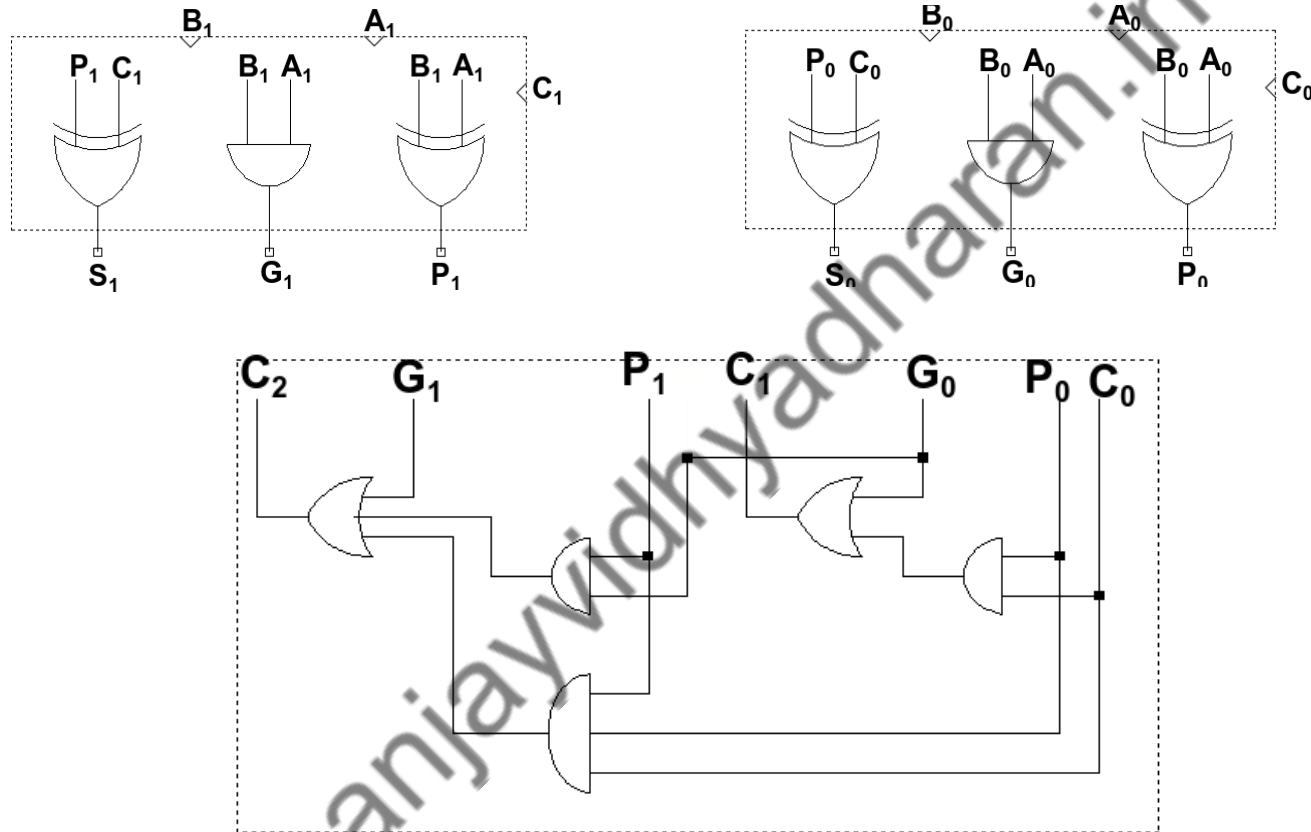

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_1 = G_0 + P_0 C_0$$

Carry Look-Ahead Adder


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$





$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

Carry Look-Ahead Adder

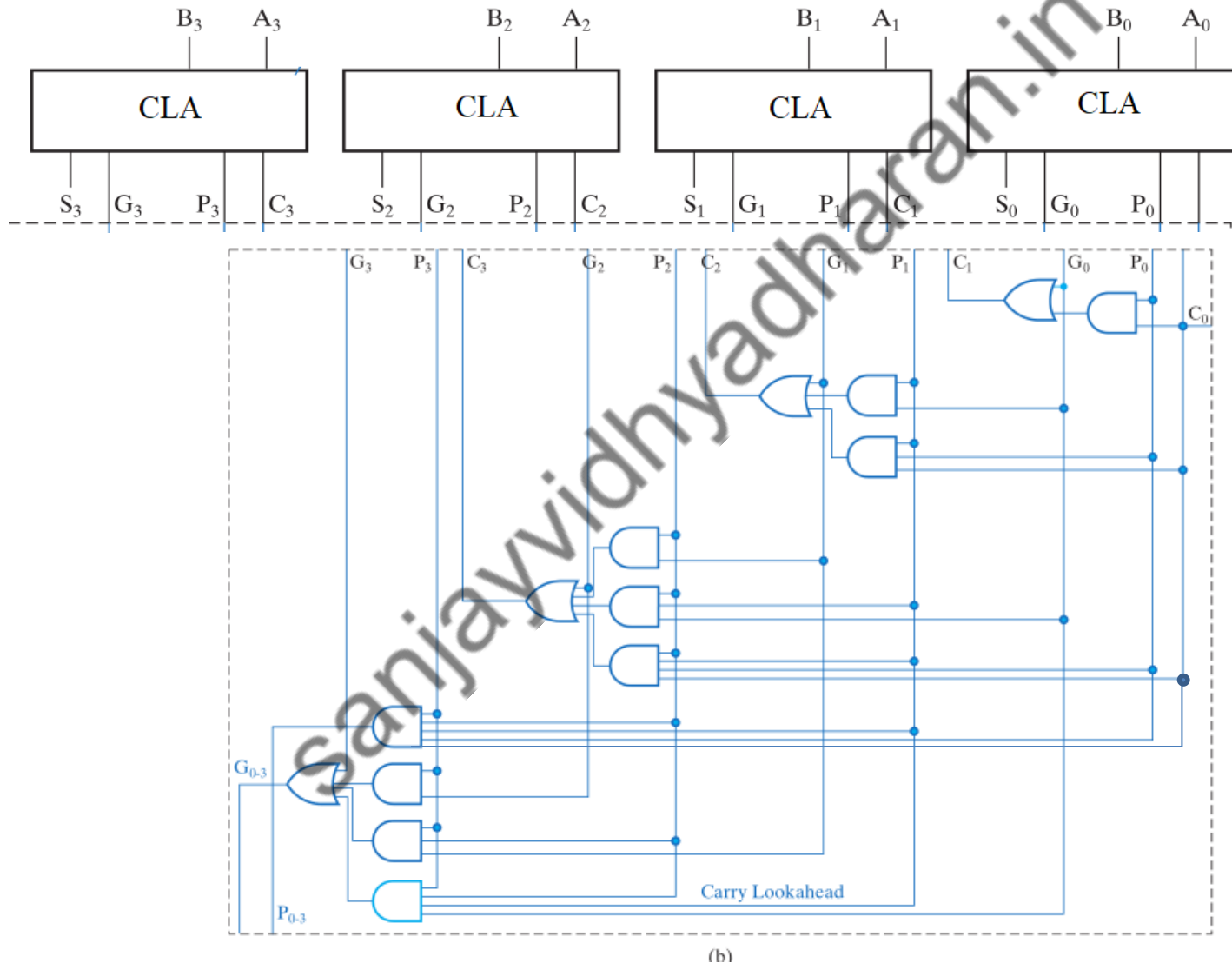

Carry Look-Ahead Adder



8 Bit Full Adder

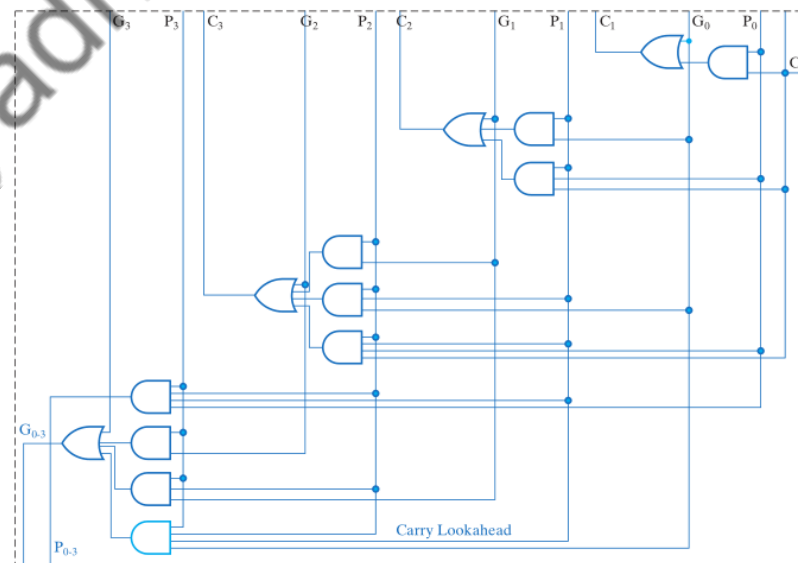   


Delay = $2 \times 3 = 6$ Gate Delay

Ripple Carry Adder

8 Bit Full Adder

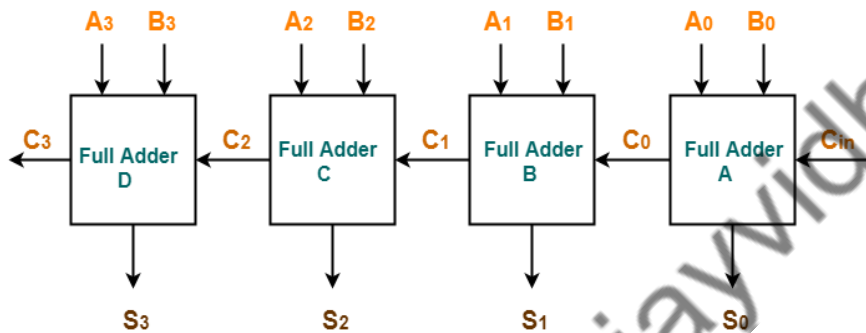 


4-bit Ripple Carry Adder

 

4-bit Ripple Carry Adder

Delay = 8 X 3 Gate Delay

Serial Adder

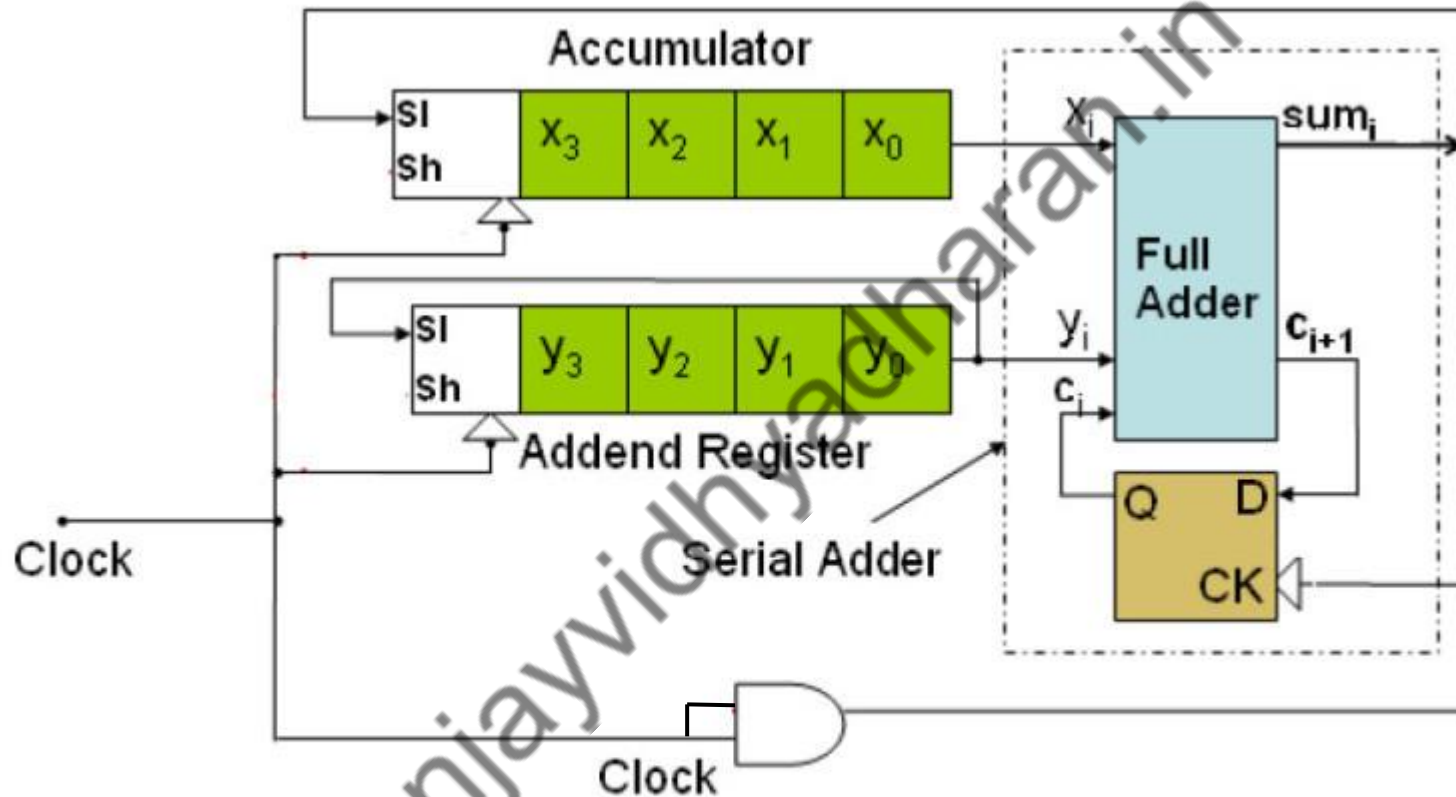

Block Diagram of a 4-bit Serial Adder with Accumulator

4 Bit-Adder Subtractor

Add 4 & -3

```

0100
1101
1 0001
    
```

Add -4 & -5

```

1100
1011
1 0111
    
```

Add -8 & 4


```

1000
0100
1100
    
```

Add 4 & 4

```

0100
0100
1000
    
```

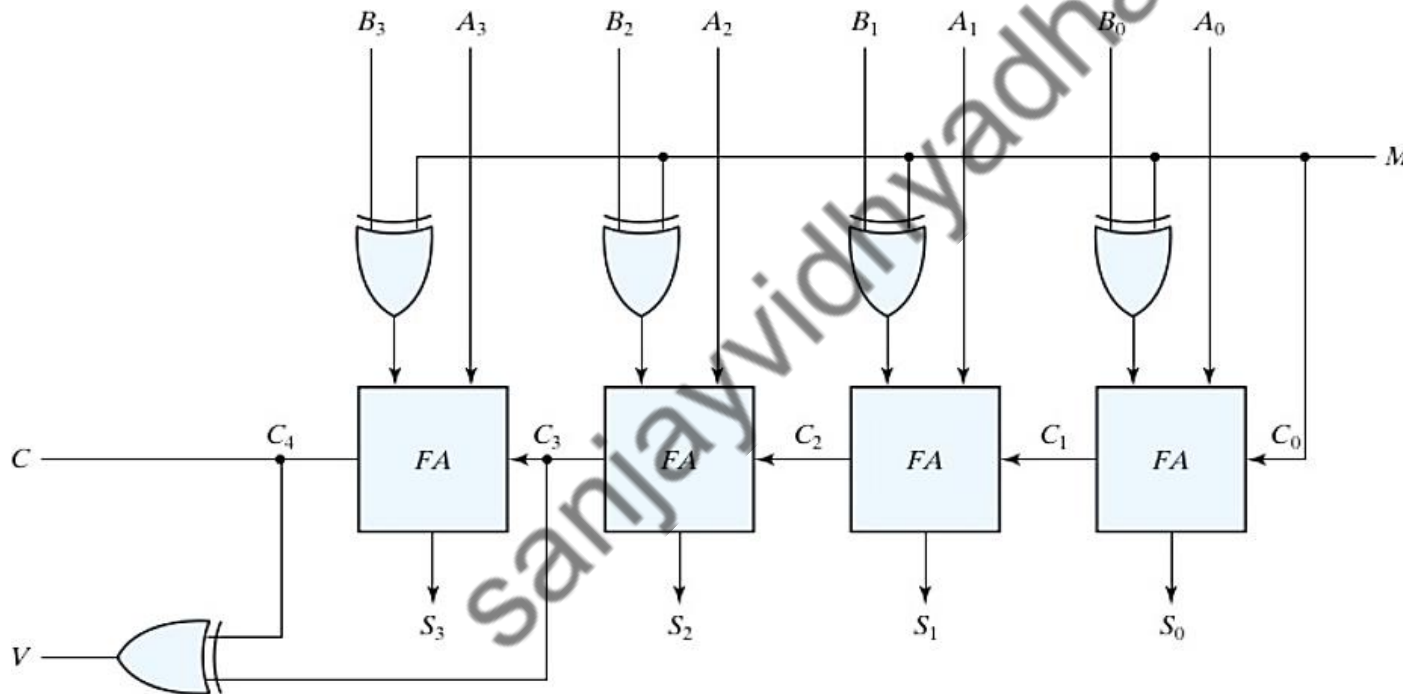

Overflow

Decimal	2's comp.
7	0111
6	0110
5	0101
4	0100
3	0011
2	0010
1	0001
0	0000
-0	-
-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001
-8	1000

Binary Multiplier

$$\begin{array}{r} 23 \\ \times 52 \\ \hline 46 \\ 115 \\ \hline 1196 \end{array}$$

$$\begin{array}{r} 10 \\ \times 11 \\ \hline 10 \\ 100 \\ \hline 1100 \end{array}$$


$$2 \times 3 = 6$$

Binary Multiplier (2-bit x 2-bit)


$$\begin{array}{r}
 B_1 B_0 \\
 \times A_1 A_0 \\
 \hline
 B_1 A_0 B_0 A_0 \\
 B_1 A_1 B_0 A_1 \\
 \hline
 P_3 P_2 P_1 P_0
 \end{array}$$

Gate for 1-bit Multiplication ($B_0 A_0$) ?

A_0	B_0	F
0	0	0
0	1	0
1	0	0
1	1	1

 


Binary Multiplier (2-bit x 2-bit)

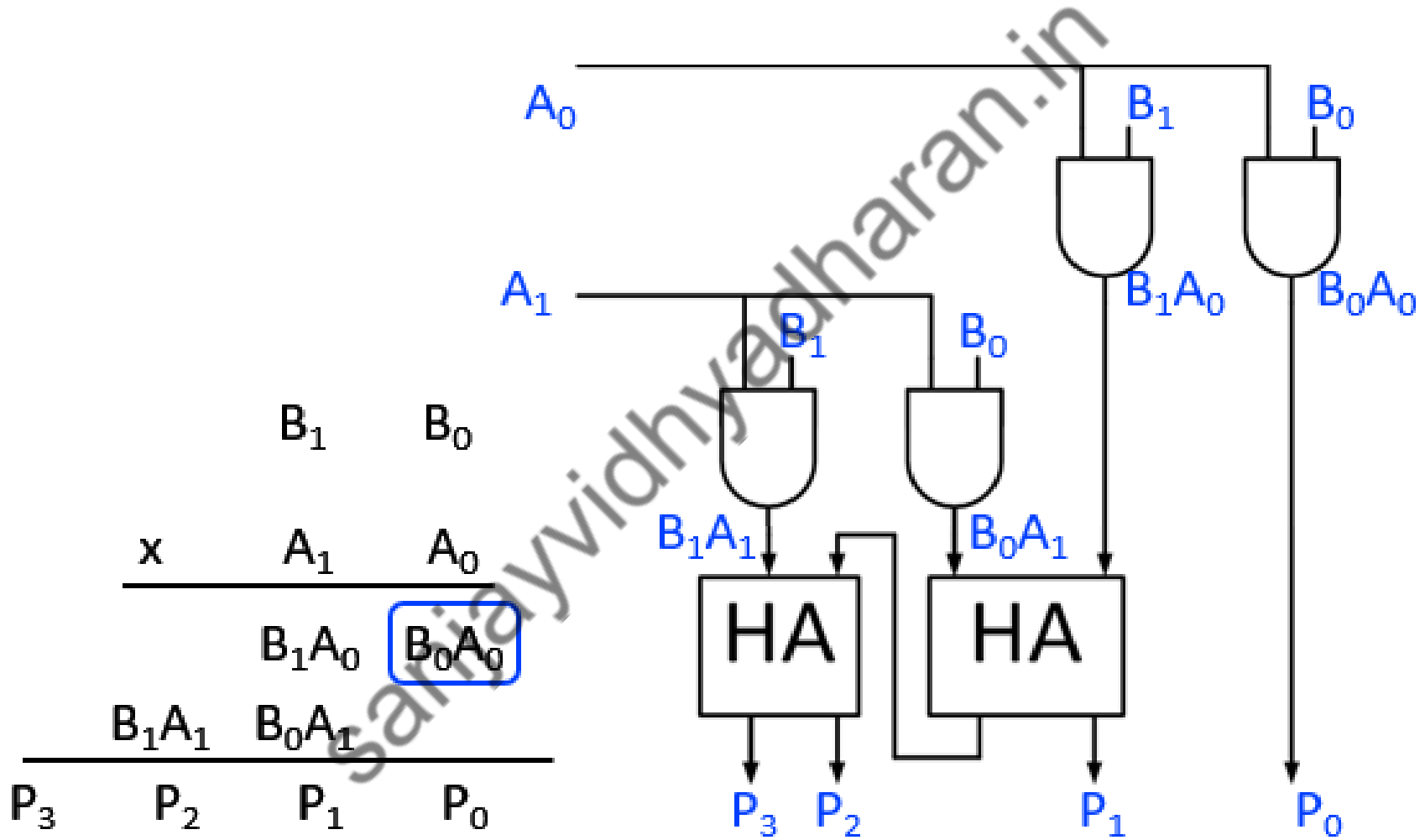

Binary Multiplier (4-bit x 4-bit)

$$\begin{array}{r} \text{(Multiplicand)} \quad B_3 \ B_2 \ B_1 \ B_0 \\ \text{(Multiplier)} \quad A_3 \ A_2 \ A_1 \ A_0 \\ \hline A_0 B_3 \ A_0 B_2 \ A_0 B_1 \ A_0 B_0 \\ A_1 B_3 \ A_1 B_2 \ A_1 B_1 \ A_1 B_0 \\ A_2 B_3 \ A_2 B_2 \ A_2 B_1 \ A_2 B_0 \\ A_3 B_3 \ A_3 B_2 \ A_3 B_1 \ A_3 B_0 \\ \hline \end{array}$$

Binary Multiplier (4-bit x 4-bit)

 


Booth Algorithm

B: 1 0 1 1 0 1 1 0
A: 1 0 0 1 0 1 0 0

0 0 0 0 0 0 0 0
0 0 0 0 0 0 0 0
1 0 1 1 0 1 1 0
0 0 0 0 0 0 0 0
1 0 1 1 0 1 1 0
0 0 0 0 0 0 0 0
0 0 0 0 0 0 0 0
1 0 1 1 0 1 1 0

1 1 0 1 0 0 1 0 0 1 1 1 0 0 0

Booth Algorithm

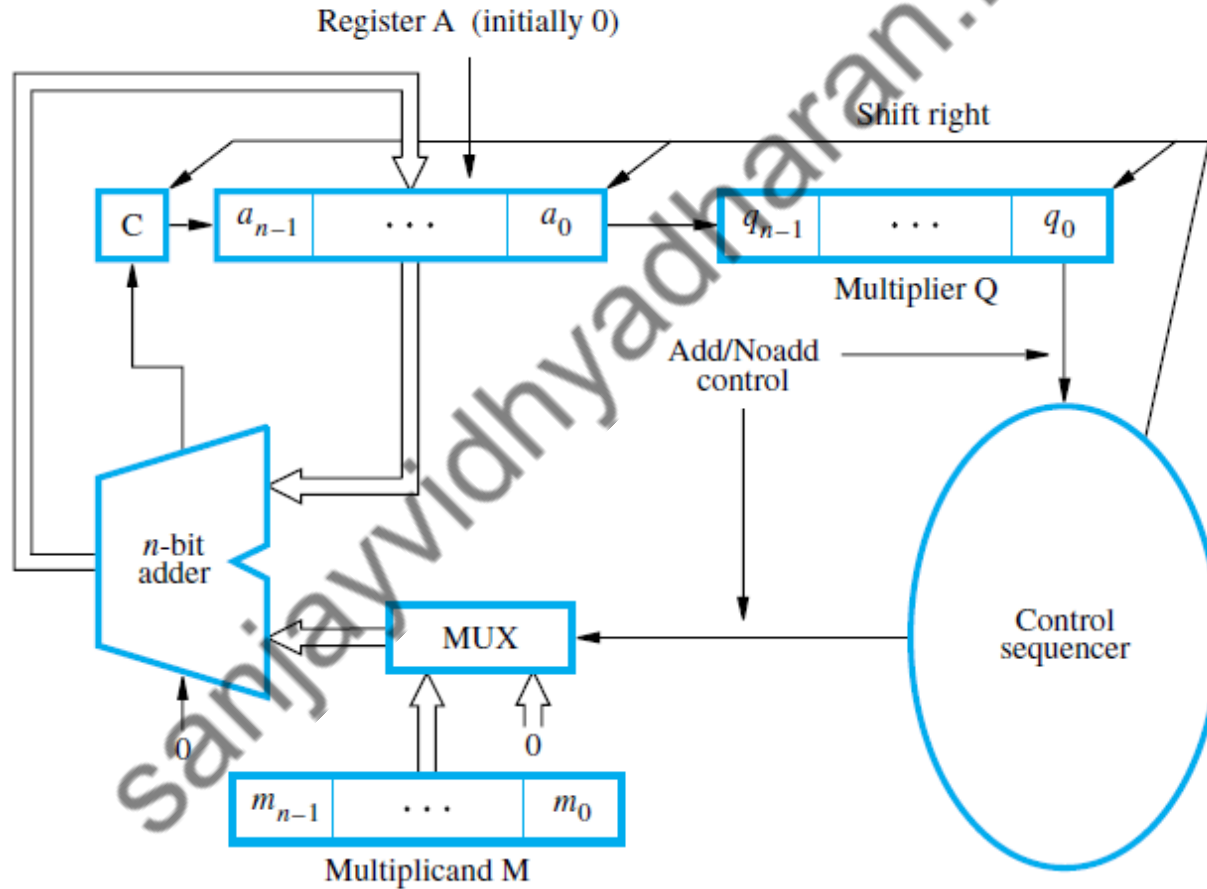

(a) Register configuration

Booth Algorithm

	3x5			
	M	A	Q	
Initial Condition	0011	00000	010 1	
Clk ↑ (Load)	0011	00011	0101	1
Clk ↓ (Shift Right)	0011	00001	101 0	
Clk ↑ (Load)	0011	00001	101 0	2
Clk ↓ (Shift Right)	0011	00000	110 1	
Clk ↑ (Load)	0011	00011	110 1	3
Clk ↓ (Shift Right)	0011	00001	111 0	
Clk ↑ (Load)	0011	00001	111 0	4
Clk ↓ (Shift Right)	0011	00000	1111	

Thank you