



# **Advanced VLSI Design: 2021-22**

## **Lecture 12-A: Low Power VLSI Design**


### **Part-1: Gate Level Optimization**

**By Dr. Sanjay Vidhyadharan**

sanjayvidhyadharan.in
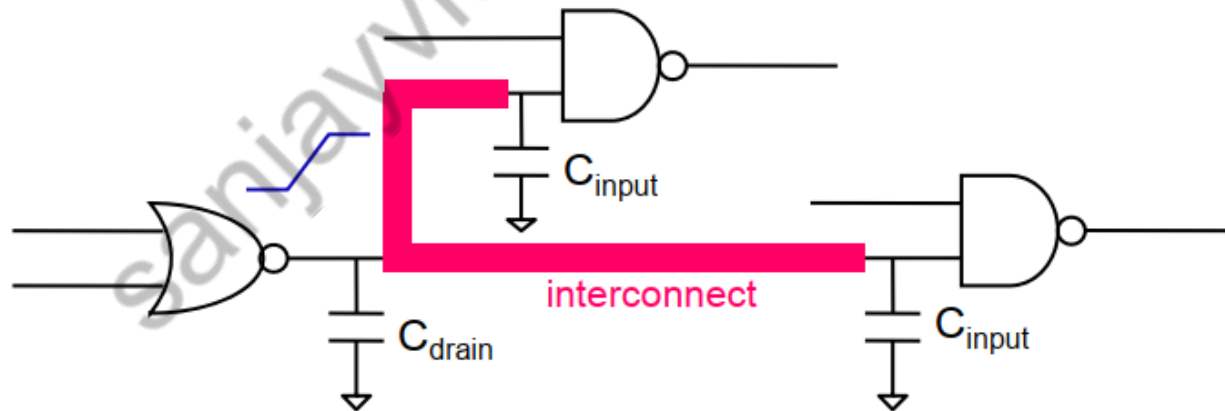
# Overview of Power Consumption

- Average power consumption
  - Dynamic power consumption
  - Short-circuit power consumption
  - Leakage power consumption
  - Static power consumption
- Dynamic power dissipation during switching



# Overview of Power Consumption

- The average power consumption can be expressed as


$$P_{avg} = \frac{1}{T} C_{load} V_{DD}^2 = C_{load} V_{DD}^2 f_{CLK}$$

- The node transition rate can be slower than the clock rate. To better represent this behavior, a node transition factor ( $\alpha_T$ ) should be introduced

$$P_{avg} = \alpha_T C_{load} V_{DD}^2 f_{CLK}$$

- The switching power expressed above are derived by taking into account the output node load capacitance

# Overview of Power Consumption

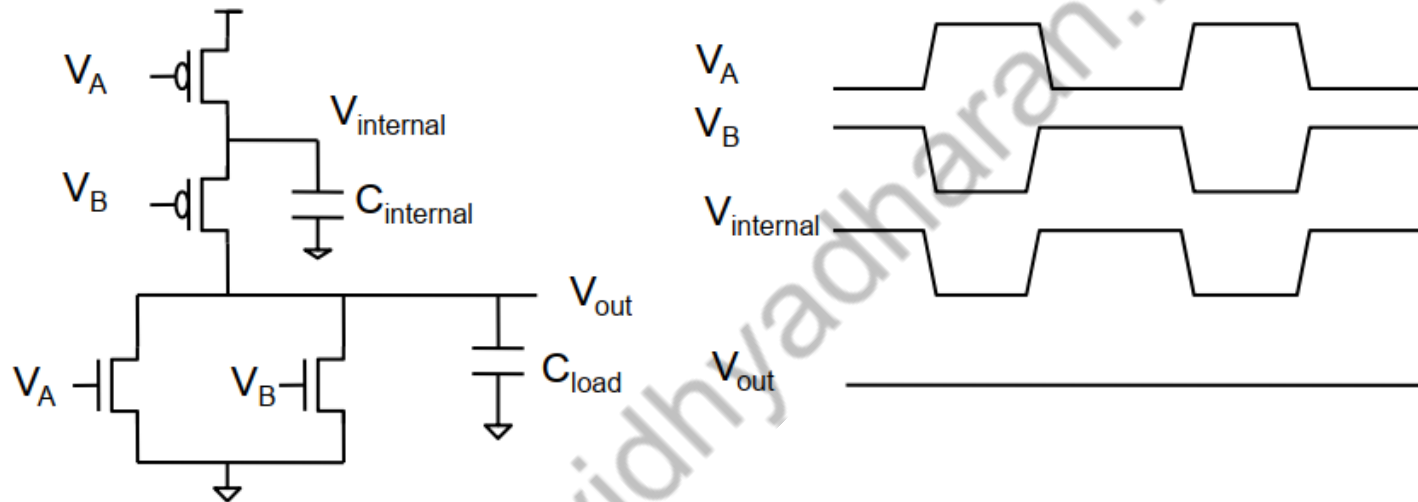

The generalized expression for the average power dissipation can be rewritten as

$$P_{avg} = \left( \sum_{i=1}^{\#ofnodes} \alpha_{Ti} C_i V_i \right) V_{DD} f_{CLK}$$

# Transition Activity

- ❑ Switching activity,  $P_{0 \rightarrow 1}$ , has two components
  - A static component – function of the logic topology
  - A dynamic component – function of the timing behavior (glitching)

2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Static transition probability

$$\begin{aligned} P_{0 \rightarrow 1} &= P_{\text{out}=0} \times P_{\text{out}=1} \\ &= P_0 \times (1 - P_0) \end{aligned}$$

With input signal probabilities

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$

NOR static transition probability

$$= 3/4 \times 1/4 = 3/16$$

# Transition Activity

<i>A</i>	<i>B</i>	<i>Out</i>
0	0	0
0	1	1
1	0	1
1	1	0

Assume **signal probabilities**

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then **transition probability**

$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$


$$= 1/2 \times 1/2 = 1/4$$

If inputs switch in every cycle

$$P_{0 \rightarrow 1} = 1/4$$

# Transition Activity

	$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$
NOR	$(1 - (1 - P_A)(1 - P_B)) \times (1 - P_A)(1 - P_B)$
OR	$(1 - P_A)(1 - P_B) \times (1 - (1 - P_A)(1 - P_B))$
NAND	$P_A P_B \times (1 - P_A P_B)$
AND	$(1 - P_A P_B) \times P_A P_B$
XOR	$(1 - (P_A + P_B - 2P_A P_B)) \times (P_A + P_B - 2P_A P_B)$

 

For X:  $P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_A) P_A$   
 $= 0.5 \times 0.5 = 0.25$

For Z:  $P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_X P_B) P_X P_B$   
 $= (1 - (0.5 \times 0.5)) \times (0.5 \times 0.5) = 3/16$

# Transition Activity

- Low-Power Gate-Level Design
- Low-Power Architecture-Level Design
- Algorithmic-Level Power Reduction
- RTL Techniques for Optimizing Power




# Gate-Level Design – Technology Mapping

- The objective of logic minimization is to reduce the boolean function.
- For low-power design, the signal switching activity is minimized by restructuring a logic circuit
- The power minimization is constrained by the delay, however, the area may increase.
- During this phase of logic minimization, the function to be minimized is


$$\sum_i P_i (1 - P_i) C_i$$
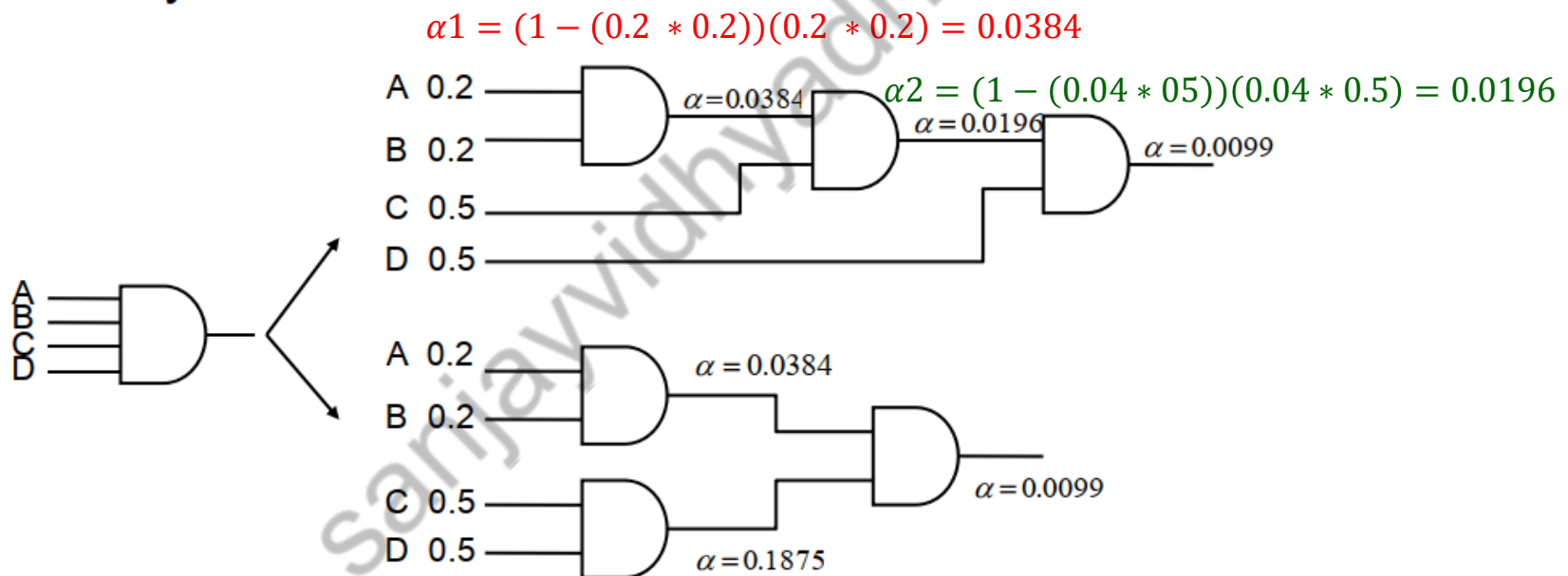
# Gate-Level Design – Technology Mapping


- The first step in technology mapping is to decompose each logic function into two-input gates
- The objective of this decomposition is to minimizing the total power dissipation by reducing the total switching activity



# Gate-Level Design – Technology Mapping

 


(a)

 


(b)  $f_{SOP} = \bar{W}\bar{Y} + XZ + \bar{Y}Z + \bar{W}X$

Figure 2. Minimal sum-of-products implementation for Example 3


 


(a)

 


(b)  $F = (\bar{W} + \bar{Y}) + XZ + \bar{X}\bar{Y}Z + \bar{W}XZ$


# Gate-Level Design – Phase Assignment

  

# Gate-Level Design – Pin Swapping

 

 
*delay determined by time to discharge  $C_L$ ,  $C_1$  and  $C_2$*



*delay determined by time to discharge  $C_L$*


- An input signal to a gate is called critical if it is the last signal of all inputs to assume a stable value.
- The path through the logic which determines the ultimate speed of the structure is called the critical path.
- Putting the critical-path transistors closer to the output of the gate can result in a speed-up.

# Gate-Level Design – Pin Swapping

 

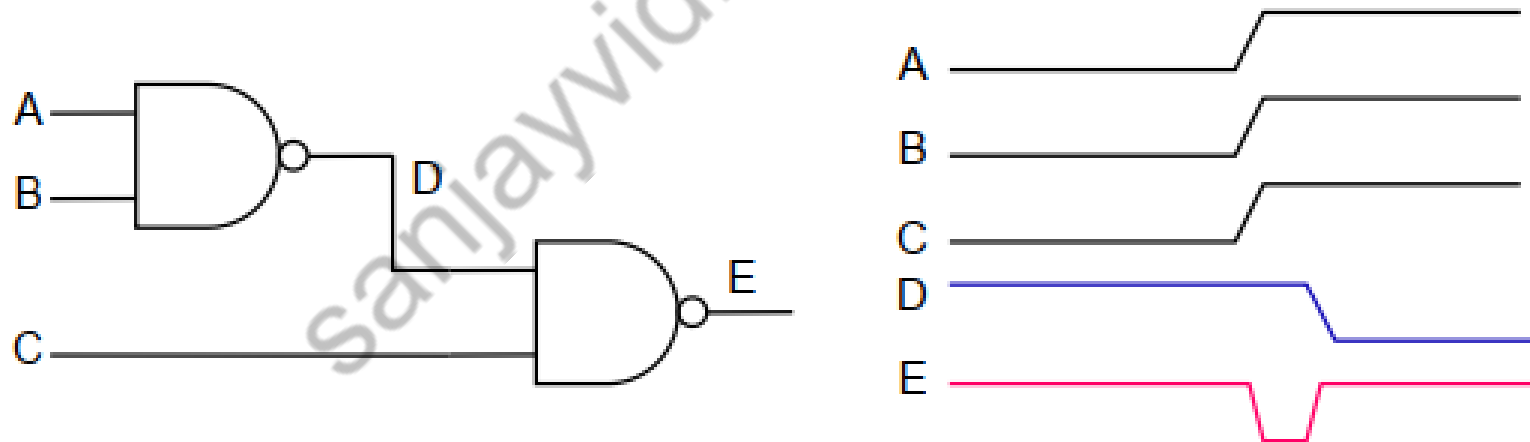
# Gate-Level Design – Glitching Power

- Glitches
  - spurious transitions due to imbalanced path delays
- A design has more balanced delay paths
  - has fewer glitches, and thus has less power dissipation
- Note that there will be no glitches in a dynamic CMOS logic



 
# Gate-Level Design – Glitching Power

- A chain structure has more glitches
- A tree structure has fewer glitches



Chain structure

 

Tree structure





# Static Glitch Example

Consider the following circuit with delays where only one input (input b) changes...

Draw a timing diagram to see what happens at output with delays.

From the logic expression, we see that b changing should result in the output remaining at logic level 1...

  Due to delay, the output goes 1->0->1 and this is an output glitch; **we see a static-1 hazard.**



# Static Glitch Elimination


		bc			
		00	01	11	10
a	0	0	1	0	0
	1	0	1	1	1

$$f = ab + b'c + ac$$


The extra product term does not include the changing input variable, and therefore serves to prevent possible momentary output glitches due to this variable.
 
# Static Glitch Elimination


The redundant product term is not influenced by the changing input.




# Gate-Level Design – Precomputation

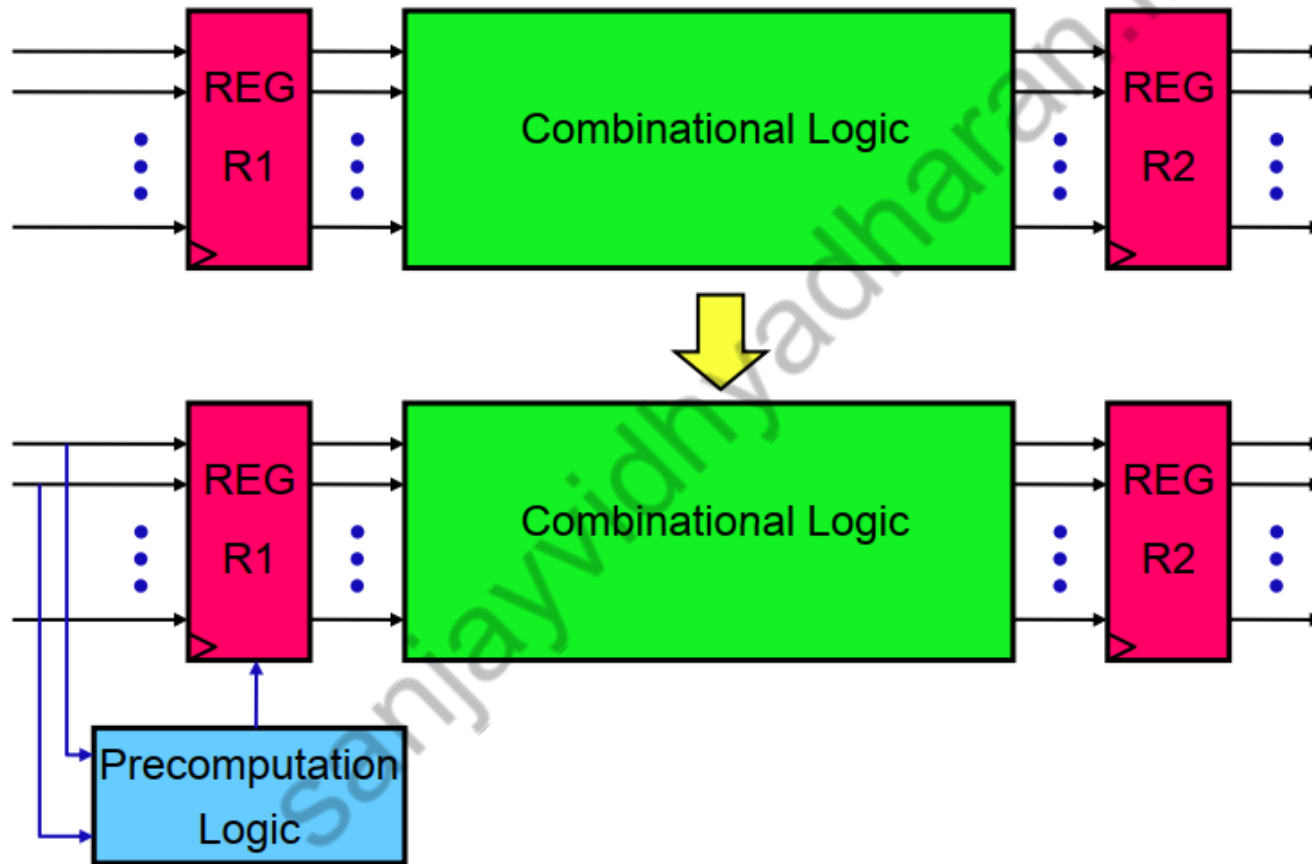


# Gate-Level Design – Precomputation

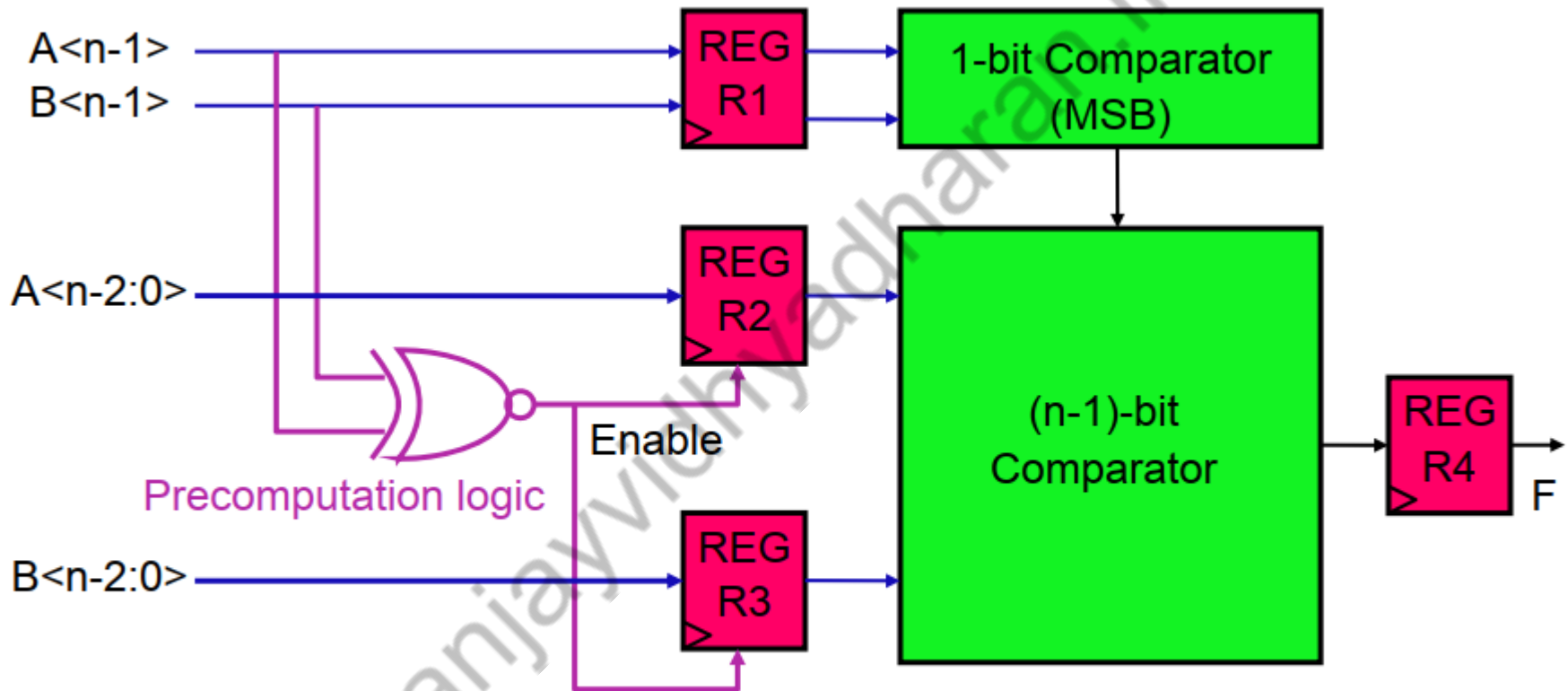


# Gate-Level Design – Clock Gating

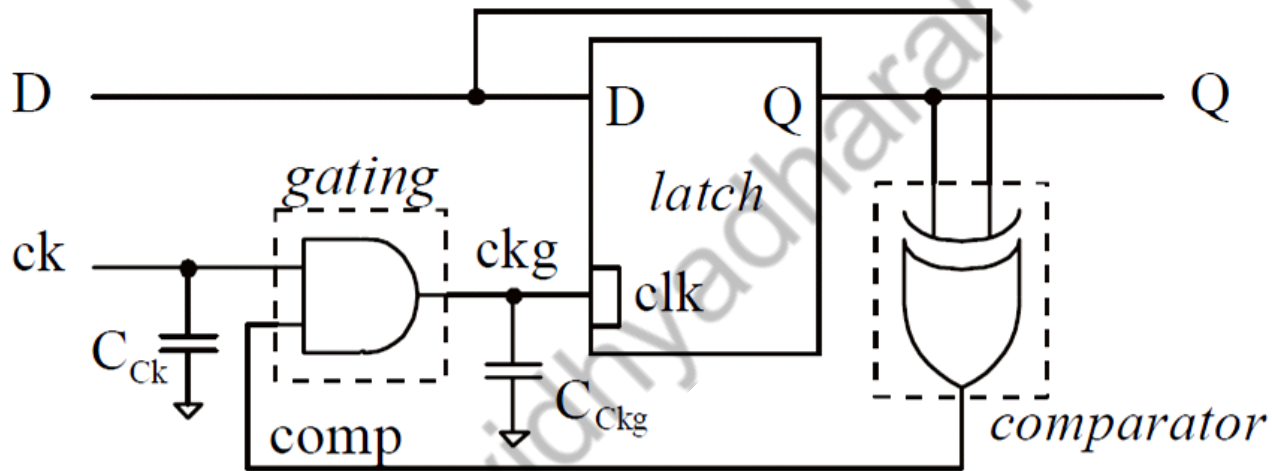

# Gate-Level Design – Clock Gating

 


Fail DFT rule checking

 


Add control pin to solve DFT violation problem

# Gate-Level Design – Input Gating

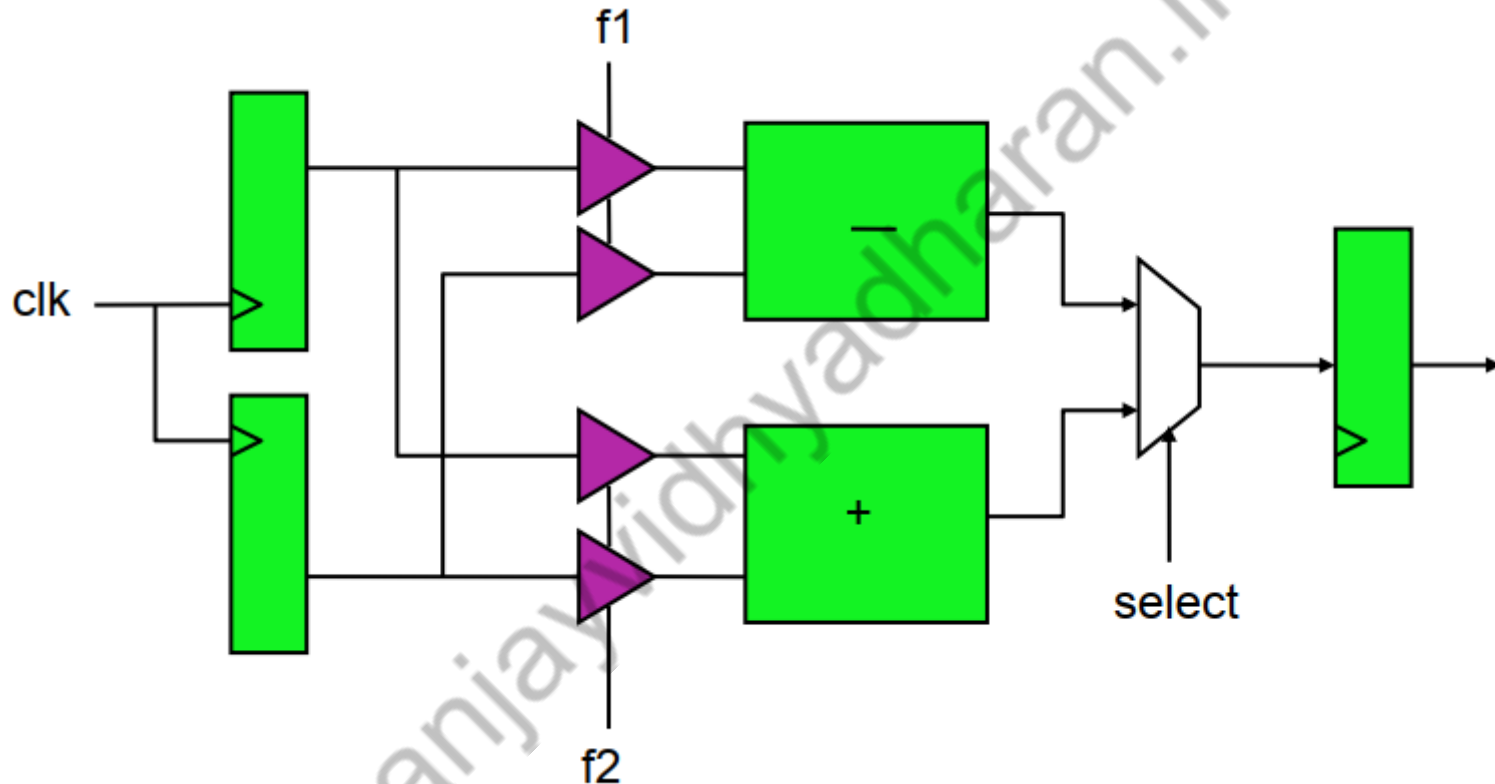



# Reduced-Power Shift Register

 

Flip-flops are operated at full voltage and half the clock frequency.



**Thank you**

sanjayvidhyadharan.in